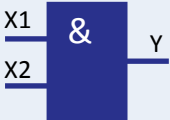
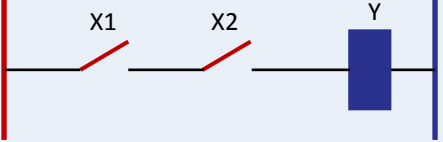
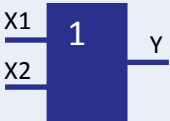
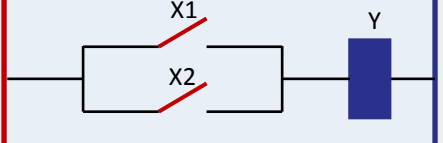
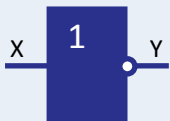
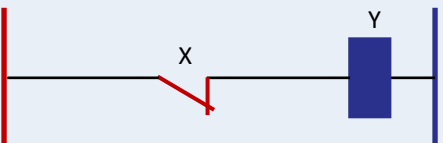
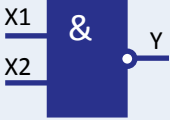
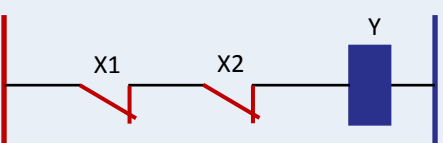
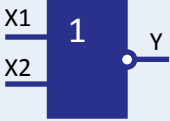
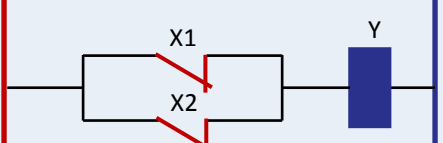
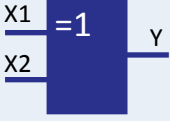
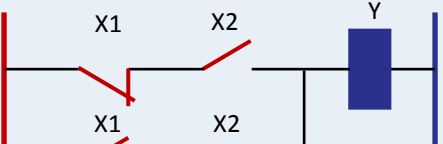


Функция	Обозначение	Таблица истинности			Операция	Релейно-контактная схема
		X1	X2	Y		
И		0	0	0	$X1 \times X2$	
		0	1	0		
		1	0	0		
		1	1	1		
ИЛИ		0	0	0	$X1 + X2$	
		0	1	1		
		1	0	1		
		1	1	1		
НЕ			0	0	\bar{X}	
			1	1		
И-НЕ		0	0	1	$\overline{X1 \times X2}$	
		0	1	0		
		1	0	0		
		1	1	0		
ИЛИ-НЕ		0	0	1	$\overline{X1 + X2}$	
		0	1	1		
		1	0	1		
		1	1	0		
Исключающее ИЛИ		0	0	0	$X1 \oplus X2$	
		0	1	1		
		1	0	1		
		1	1	0		