
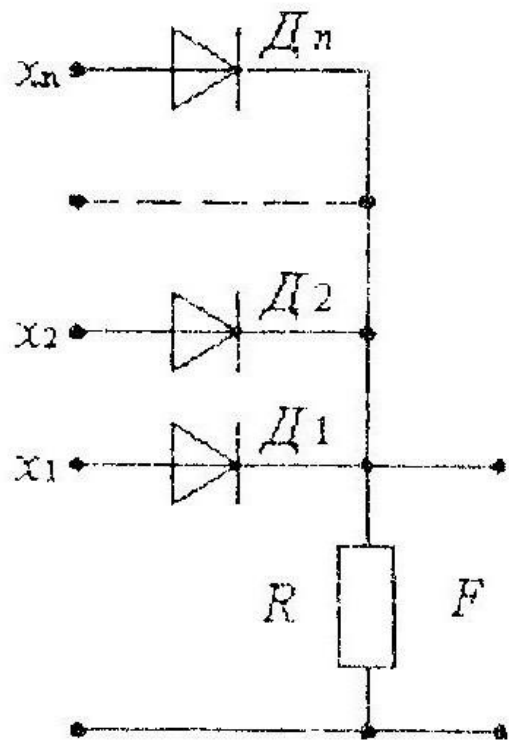


Логические элементы и их схемная реализация

Логический элемент «ИЛИ»

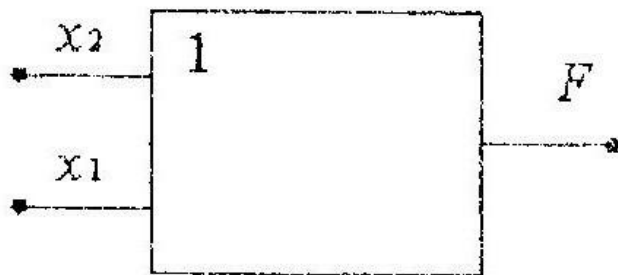

а





б

x_1	x_2	F
0	0	0
0	1	1
1	0	1
1	1	1

в



Логический элемент «И»

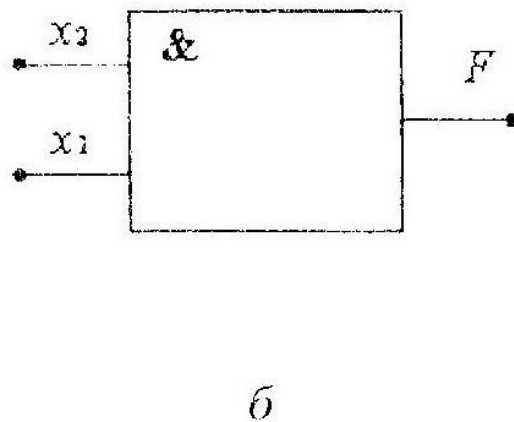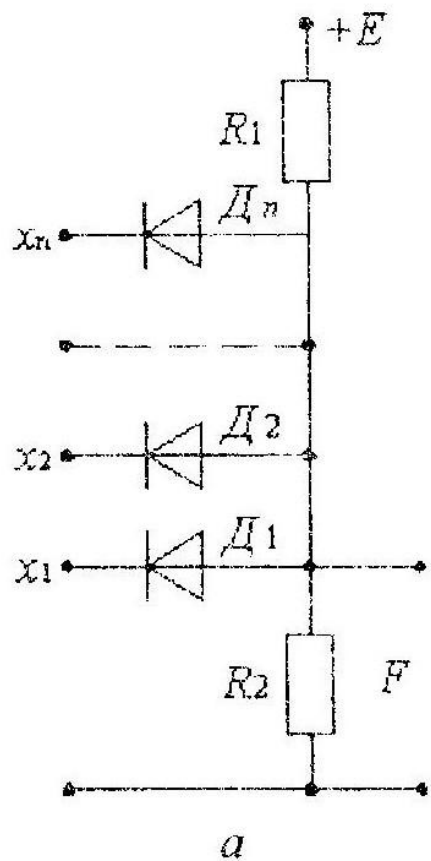

x_1	x_2	F
0	0	0
0	1	0
1	0	0
1	1	1

в


Логический элемент «НЕ»

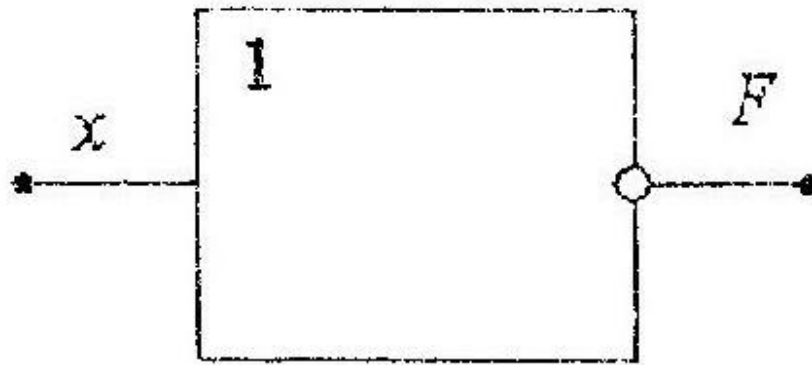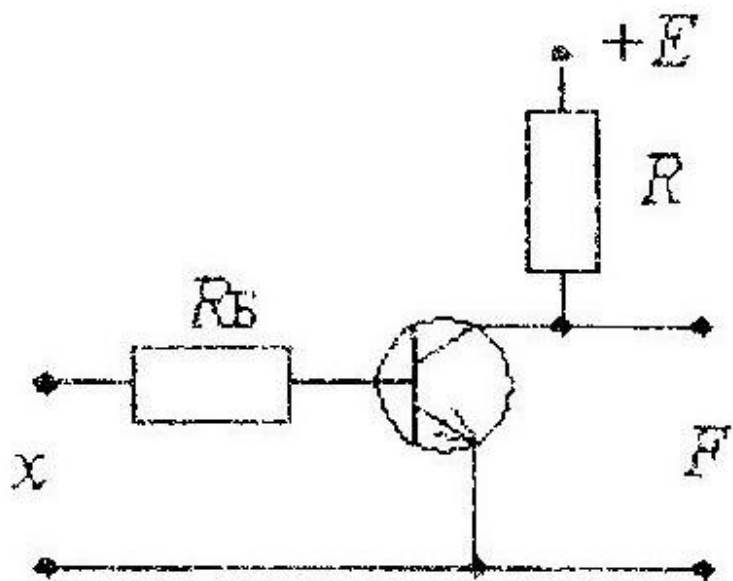


x_1	F
0	1
1	0

в

Логический элемент «ИЛИ-НЕ»

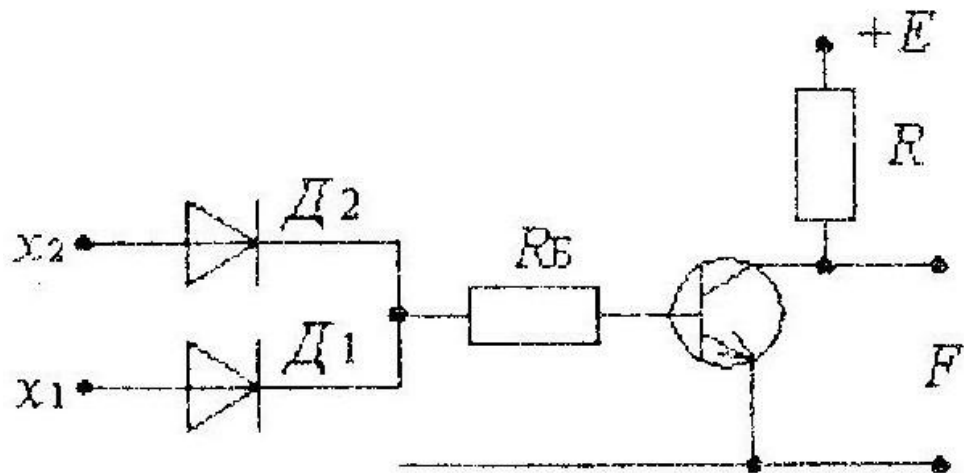

a

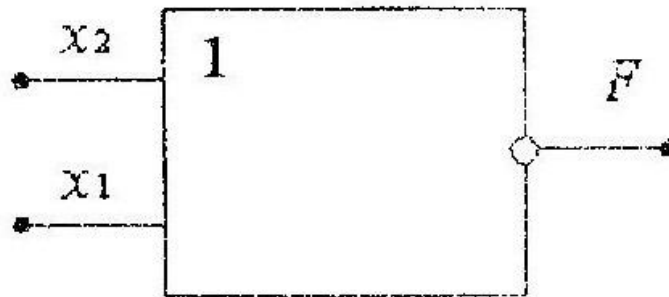


б


x_1	x_2	F
0	0	1
0	1	0
1	0	0
1	1	0

в

Логический элемент «И-НЕ»

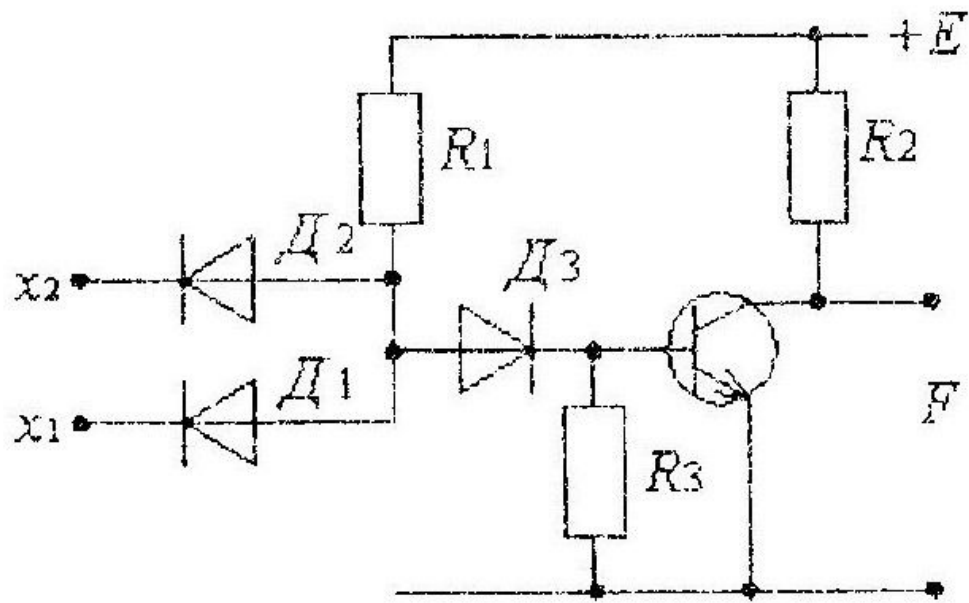

a

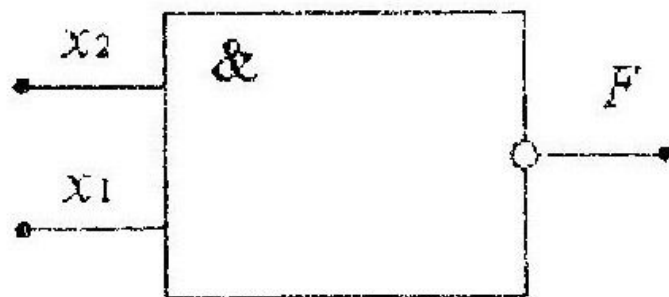

б

x_1	x_2	F
0	0	1
0	1	1
1	0	1
1	1	0

в