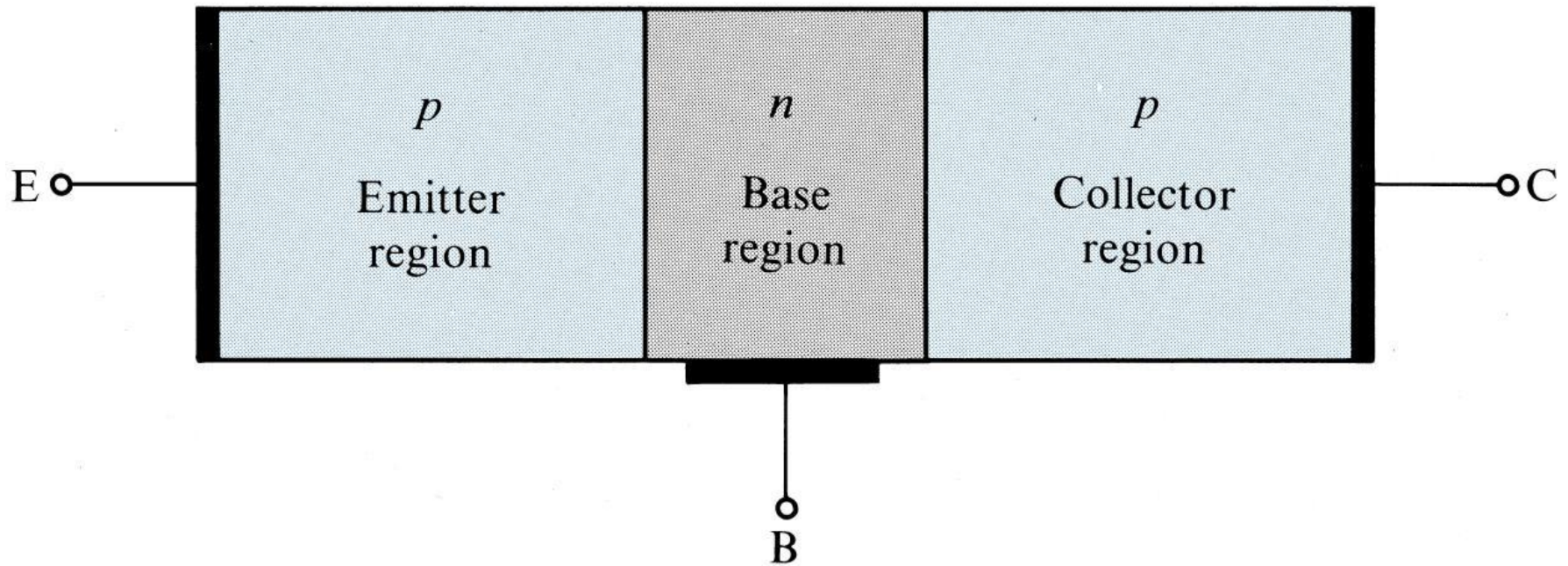


BJT


Bipolar Junction Transistor

- Widely used in amplifier circuits
- Formed by junction of 3 materials
- npn or pnp structure

pnp transistor




Operation of npn transistor

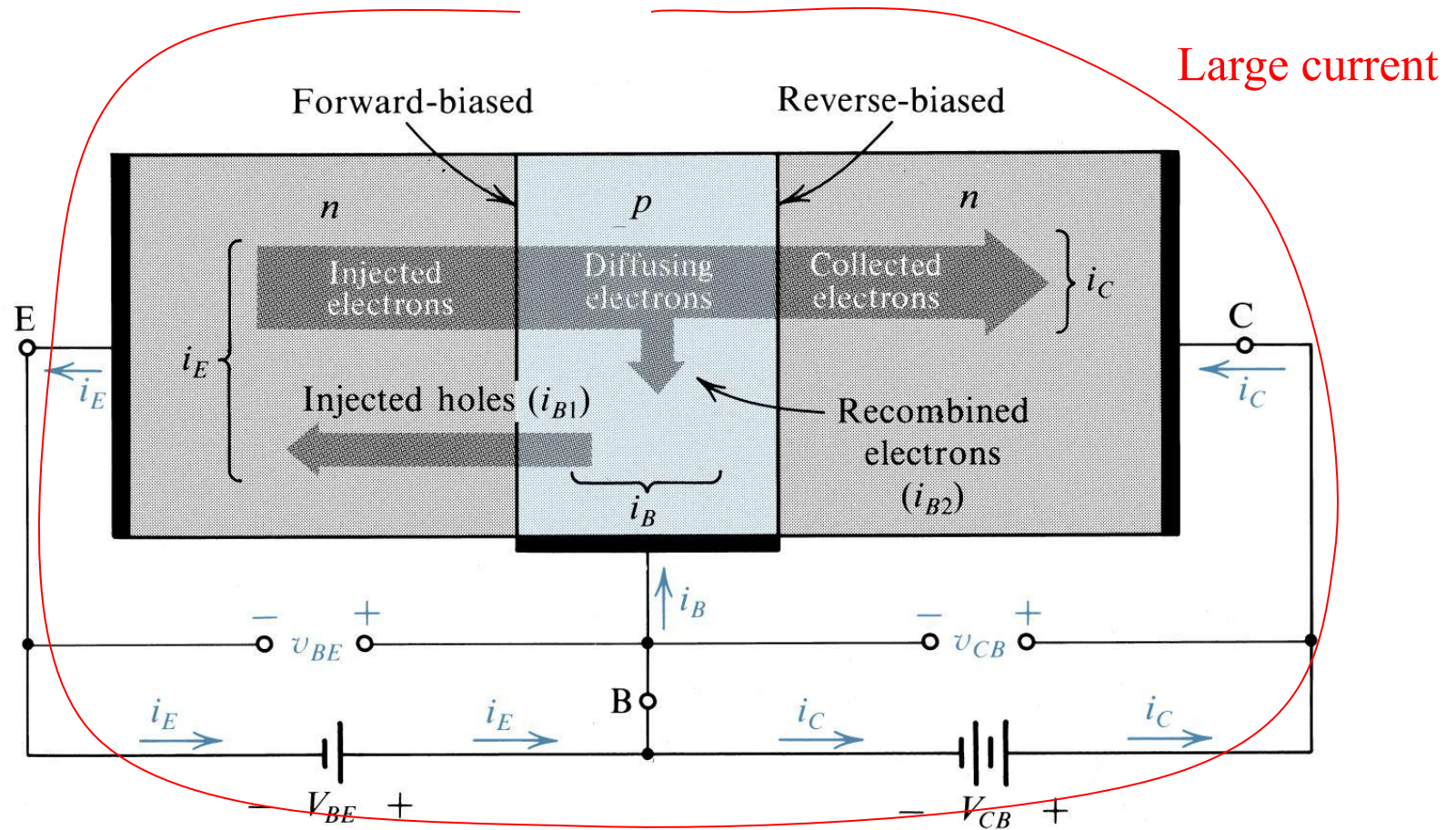


Modes of operation of a BJT transistor

<u>Mode</u>	<u>BE junction</u>	<u>BC junction</u>
cutoff	reverse biased	reverse biased
linear(active)	forward biased	reverse biased
saturation	forward biased	forward biased

Summary of *npn* transistor behavior

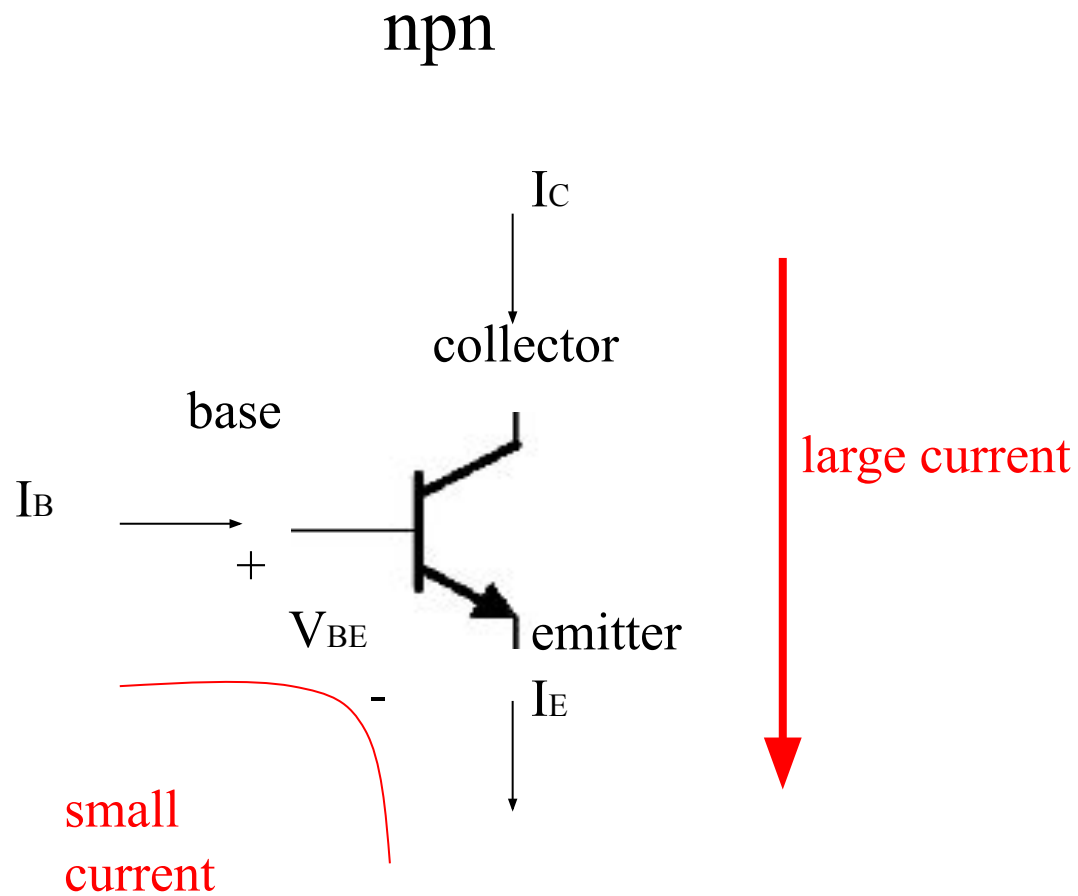

Summary of pnp transistor behavior

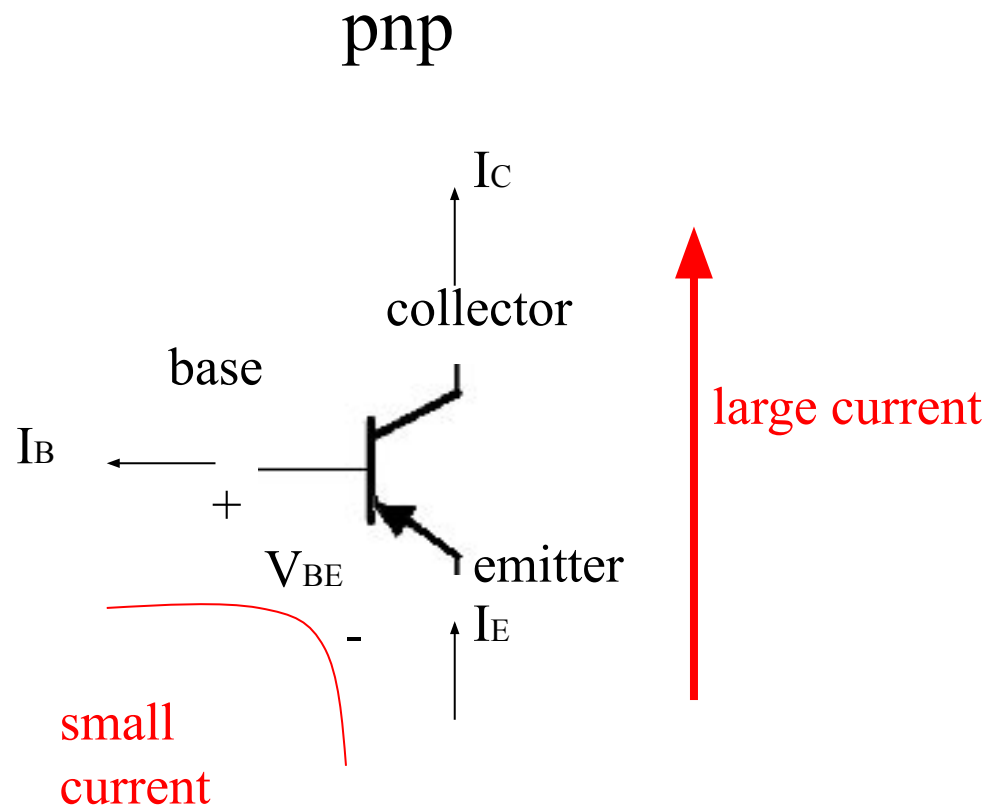

Summary of equations for a BJT

$$I_E \approx I_C$$


$$I_C = \beta I_B$$

β is the current gain of the transistor ≈ 100


$$V_{BE} = 0.7V(\text{nnp})$$

$$V_{BE} = -0.7V(\text{pnp})$$

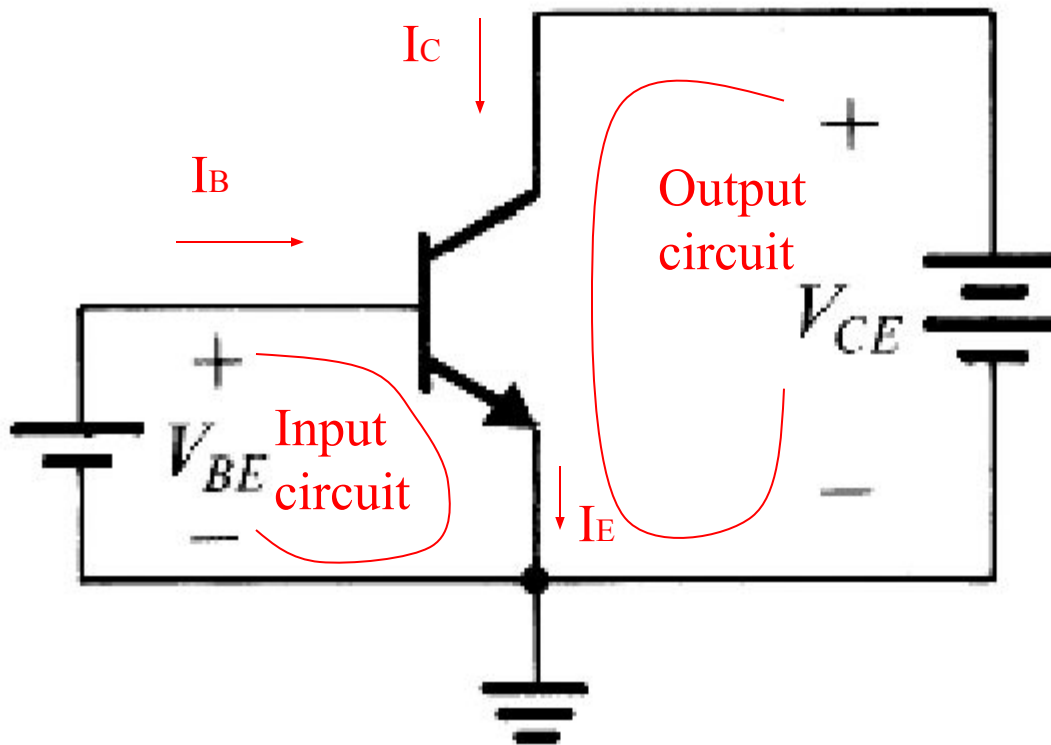Graphical representation of transistor characteristics




Input characteristics

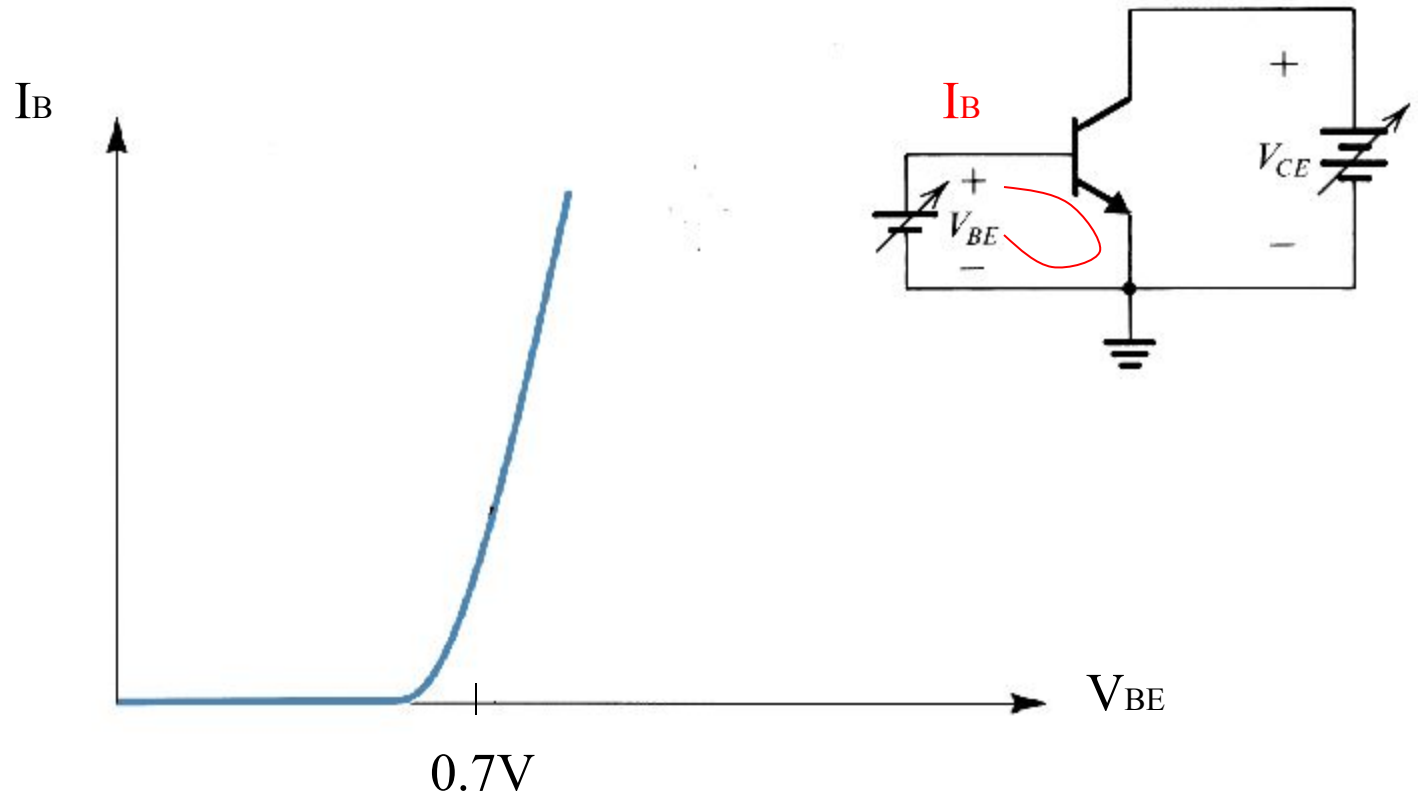

- Acts as a diode
- $V_{BE} \approx 0.7V$


Output characteristics

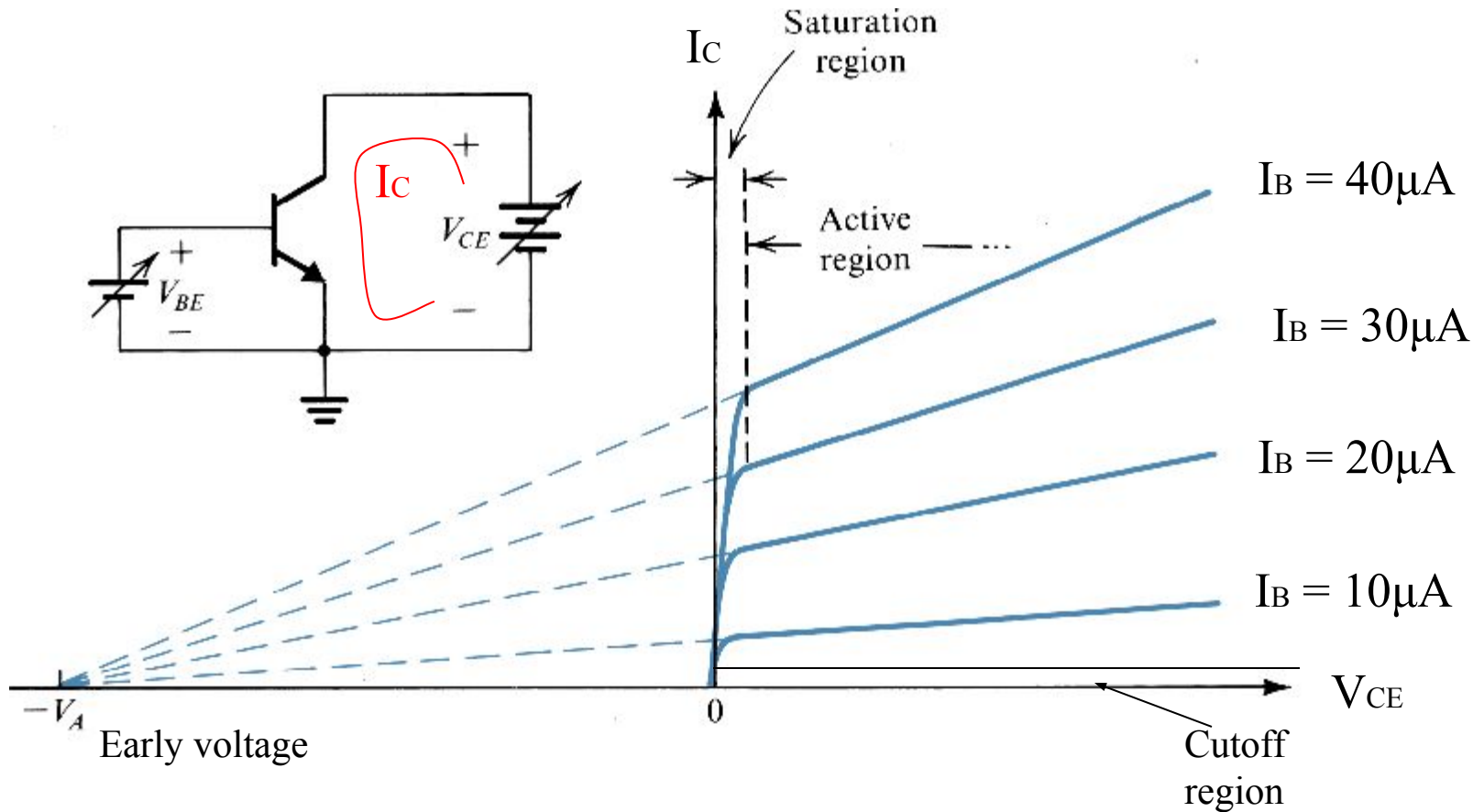


- At a fixed I_B , I_C is not dependent on V_{CE}
- Slope of output characteristics in linear region is near 0 (scale exaggerated)

Biasing a transistor

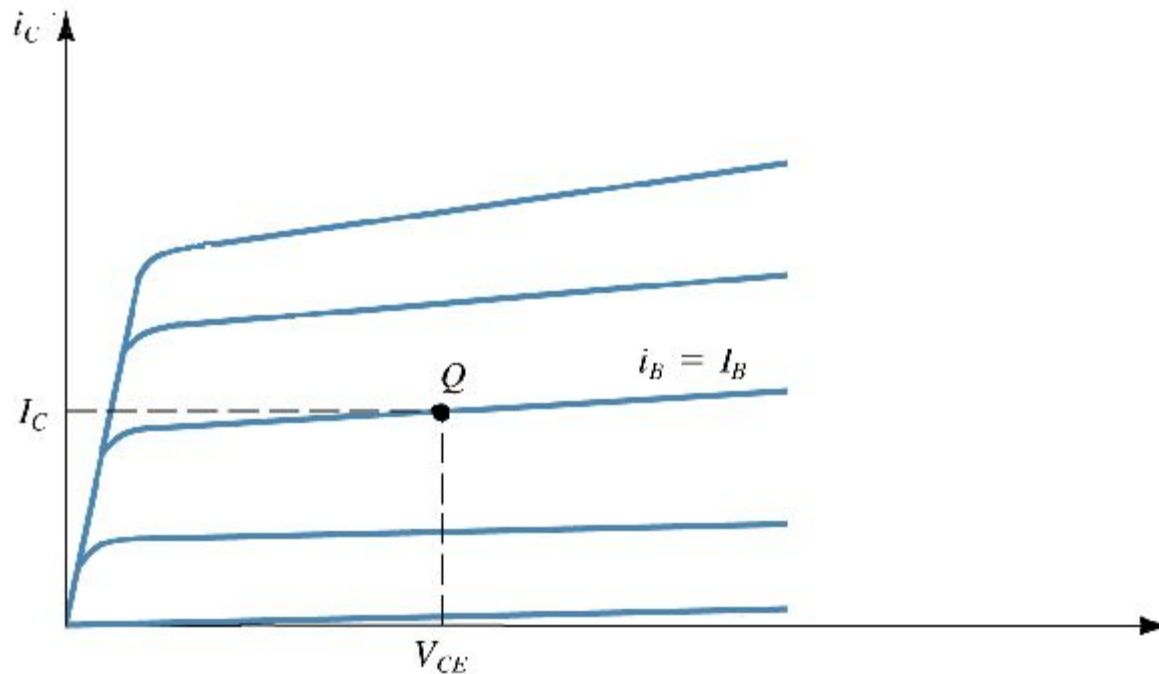- We must operate the transistor in the linear region.
- A transistor's operating point (Q-point) is defined by I_C , V_{CE} , and I_B .




Transconductance

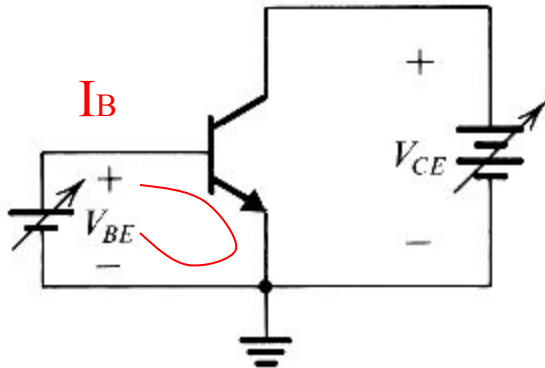

A small ac signal v_{be} is superimposed on the DC voltage V_{BE} . It gives rise to a collector signal current i_c , superimposed on the dc current I_C .

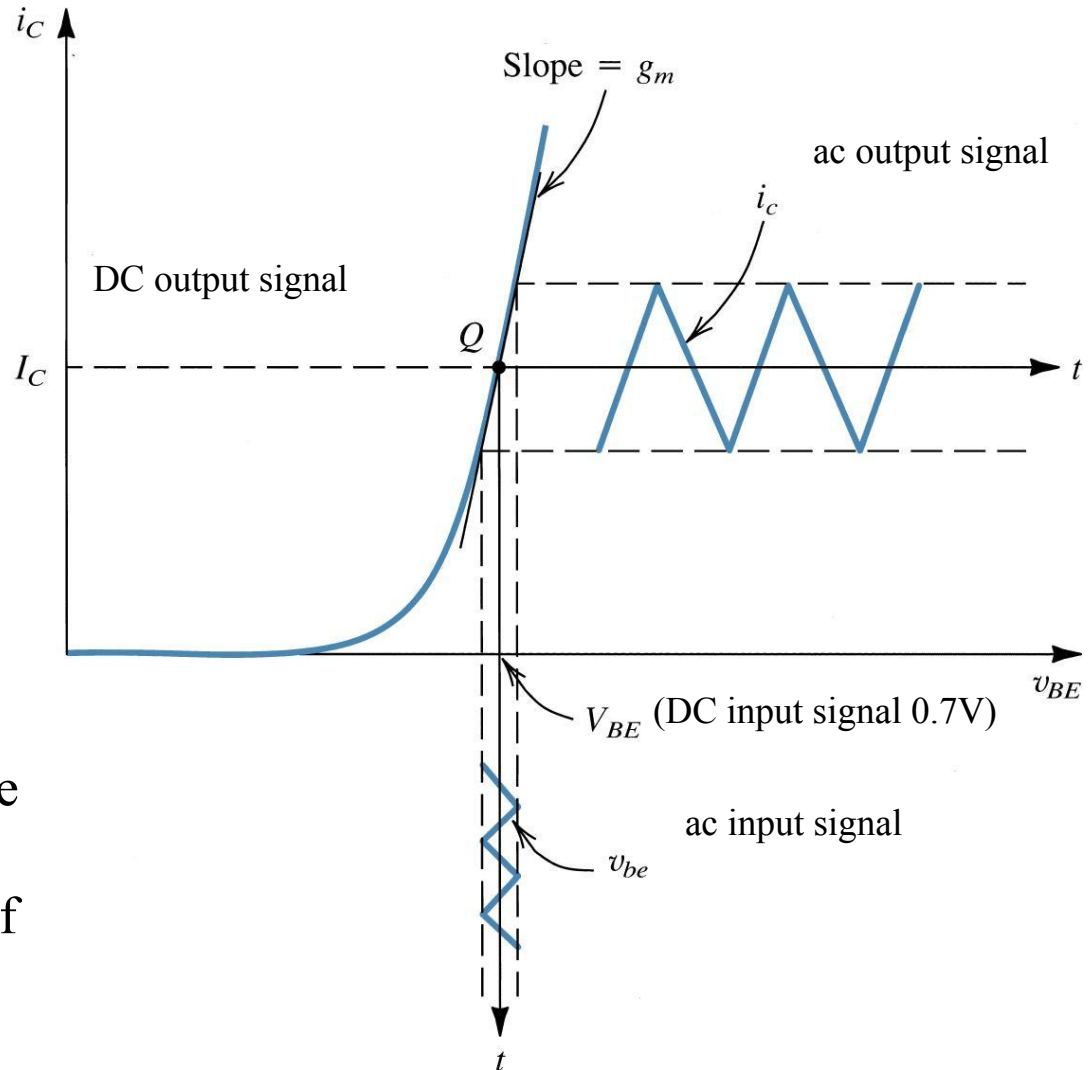The slope of the $i_c - v_{BE}$ curve at the bias point Q is the **transconductance** g_m : the amount of ac current produced by an ac voltage.



Analysis of transistor circuits at DC

For all circuits: assume transistor operates in linear region
write B-E voltage loop
write C-E voltage loop

Example -1


B-E junction acts like a diode

$$V_E = V_B - V_{BE} = 4V - 0.7V = 3.3V$$


$$I_E = (V_E - 0)/R_E = 3.3/3.3K = 1mA$$

$$I_C \approx I_E = 1mA$$
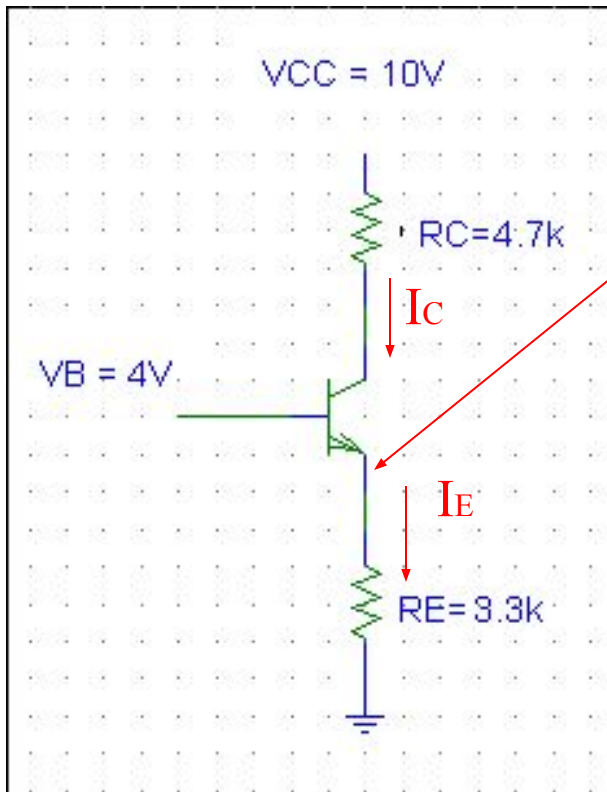
$$V_C = 10 - I_C R_C = 10 - 1(4.7) = 5.3V$$



Example-2

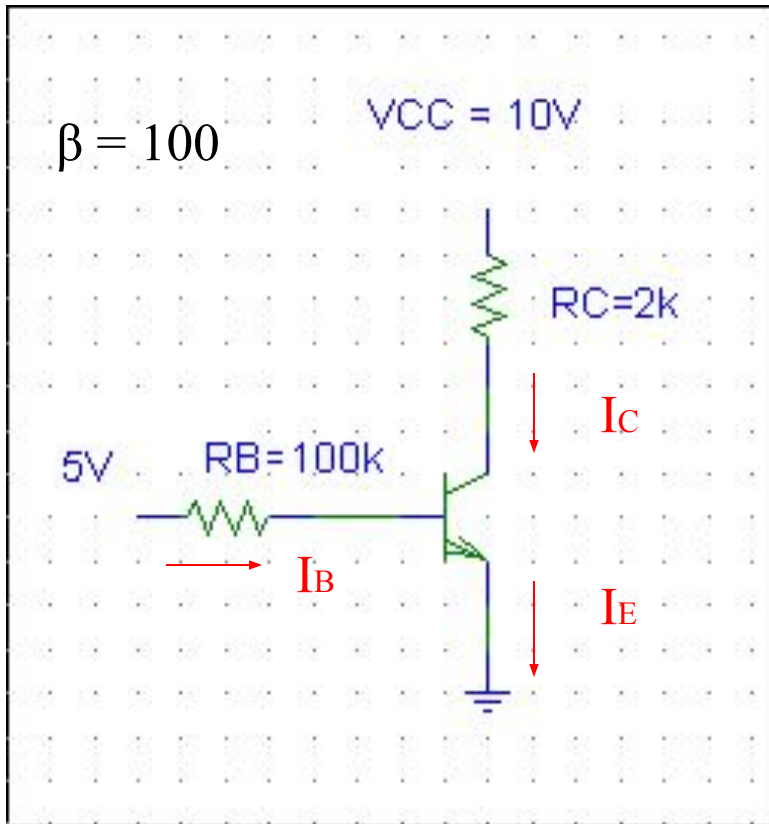

B-E Voltage loop


$$5 = I_B R_B + V_{BE}, \text{ solve for } I_B$$

$$I_B = (5 - V_{BE}) / R_B = (5 - 0.7) / 100k = 0.043mA$$

$$I_C = \beta I_B = (100) 0.043mA = 4.3mA$$

$$V_C = 10 - I_C R_C = 10 - 4.3(2) = 1.4V$$

Exercise-3

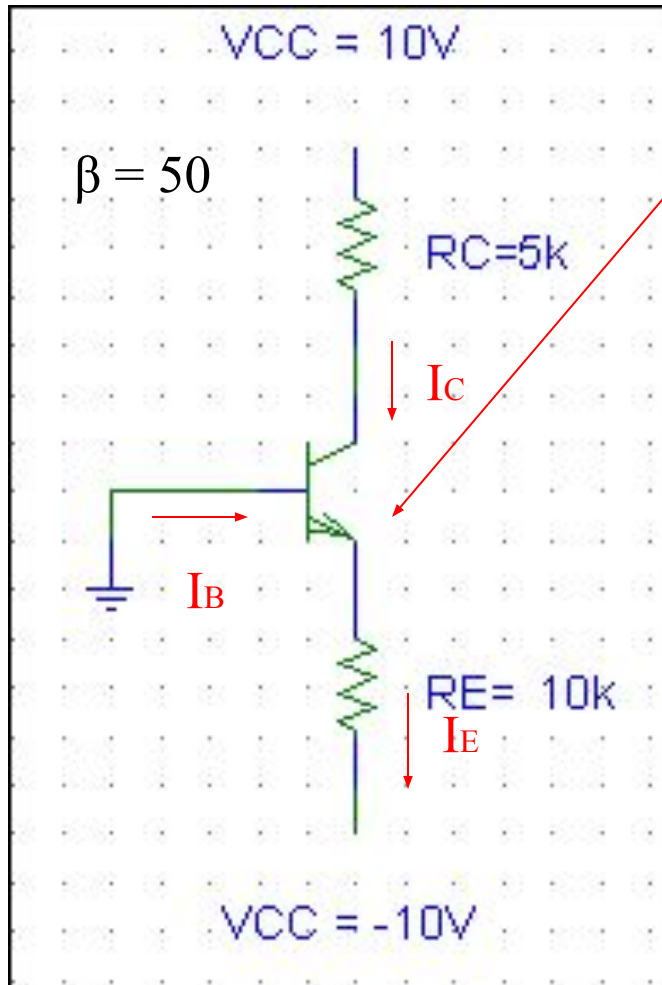

$$V_E = 0 - .7 = -0.7V$$

$$I_E = (V_E - -10)/R_E = (-.7 + 10)/10K = 0.93mA$$


$$I_C \approx I_E = 0.93mA$$

$$I_B = I_E/\beta = .93mA/50 = 18.6\mu A$$

$$V_C = 10 - I_C R_C = 10 - .93(5) = 5.35V$$

Prob.

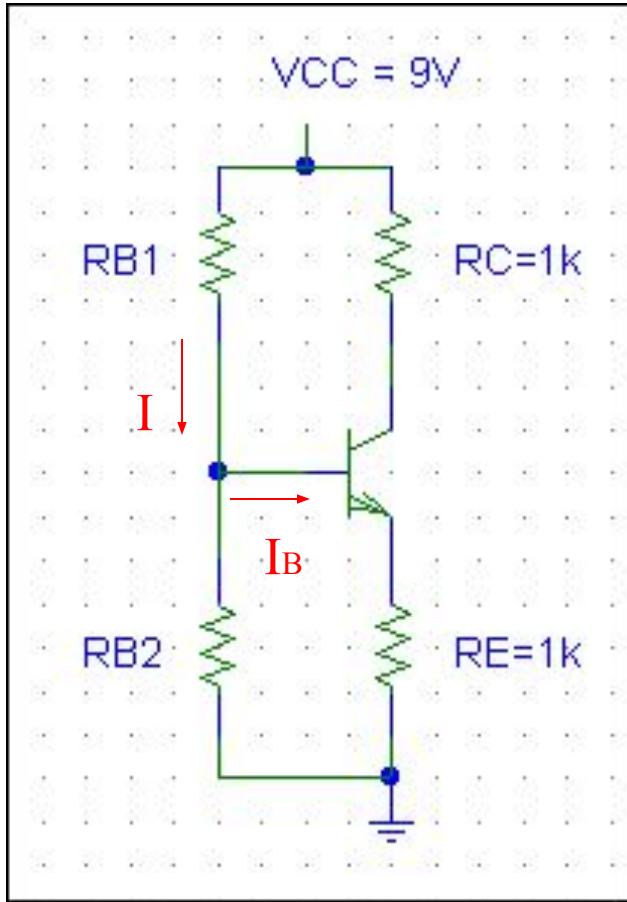- Use a voltage divider, R_{B1} and R_{B2} to bias V_B to avoid two power supplies.
- Make the current in the voltage divider about 10 times I_B to simplify the analysis. Use $V_B = 3V$ and $I = 0.2mA$.



(a) R_{B1} and R_{B2} form a voltage divider.

Assume $I \gg I_B$ $I = V_{CC}/(R_{B1} + R_{B2})$

$$.2mA = 9 / (R_{B1} + R_{B2})$$

AND


$$V_B = V_{CC} [R_{B2} / (R_{B1} + R_{B2})]$$

$$3 = 9 [R_{B2} / (R_{B1} + R_{B2})], \text{ Solve for } R_{B1} \text{ and } R_{B2}.$$

$$R_{B1} = 30K\Omega, \text{ and } R_{B2} = 15K\Omega.$$

Prob.


Find the operating point

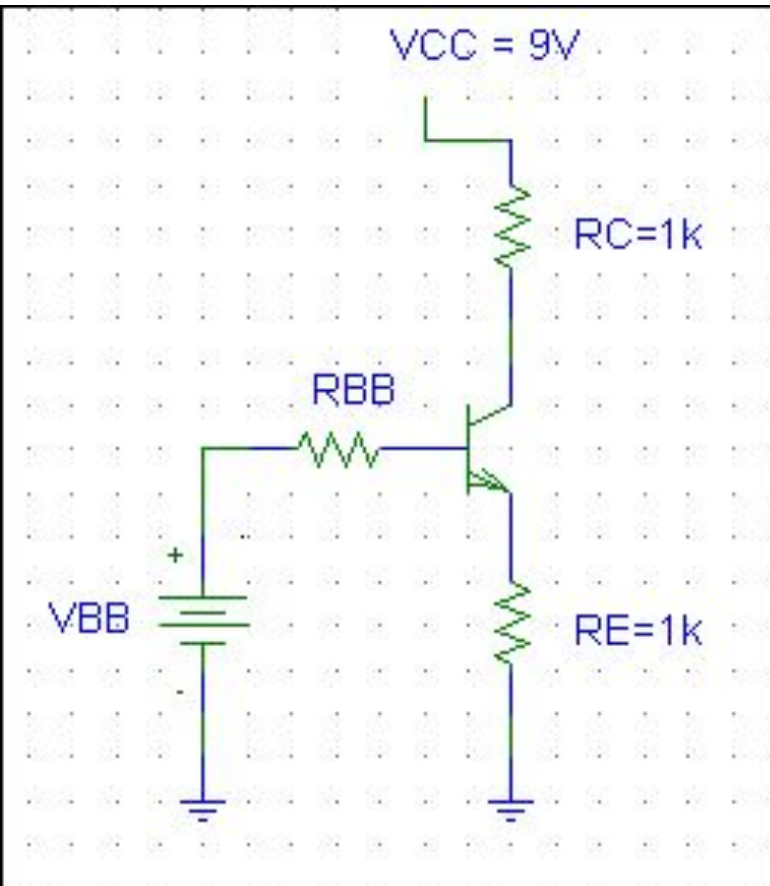

- Use the Thevenin equivalent circuit for the base
- Makes the circuit simpler
- $V_{BB} = V_B = 3V$
- R_{BB} is measured with voltage sources grounded
- $R_{BB} = R_{B1} \parallel R_{B2} = 30K\Omega \parallel 15K\Omega = 10K\Omega$

Prob.

Write B-E loop and C-E loop

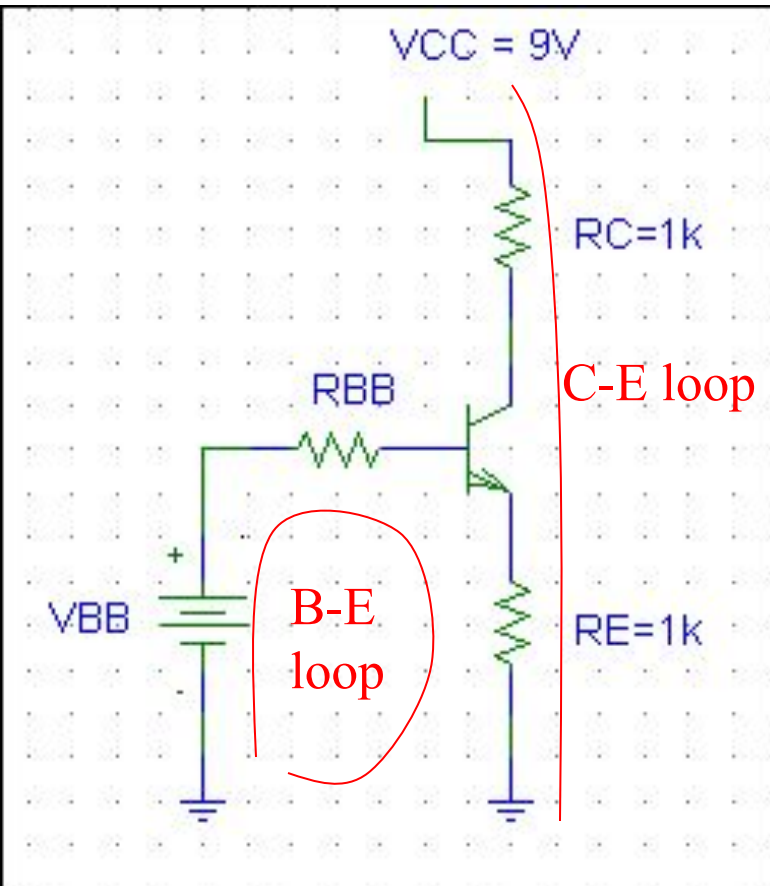

B-E loop

$$V_{BB} = I_B R_{BB} + V_{BE} + I_E R_E$$

$$I_E = 2.09 \text{ mA}$$

C-E loop


$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$V_{CE} = 4.8 \text{ V}$$

This is how all DC circuits are analyzed and designed!

Exercise-4

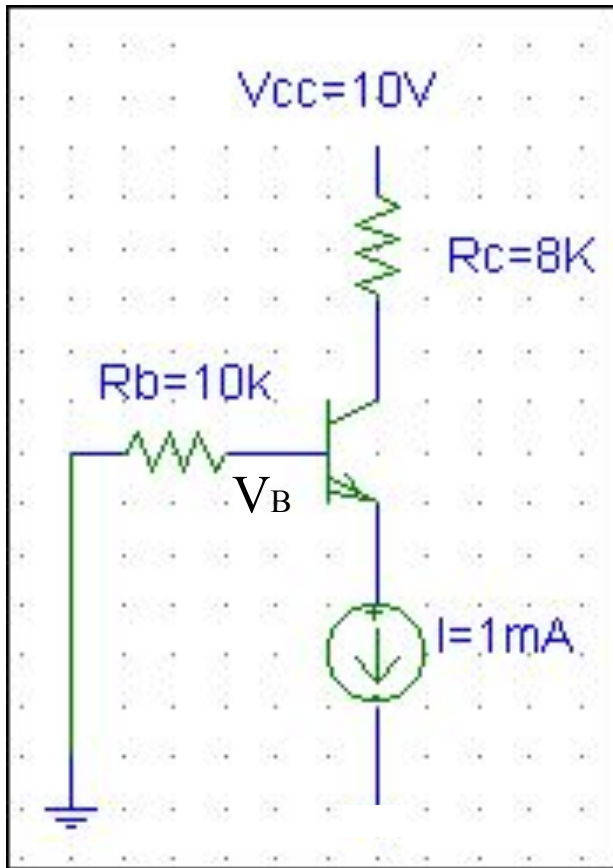(a) Find V_C , V_B , and V_E , given: $\beta = 100$, $V_A = 100V$



$$I_E = 1 \text{ mA}$$


$$I_B \approx I_E / \beta = 0.01 \text{ mA}$$

$$V_B = 0 - I_B 10K = -0.1V$$

$$V_E = V_B - V_{BE} = -0.1 - 0.7 = -0.8V$$

$$V_C = 10V - I_C 8K = 10 - 1(8) = 2V$$

Example-5

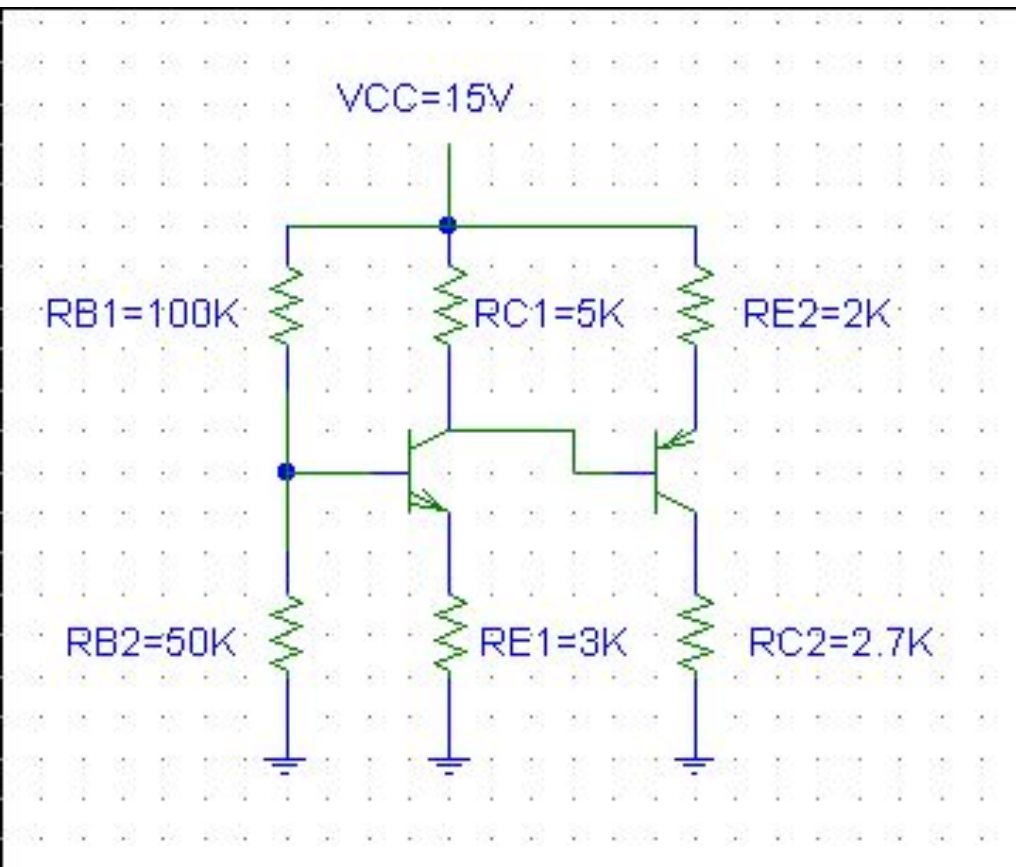

- 2-stage amplifier, 1st stage has an npn transistor; 2nd stage has an pnp transistor.

$$I_C = \beta I_B$$

$$I_C \approx I_E$$


$$V_{BE} = 0.7_{(nnp)} = -0.7_{(pnp)}$$

$$\beta = 100$$

Find I_{C1} , I_{C2} , V_{CE1} , V_{CE2}

- Use Thevenin circuits.

Example -5

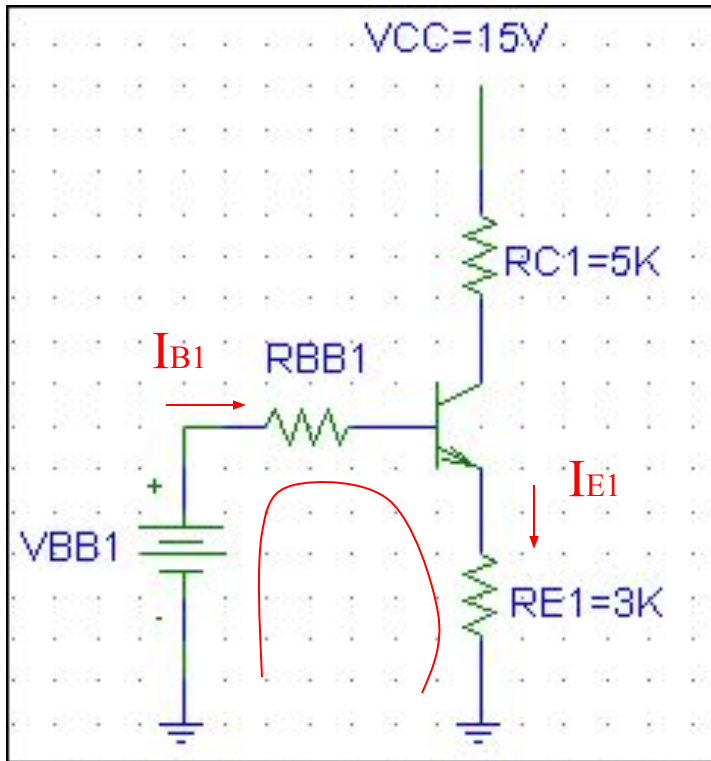

- $R_{BB1} = R_{B1} || R_{B2} = 33K$

- $V_{BB1} = V_{CC} [R_{B2} / (R_{B1} + R_{B2})]$

$$V_{BB1} = 15 [50K / 150K] = 5V$$

Stage 1

- B-E loop


$$V_{BB1} = I_{B1} R_{BB1} + V_{BE} + I_{E1} R_{E1}$$

Use $I_{B1} \approx I_{E1} / \beta$

$$5 = I_{E1} 33K / 100 + .7 + I_{E1} 3K$$

$$I_{E1} = 1.3mA$$

Example -5

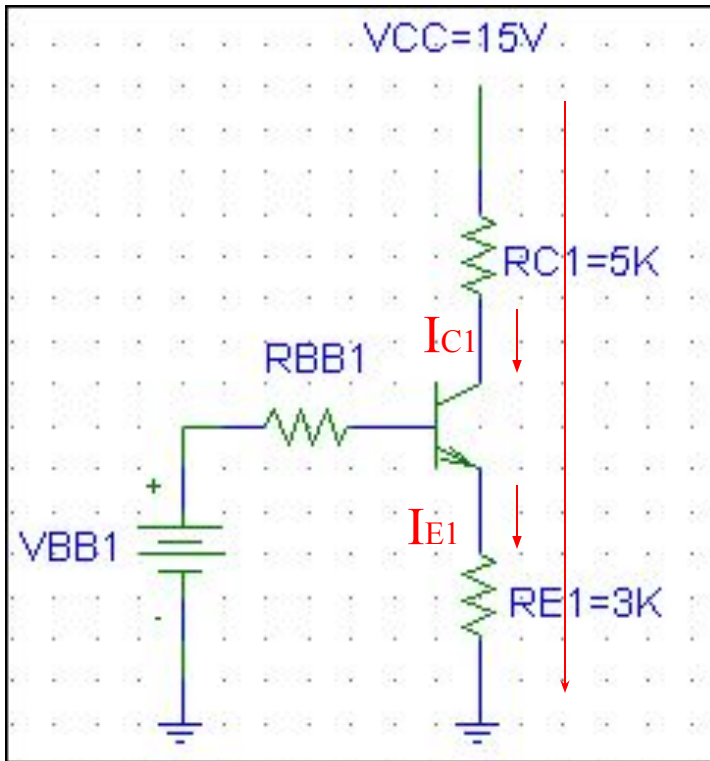

C-E loop


neglect I_{B2} because it is $I_{B2} \ll I_{C1}$

$$V_{CC} = I_{C1}R_{C1} + V_{CE1} + I_{E1}R_{E1}$$

$$15 = 1.3(5) + V_{CE1} + 1.3(3)$$

$$V_{CE1} = 4.87V$$

Example-5

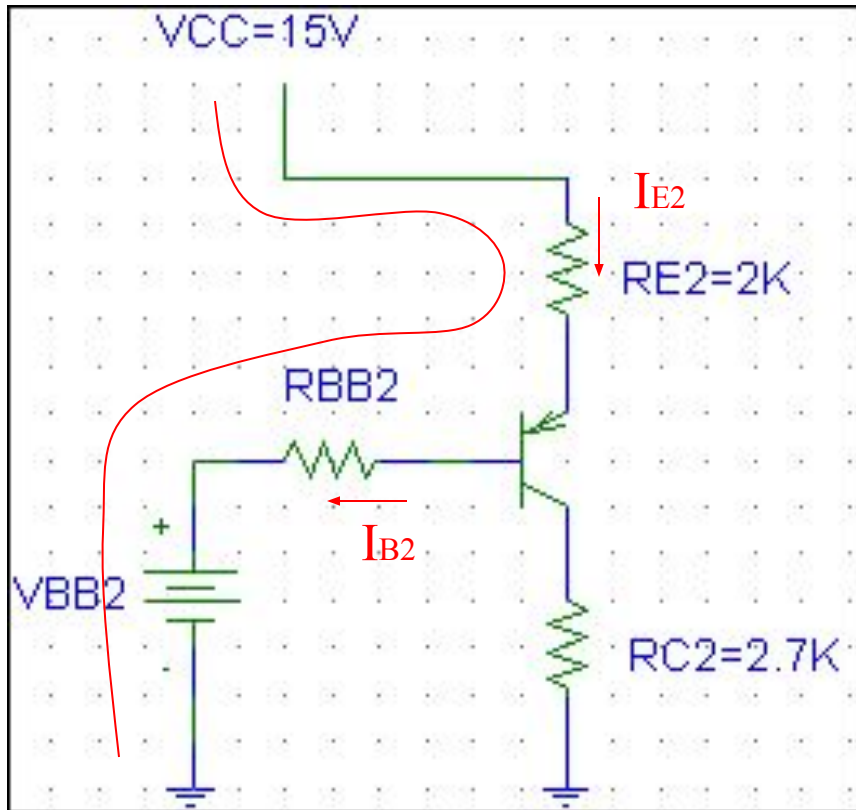

Stage 2

•B-E loop


$$V_{CC} = I_{E2}R_{E2} + V_{EB} + I_{B2}R_{BB2} + V_{BB2}$$

$$15 = I_{E2}(2K) + .7 + I_{B2}(5K) + 4.87 + 1.3(3)$$

Use $I_{B2} \approx I_{E2} / \beta$, solve for I_{E2}

$$I_{E2} = 2.8\text{mA}$$

Example-5

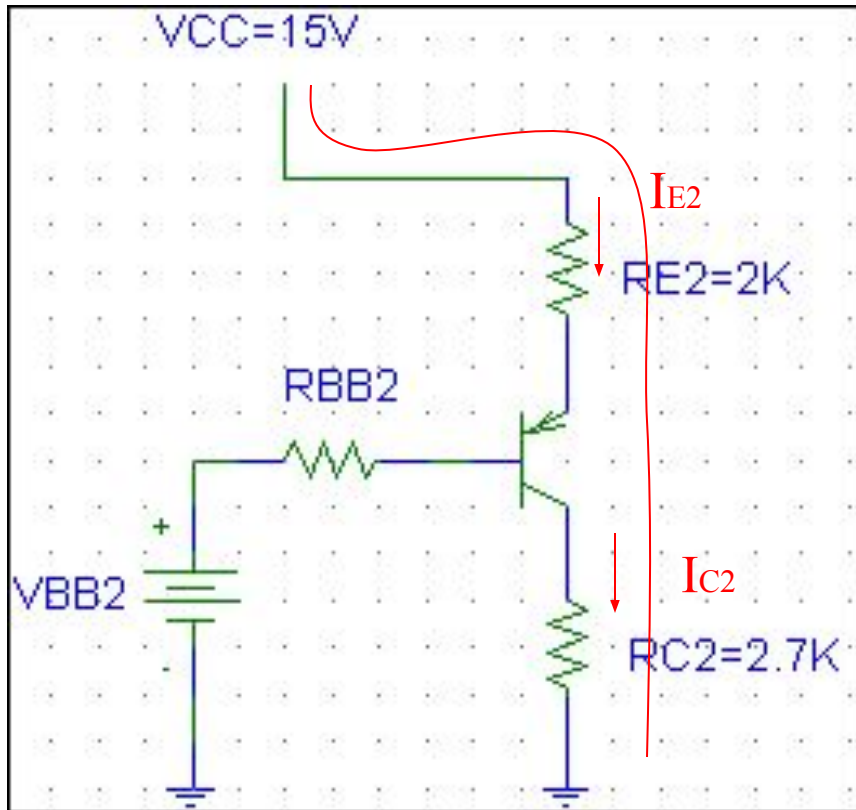

Stage 2

•C-E loop

$$V_{CC} = I_{E2}R_{E2} + V_{EC2} + I_{C2}R_{C2}$$

$$15 = 2.8(2) + V_{EC2} + 2.8(2.7)$$


solve for V_{EC2}

$$V_{CE2} = 1.84V$$

Summary of DC problem

- Bias transistors so that they operate in the linear region B-E junction forward biased, C-E junction reversed biased
- Use $V_{BE} = 0.7$ (npn), $I_C \approx I_E$, $I_C = \beta I_B$
- Represent base portion of circuit by the Thevenin circuit
- Write B-E, and C-E voltage loops.
- For analysis, solve for I_C , and V_{CE} .
- For design, solve for resistor values (I_C and V_{CE} specified).


Summary of npn transistor behavior

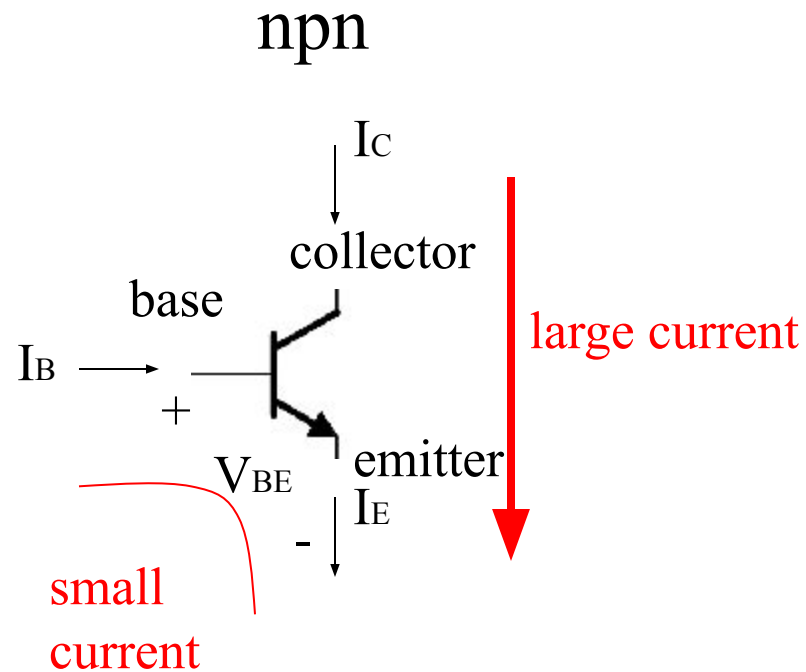

Transistor as an amplifier


- Transistor circuits are analyzed and designed in terms of DC and ac versions of the same circuit.
- An ac signal is usually superimposed on the DC circuit.
- The location of the operating point (values of I_C and V_{CE}) of the transistor affects the ac operation of the circuit.
- There are at least two ac parameters determined from DC quantities.

Transconductance

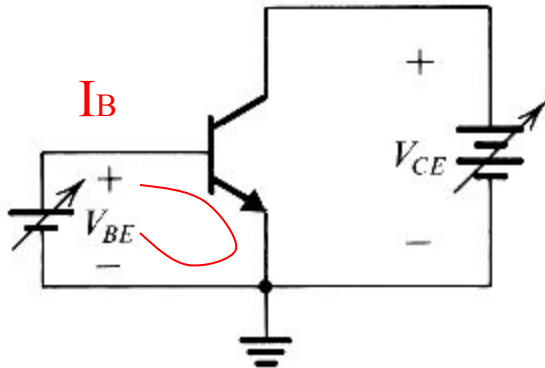

A small ac signal v_{be} is superimposed on the DC voltage V_{BE} . It gives rise to a collector signal current i_c , superimposed on the dc current I_C .

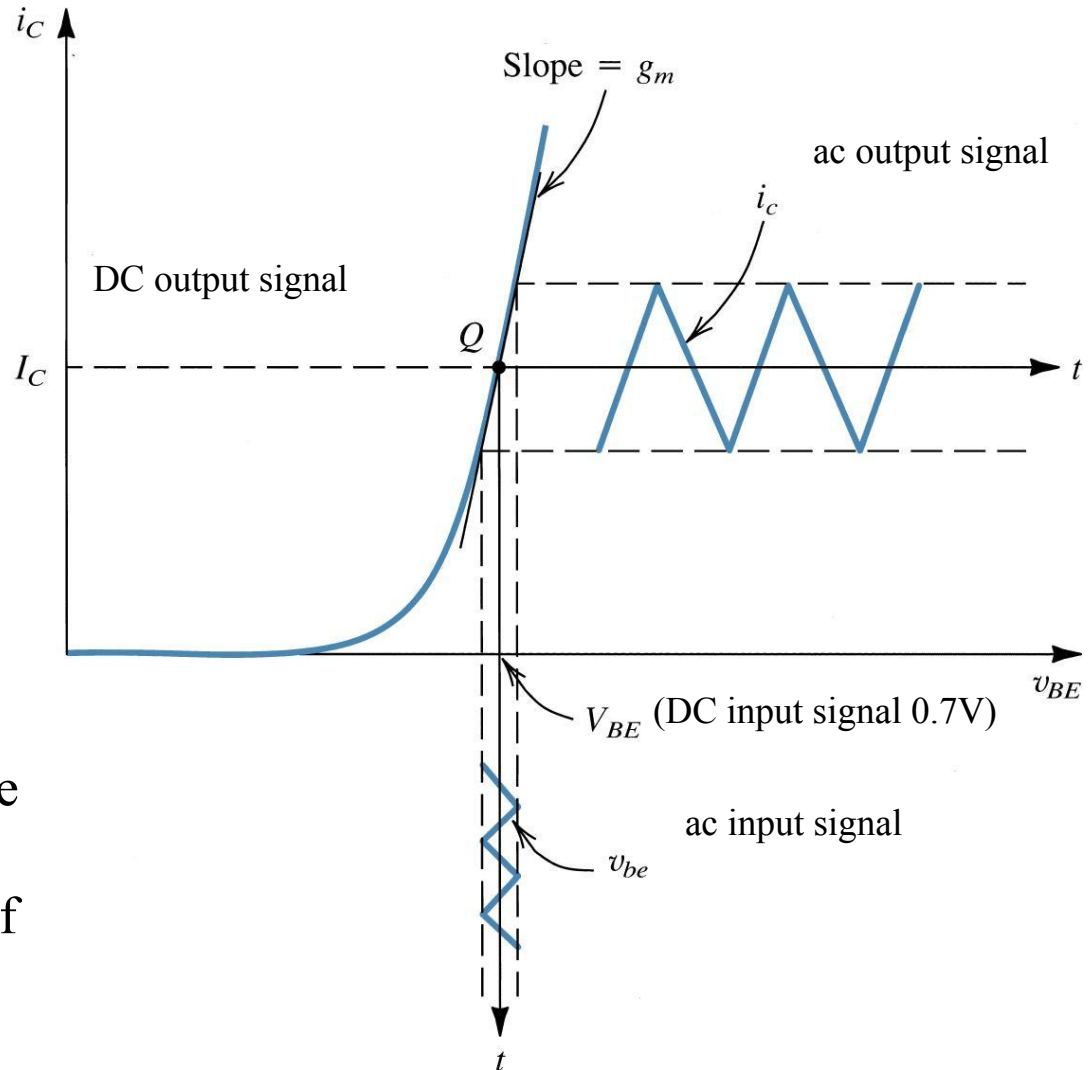The slope of the $i_c - v_{BE}$ curve at the bias point Q is the **transconductance** g_m : the amount of ac current produced by an ac voltage.



Transconductance


Transconductance = slope at Q point

$$g_m = \left. di_c / dv_{BE} \right|_{i_c = I_{CQ}}$$


where $I_C = I_S [\exp(-V_{BE}/V_T) - 1]$; the equation for a diode.

$$g_m = I_S \exp(-V_{BE}/V_T) (1/V_T)$$

$$g_m \approx I_C / V_T \text{ (A/V)}$$

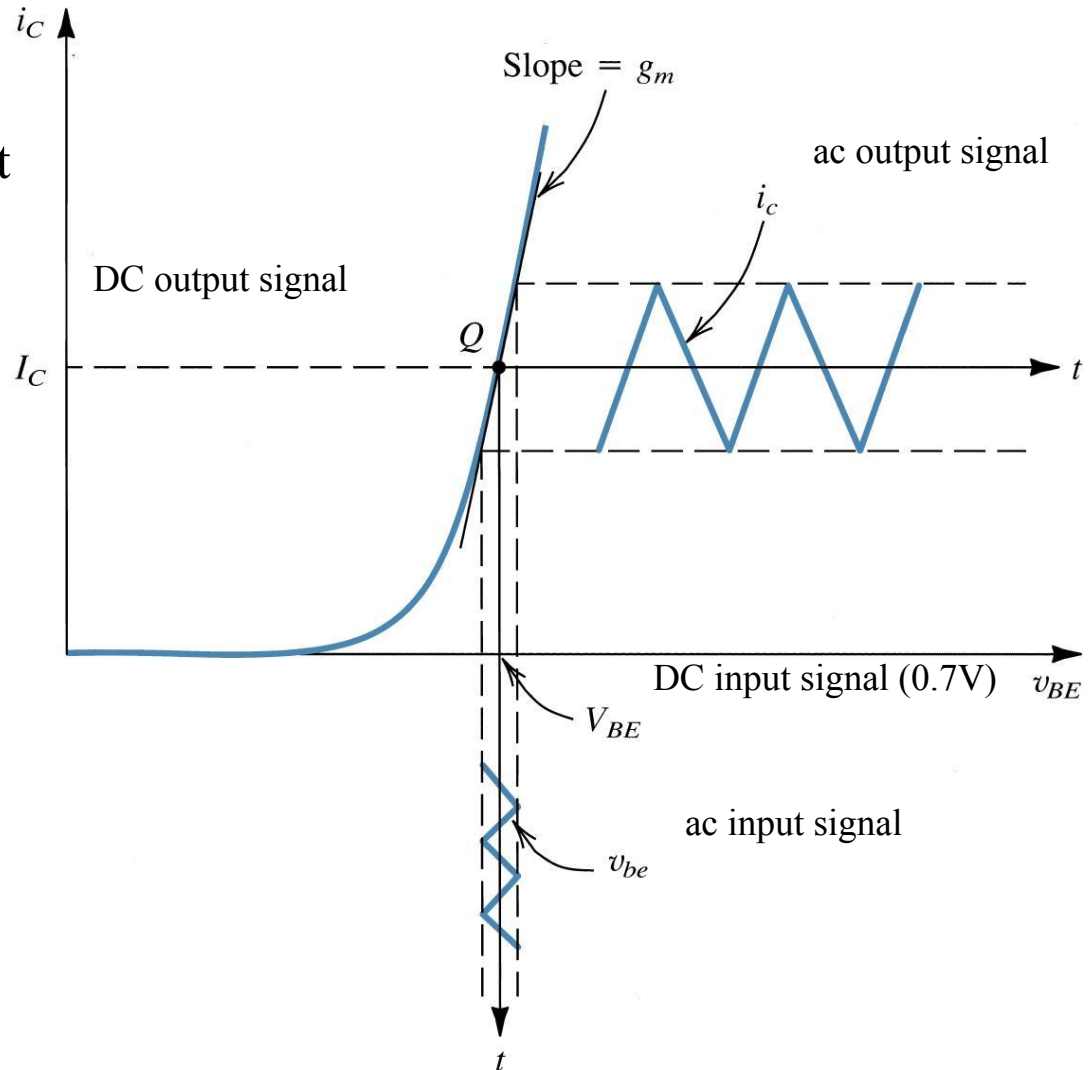

ac input resistance of transistor

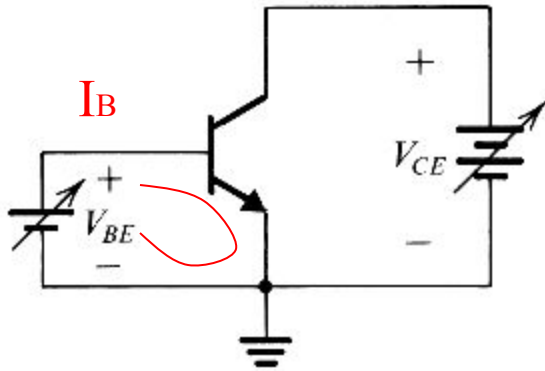


ac input resistance $\propto 1/\text{slope at } Q$
point


$$r_{\pi} = \left. \frac{dv_{BE}}{di_b} \right|_{i_c = I_{CQ}}$$

$$r_{\pi} \approx V_T / I_B$$

$$r_e \approx V_T / I_E$$

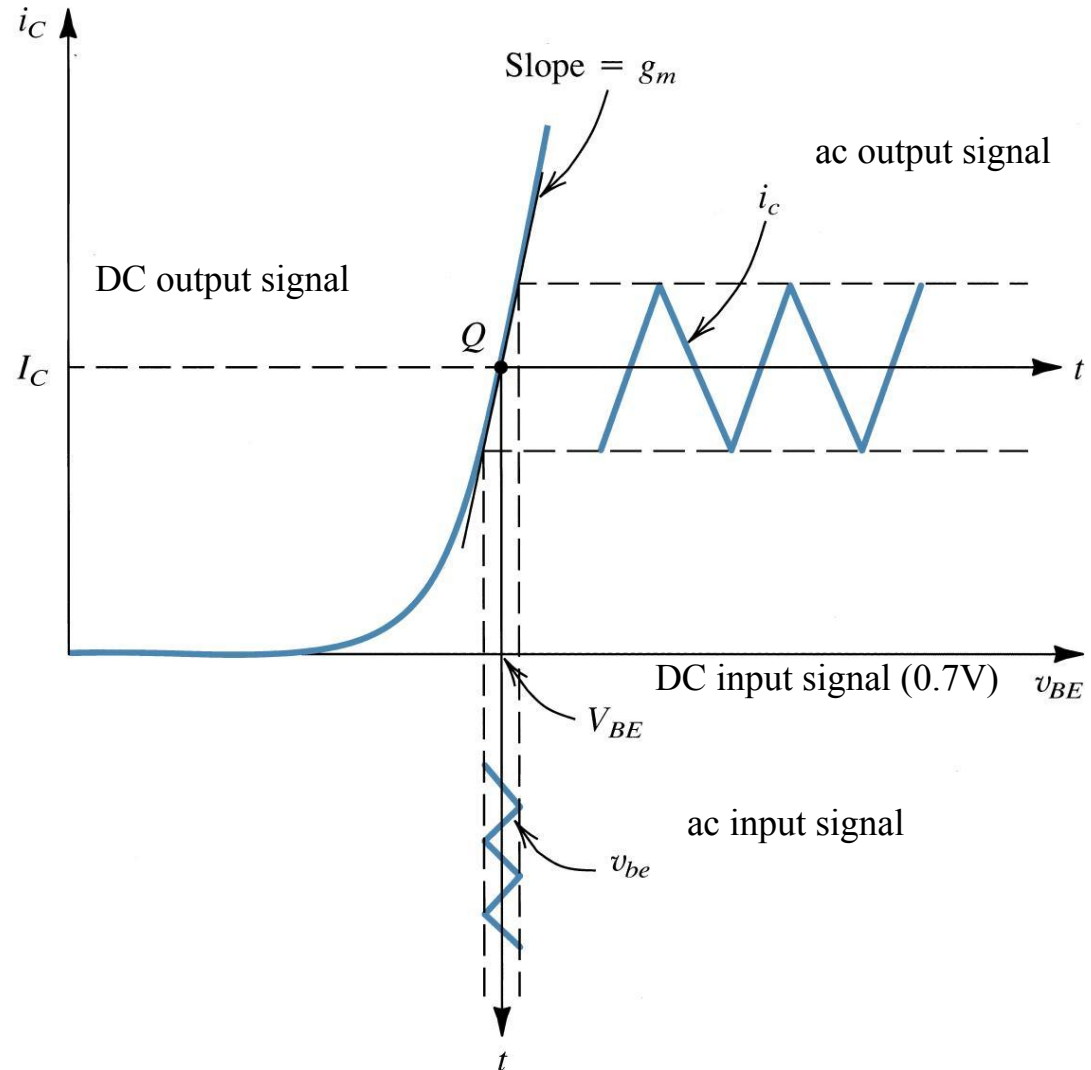

Small-signal equivalent circuit models

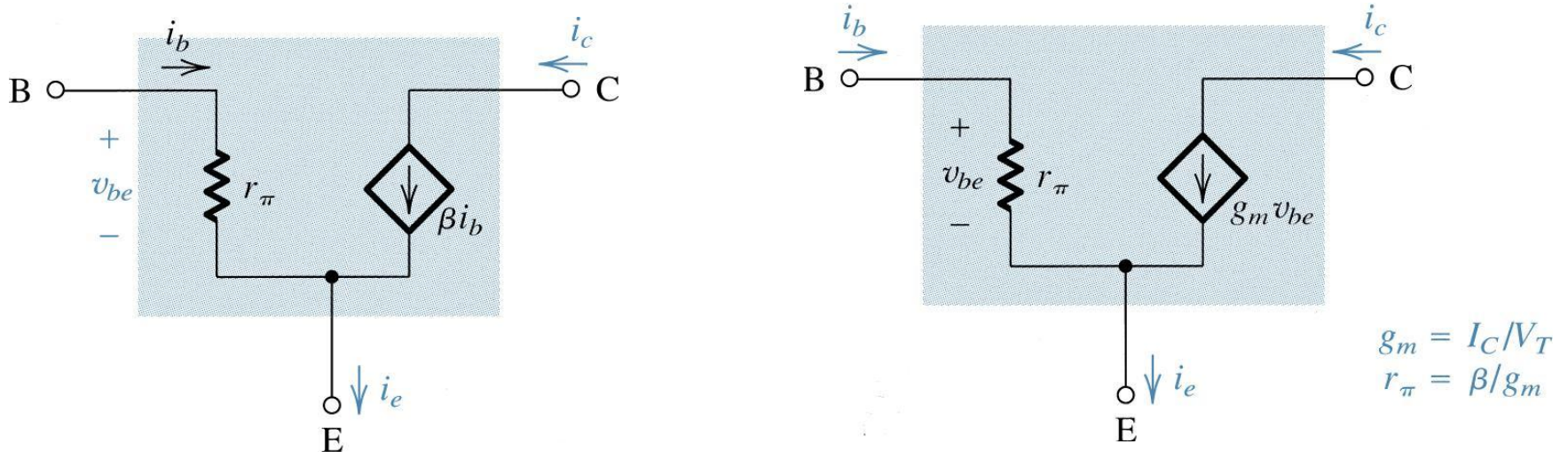

- ac model
- Hybrid- π model
- They are equivalent
- Works in linear region only

Steps to analyze a transistor circuit

1 DC problem

Set ac sources to zero, solve for DC quantities, I_C and V_{CE} .

2 Determine ac quantities from DC parameters


Find g_m , r_π , and r_e .

3 ac problem

Set DC sources to zero, replace transistor by hybrid- π model, find ac quantities, R_{in} , R_{out} , A_v , and A_i .

Example-6

Find v_{out}/v_{in} , ($\beta = 100$)

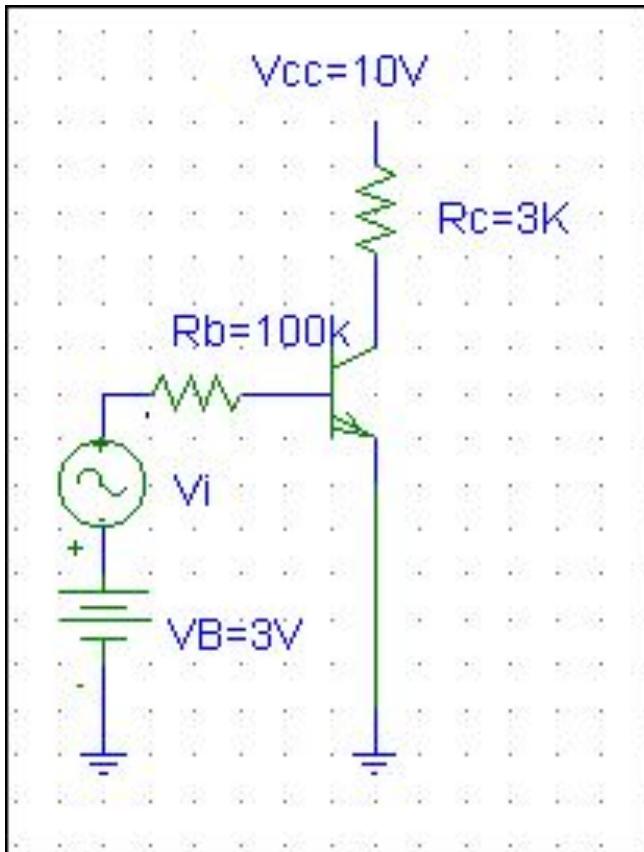

DC problem

Short v_i , determine I_C and V_{CE}

B-E voltage loop

$$3 = I_B R_B + V_{BE}$$

$$I_B = (3 - 0.7)/R_B = 0.023mA$$

C-E voltage loop


$$V_{CE} = 10 - I_C R_C$$

$$V_{CE} = 10 - (2.3)(3)$$

$$V_{CE} = 3.1V$$

Q point: $V_{CE} = 3.1V$, $I_C = 2.3mA$

Example -6

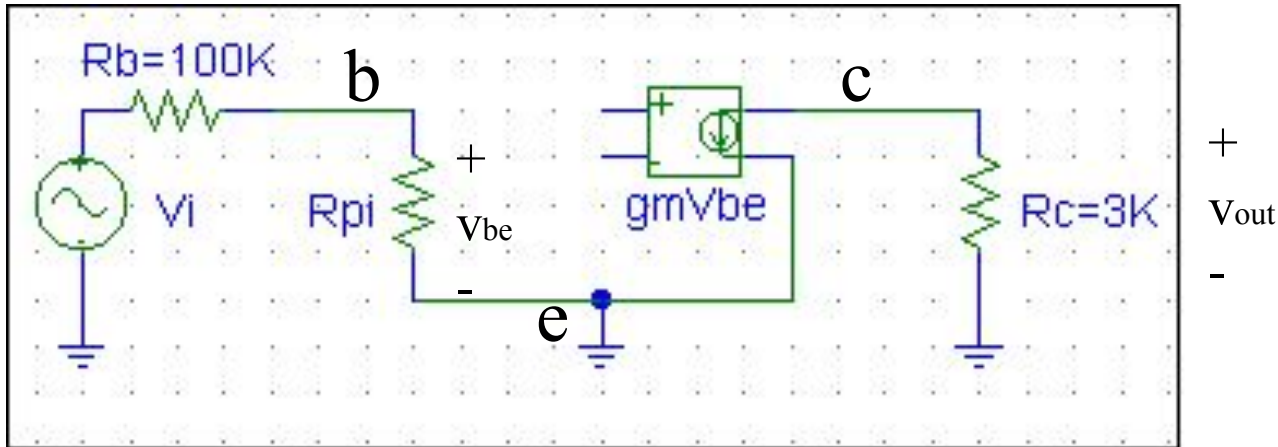

ac problem

Short DC sources, input and output circuits are separate, only coupled mathematically

$$g_m = I_C / V_T = 2.3\text{mA} / 25\text{mV} = 92\text{mA/V}$$

$$r_\pi = V_T / I_B = 25\text{mV} / .023\text{mA} = 1.1K$$

$$V_{be} = V_i [r_\pi / (100K + r_\pi)] = 0.011V_i$$

$$V_{out} = -g_m V_{be} R_c$$

$$V_{out} = -92 (0.011V_i) 3K$$

$$V_{out}/V_i = -3.04$$

Exercise-7

Find g_m , r_π , and r_o , given: $\beta = 100$, $V_A = 100V$, $I_C = 1 \text{ mA}$

$$g_m = I_C / V_T = 1 \text{ mA} / 25 \text{ mV} = 40 \text{ mA/V}$$

$$r_\pi = V_T / I_B = 25 \text{ mV} / .01 \text{ mA} = 2.5 \text{ K}$$

r_o = output resistance of transistor

$r_o = 1 / \text{slope of transistor output characteristics}$

$$r_o = |V_A / I_C| = 100 \text{ K}$$

Summary of transistor analysis


- Transistor circuits are analyzed and designed in terms of DC and ac versions of the same circuit.
- An ac signal is usually superimposed on the DC circuit.
- The location of the operating point (values of I_C and V_{CE}) of the transistor affects the ac operation of the circuit.
- There are at least two ac parameters determined from DC quantities.

Steps to analyze a transistor circuit


1 DC Analysis Set ac sources to zero, solve for DC quantities, I_c and V_{CE} .

2 Determine ac quantities from DC parameters
Find g_m , r_π , and r_o .

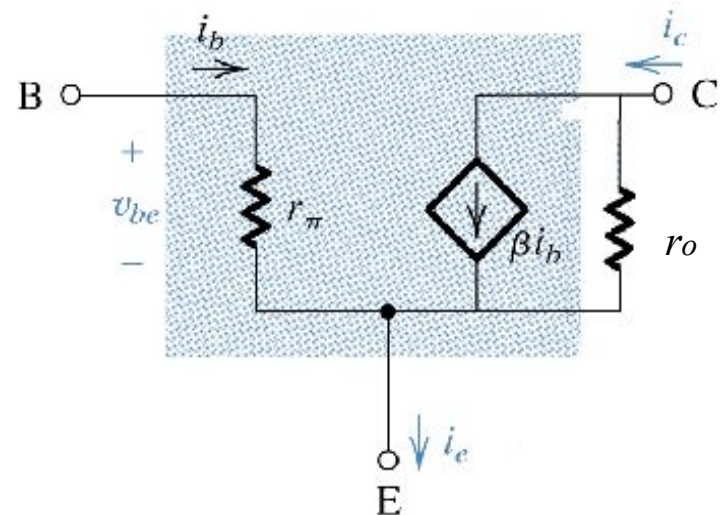3 AC Analysis
Set DC sources to zero, replace transistor by hybrid- π model, find ac quantities, R_{in} , R_{out} , A_v , and A_i .



Circuit

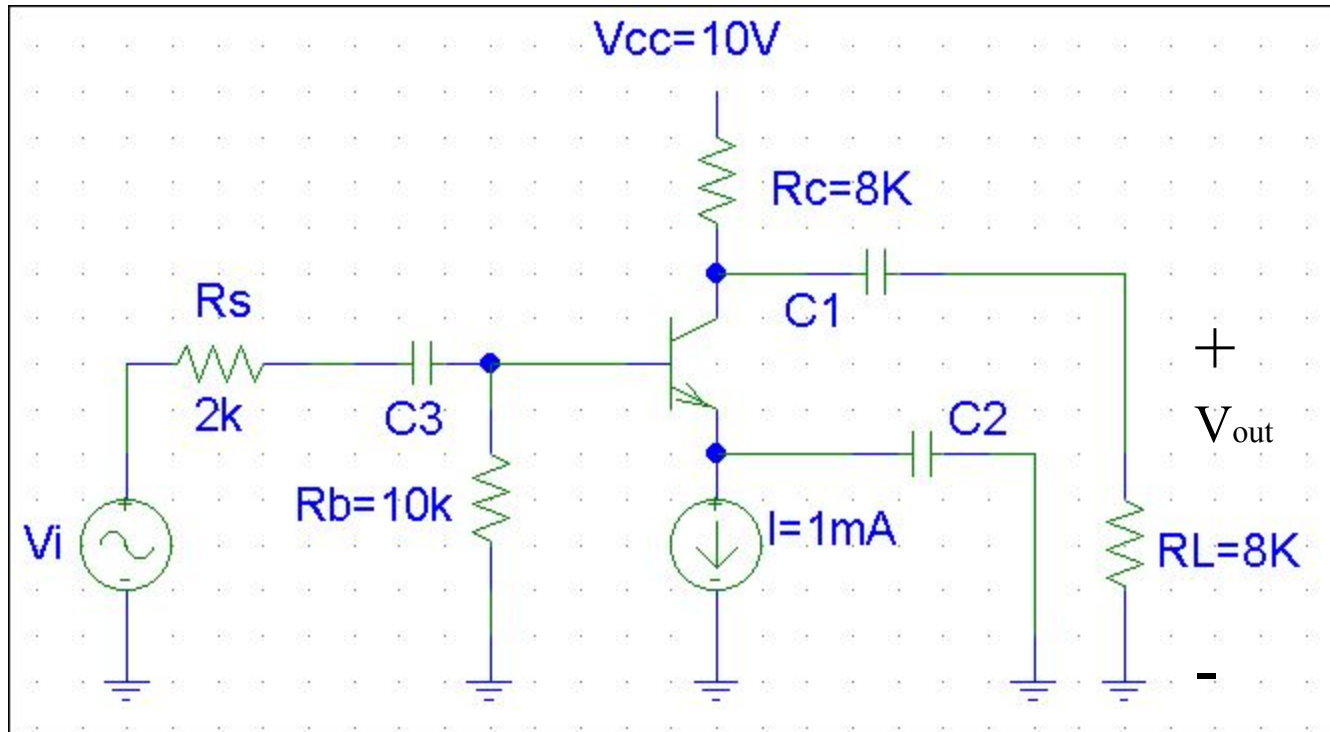

$$I_E = 1 \text{ mA}$$

$$V_C = 10V - I_C 8K = 10 - 1(8) = 2V$$

$$I_B \approx I_E / \beta = 0.01 \text{ mA}$$


$$g_m = I_C / V_T = 1 \text{ mA} / 25 \text{ mV} = 40 \text{ mA/V}$$

$$V_B = 0 - I_B 10K = -0.1V$$

$$r_\pi = V_T / I_B = 25 \text{ mV} / 0.01 \text{ mA} = 2.5K$$

$$V_E = V_B - V_{BE} = -0.1 - 0.7 = -0.8V$$

ac equivalent circuit

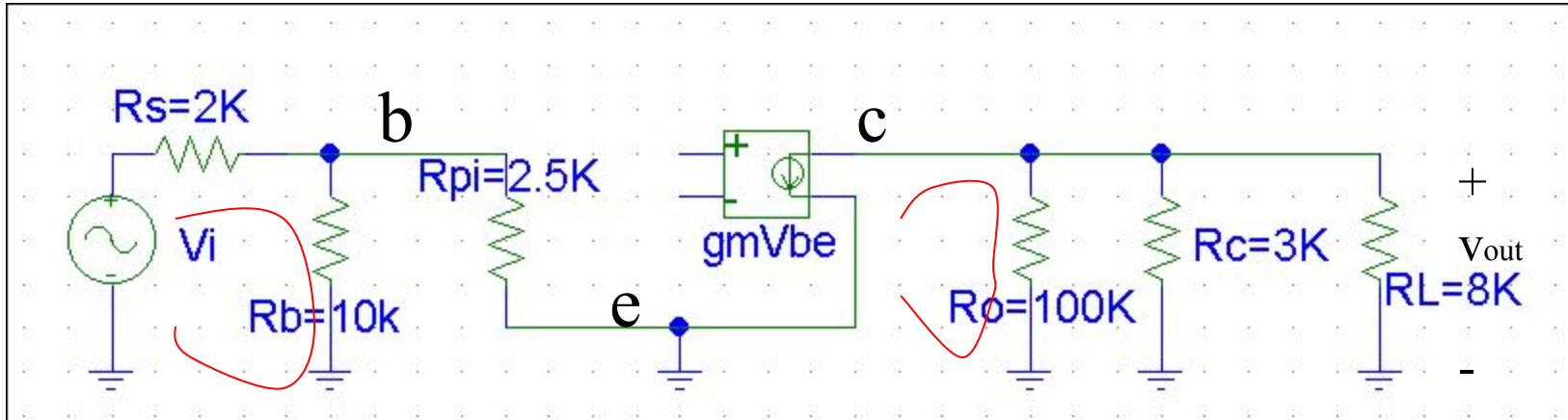

$$V_{be} = (R_b \parallel R_{pi}) / [(R_b \parallel R_{pi}) + R_s] V_i$$

$$V_{be} = 0.5 V_i$$

$$V_{out} = -(g_m V_{be}) \parallel (R_o \parallel R_c \parallel R_L)$$

$$V_{out} = -154 V_{be}$$


$$A_v = V_{out} / V_i = -77$$

Neglecting R_o


$$V_{out} = -(g_m V_{be}) \parallel (R_c \parallel R_L)$$

$$A_v = V_{out} / V_i = -80$$

Prob.

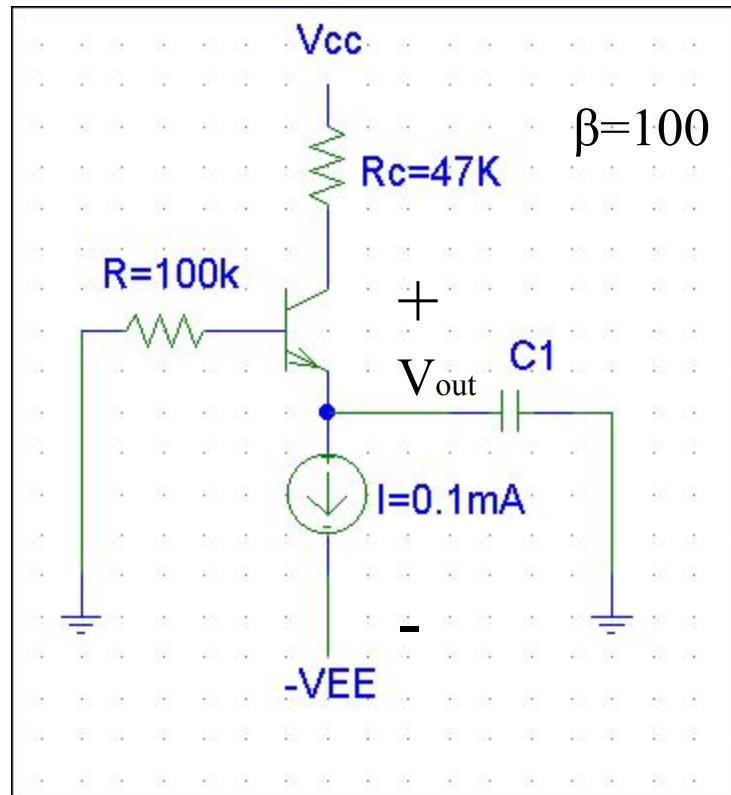

Prob.

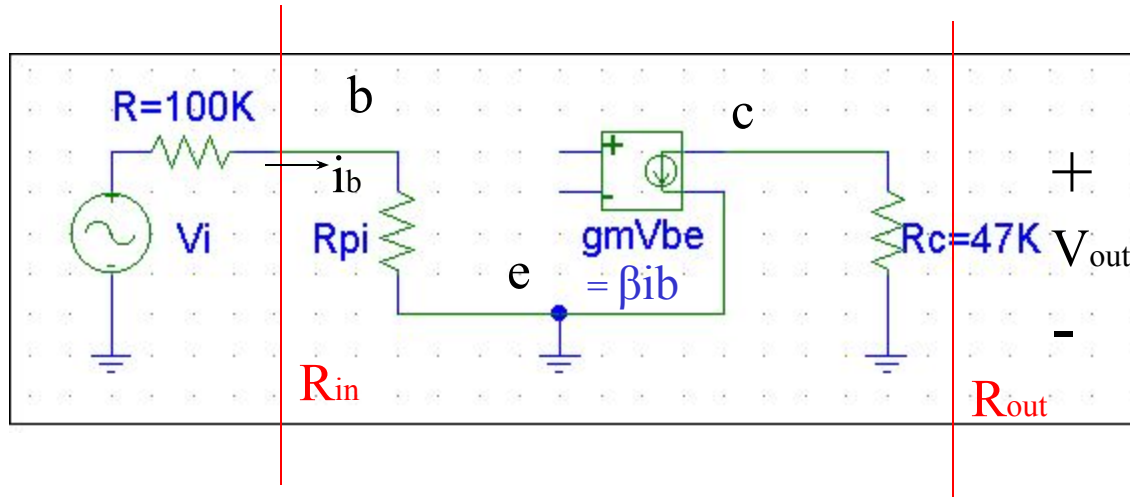

(a) Find R_{in}

$$R_{in} = R_{pi} = V_T/I_B = (25\text{mV})100/.1 = 2.5\text{K}\Omega$$

(c) Find R_{out}

$$R_{out} = R_c = 47\text{K}\Omega$$


(b) Find $A_v = V_{out}/V_{in}$

$$V_{out} = -\beta i_b R_c$$

$$V_{in} = i_b (R + R_{pi})$$

$$\begin{aligned} A_v &= V_{out}/V_{in} = -\beta i_b R_c / i_b (R + R_{pi}) \\ &= -\beta R_c / (R + R_{pi}) \\ &= -100(47\text{K}) / (100\text{K} + 2.5\text{K}) \\ &= -37.6 \end{aligned}$$

Graphical analysis

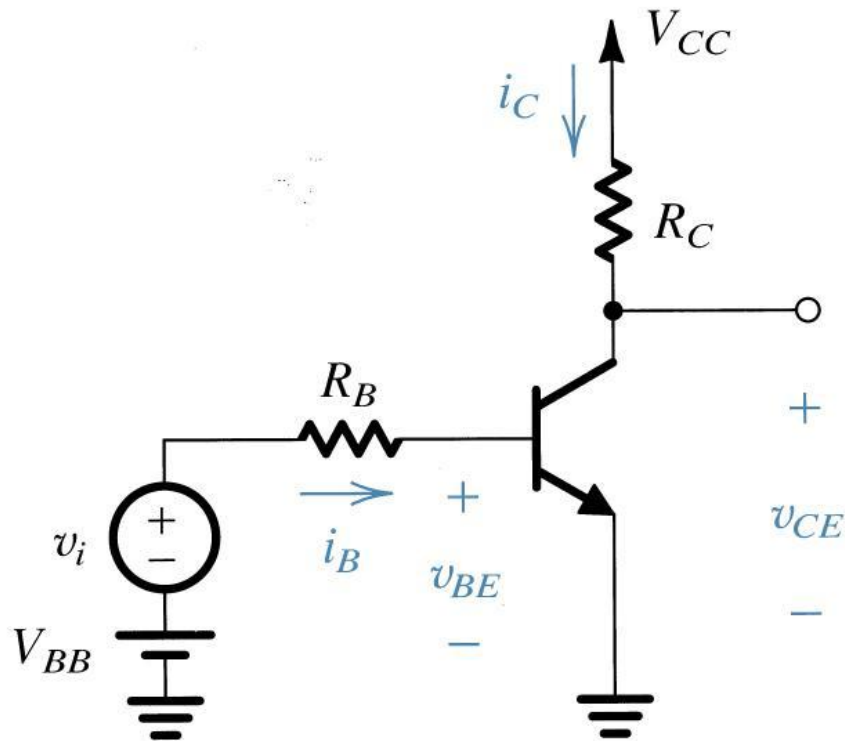


Input circuit

B-E voltage loop

$$V_{BB} = I_B R_B + V_{BE}$$

$$I_B = (V_{BB} - V_{BE})/R_B$$

Graphical construction of I_B and V_{BE}

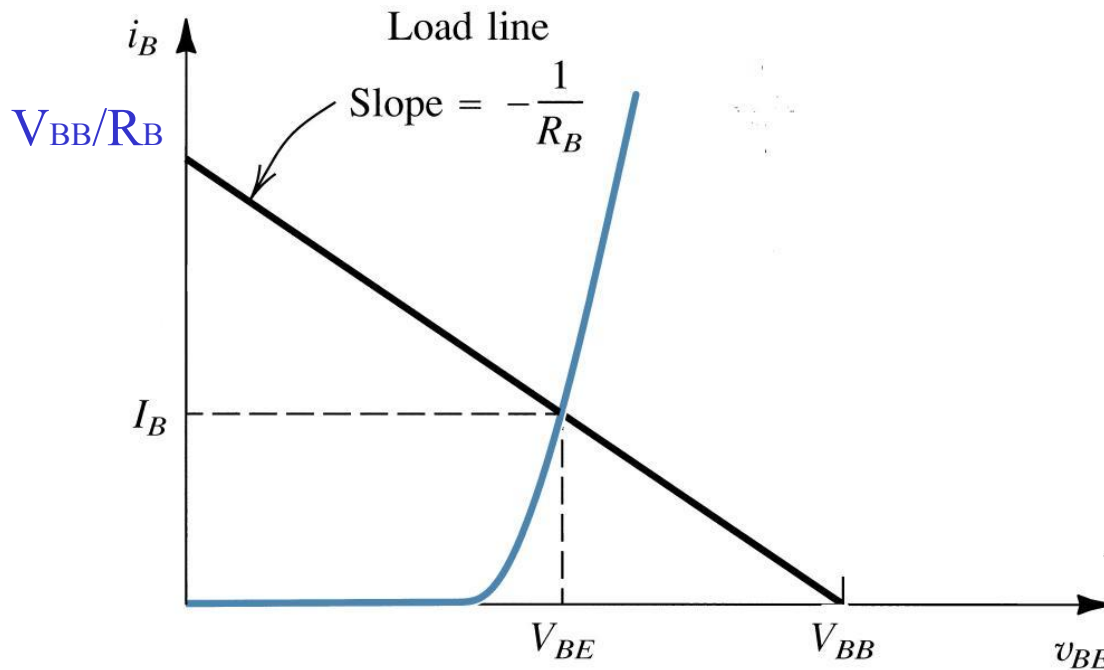


$$I_B = (V_{BB} - V_{BE})/R_B$$

$$\text{If } V_{BE} = 0, I_B = V_{BB}/R_B$$

$$\text{If } I_B = 0, V_{BE} = V_{BB}$$

Load line

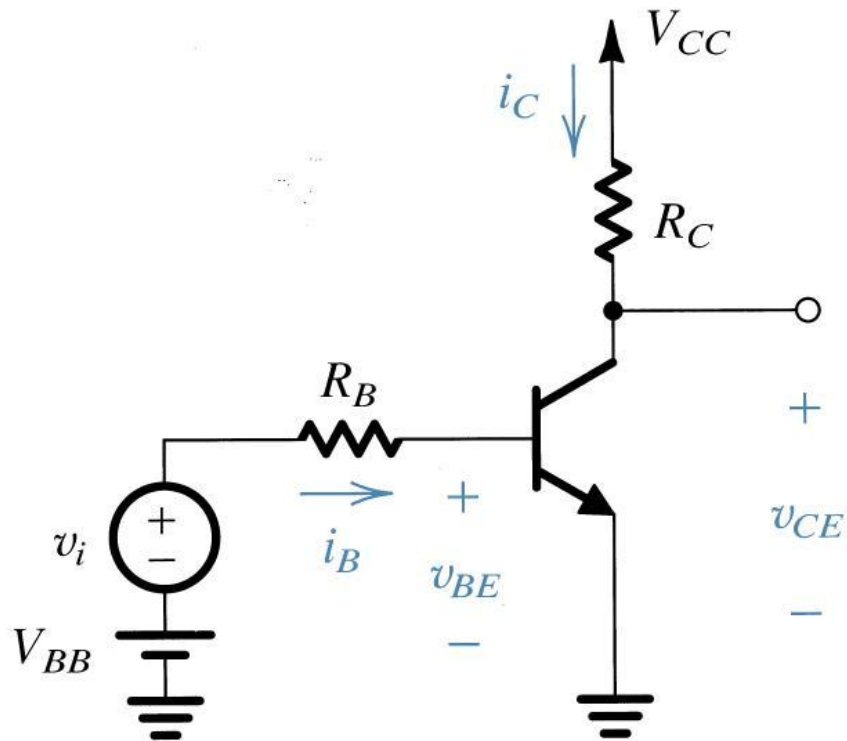


Output circuit

C-E voltage loop

$$V_{CC} = I_C R_C + V_{CE}$$

$$I_C = (V_{CC} - V_{CE})/R_C$$

Graphical construction of I_C and V_{CE}


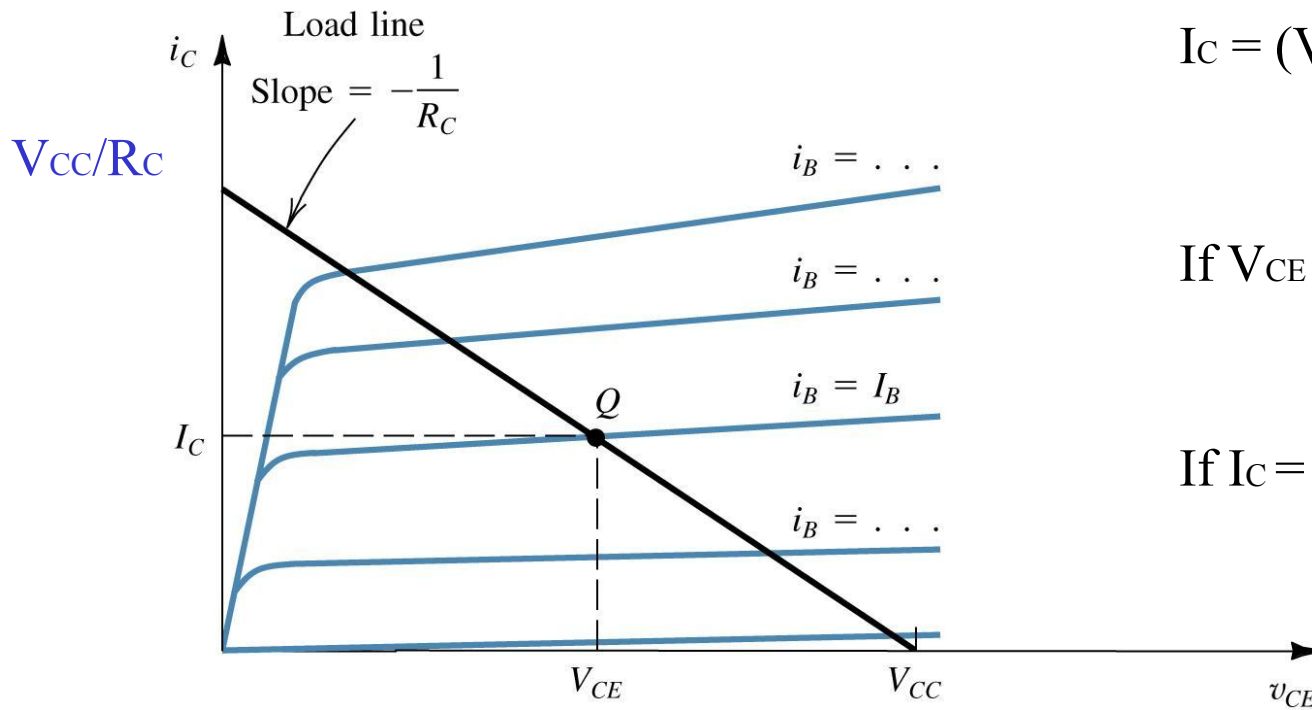


$$I_C = (V_{CC} - V_{CE})/R_C$$


If $V_{CE} = 0$, $I_C = V_{CC}/R_C$

If $I_C = 0$, $V_{CE} = V_{CC}$

Graphical analysis

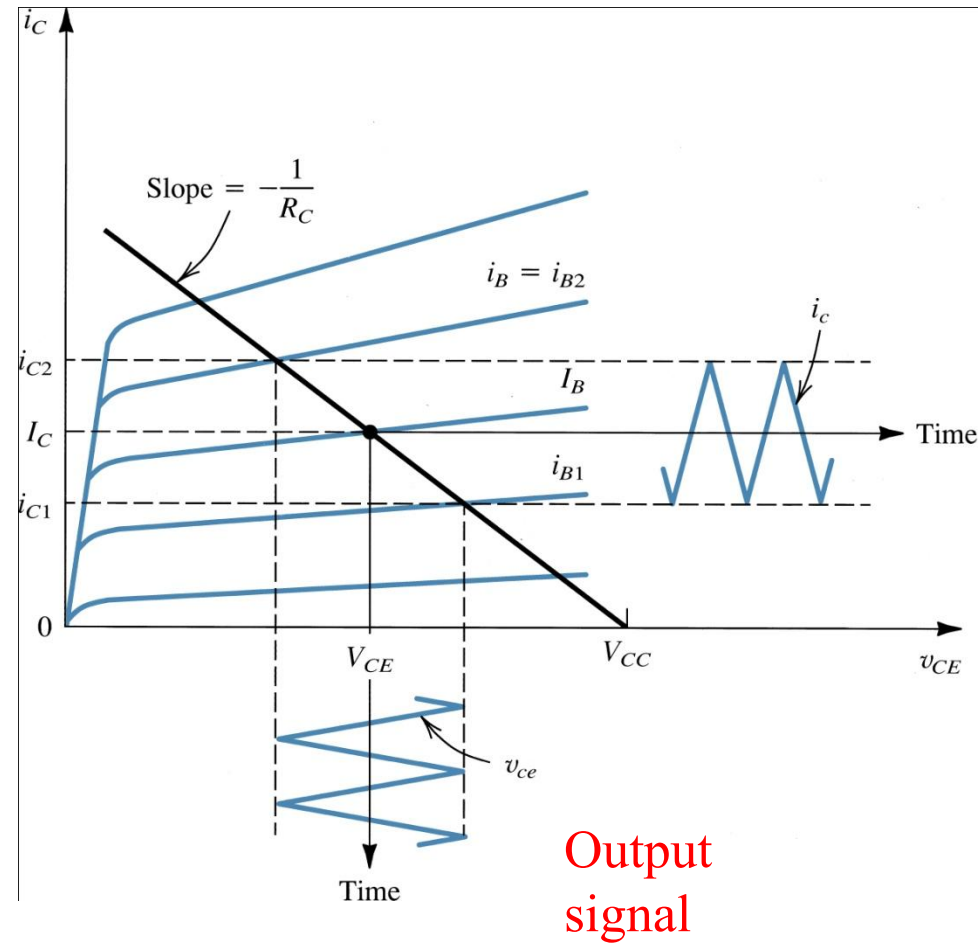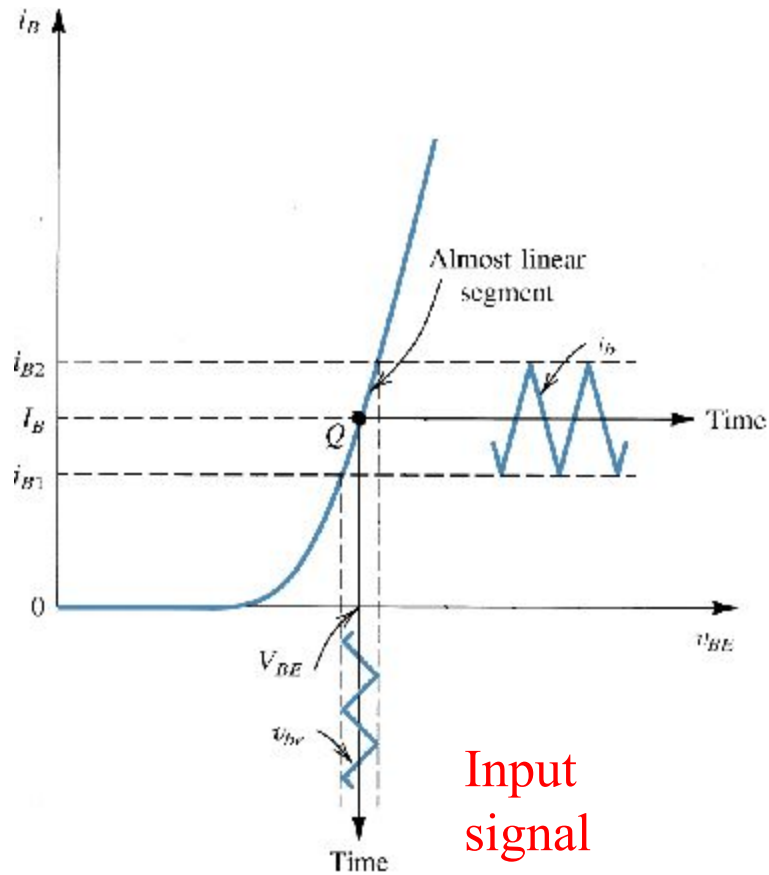

Bias point location effects

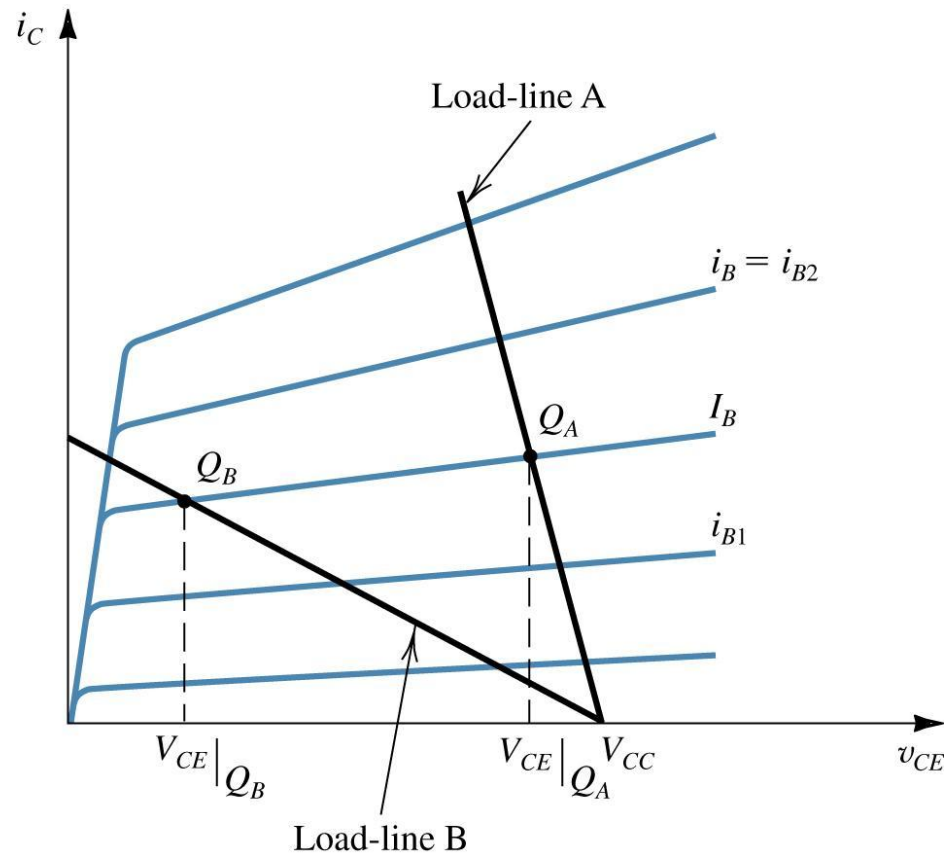



- Load-line A results in bias point Q_A which is too close to V_{CC} and thus limits the positive swing of v_{CE} .
- Load-line B results in an operating point too close to the saturation region, thus limiting the negative swing of v_{CE} .

Basic single-stage BJT amplifier configurations

We will study 3 types of BJT amplifiers

- **CE - common emitter**, used for A_v , A_i , and general purpose
 - **CE with R_E - common emitter with R_E** ,
same as CE but more stable
 - **CC common collector**, used for A_i , low output resistance,
used as an output stage
- CB common base (not covered)

Common emitter amplifier

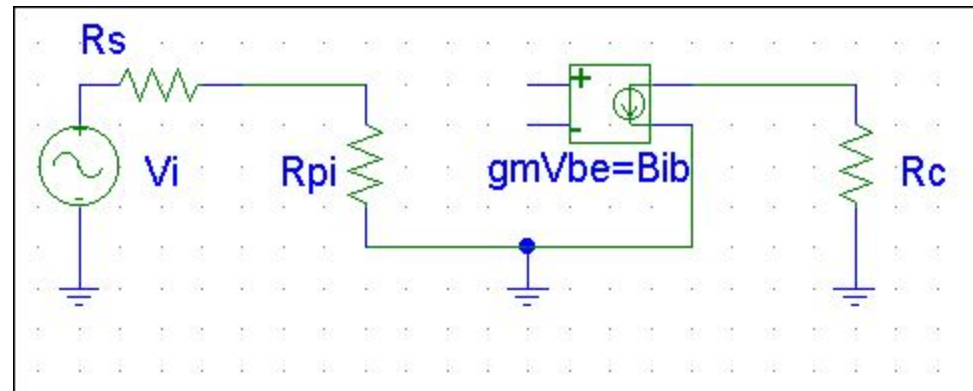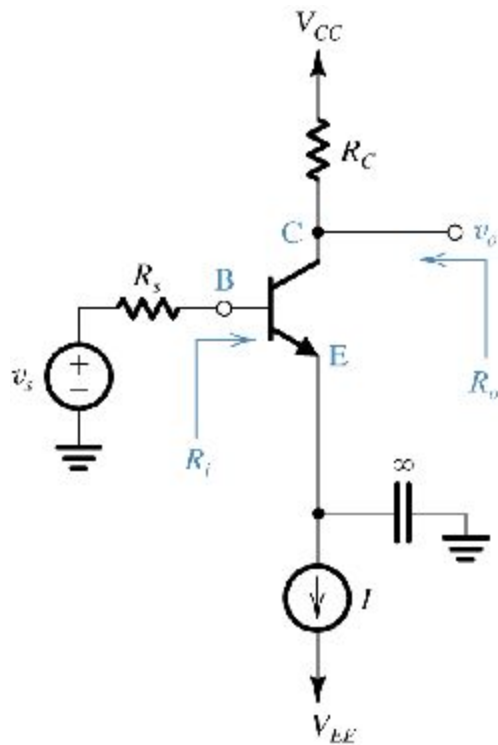

ac equivalent circuit

Common emitter amplifier

R_{in}

(Does not include source)

$$R_{in} = R_{pi}$$

R_{out}

(Does not include load)

$$R_{out} = R_C$$

A_v

$$= V_{out}/V_{in}$$

$$V_{out} = -\beta i_b R_C$$

$$V_{in} = i_b (R_s + R_{pi})$$

$$A_v = -\beta R_C / (R_s + R_{pi})$$


A_i

$$= i_{out}/i_{in}$$


$$i_{out} = -\beta i_b$$

$$i_{in} = i_b$$


$$A_i = -\beta$$

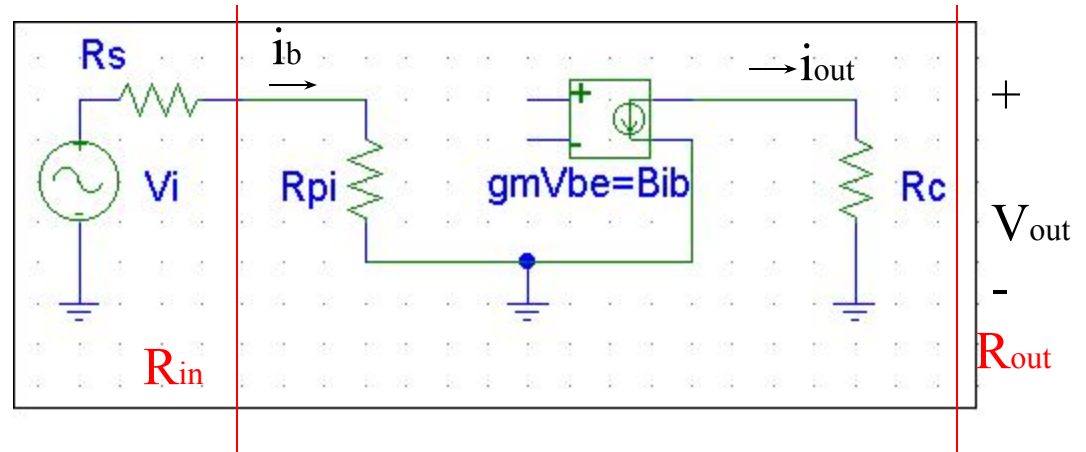

Common emitter with R_E amplifier

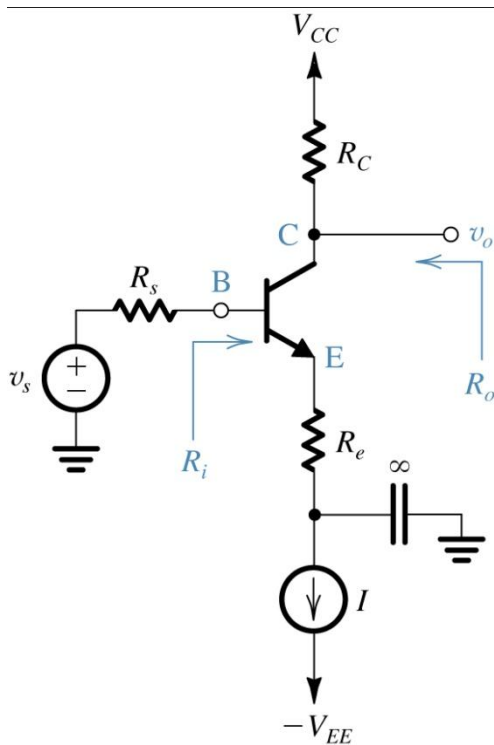

(a)

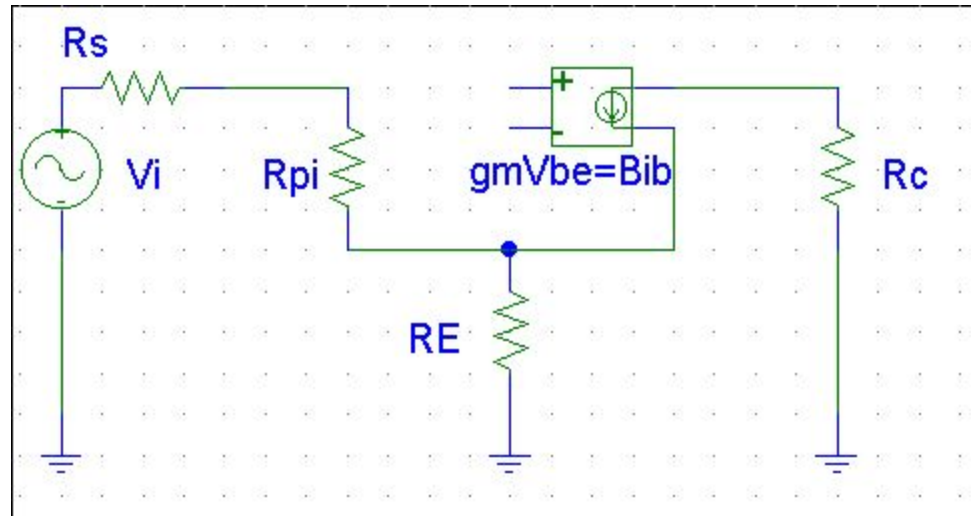

ac equivalent circuit

Common emitter with R_E amplifier


R_{in}

$$R_{in} = V/i_b$$

$$V = i_b R_{pi} + (i_b + \beta i_b) R_E$$

$$R_{in} = R_{pi} + (1 + \beta) R_E$$

(usually large)

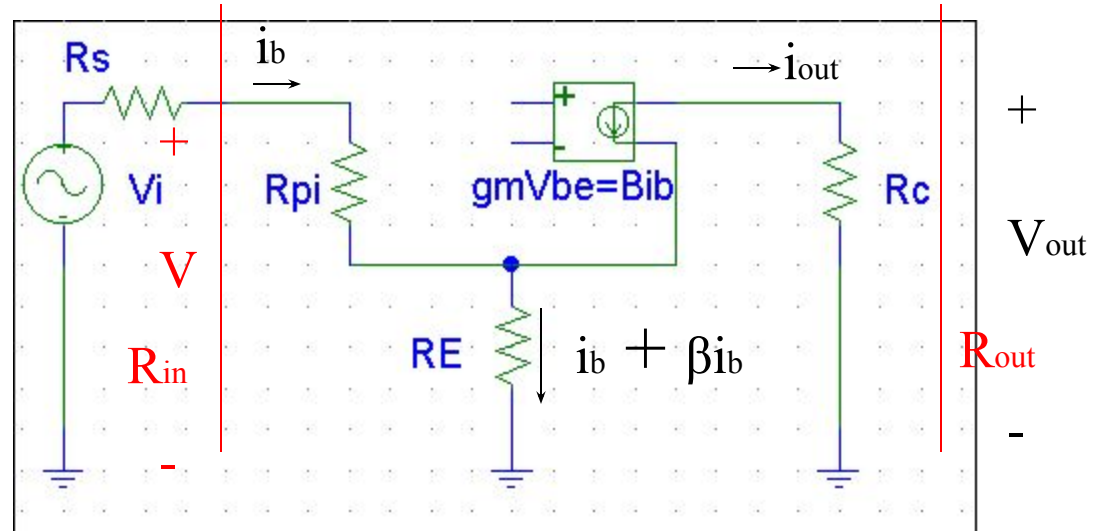

R_{out}

$$R_{out} = R_C$$

A_v

$$= V_{out}/V_{in}$$

$$V_{out} = -\beta i_b R_C$$

$$V_{in} = i_b R_s + i_b R_{pi} + (i_b + \beta i_b) R_E$$

$$A_v = -\beta R_C / (R_s + R_{pi} + (1 + \beta) R_E)$$

(less than CE, but less sensitive to β variations)

A_i


$$= i_{out}/i_{in}$$

$$i_{out} = -\beta i_b$$


$$i_{in} = i_b$$

$$A_i = -\beta$$

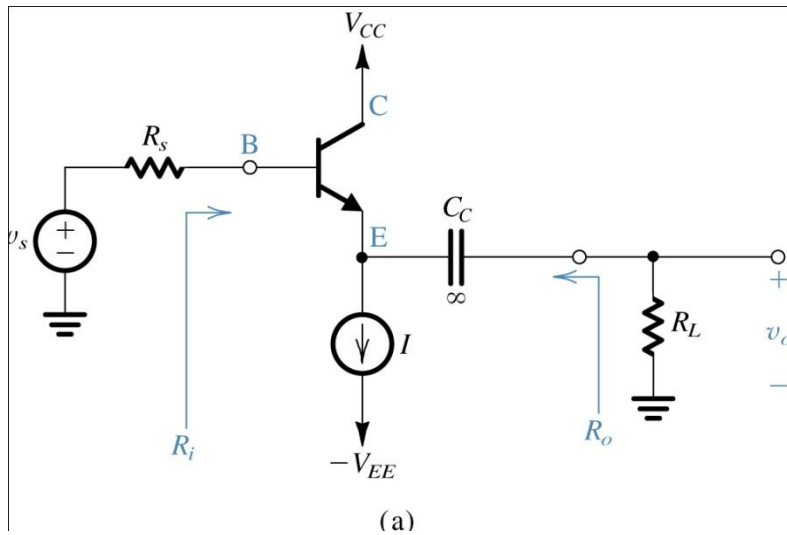Common collector (emitter follower) amplifier



(V_{out} at emitter)

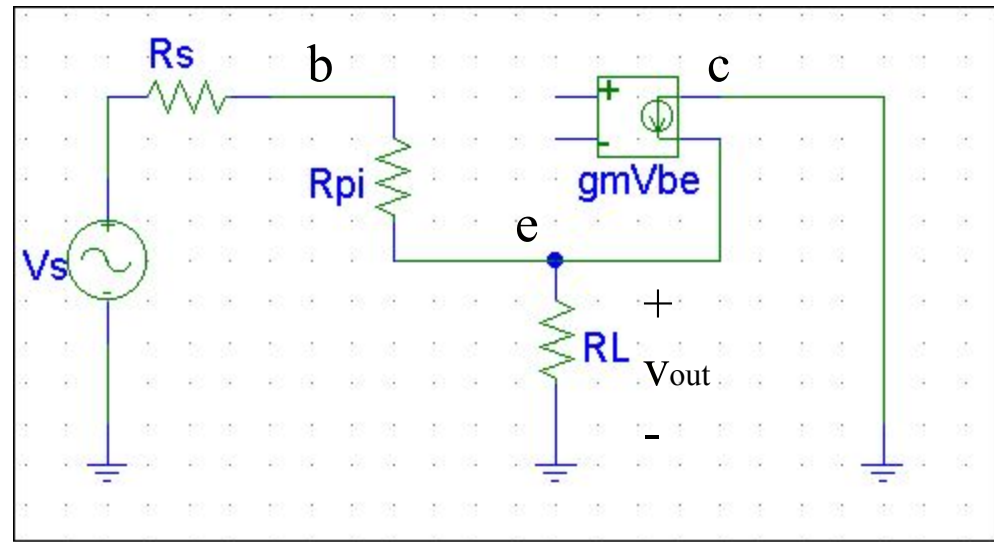

ac equivalent circuit


Common collector amplifier

R_{in}

$$R_{in} = V/i_b$$

$$V = i_b R_{pi} + (i_b + \beta i_b) R_L$$

$$R_{in} = R_{pi} + (1 + \beta) R_L$$

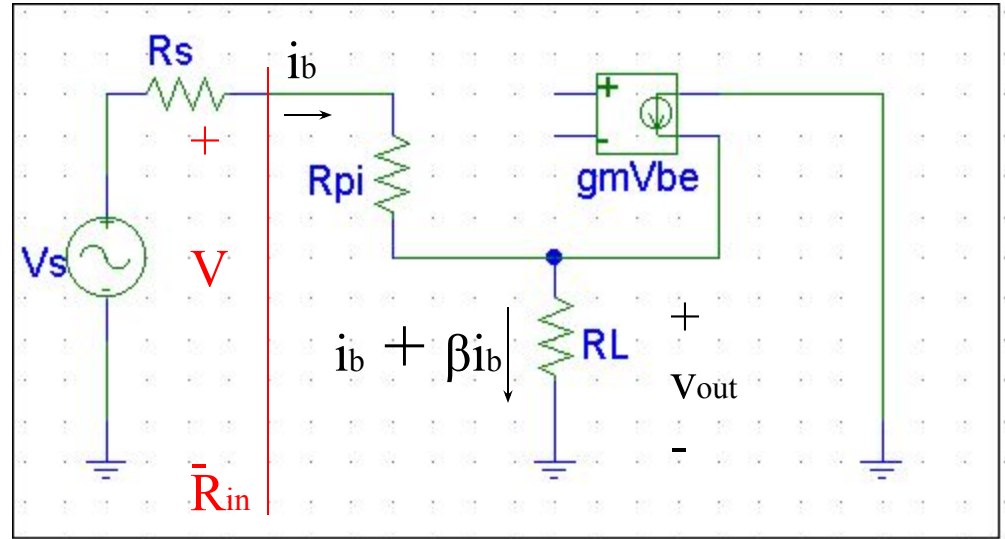

A_v

$$= V_{out}/V_s$$

$$V_{out} = (i_b + \beta i_b) R_L$$


$$V_s = i_b R_s + i_b R_{pi} + (i_b + \beta i_b) R_L$$

$$A_v = (1 + \beta) R_L / (R_s + R_{pi} + (1 + \beta) R_L)$$

(always ≤ 1)

Common collector amplifier
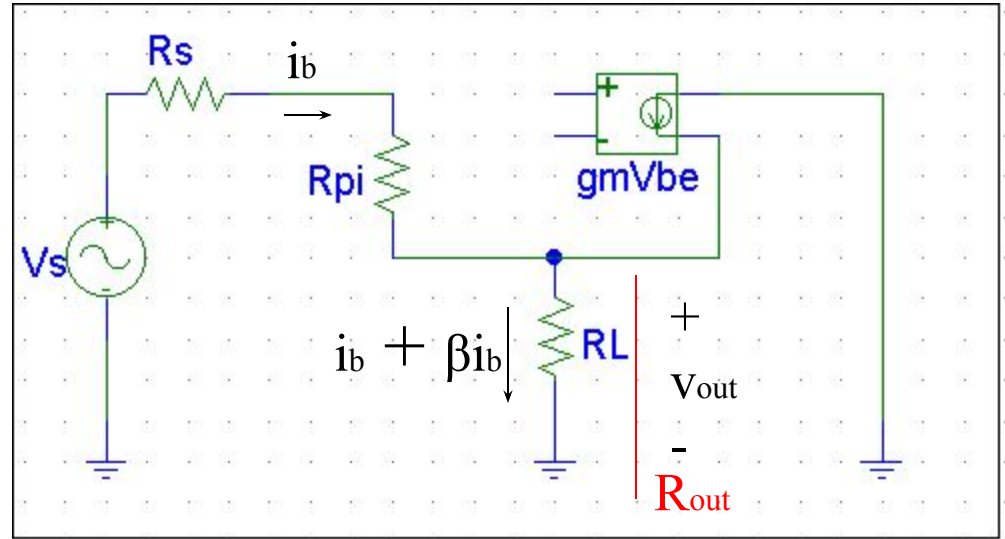
$$\begin{aligned}
 A_i &= i_{out}/i_{in} \\
 i_{out} &= i_b + \beta i_b \\
 i_{in} &= i_b \\
 A_i &= \beta + 1
 \end{aligned}$$



R_{out}

(don't include R_L , set $V_s = 0$)

$$R_{out} = V_{out} / - (i_b + \beta i_b)$$


$$V_{out} = -i_b R_{pi} + -i_b R_s$$

$$R_{out} = (R_{pi} + R_s) / (1 + \beta)$$


(usually low)

Prob

Given

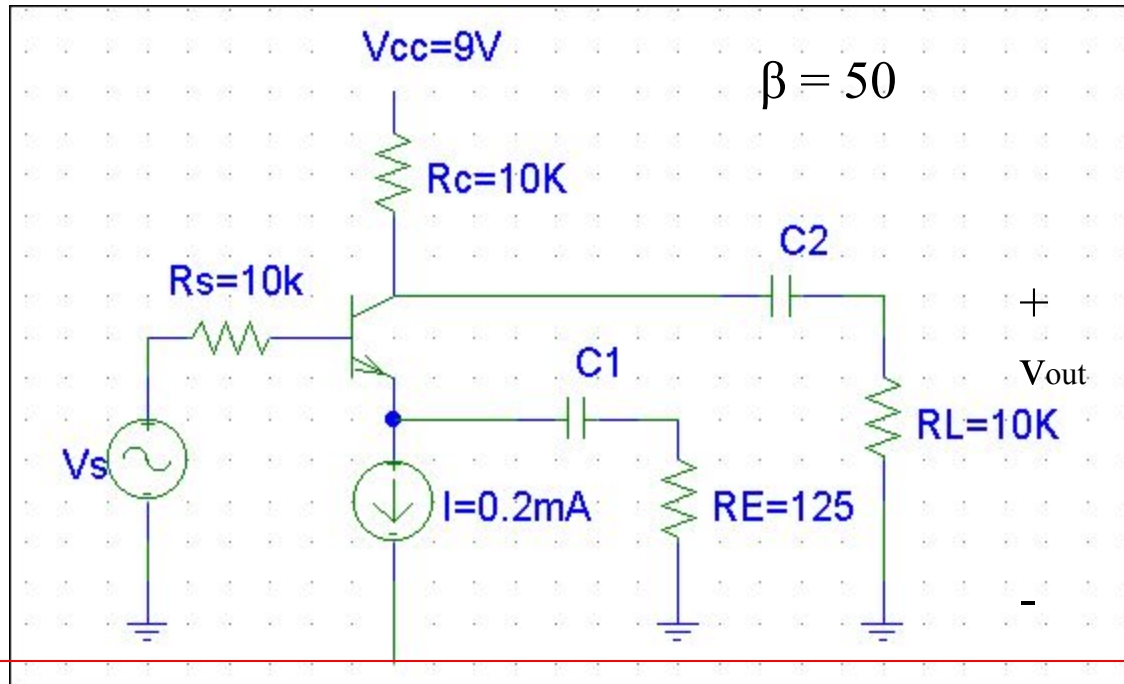


ac
circuit

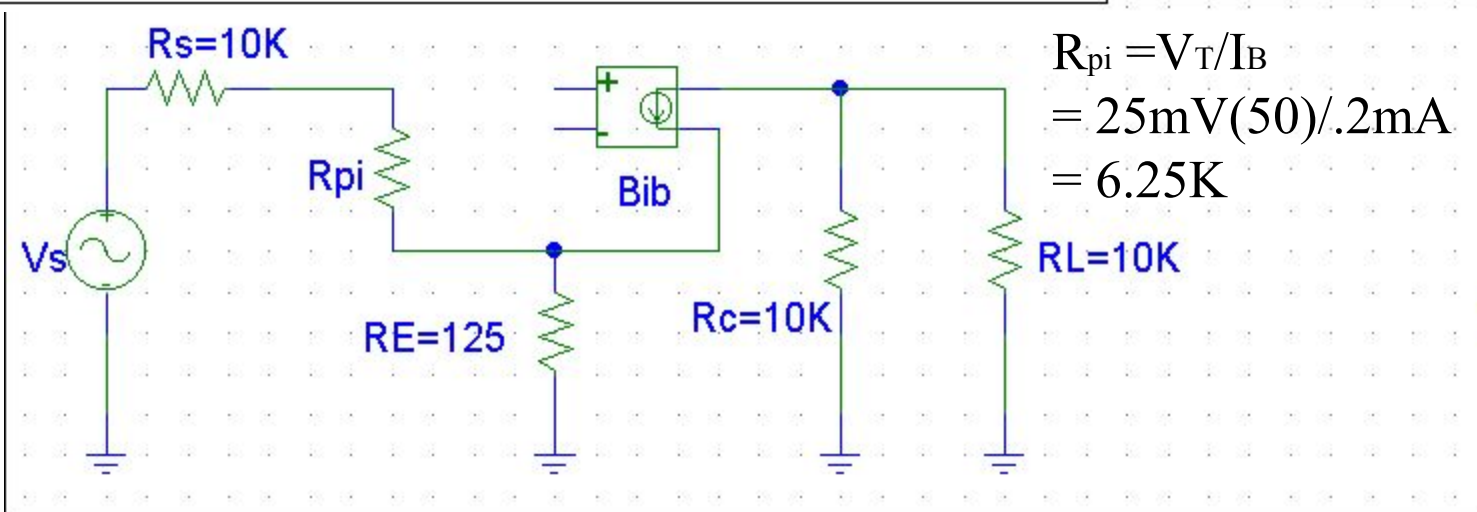

CE with R_E
amp, because R_E
is in ac circuit

Prob.

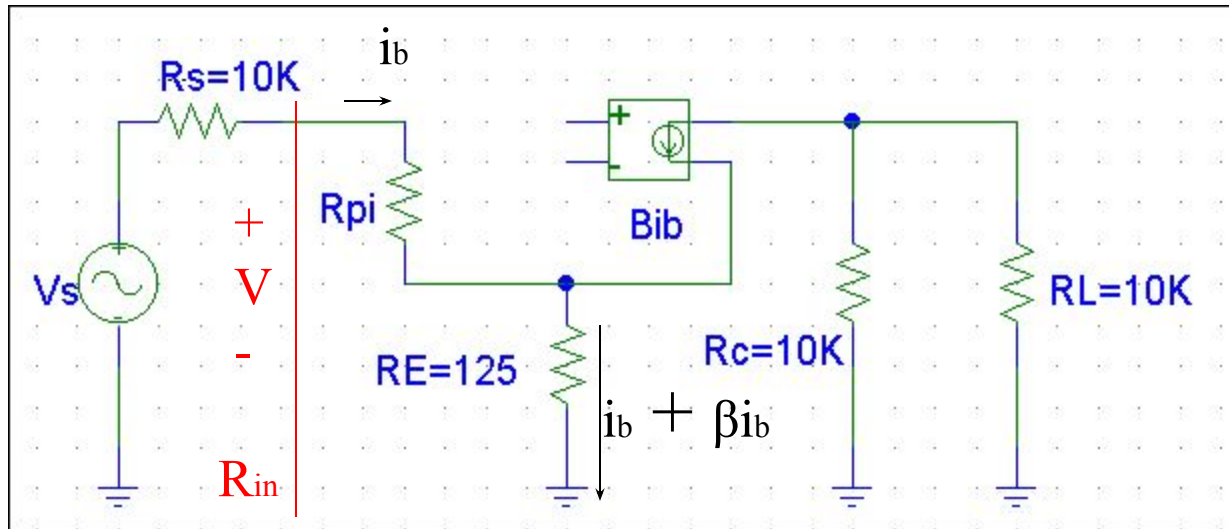

(a) Find R_{in}

$$R_{in} = V/i_b$$


$$V = i_b R_{pi} + (i_b + \beta i_b) R_E$$

$$R_{in} = R_{pi} + (1 + \beta) R_E$$

$$R_{in} = 6.25K + (1 + 50)125$$

$$R_{in} \approx 12.62K$$

Prob.

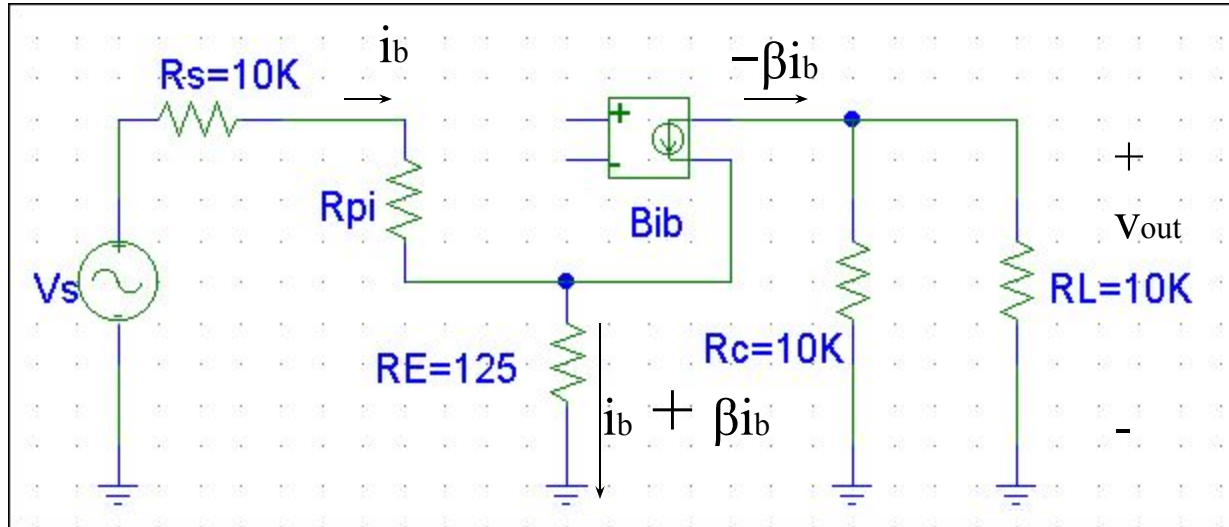

(b) Find $A_V = v_{out}/v_s$

$$V_{out} = -\beta i_b (R_C || R_L)$$


$$V_s = i_b R_s + i_b R_{pi} + (i_b + \beta i_b) R_E$$

$$A_V = -\beta (R_C || R_L) / (R_s + R_{pi} + (1 + \beta) R_E)$$

$$A_V = -50 (10K || 10K) / (10K + 6.25K + (1 + 50)125)$$

$$A_V \approx -11$$

Prob.

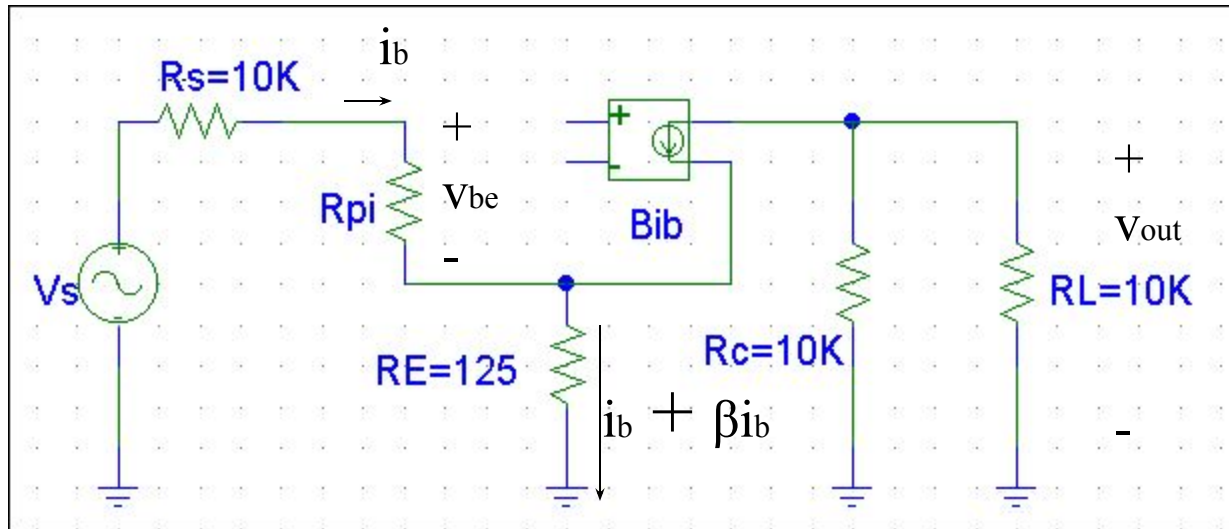

(c) If v_{be} is limited to 5mV, what is the largest signal at input and output?

$$v_{be} = i_b R_{pi} = 5\text{mV}$$


$$i_b = v_{be} / R_{pi} = 5\text{mV} / 6.25\text{K} = 0.8\mu\text{A} \text{ (ac value)}$$

$$v_s = i_b R_s + i_b R_{pi} + (i_b + \beta i_b) R_E$$

$$v_s = (0.8\mu\text{A})10\text{K} + (0.8\mu\text{A}) 6.25\text{K} + (0.8\mu\text{A} + (50)0.8\mu\text{A})125$$

$$v_s \approx 18\text{mV}$$

Prob.

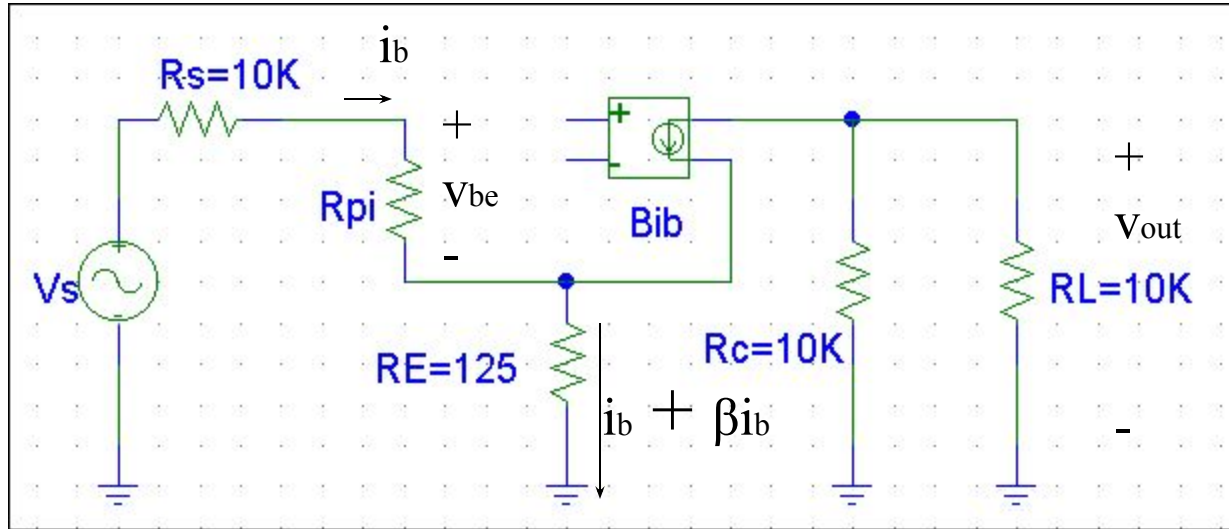


(c) If v_{be} is limited to 5mV, what is the largest signal at input and output?

$$V_{out} = v_s A_v$$

$$V_{out} = 17.4\text{mV}(-11)$$

$$V_{out} \approx -191\text{mV (ac value)}$$

Prob.

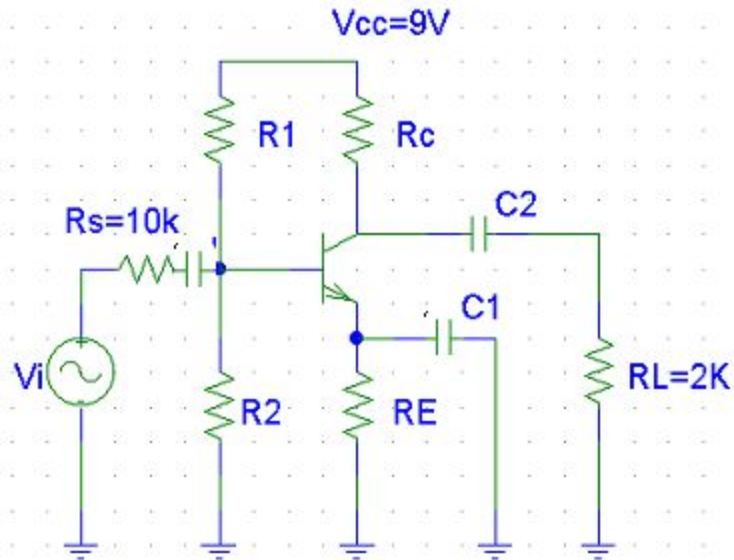

$$\beta = 100$$

Using this circuit, design an amp with:

$$I_E = 2mA$$

$$A_V = -8$$

current in voltage divider $I = 0.2mA$

(CE amp because R_E is not in ac circuit)

Voltage divider

$$V_{cc}/I = 9/0.2mA = 45K$$

$$45K = R_1 + R_2$$

Choose $V_B \approx 1/3 V_{cc}$ to put operating point near the center of the transistor characteristics

$$R_2/(R_1 + R_2) = 3V$$

Combining gives, $R_1 = 30K$, $R_2 = 15K$

Prob.

Find R_E (input circuit)

Use Thevenin equivalent

B-E loop


$$V_{BB} = I_B R_{BB} + V_{BE} + I_E R_E$$

using $I_B \approx I_E / \beta$


$$R_E = [V_{BB} - V_{BE} - (I_E / \beta) R_{BB}] / I_E$$

$$R_E = [3 - .7 - (2\text{mA}/100)10\text{K}] / 2\text{mA}$$

$$R_E = 1.05\text{K}\Omega$$

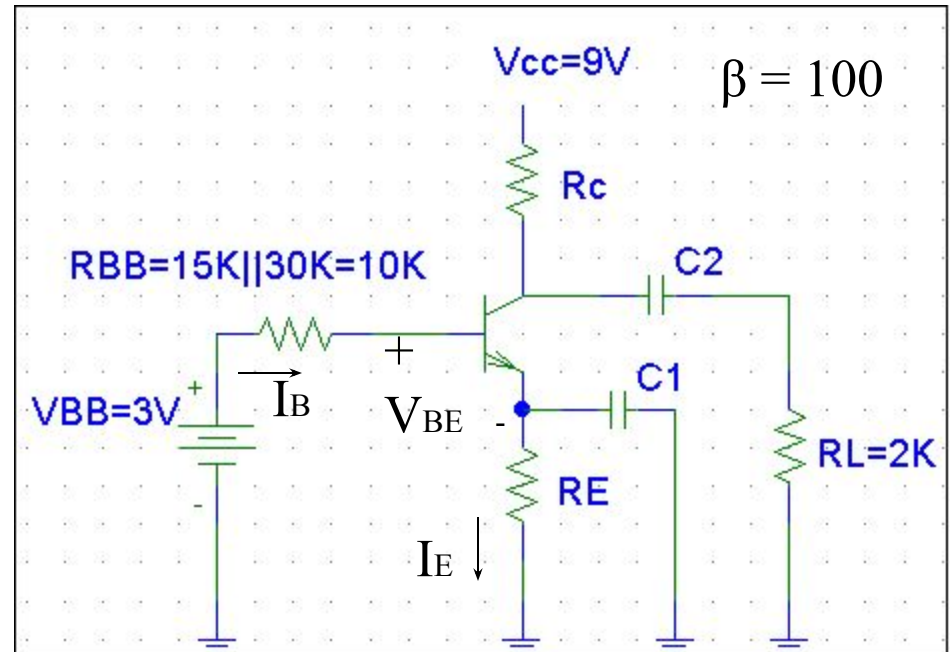

Prob.

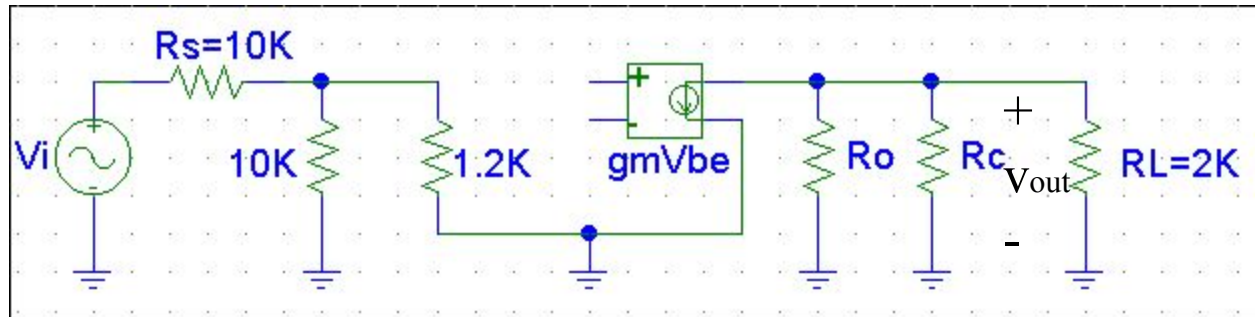

Find Rc (ac circuit)

$$R_{pi} = V_T / I_B = 25\text{mV}(100) / 2\text{mA} = 1.25\text{K}$$

$$R_o = V_A / I_C = 100 / 2\text{mA} = 50\text{K}$$

$$A_v = V_{out} / V_{in}$$


$$V_{out} = -g_m V_{be} (R_o || R_c || R_L)$$

$$V_{be} = 10\text{K} || 1.2\text{K} / [10\text{K} + 10\text{K} || 1.2\text{K}] V_i$$


$$A_v = -g_m (R_o || R_c || R_L) (10\text{K} || 1.2\text{K}) / [10\text{K} || 1.2\text{K} + R_s]$$

Set $A_v = -8$, and solve for R_c , $R_c \approx 2\text{K}$

CE amplifier

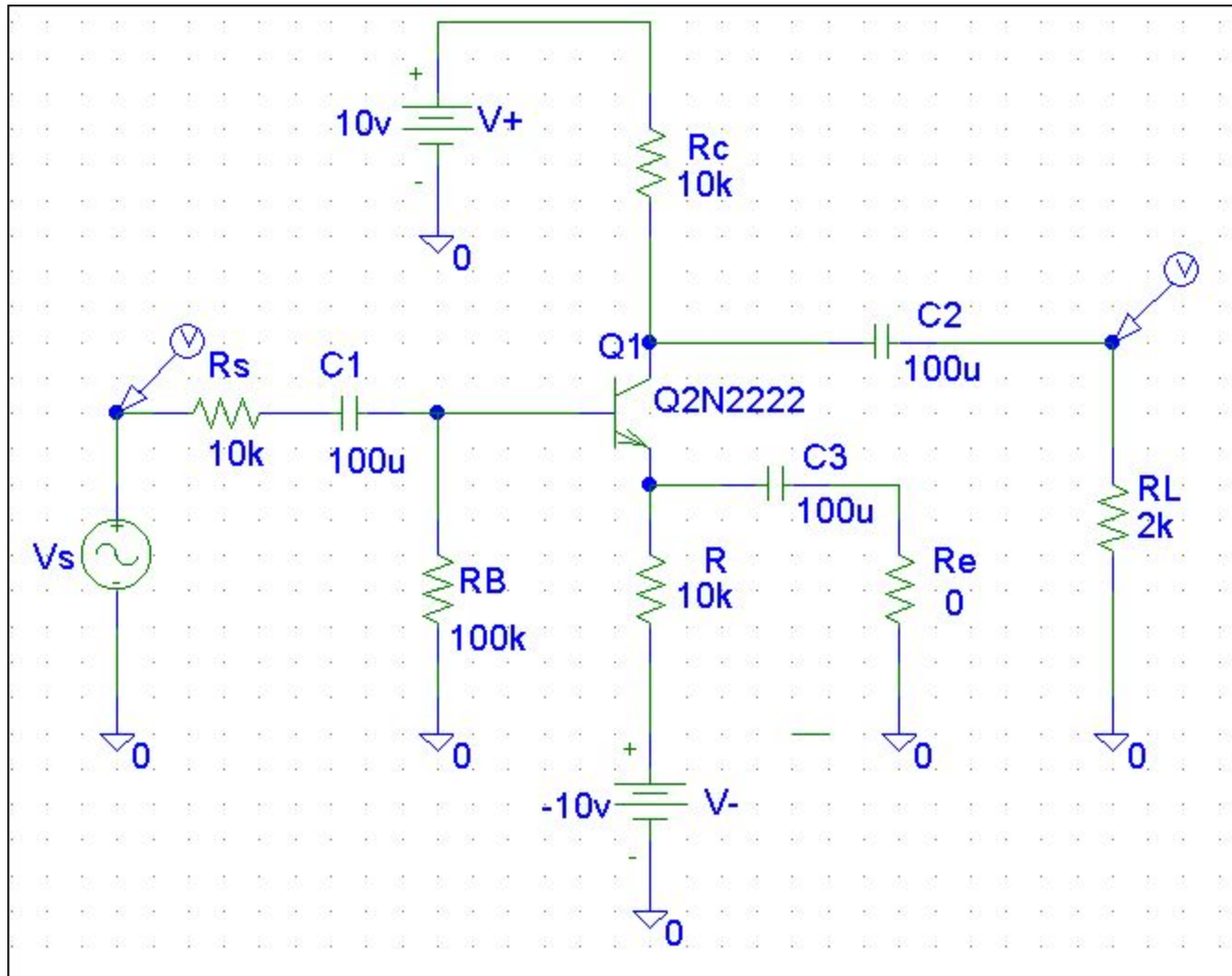

CE amplifier

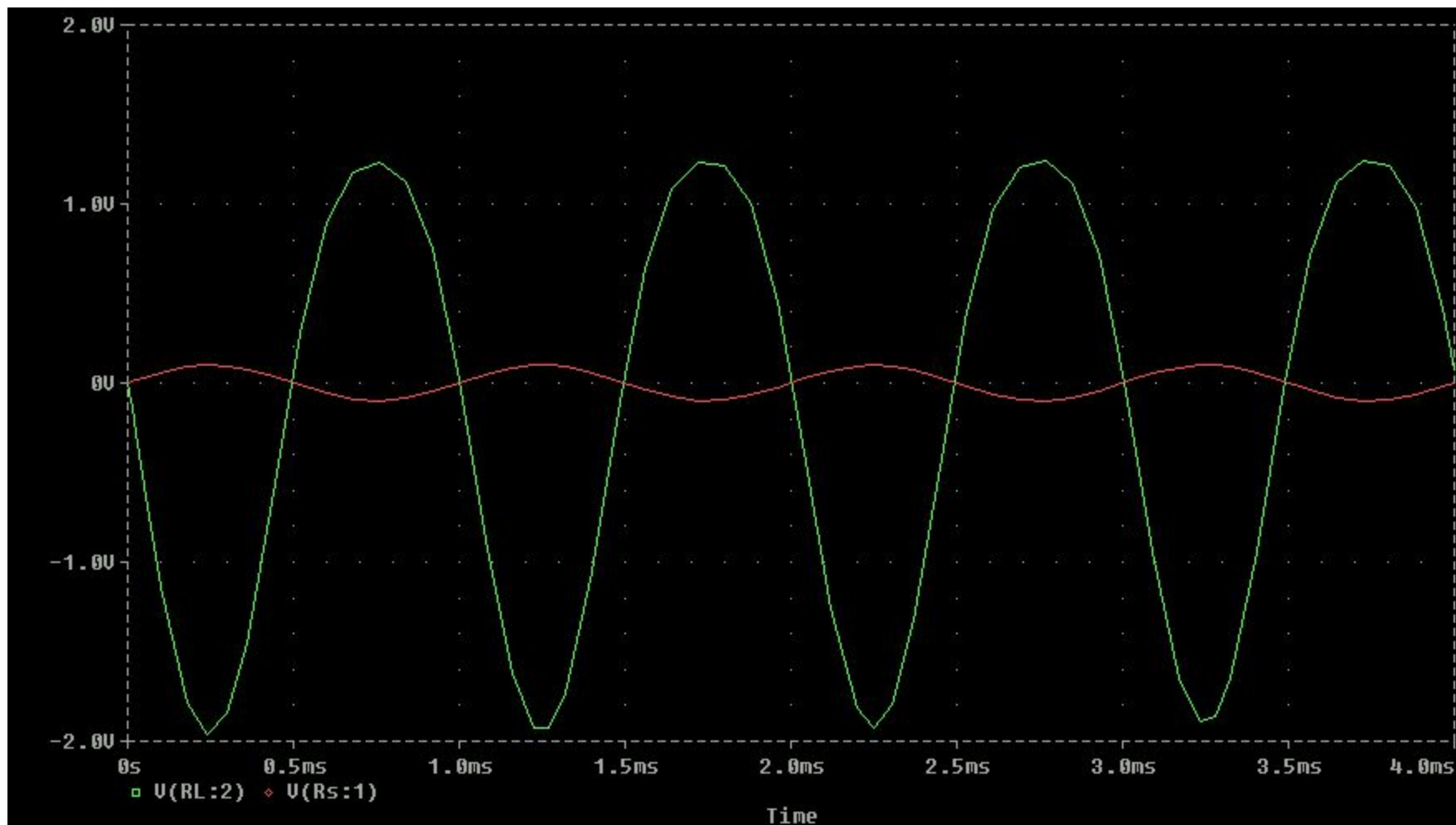

$$A_v \approx -12.2$$

CE amplifier


FOURIER COMPONENTS OF TRANSIENT RESPONSE V(\$N_0009)

DC COMPONENT = -1.226074E-01


HARMONIC NO	FREQUENCY (HZ)	FOURIER COMPONENT	NORMALIZED COMPONENT	PHASE (DEG)	NORMALIZED PHASE (DEG)
1	1.000E+03	1.581E+00	1.000E+00	-1.795E+02	0.000E+00
2	2.000E+03	1.992E-01	1.260E-01	9.111E+01	2.706E+02
3	3.000E+03	2.171E-02	1.374E-02	-1.778E+02	1.668E+00
4	4.000E+03	3.376E-03	2.136E-03	-1.441E+02	3.533E+01

TOTAL HARMONIC DISTORTION = 1.267478E+01 PERCENT

CE amplifier with R_E

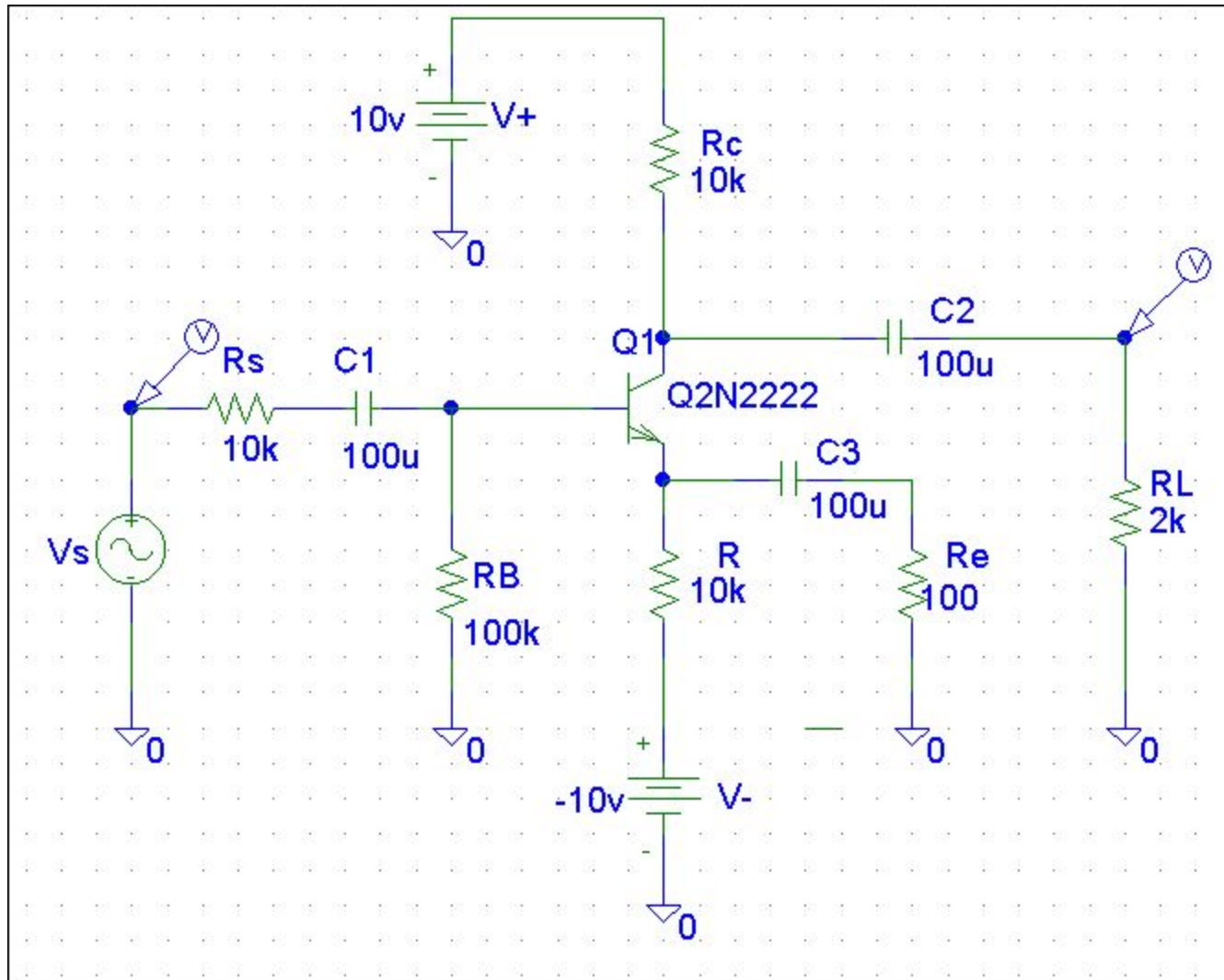

CE amplifier with R_E

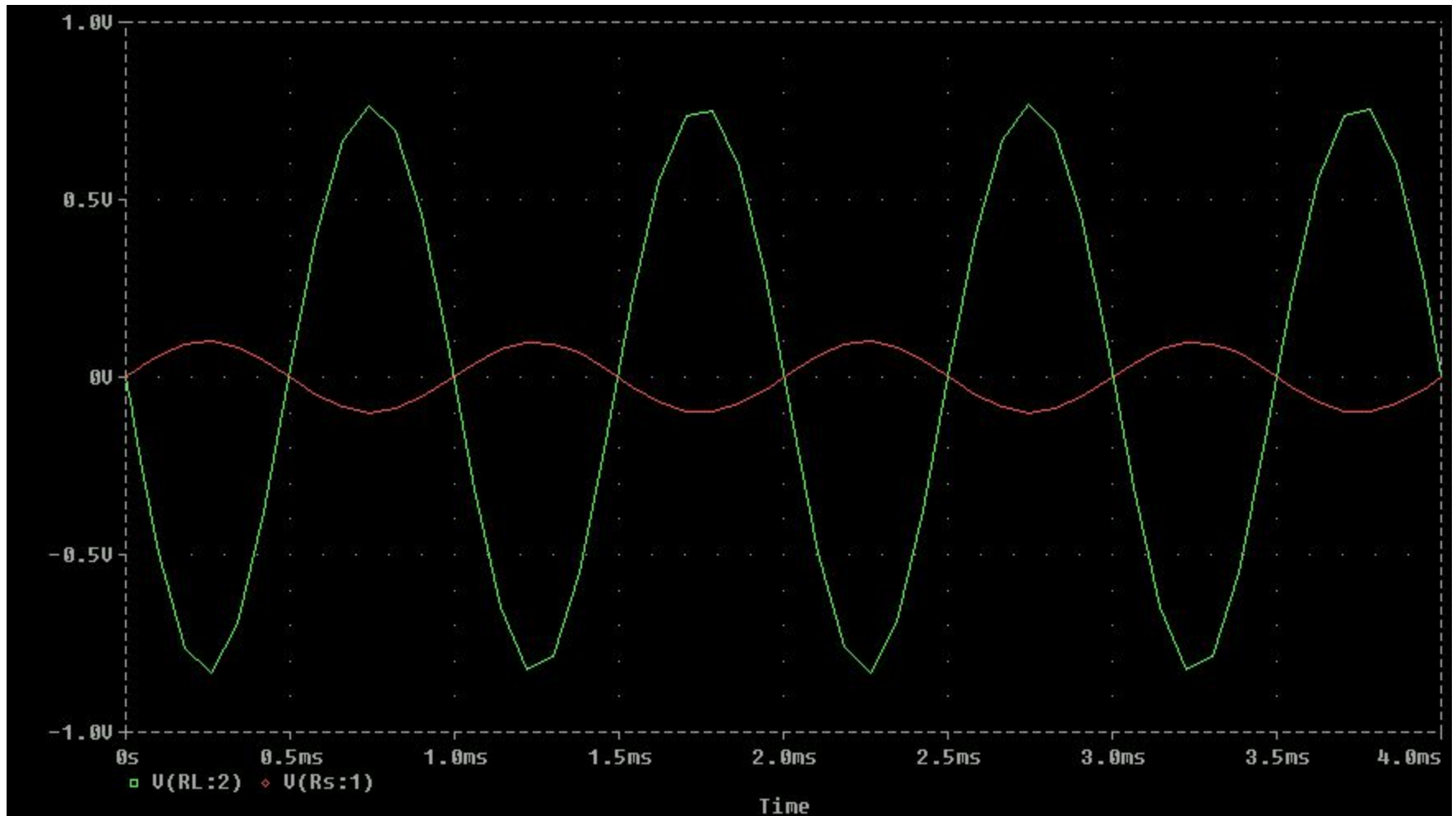

$$A_v \approx -7.5$$

FOURIER COMPONENTS OF TRANSIENT RESPONSE V(\$N_0009)

DC COMPONENT = -1.353568E-02


HARMONIC NO	FREQUENCY (HZ)	FOURIER COMPONENT	NORMALIZED COMPONENT	PHASE (DEG)	NORMALIZED PHASE (DEG)
1	1.000E+03	7.879E-01	1.000E+00	-1.794E+02	0.000E+00
2	2.000E+03	1.604E-02	2.036E-02	9.400E+01	2.734E+02
3	3.000E+03	5.210E-03	6.612E-03	-1.389E+02	4.056E+01
4	4.000E+03	3.824E-03	4.854E-03	-1.171E+02	6.231E+01

TOTAL HARMONIC DISTORTION = 2.194882E+00 PERCENT

Summary

	A_v	THD
CE	-12.2	12.7%
CE w/ R_E ($R_E = 100$)	-7.5	2.19%

Prob.

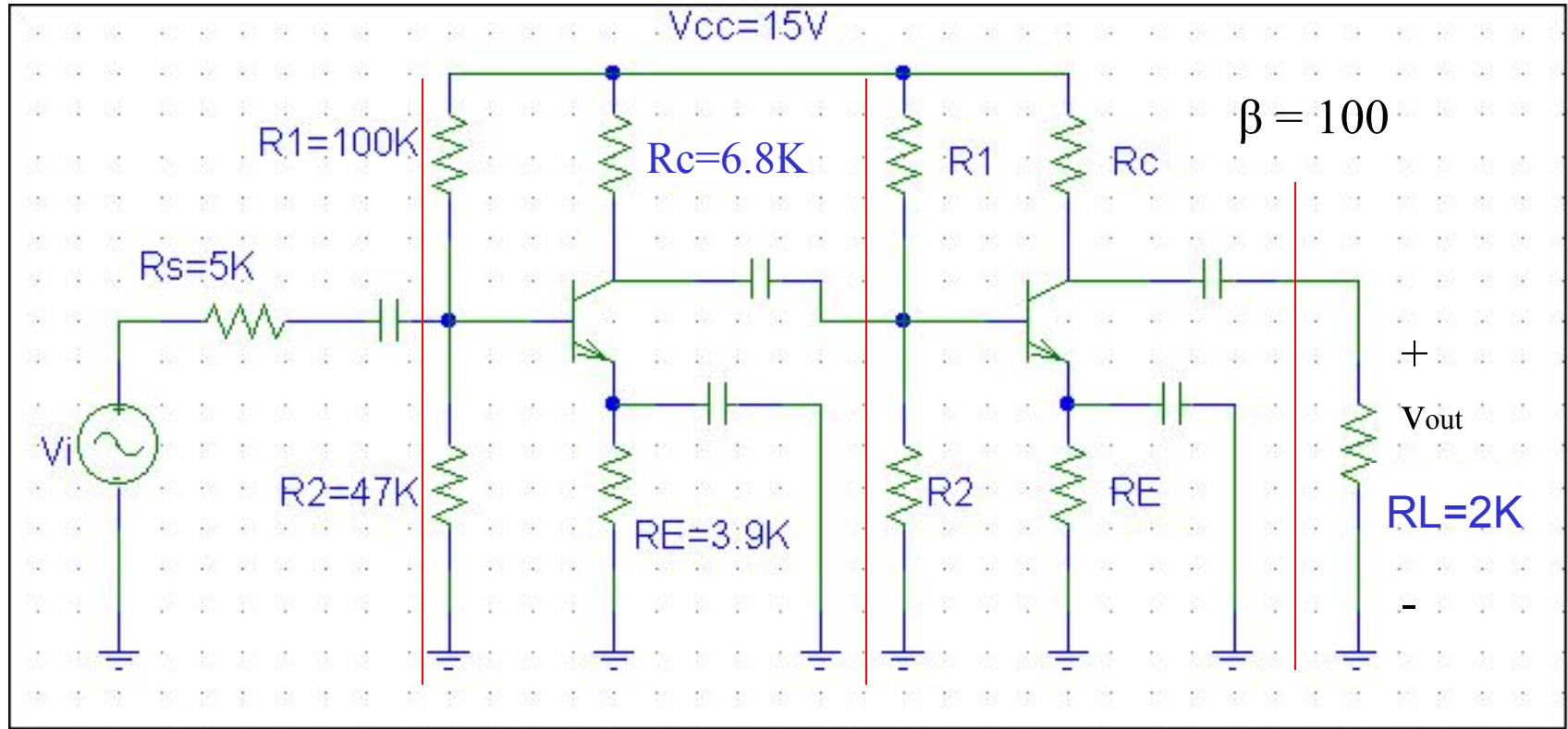

- 2 stage amplifier
- Both stages are the same
- Capacitively coupled

(a) Find I_C and V_C of each transistor
(same for each stage)

Prob.

(a) Find I_C and V_C of each transistor
(same for each stage)

B-E voltage loop

$$V_{BB} = I_B R_{BB} + V_{BE} + I_E R_E$$


where $R_{BB} = R_1 \parallel R_2 = 32K$

$V_{BB} = V_{CC} R_2 / (R_1 + R_2) = 4.8V$, and

$$I_B \approx I_E / \beta$$

$$I_E = [V_{BB} - V_{BE}] / [R_{BB} / \beta + R_E]$$

$$I_E = 0.97mA$$

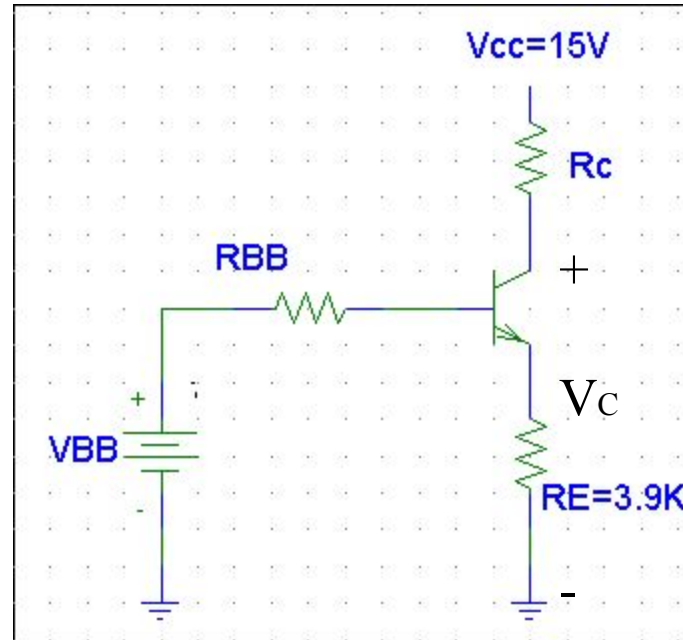


$$V_C = V_{CC} - I_C R_C$$

$$V_C = 15 - .97(6.8)$$

$$V_C = 8.39V$$

Prob.

(b) find ac circuit

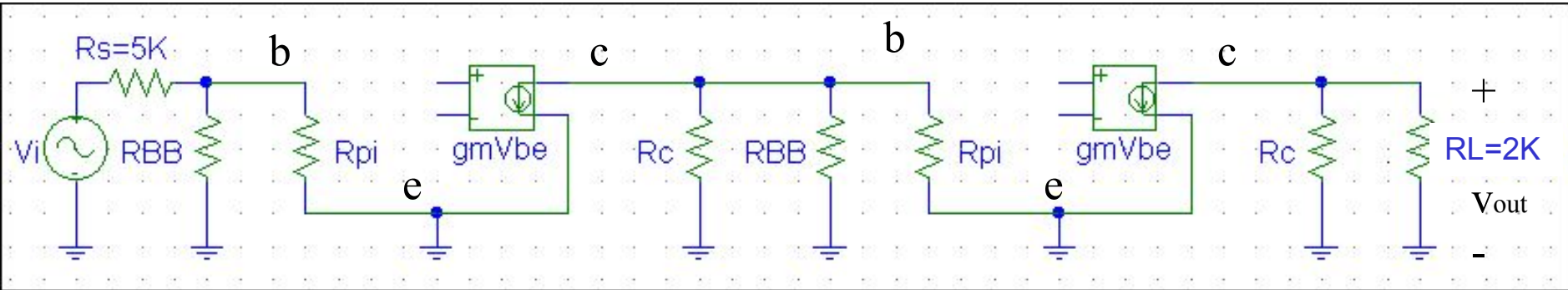


$$R_{BB} = R_1 || R_2 = 100K || 47K = 32K\Omega$$

$$R_{pi} = V_T / I_B = 25mV(100) / .97mA \approx 2.6K\Omega$$

$$g_m = I_C / V_T = .97mA / 25mV \approx 39mA/V$$

Prob.

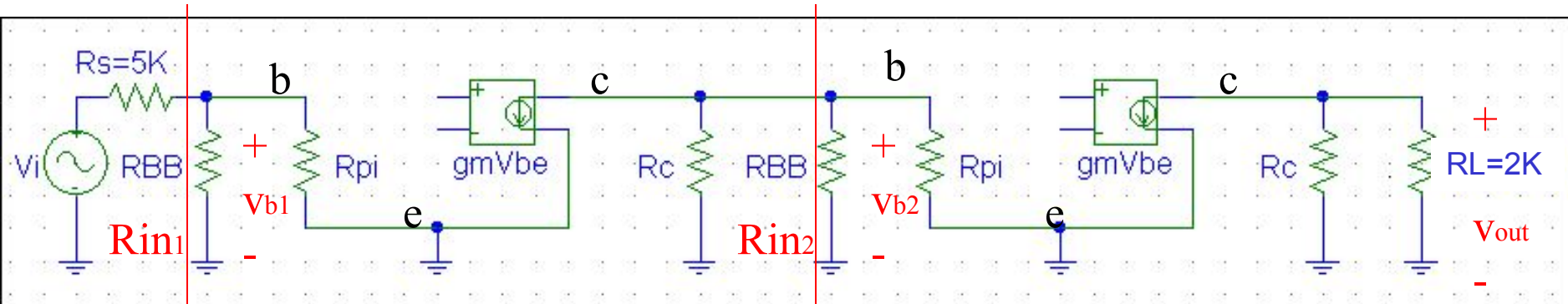

(c) find R_{in1}

$$\begin{aligned} R_{in1} &= R_{BB} \parallel R_{pi} \\ &= 32K \parallel 2.6K \\ &= 2.4K\Omega \end{aligned}$$

find v_{b1}/v_i

$$\begin{aligned} &= R_{in1} / [R_{in1} + R_s] \\ &= 2.4K / [2.4K + 5K] \\ &= 0.32 \end{aligned}$$


(d) find R_{in2}

$$\begin{aligned} R_{in2} &= R_{BB} \parallel R_{pi} \\ &= 2.4K\Omega \end{aligned}$$

find v_{b2}/v_{b1}

$$\begin{aligned} v_{b2} &= -g_m v_{be1} [R_C \parallel R_{BB} \parallel R_{pi}] \\ v_{b2}/v_{be1} &= -g_m [R_C \parallel R_{BB} \parallel R_{pi}] \\ v_{b2}/v_{b1} &= -(39mA/V) [6.8 \parallel 32K \parallel 2.6K] \\ &= -69.1 \end{aligned}$$

Prob.

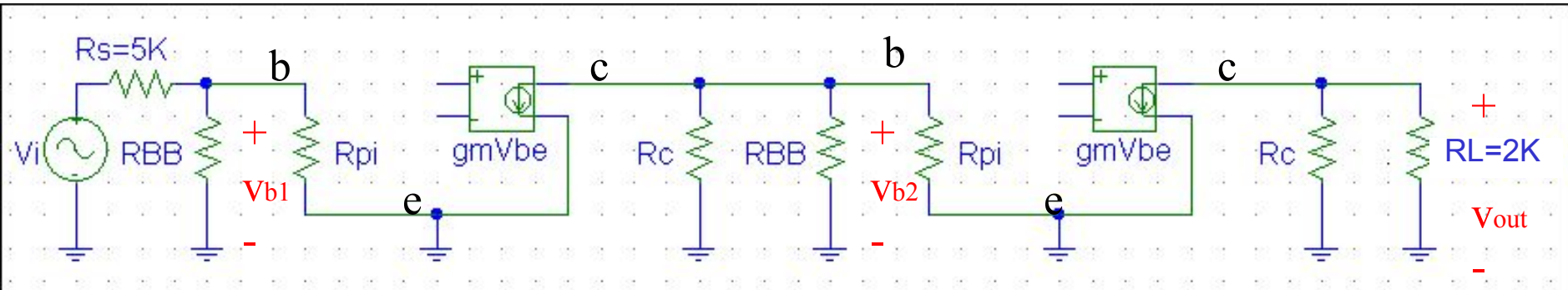

(e) find v_{out}/v_{b2}

$$v_{out} = -g_m v_{be2} [R_C || R_L]$$

$$v_{out}/v_{be2} = -g_m [R_C || R_L]$$

$$\begin{aligned} v_{b2}/v_{b1} &= -(39 \text{ mA/V}) [6.8 \text{ K} || 2 \text{ K}] \\ &= -60.3 \end{aligned}$$


(f) find overall voltage gain

$$v_{out}/v_i = (v_{b1}/v_i) (v_{b2}/v_{b1}) (v_{out}/v_{b2})$$

$$v_{out}/v_i = (0.32) (-69.1) (-60.3)$$

$$v_{out}/v_i = 1332$$

Prob.

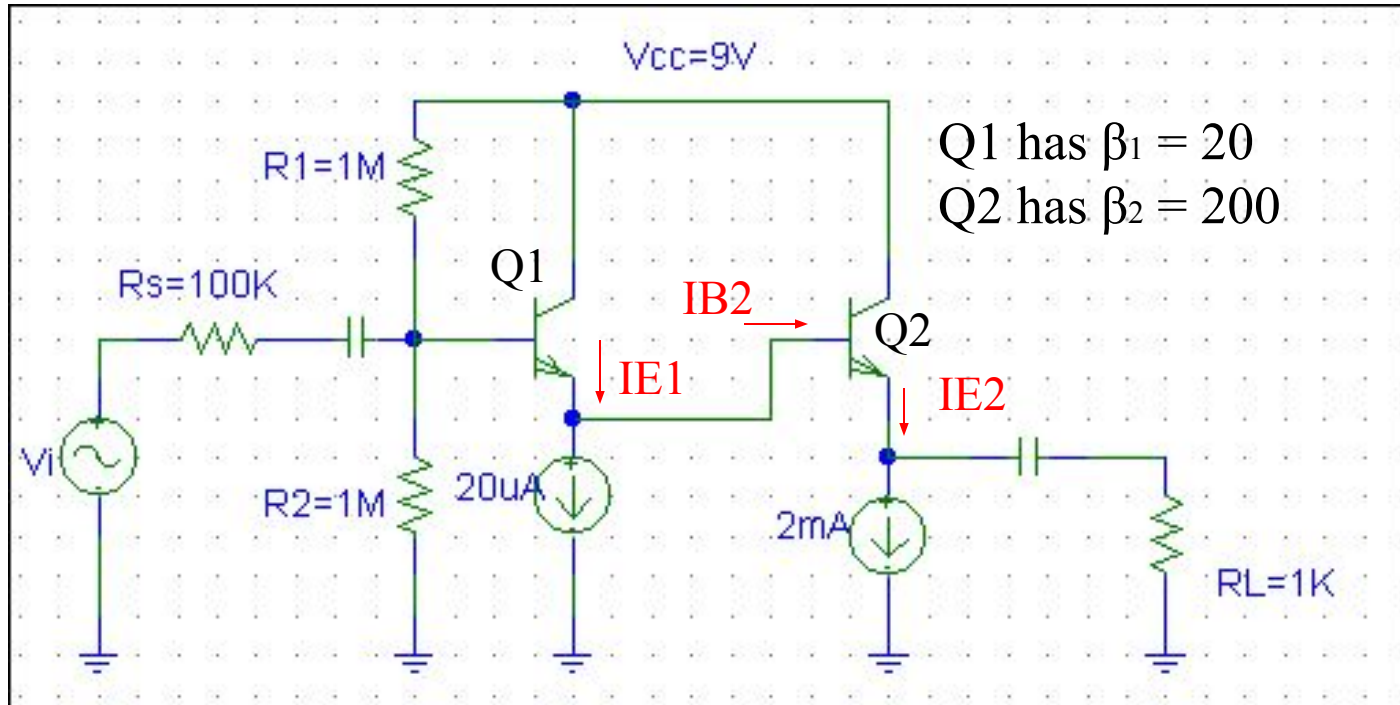

Find I_{E1} , I_{E2} , V_{B1} , and V_{B2}

$$I_{E2} = 2mA$$

$$I_{E1} = I_{20\mu A} + I_{B2}$$

$$I_{E1} = I_{20\mu A} + I_{E2}/\beta_2$$

$$I_{E1} = 20\mu A + 10\mu A$$

$$I_{E1} = 30\mu A$$


Prob.

Find V_{B1} , and V_{B2}


Use Thevenin equivalent

$$\begin{aligned} V_{B1} &= V_{BB1} - I_{B1}(R_{BB1}) \\ &= 4.5 - (30\mu\text{A}/20)500\text{K} \\ &= 3.8\text{V} \end{aligned}$$
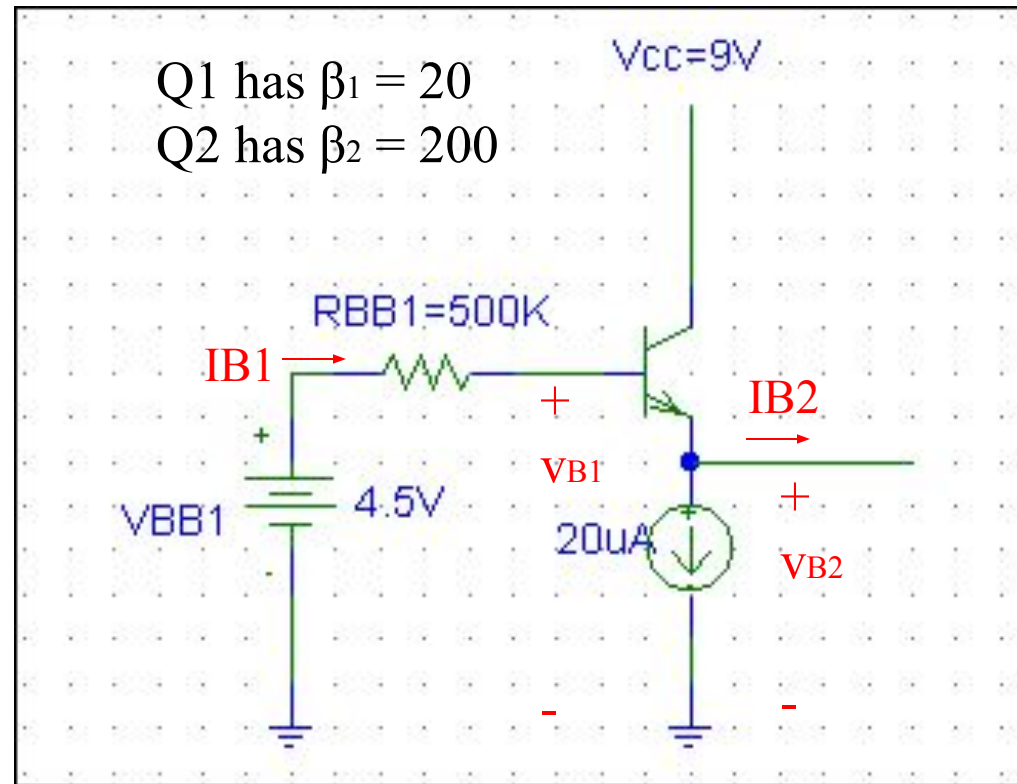
$$\begin{aligned} V_{B2} &= V_{B1} - V_{BE} \\ &= 3.8\text{V} - 0.7 \\ &= 3.1\text{V} \end{aligned}$$



Prob.

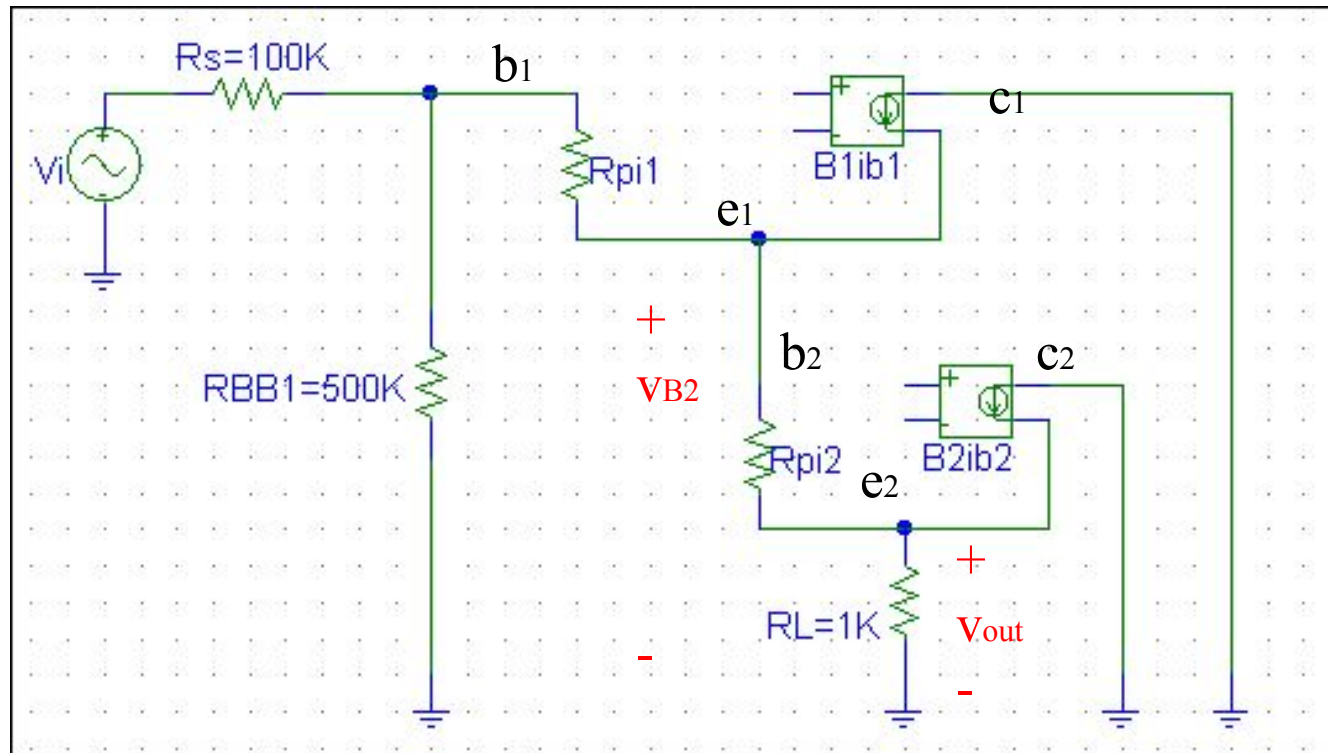

$$\begin{aligned}
 R_{pi2} &= V_T / I_{B2} \\
 &= V_T \beta_2 / I_{E2} \\
 &= 25\text{mV}(200) / 2\text{mA} \\
 &= 2.5\text{K}\Omega
 \end{aligned}$$


(b) find V_{out}/V_{b2}

$$V_{out} = (i_{b2} + \beta_2 i_{b2}) R_L$$

$$V_{b2} = (i_{b2} + \beta_2 i_{b2}) R_L + i_{b2} R_{pi2}$$

$$\begin{aligned}
 V_{out}/V_{b2} &= (1 + \beta_2) R_L / [(1 + \beta_2) R_L + R_{pi2}] \\
 &= (1 + 200) 1\text{K} / [(1 + 200) 1\text{K} + 2.5\text{K}] \\
 &\approx 0.988
 \end{aligned}$$

Prob.

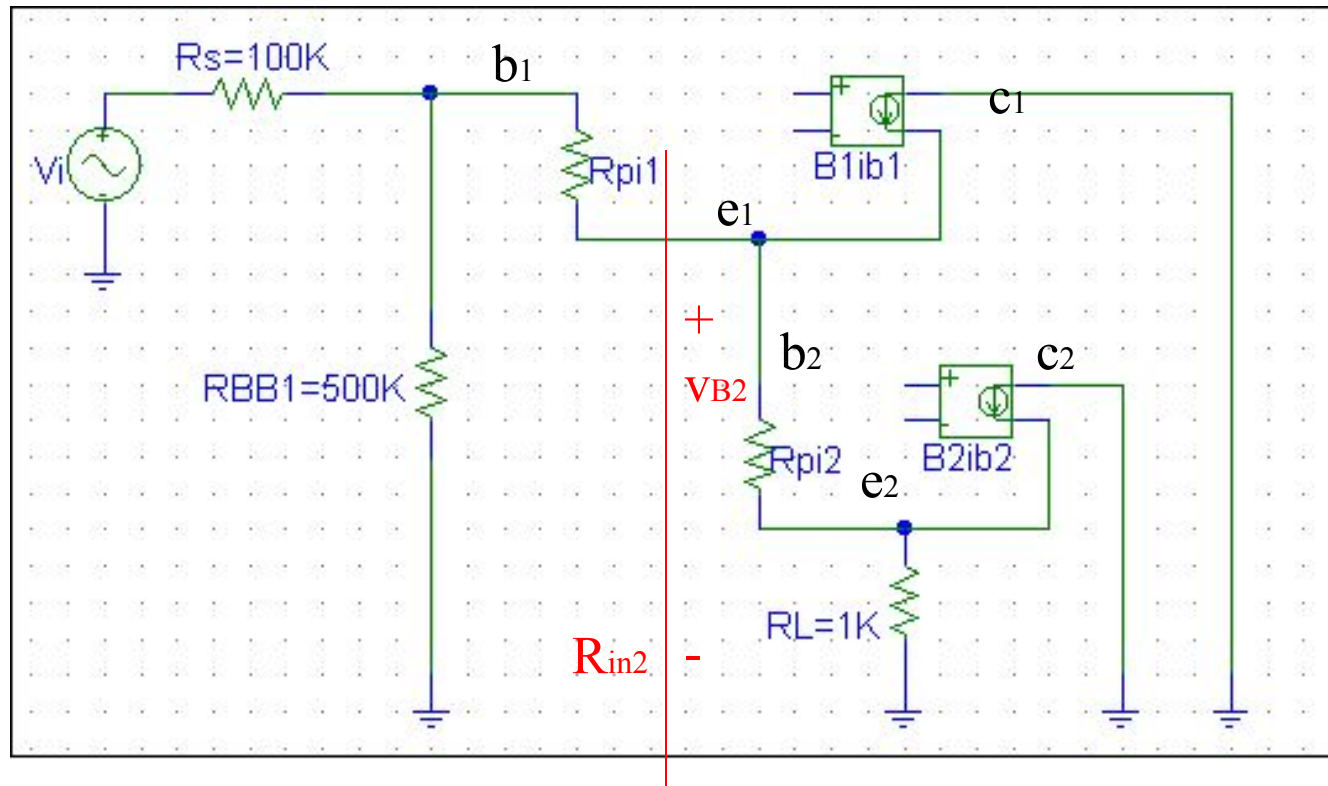


(b) find $R_{in2} = v_{b2}/i_{b2}$

$$v_{b2} = (i_{b2} + \beta_2 i_{b2})R_L + i_{b2}R_{pi2}$$


$$\begin{aligned} R_{in2} &= v_{b2}/i_{b2} = (1 + \beta_2)R_L + R_p \\ &= (1 + 200)1K + 2.5K \\ &\approx 204K \end{aligned}$$

Prob.

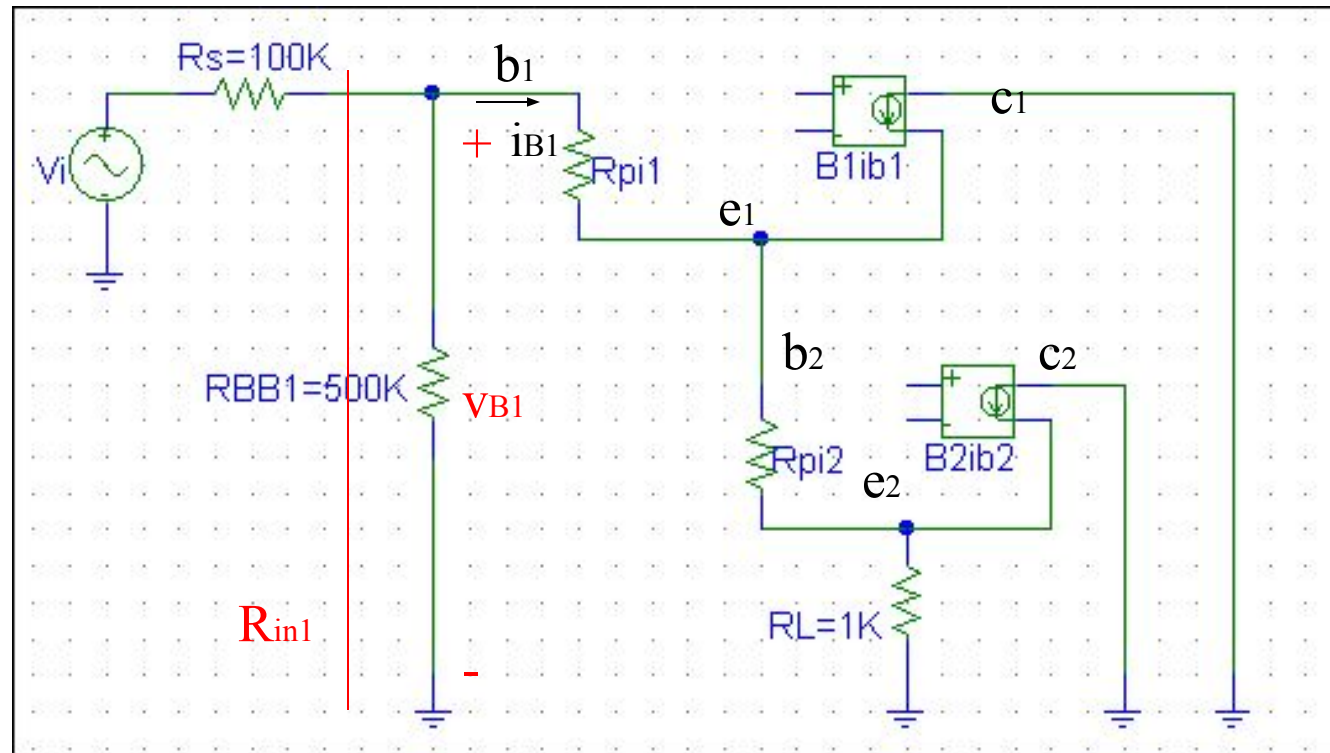

$$\begin{aligned}
 \text{(c) find } R_{in1} &= R_{BB1} \parallel (V_{b1}/i_{b1}) \\
 &= R_{BB1} \parallel [i_{b1}R_{pi1} + (i_{b1} + \beta_1 i_{b1})R_{in2}]/i_{b1} \\
 &= R_{BB1} \parallel [R_{pi1} + (1 + \beta_1)R_{in2}], \\
 \text{where } R_{pi1} &= V_T \beta_1 / I_{E1} = 25\text{mV}(20)/30\mu\text{A} = 16.7\text{K} \\
 &= 500\text{K} \parallel [16.7\text{K} + (1 + 20)204\text{K}] \\
 &\approx 500\text{K}\Omega
 \end{aligned}$$

Prob.

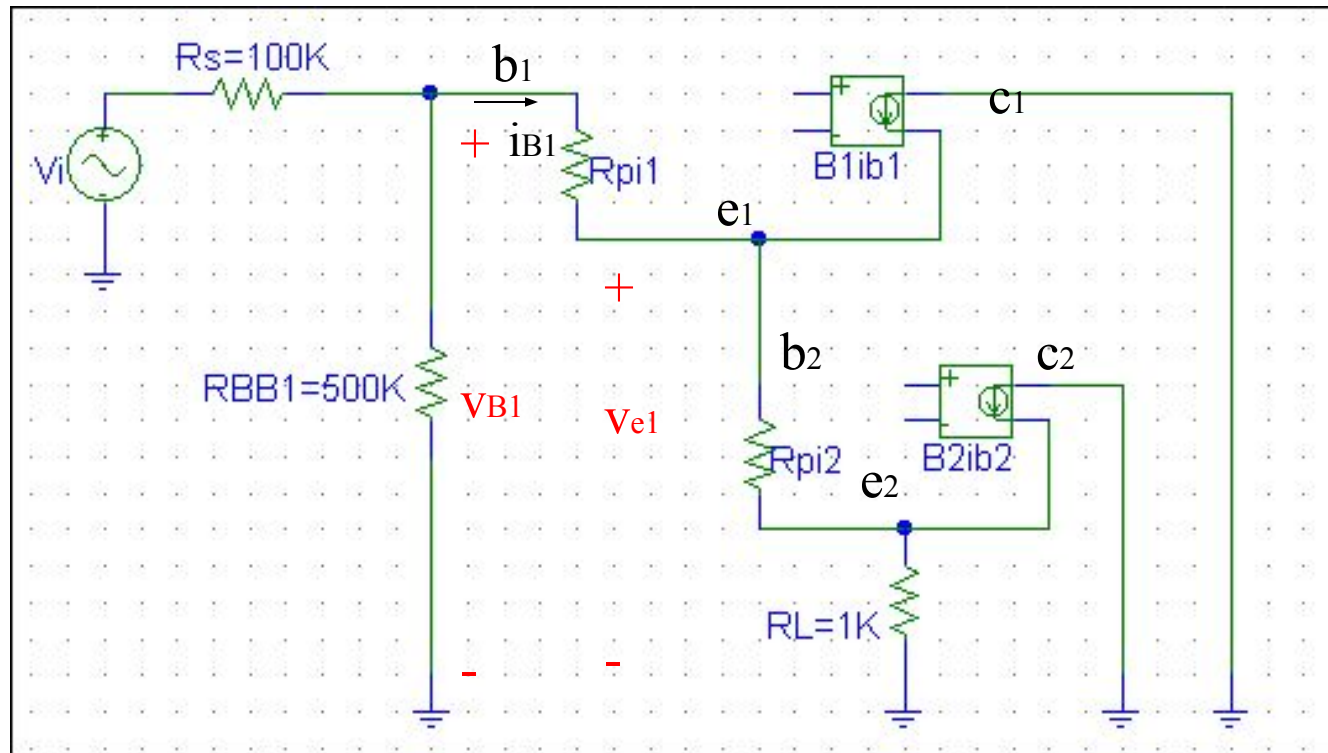


(c) find v_{e1}/v_{b1}

$$v_{e1} = (i_{b1} + \beta_1 i_{b1}) R_{in2}$$

$$v_{b1} = (i_{b1} + \beta_1 i_{b1}) R_{in2} + i_{b1} R_{pi1}$$

$$\begin{aligned} v_{e1}/v_{b1} &= (1 + \beta_1) R_{in2} / [(1 + \beta_1) R_{in2} + R_{pi1}] \\ &= (1 + 20) 204K / [(1 + 20) 204K + 16.7K] \\ &\approx 0.996 \end{aligned}$$

Prob.

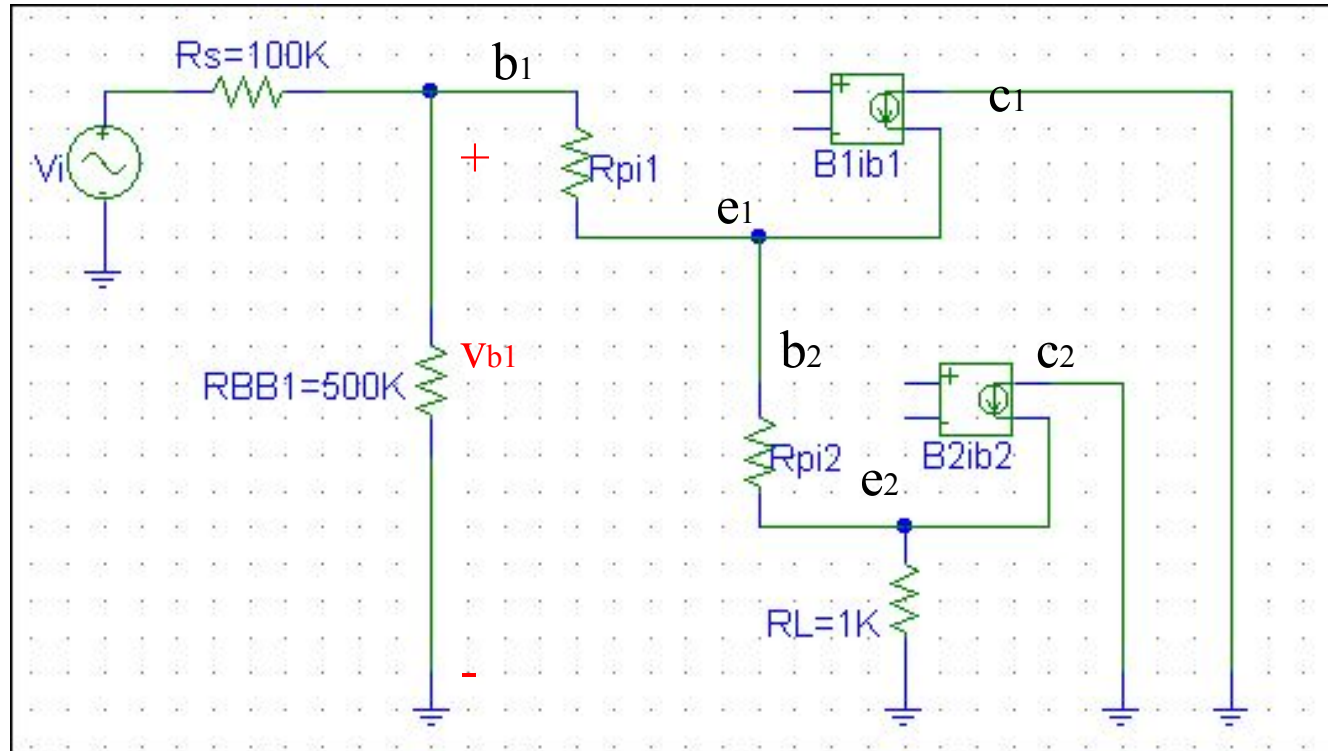


(d) find v_{b1}/v_i

$$\begin{aligned} v_{b1}/v_i &= R_{in1}/[R_S + R_{in1}] \\ &= 0.82 \end{aligned}$$

(e) find overall voltage gain


$$\begin{aligned} v_{out}/v_i &= (v_{b1}/v_i) (v_{e1}/v_{b1}) (v_{out}/v_{e1}) \\ v_{out}/v_i &= (0.82) (0.99) (0.99) \\ v_{out}/v_i &= 0.81 \end{aligned}$$

Voltage outputs at each stage

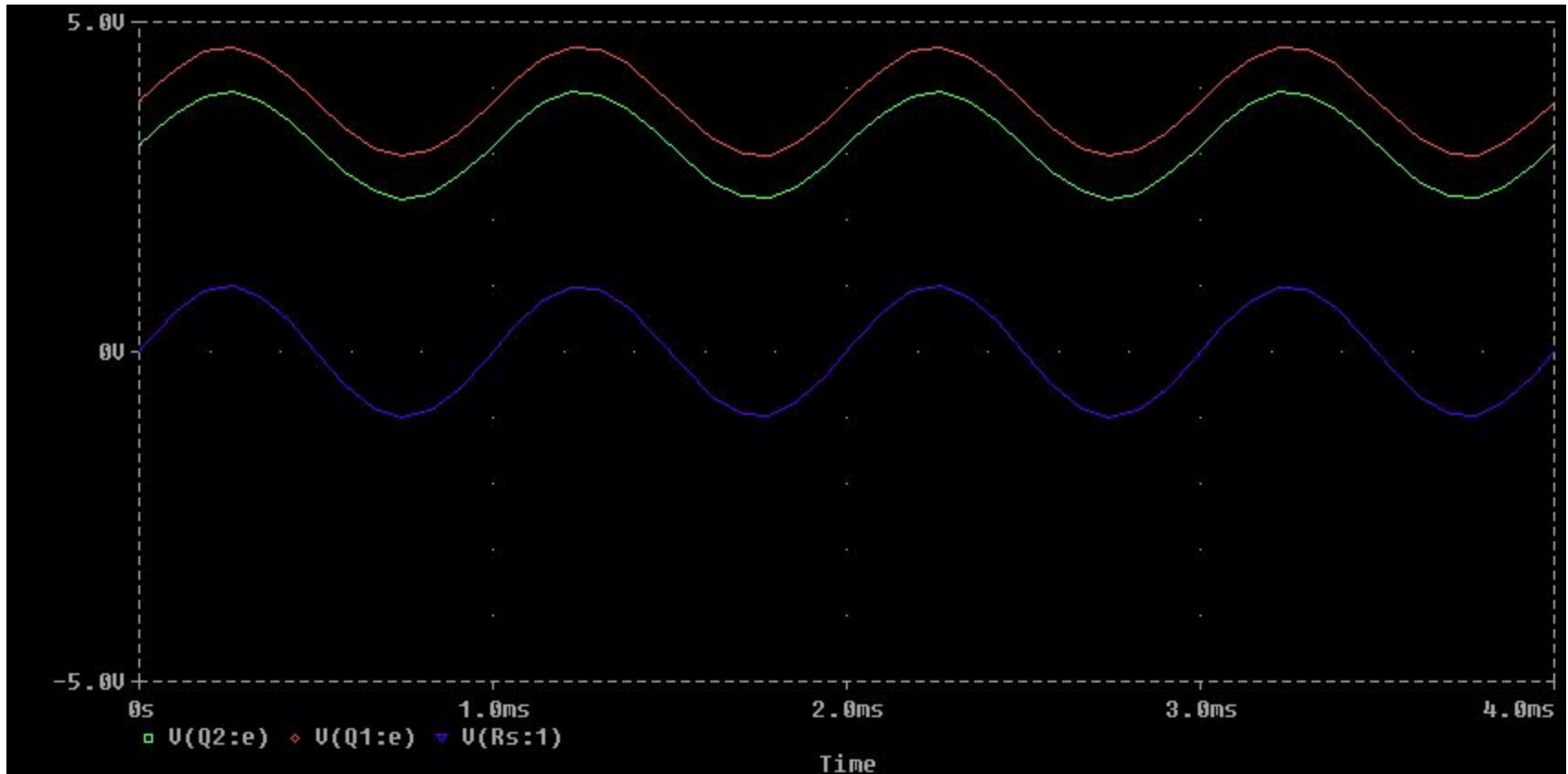

Output of stage 2 Output of stage 1 Input


Current

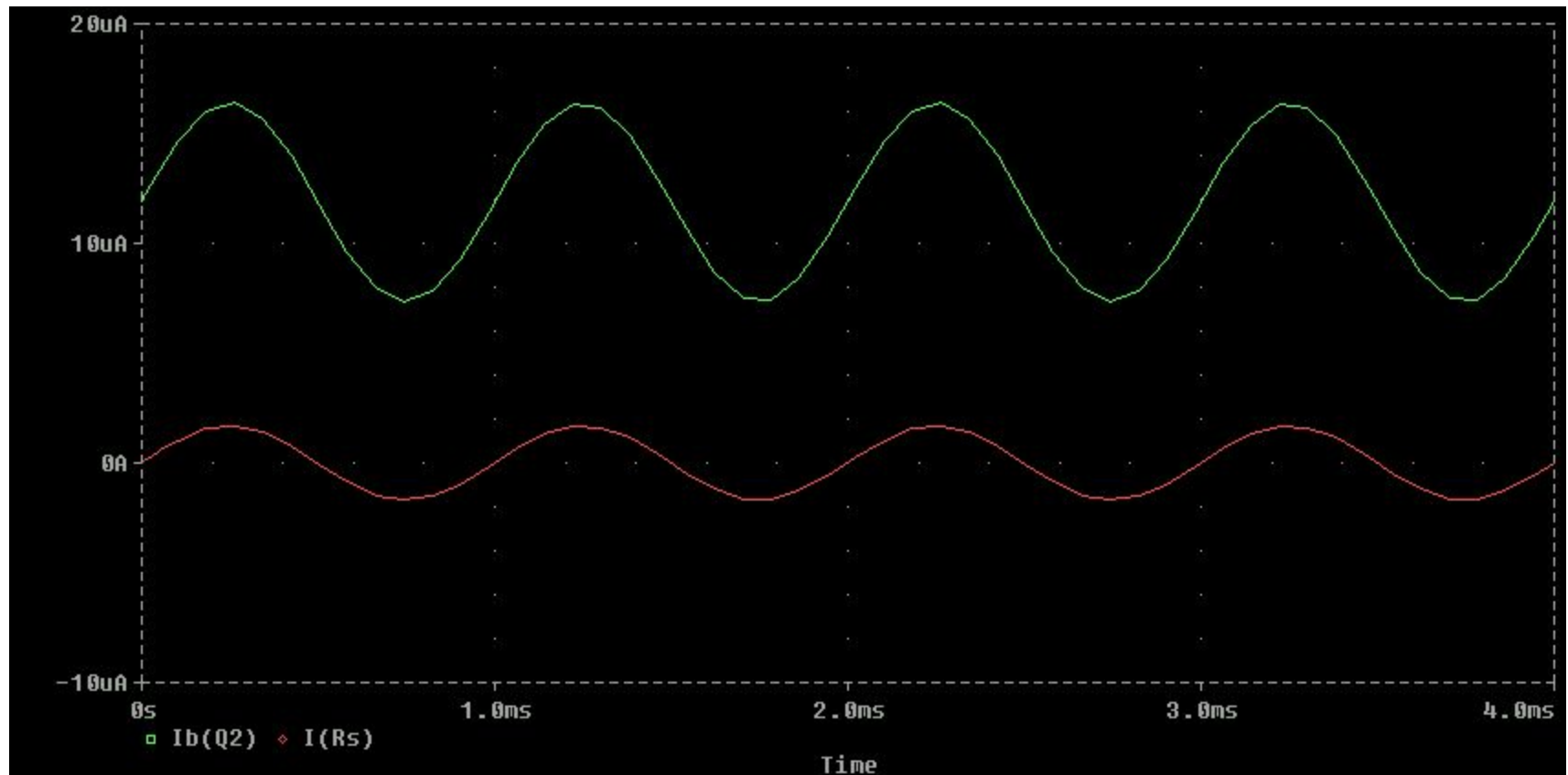

Input to
stage 2 (i_{b2})

Input
current


Current

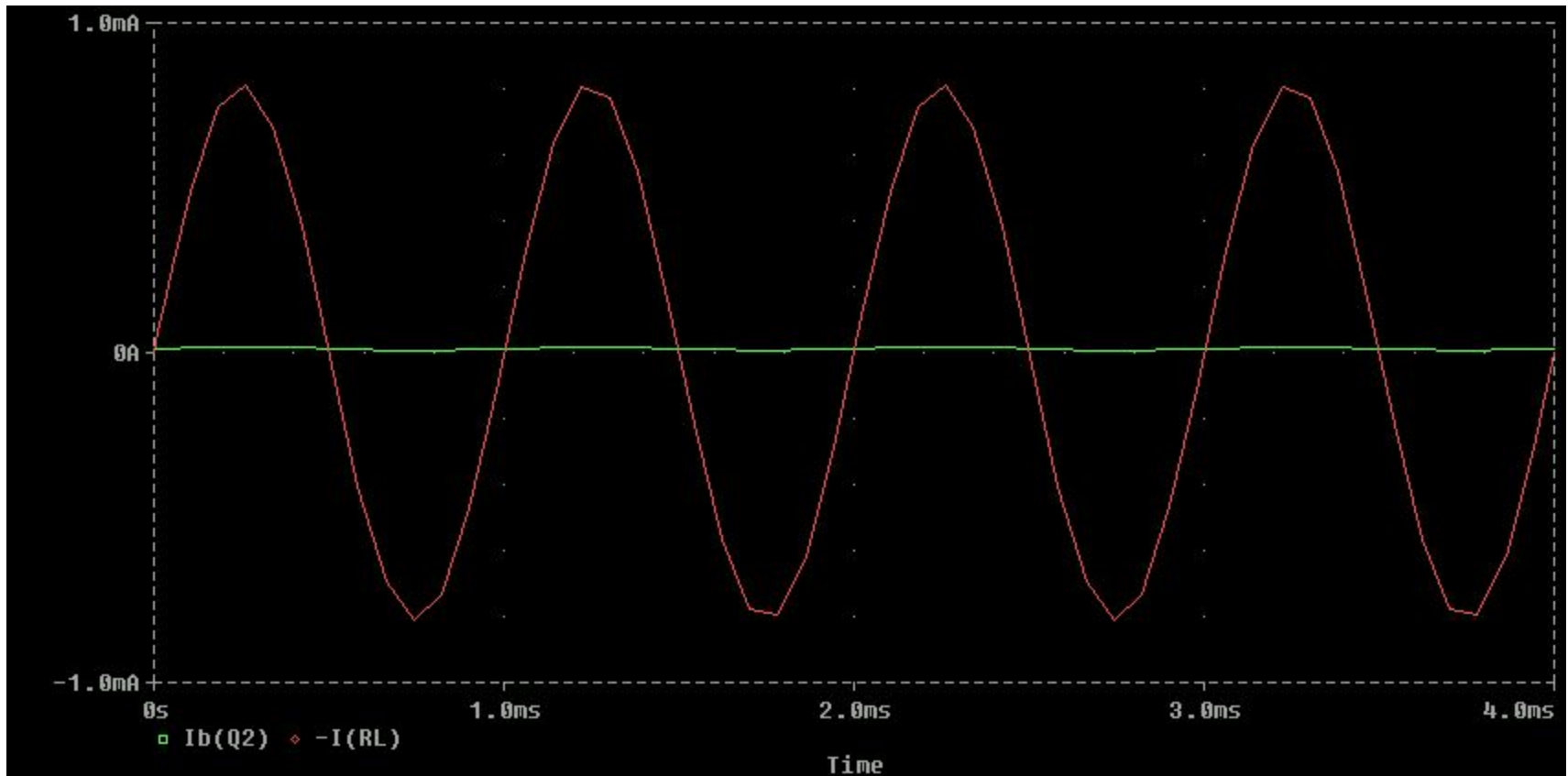

Input to
stage 2 (i_{b2})

output
current

Current

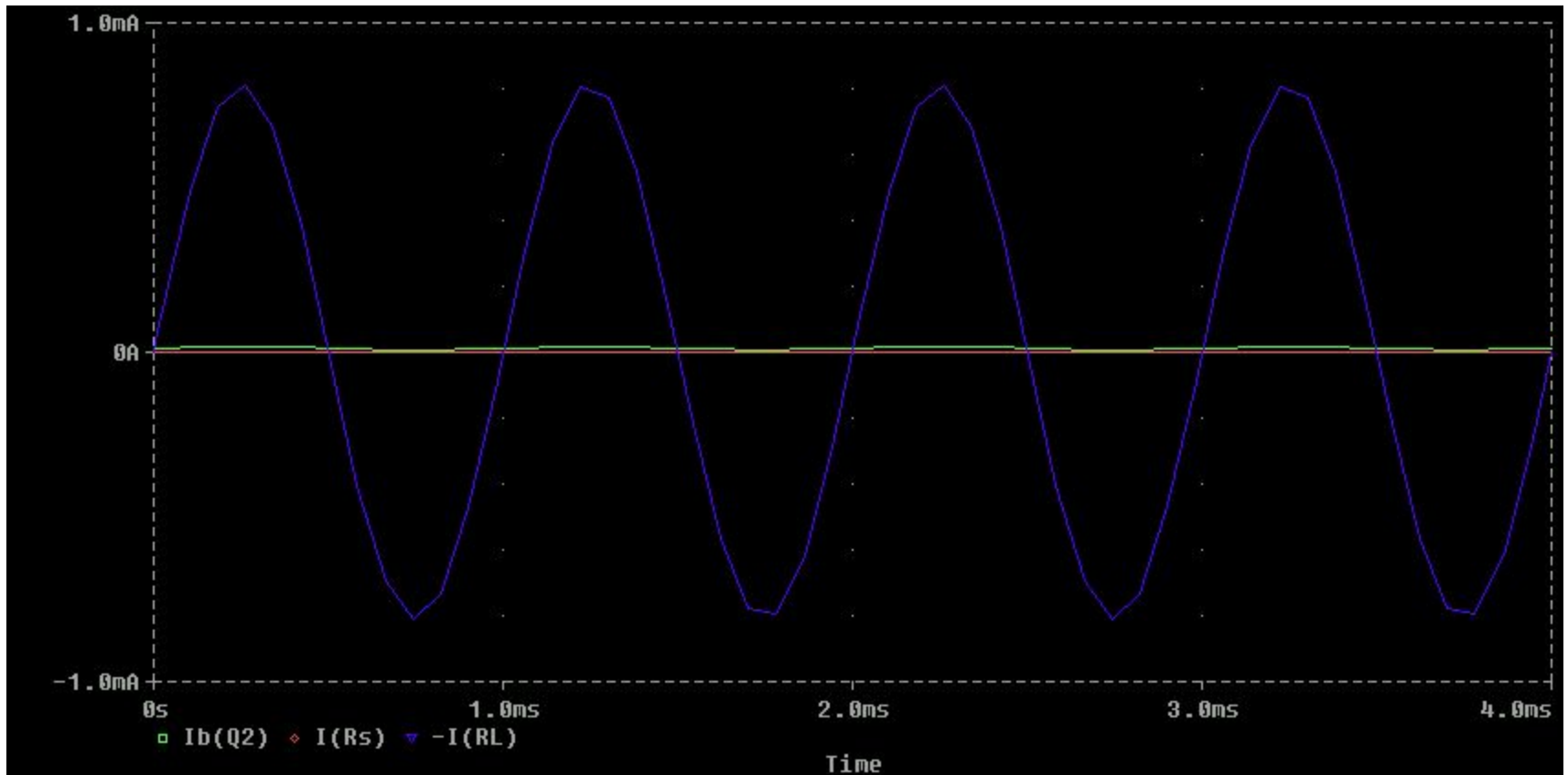

Input to
stage 2 (i_{b2})

**Input
current**

output
current

Power and current gain

$$\text{Input current} = (V_i)/R_{in} = 1/500K = 2.0\mu A$$

$$\text{output current} = (V_{out})/R_L = (0.81V)/1K = 0.81mA$$


$$\text{current gain} = 0.81mA / 2.0\mu A = 405$$

$$\text{Input power} = (V_i) (V_i)/R_{in} = 1 \times 1/500K = 2.0\mu W$$

$$\text{output power} = (V_{out}) (V_{out})/R_L = (0.81V) (0.81V)/1K = 656\mu W$$


$$\text{power gain} = 656\mu W / 2\mu W = 329$$

BJT Output Characteristics

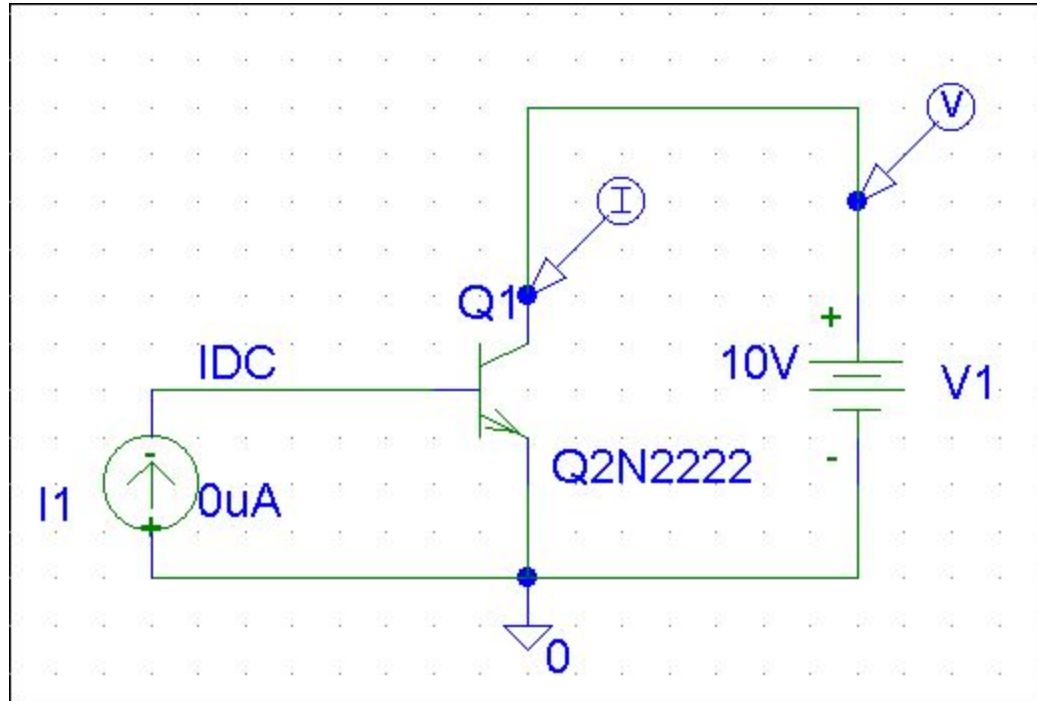


- Plot I_c vs. V_{ce} for multiple values of V_{ce} and I_b
- From **Analysis** menu use **DC Sweep**
- Use **Nested sweep** in **DC Sweep** section

Probe: BJT Output Characteristics

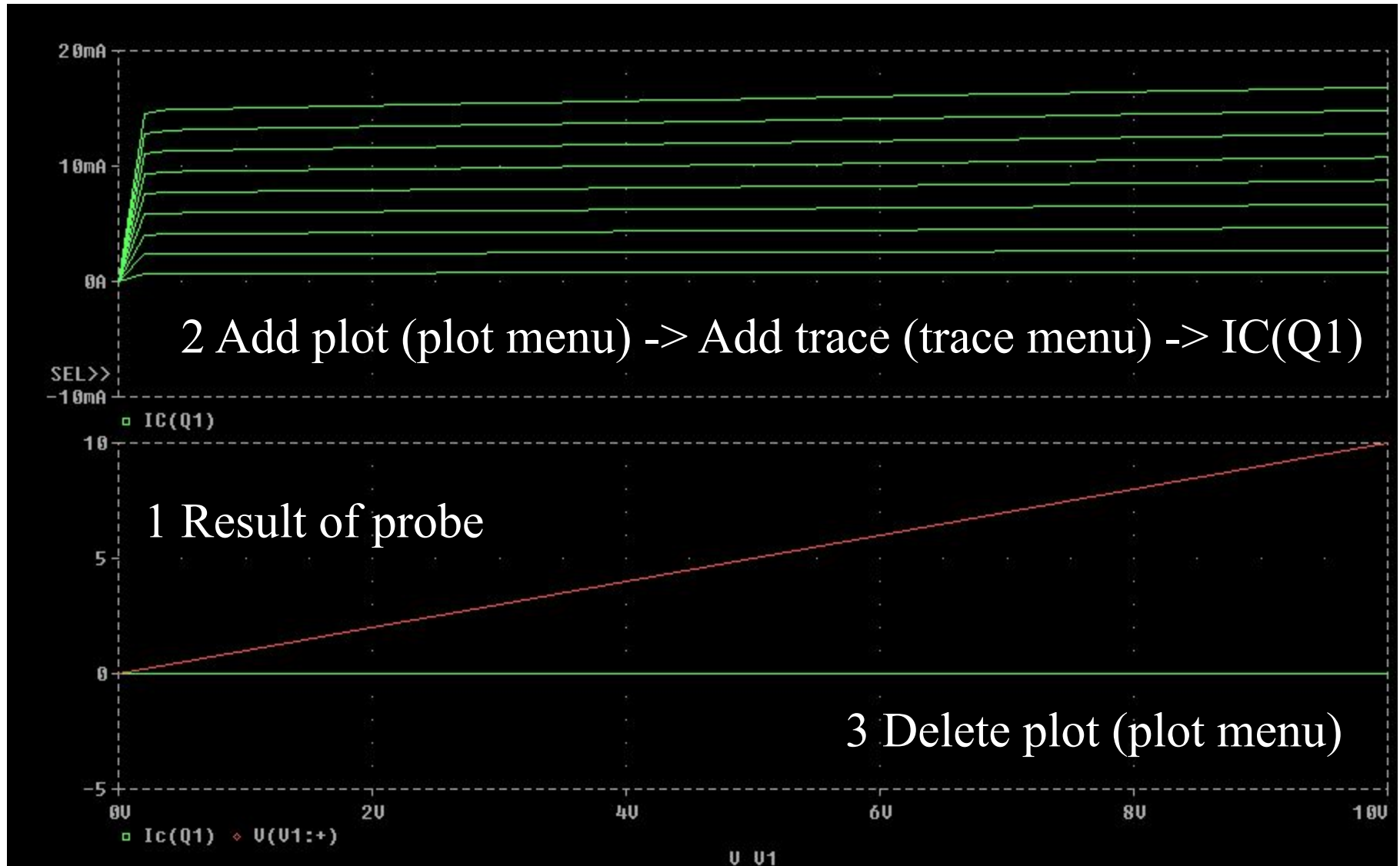


BJT Output Characteristics: current gain

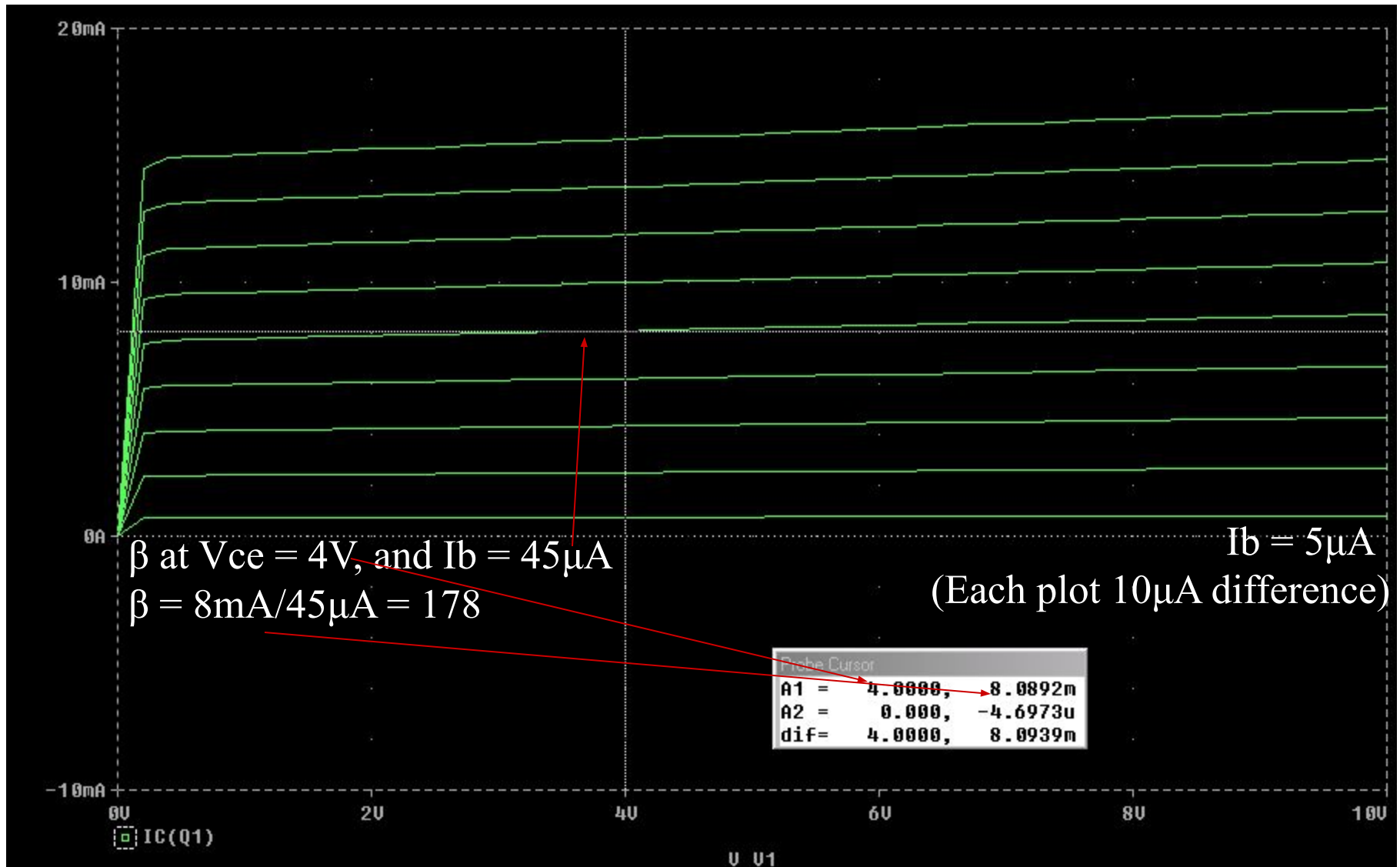

BJT Output Characteristics: transistor output resistance




CE Amplifier: Measurements with Spice

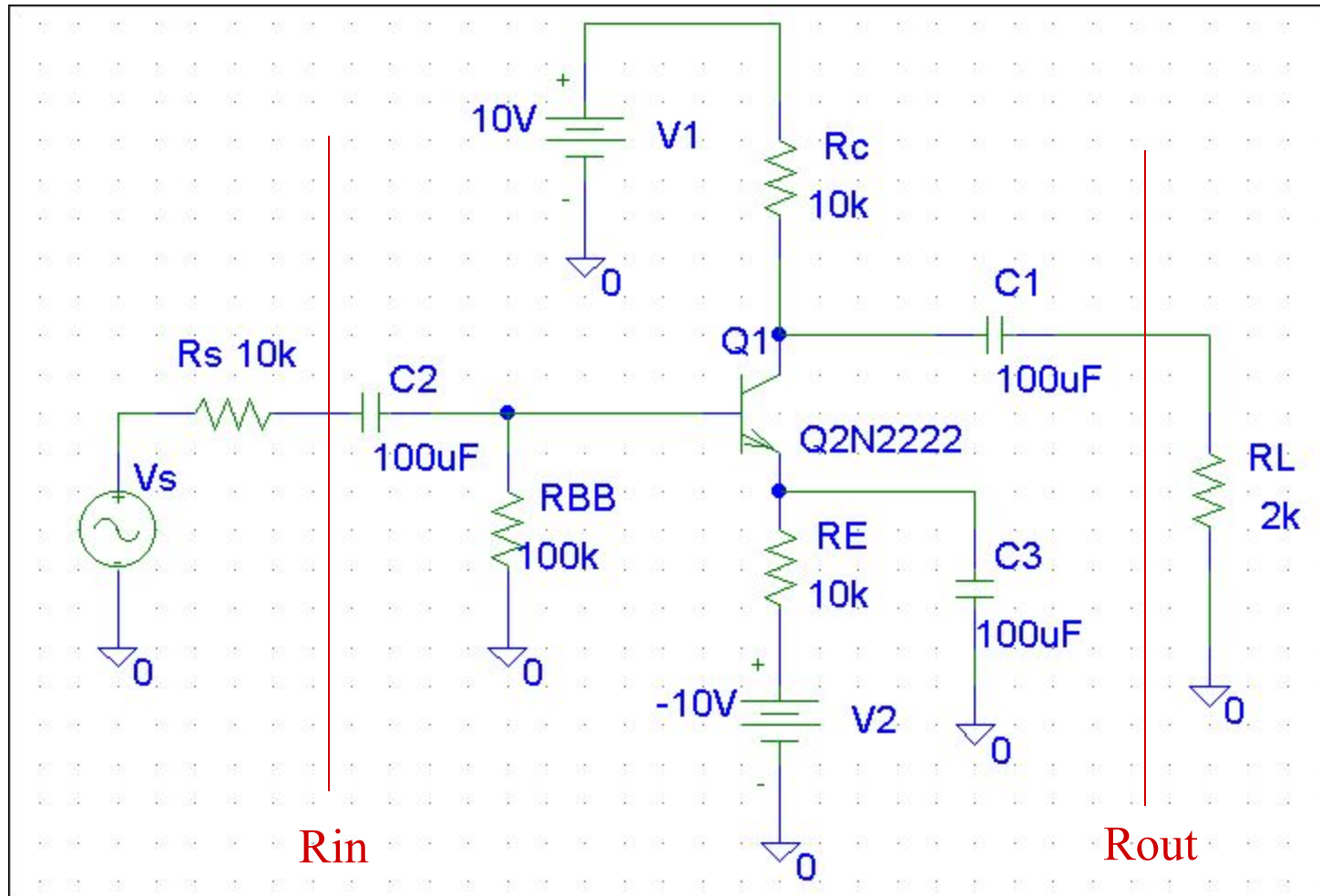


Input Resistance Measurement Using SPICE

- Replace source, V_s and R_s with V_{in} , measure $R_{in} = V_{in}/I_{in}$
- Do not change DC problem: keep capacitive coupling if present
- Source (V_{in}) should be a high enough frequency so that capacitors act as shorts: $R_{cap} = |1/\omega C|$. For $C = 100\mu F$, $\omega = 1\text{KHz}$, $R_{cap} = 1/2\pi(1\text{K})(100\text{E-}6) \cong 1.6\Omega$
- V_{in} should have a small value so operating point does not change
 $V_{in} \cong 1\text{mV}$

Rin Measurement

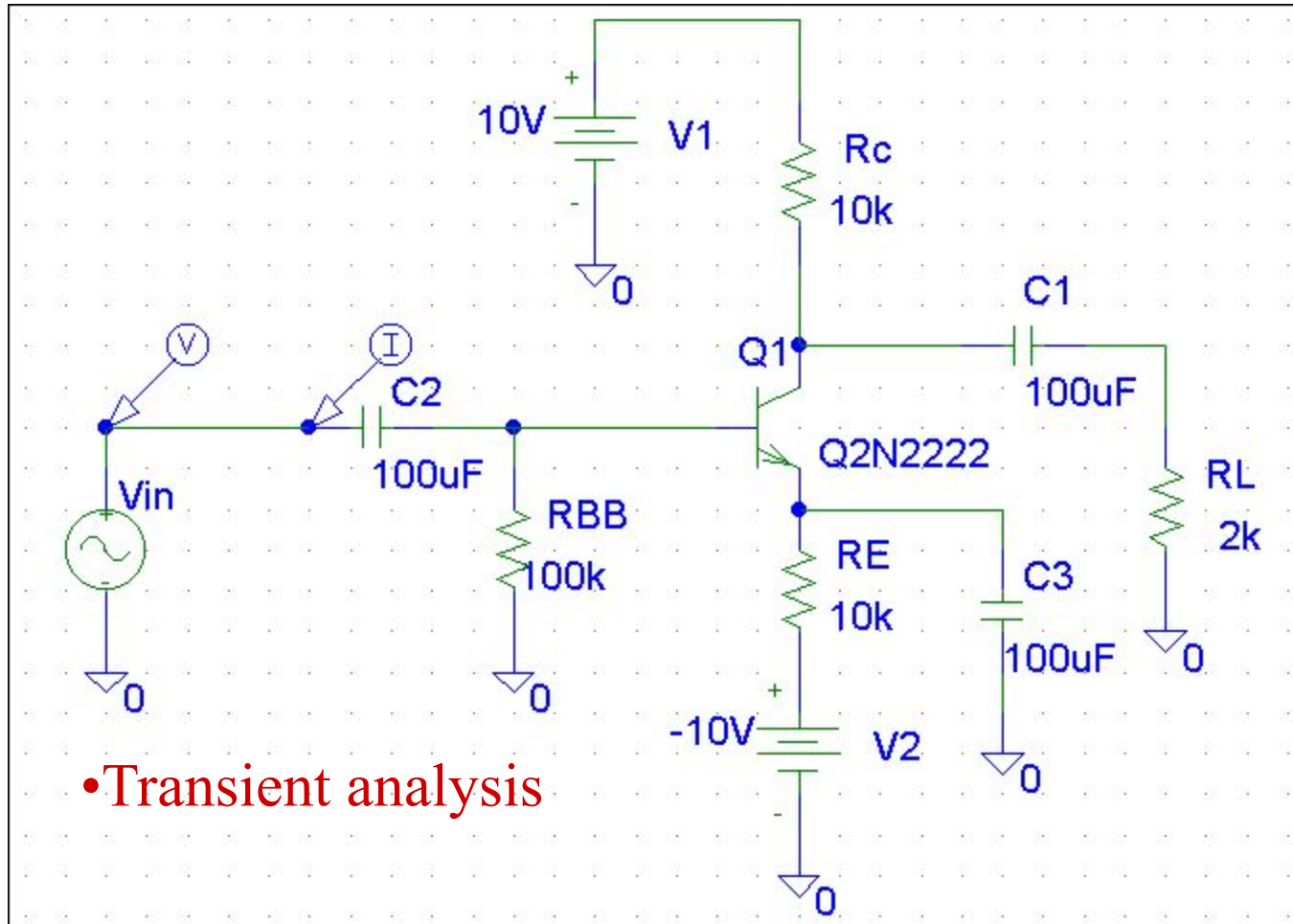


Probe results

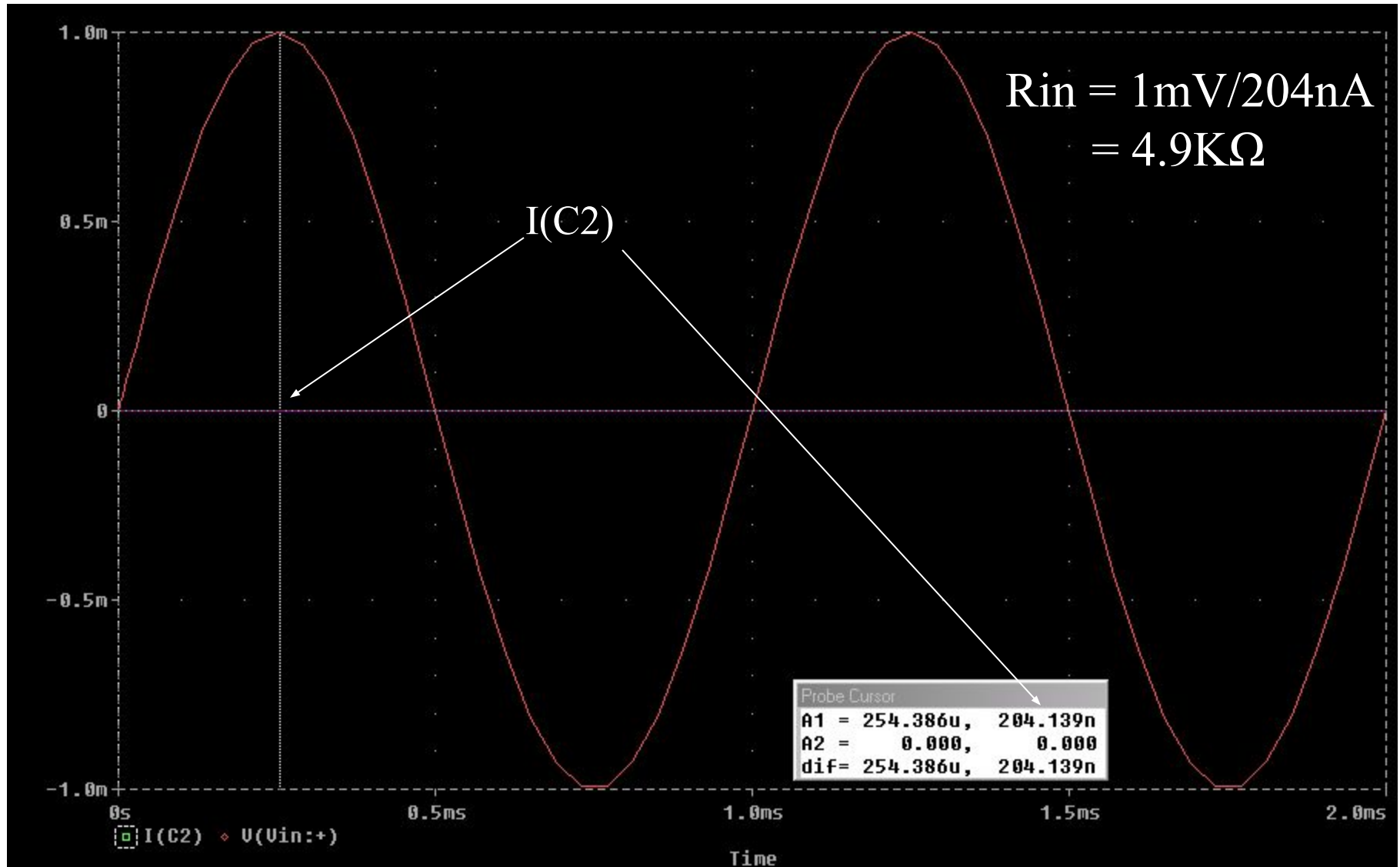


Output Resistance Measurement Using SPICE

- Replace load, R_L with V_{in} , measure $R_{in} = V_{in}/I_{in}$
- Set $V_s = 0$
- Do not change DC problem: keep capacitive coupling if present
- Source (V_{in}) should be a high enough frequency so that capacitors act as shorts: $R_{cap} = |1/\omega C|$. For $C = 100\mu F$, $\omega = 1\text{KHz}$, $R_{cap} = 1/2\pi(1\text{K})(100\text{E-}6) \cong 1.6\Omega$
- V_{in} should have a small value so operating point does not change
 $V_{in} \cong 1\text{mV}$

Route Measurement

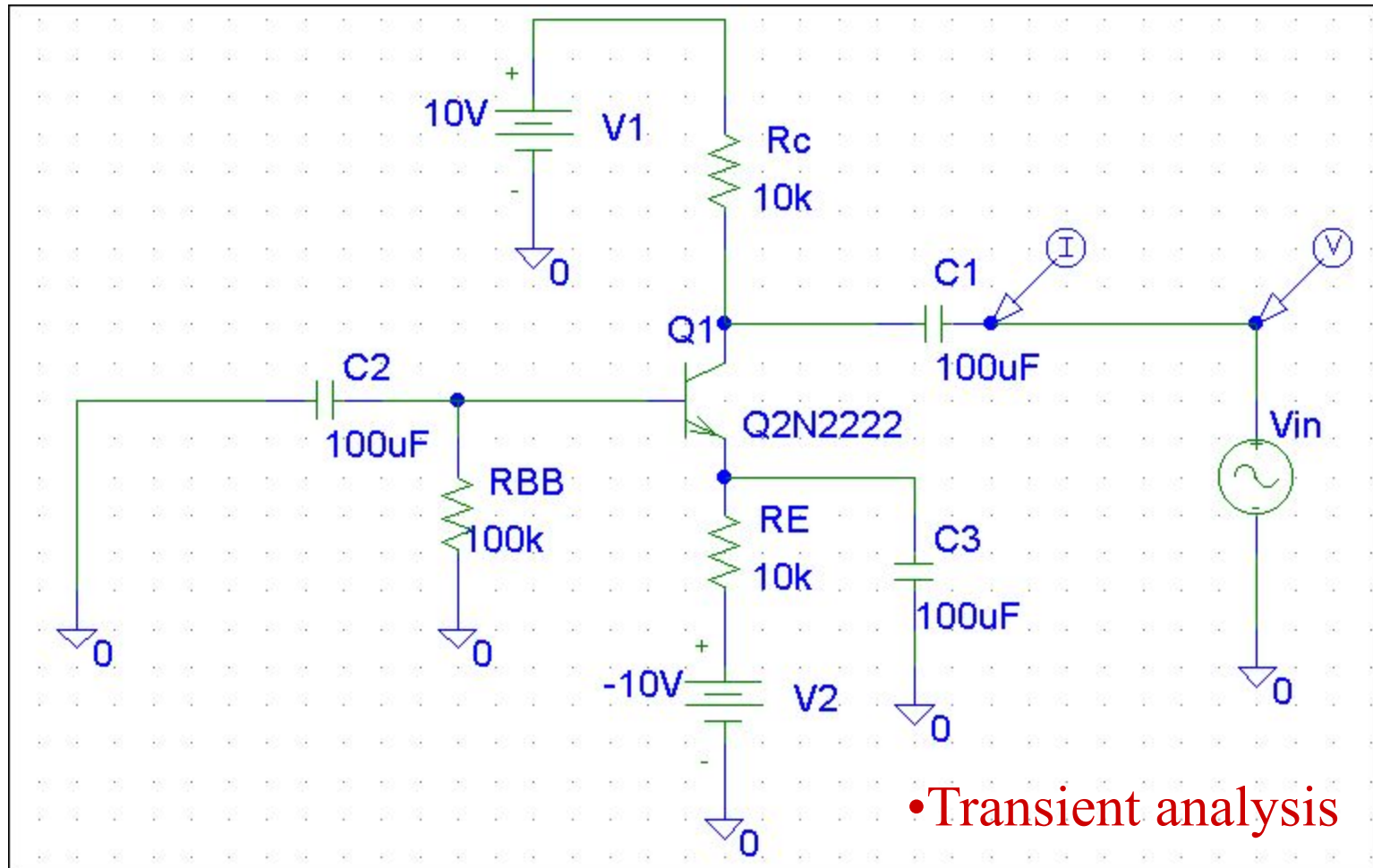


Probe results

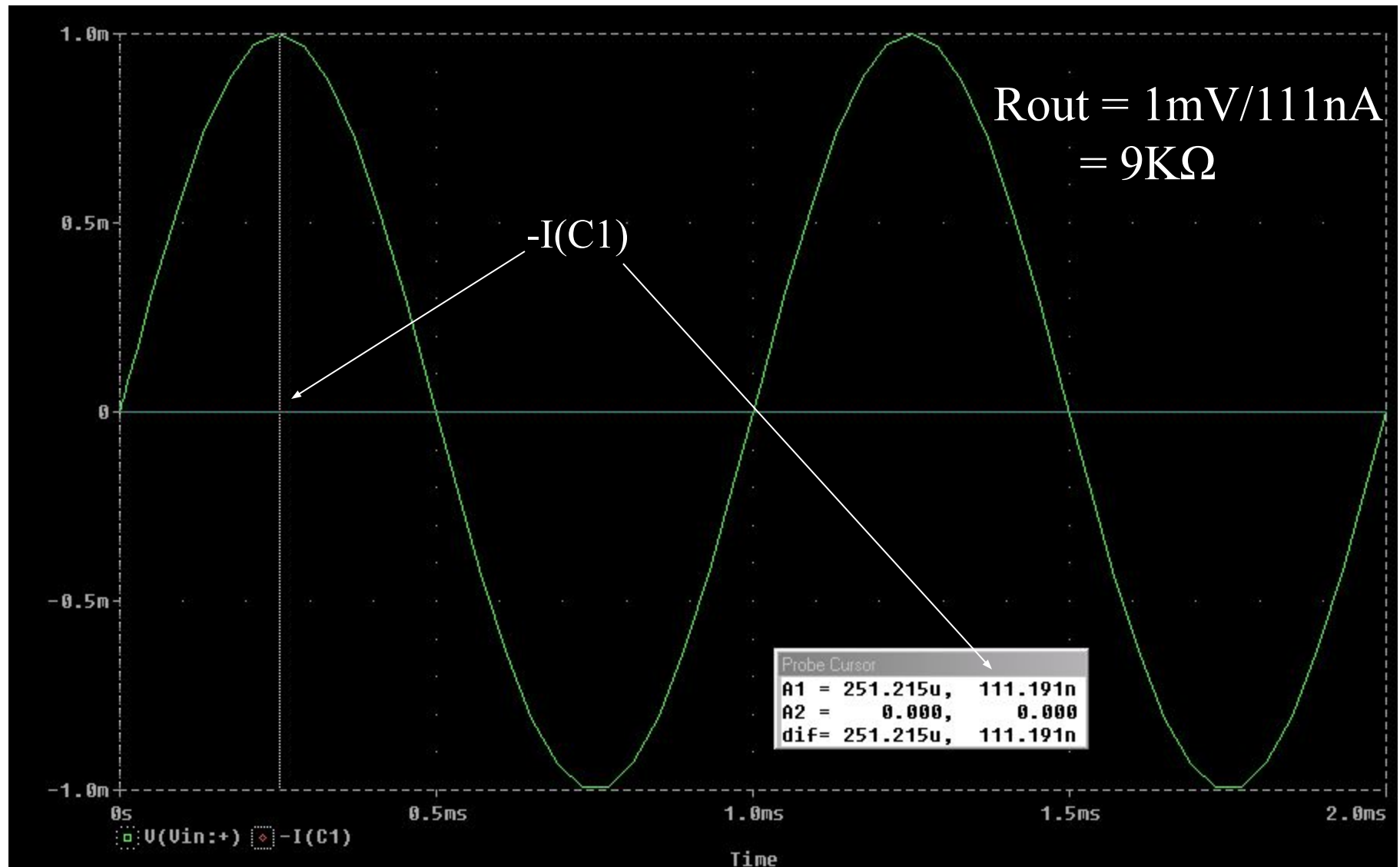

$-I(C1)$ is current in V_{in} flowing out of + terminal

DC Power measurements

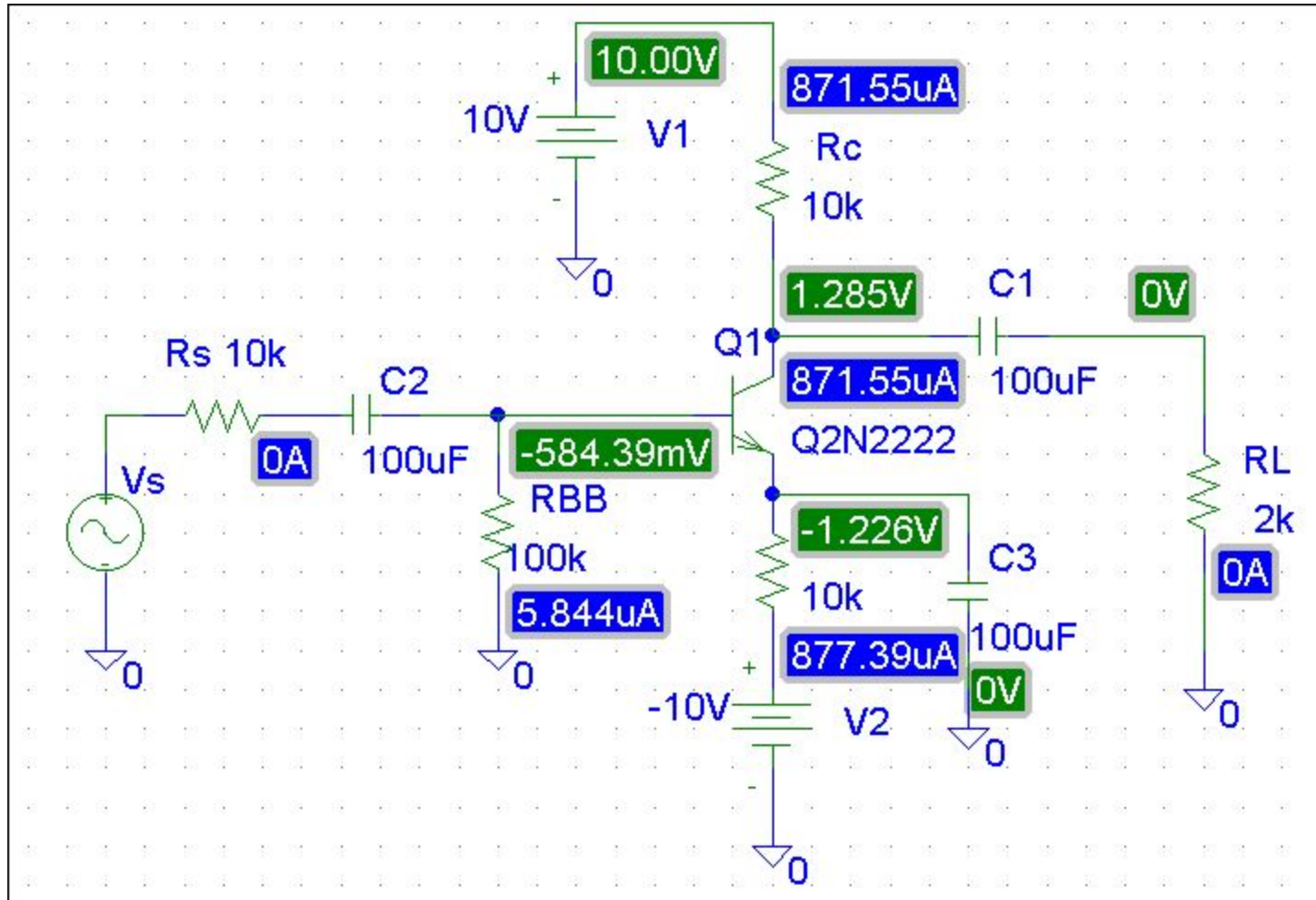

Power delivered by ± 10 sources:

$$(10)(872\mu\text{A}) + (10)(877\mu\text{A}) = 8.72\text{mW} + 8.77\text{mW} = 17.4\text{mW}$$

ac Power Measurements of Load

