

Система питания ноутбука

Введение и устранение неисправностей



PE

Mike Lee

03/29/2004

wistron

▶ Для кого эта презентация

Целевая аудитория

- Все электротехники, такие как:
 - PE, TE, FAE, CSD

Необходимые знания

- Электронные схемы
- Цифровые логические схемы
- Использование мультиметра

Содержание курса

- Система питания и последовательности
- Поиск неисправностей
- Выводы
 - Принцип передачи мощности (ШИМ-Plus импульсной модуляции & LDO –Low Drop-Out regulator)
 - Зарядное устройство

После этого курса Вы будете

- Уметь находить неисправности в цепях питания





План

План:

1. Архитектура цепей питания:

- 1.1 Введение в NB системы питания
- 1.2 Последовательность питания и управления

2. Введение в схему

питания:

- 2.1 Блок-схема цепей питания
- 2.2 NB power application
- 2.3 Multi-power device

3. No power debug

- 3.1 No power debug notice & sequence
- 3.2 DCBATOUT short(短路) to GND
- 3.2 S5 Power No Good
- 3.3 Power on logic No Good



Foreword

• Foreword :


Как мы знаем, ноутбук питание обеспечивается адаптерами (19V) или батареей (14.8V). Тем не менее, различные (不同的) напряжения питания не подходят (適合) все устройства к каждому ноутбуку. Так ряд действий по передаче напряжения необходимы для питания всех устройств. (Могут возникнуть проблемы (發生) во время передачи напряжения.)

Как ноутбук портативный компьютер, экономя энергию также очень важно, когда система находится в режиме работы от батареи.

В этом уроке, мы будем использовать схему питания Юхина внедрить систему питания ноутбука.


1. Power system architecture

1.1 NB (Yuhina) power system : AUX Power

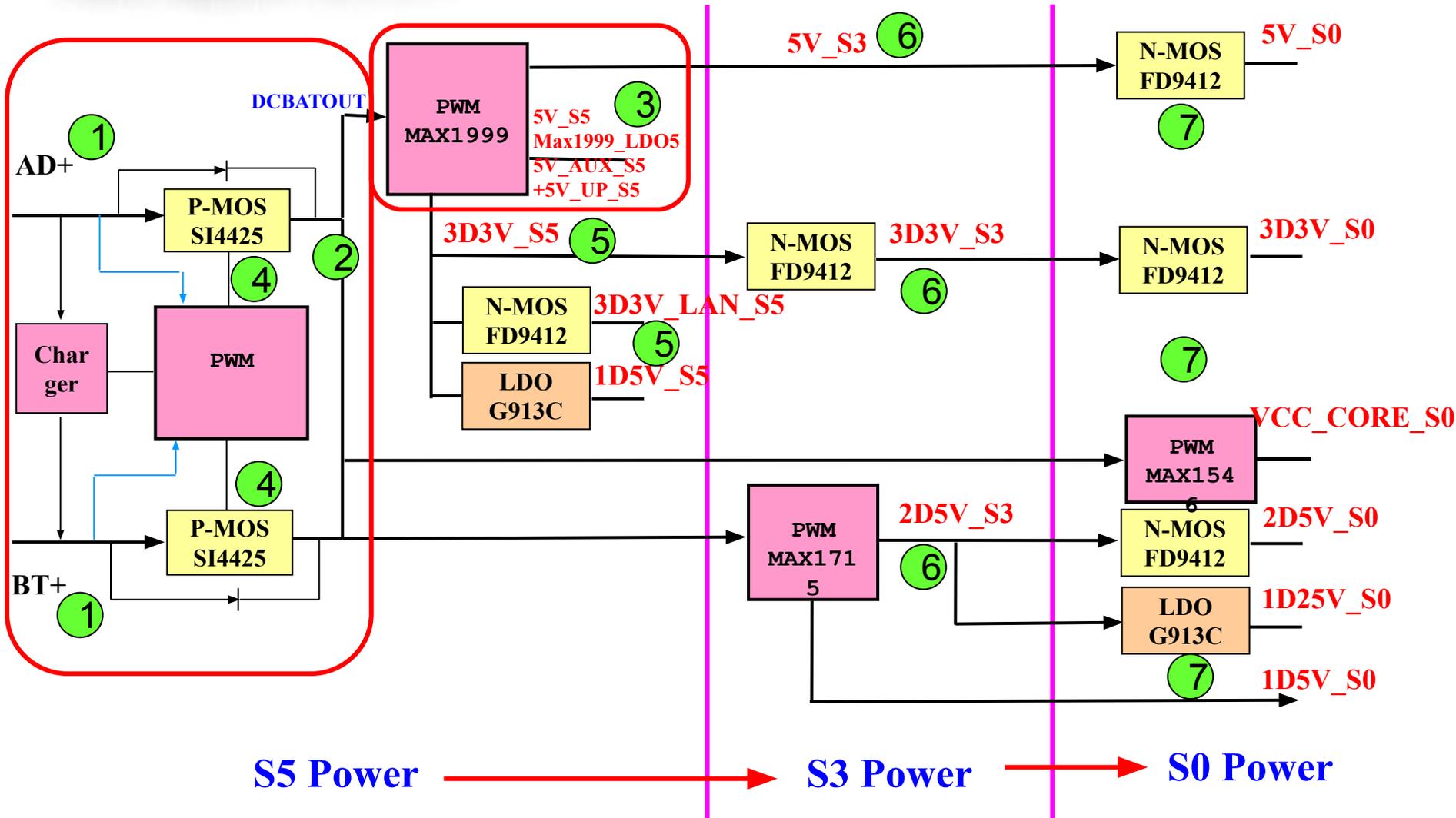


1. Power system architecture

1.1 NB (Yuhina) power system : S5 Power

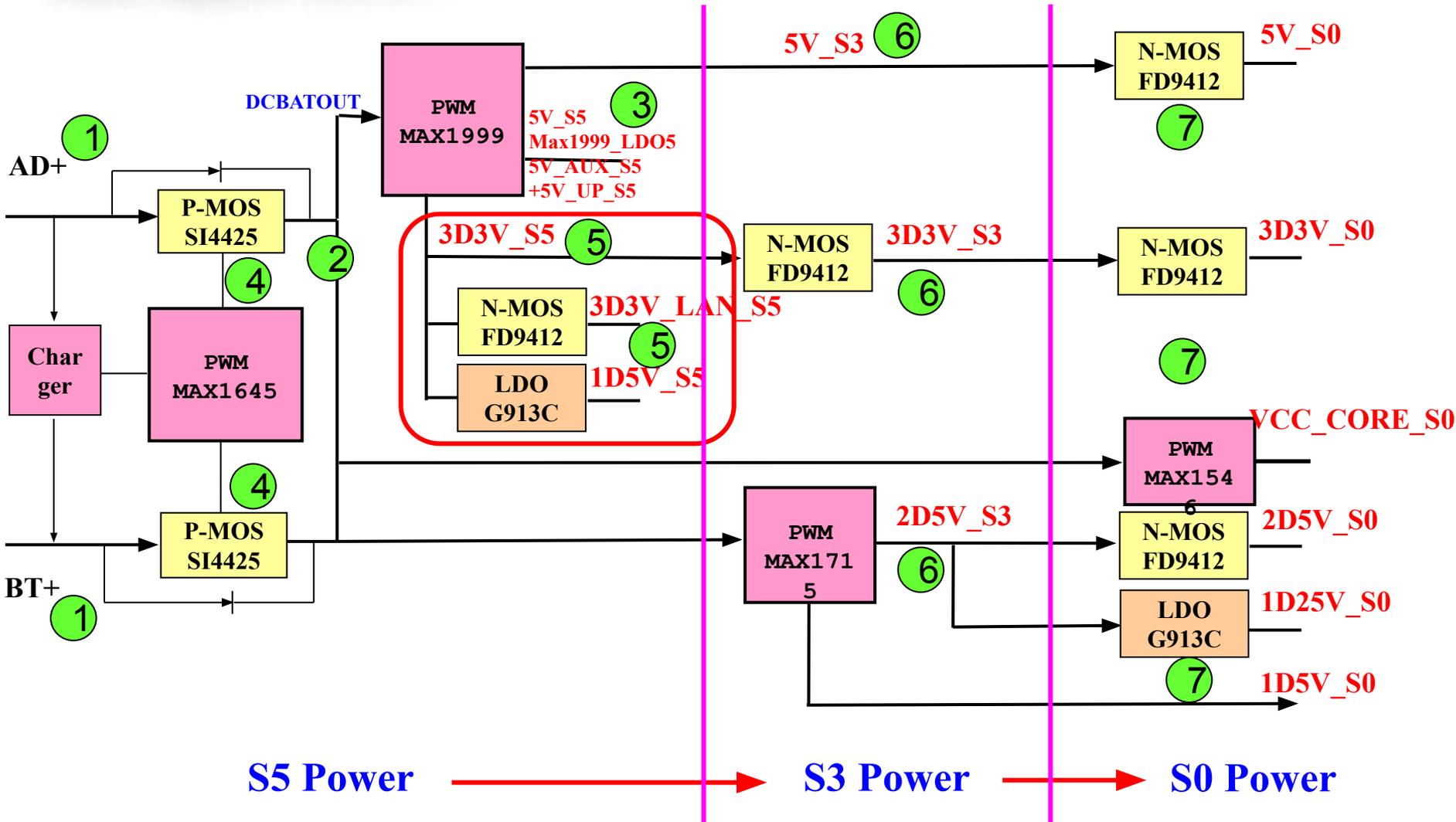


1. Power system architecture

1.1 NB (Yuhina) power system : S3 Power

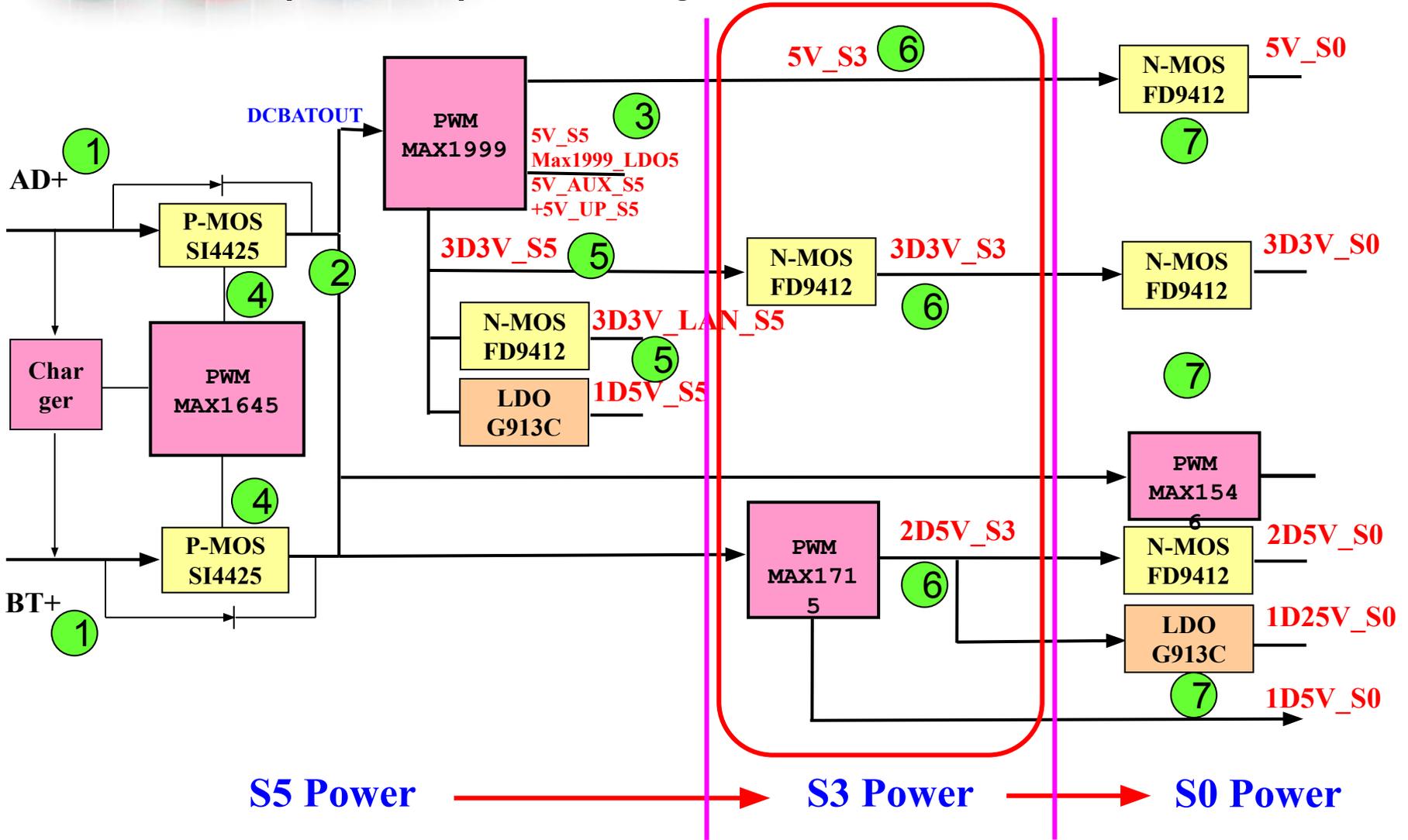

1. Power system architecture

1.1 NB (Yuhina) power system : S0 Power

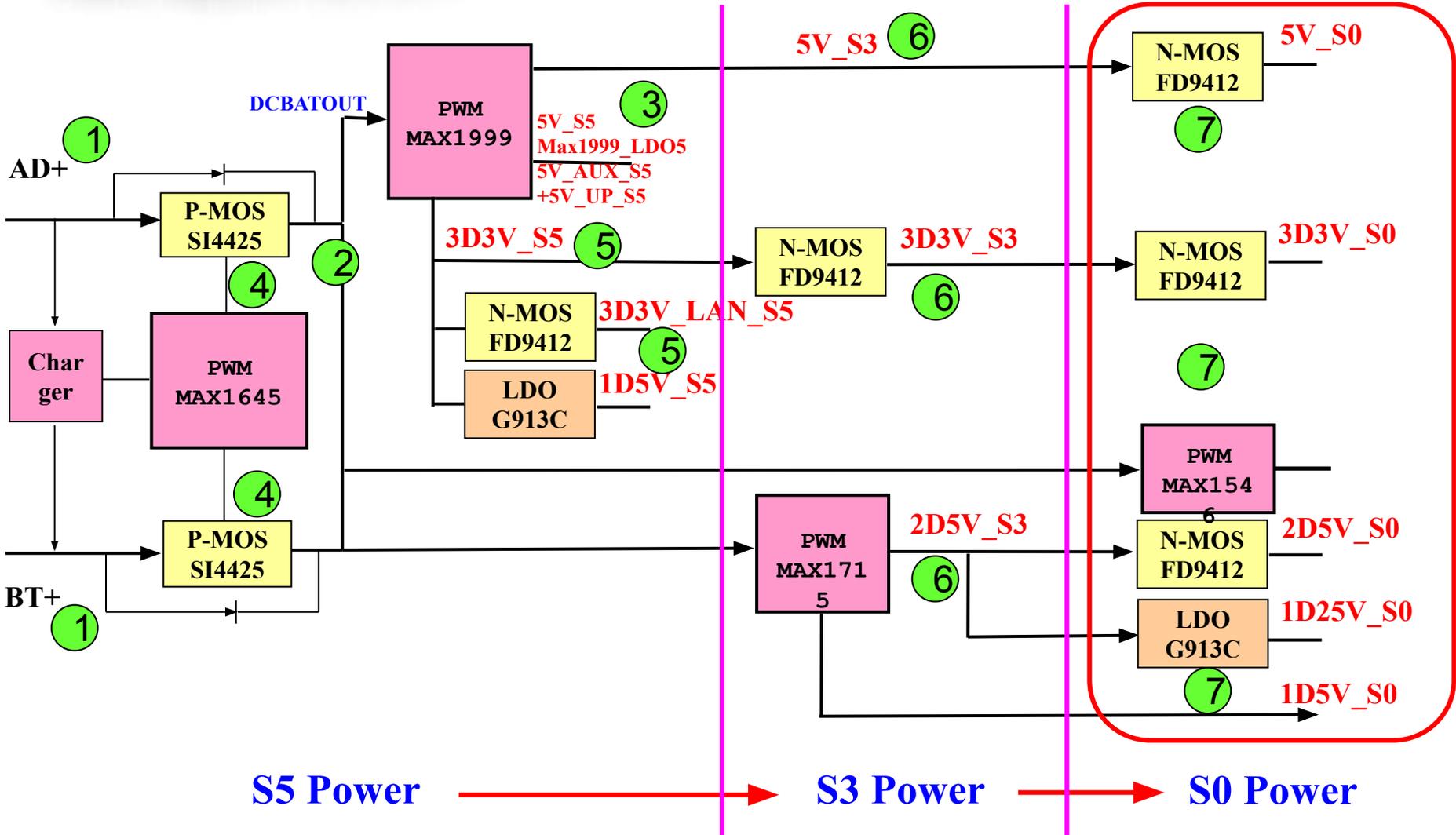




1.2 Последовательность питания и управления:

Почему мы должны различать тип питания среди (在 ... 之中) AUX, S5, S3, S0? Как мы их контролировать?

Вот ответ:


- **AUX Power** : Для использования кнопки питания, он включен с батареей только до нажатия на кнопку питания.
- **S5 Power** : Для кнопки питания и после использования на LAN, он включен с адаптером, прежде чем нажать кнопку питания.
- **S3 Power** : Для stand_by режиме использования, он включен с южного моста PM_SLP_S3 # после нажатия кнопки питания.
- **S0 Power** : Для нормального использования режима, он включен с южного моста -PM_SLP_S4 # после нажатия на кнопку питания.

Block Diagram :

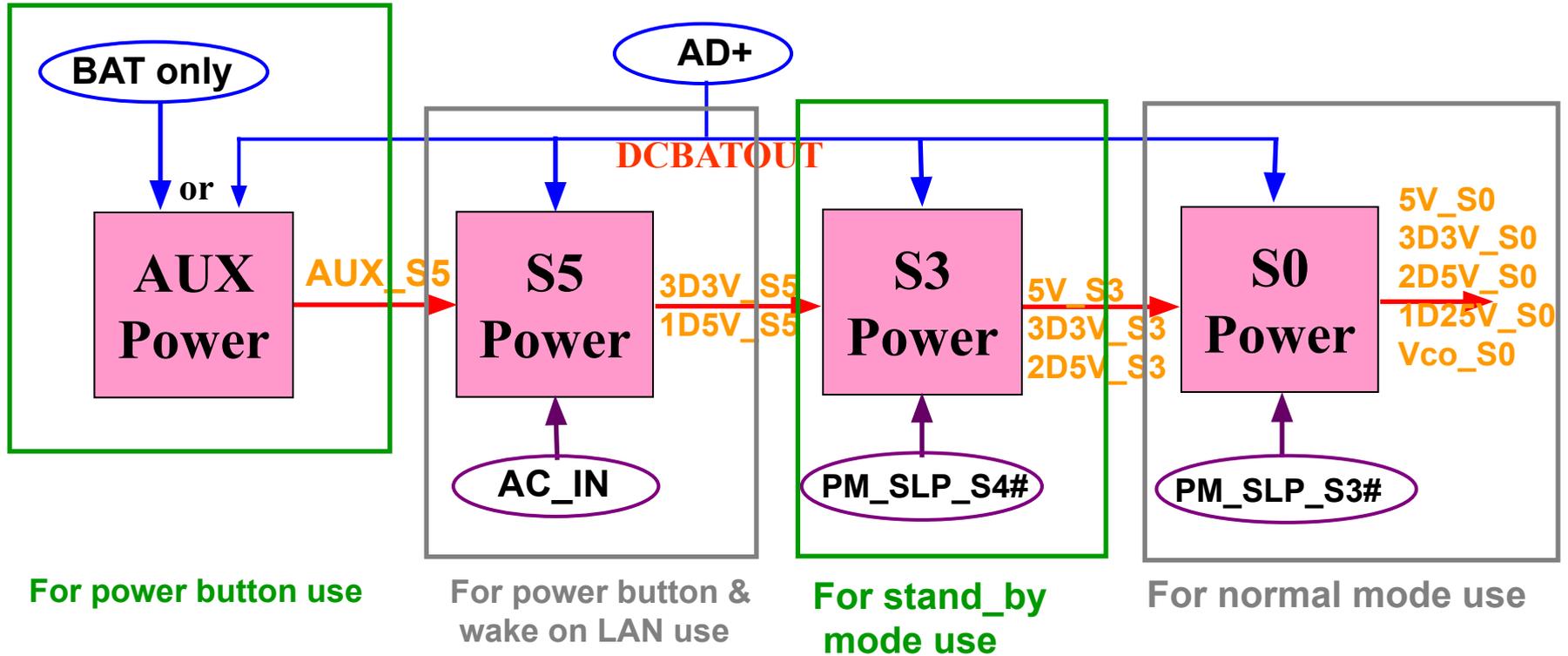

1.2.1 AUX_Power :

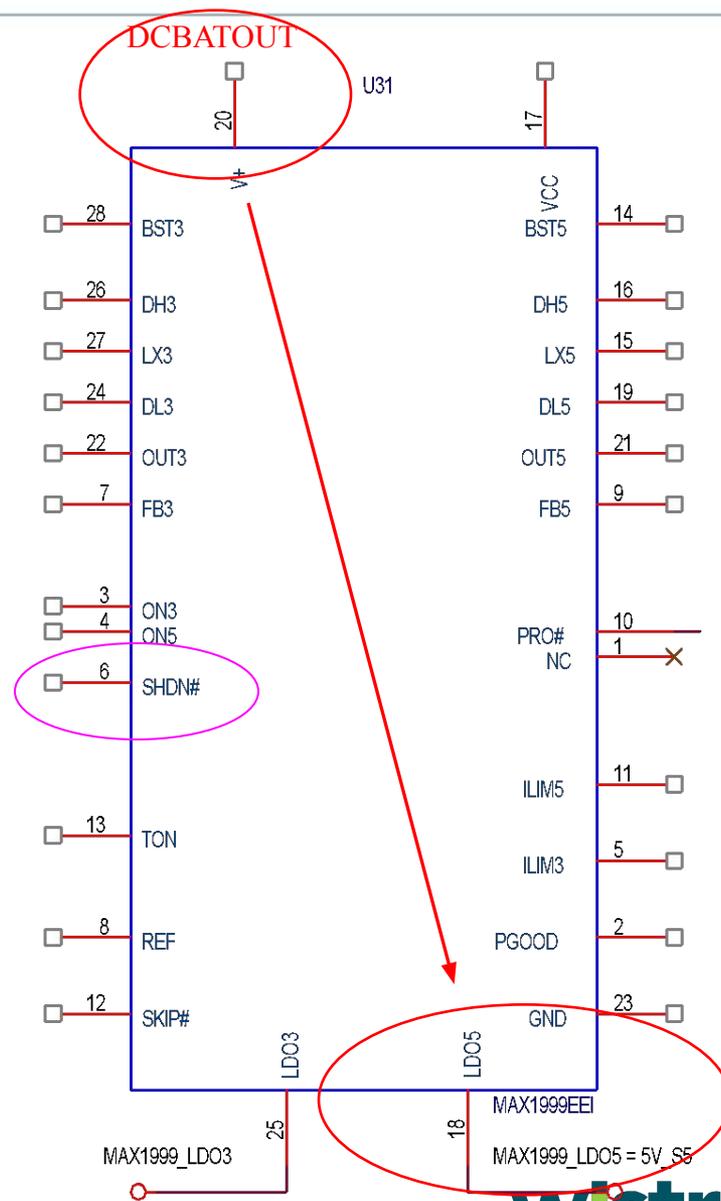
- a. Когда батарея или адаптер подключен в (插入), DCBATOUT будет вводить питание в MAX1999 контактный 20_V +, и пин-код 18 - LDO5 обеспечит питание 5V_AUX_S5.
- c. 5V_AUX_S5 никогда не выключен, когда MAX1999 работает, если что-то пойдет не так с MAX1999.
- b. Сила AUX используется на Мощность по логике и южного моста. Как только батареи, ток утечки должен быть как можно меньше. В общем, около 5 ~ 6 мА.



1.2.2 S5_Power:

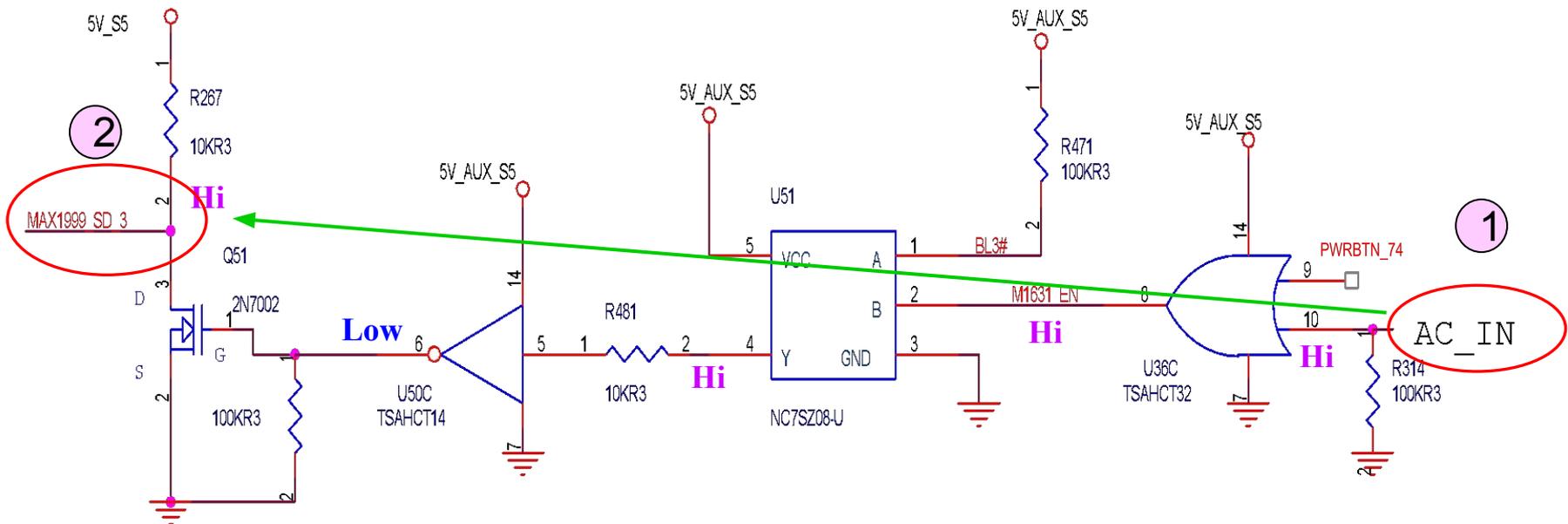a. Circuit operation – Power on logic :


- 1 Сигнал AC_IN потянули, когда адаптер был вставлен.
- 2 Мощность по логике вывода MAX1999_SD, чтобы вызвать 3D3V_S5. В результате, когда адаптер вставляется, но пока нажата кнопка питания, S5_power будет включен первым.




c. Circuit operation – LAN & 1D5V_S5 power :

- ① When AC_IN is HI,
- ② The MOS-U13 will be turned on, and 3D3V_LAN_S5 will be generated. This power is for wake on LAN function.
- ③ Мощность 1D5V_S5 LDO будет включен в 3D3V_S5.
Эта сила для южного моста для пробуждения по локальной сети использования. Потому что адаптер питания вставлен уже ток утечки батареи не относится в настоящее время.

LAN Power

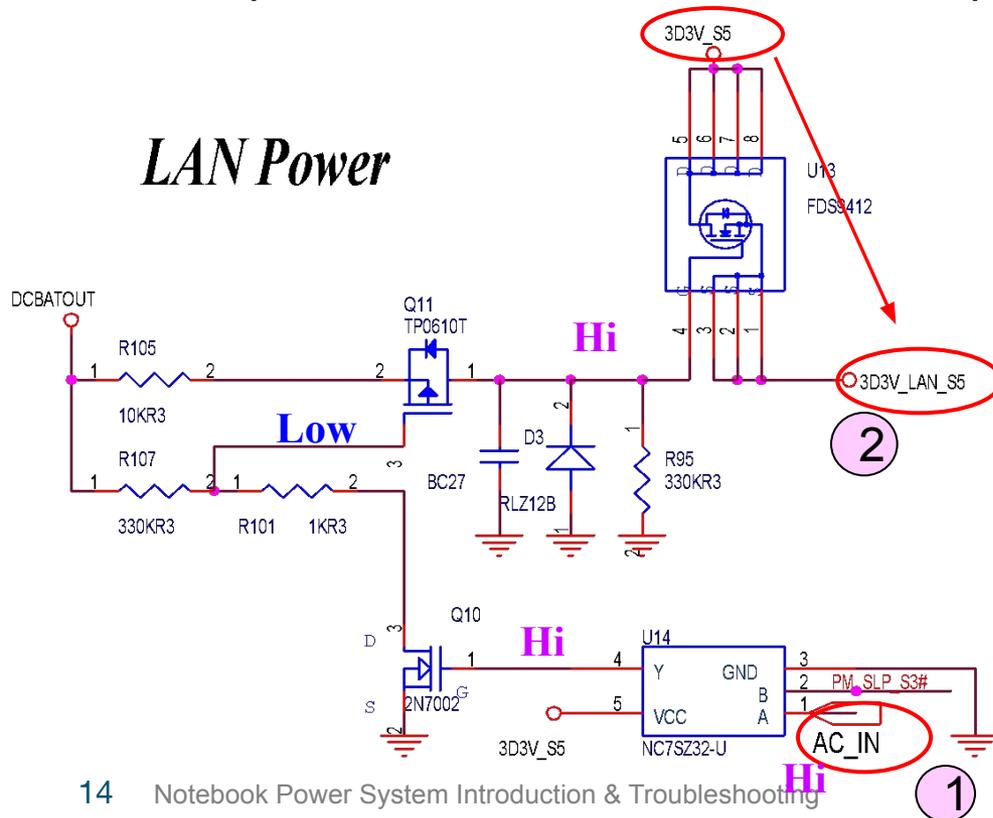


1D5V_S5 LDO

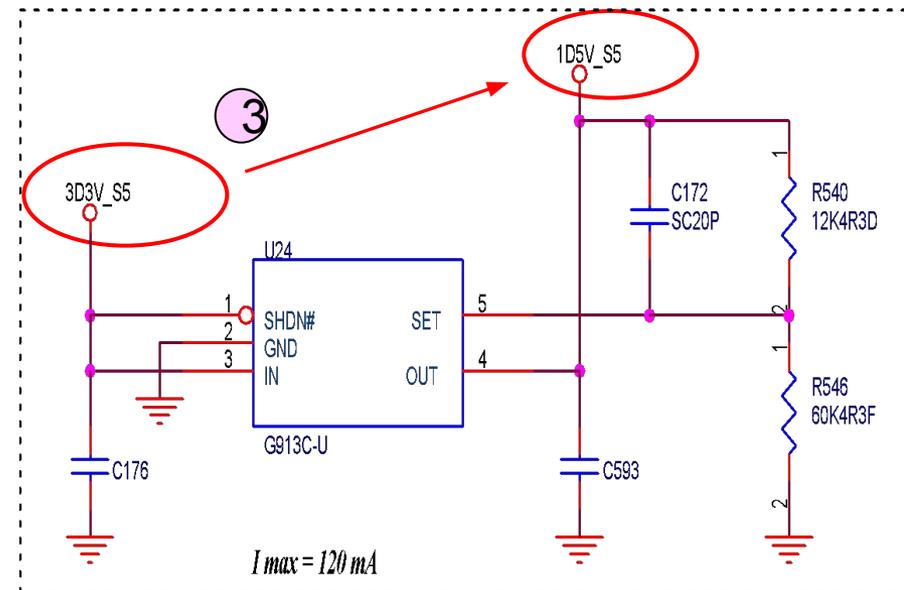

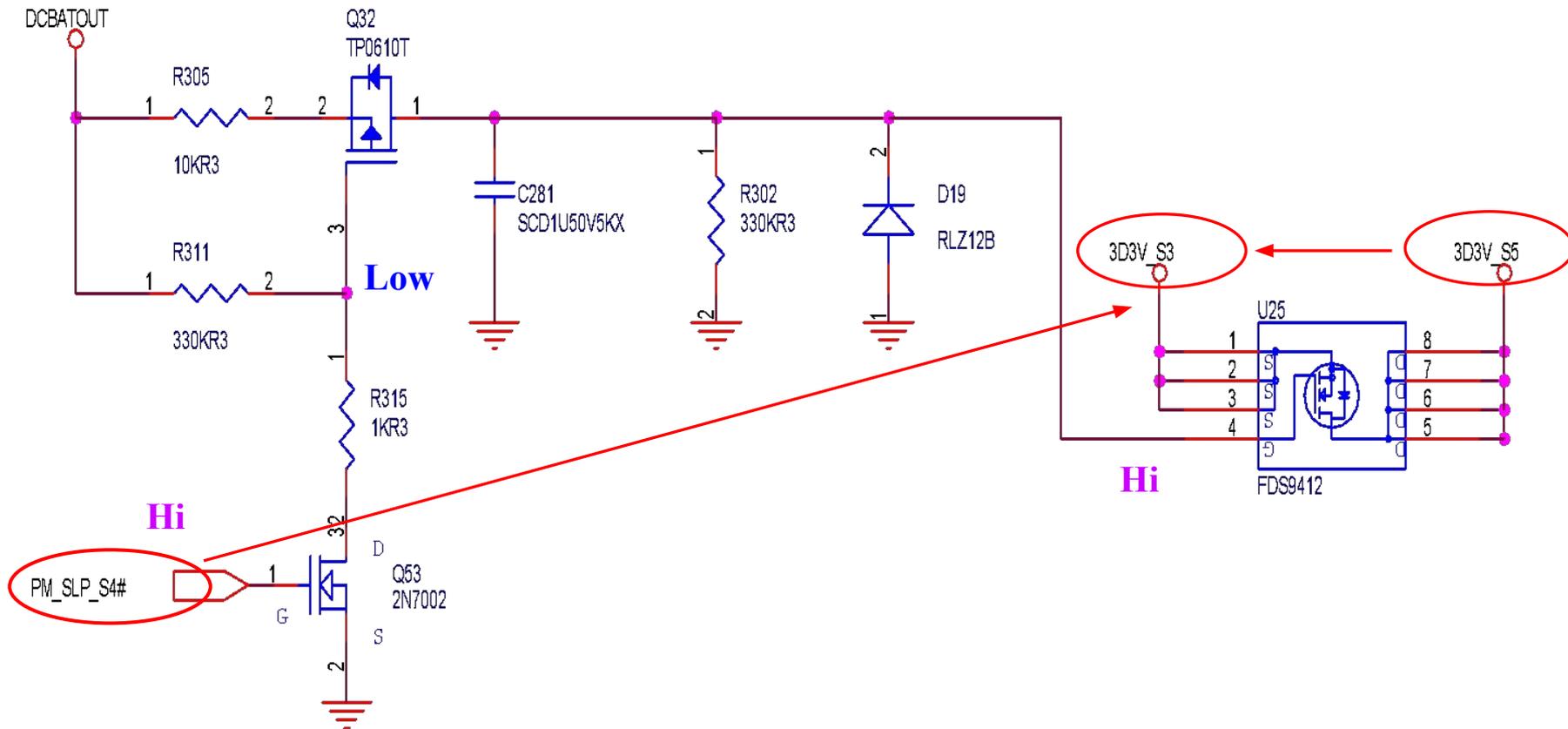
b. Circuit operation – 3D3V_S3 :

3D3V_S3 power is generated by U25 N-MOS from 3D3V_S5 when PM_SLP_S4# is hi .



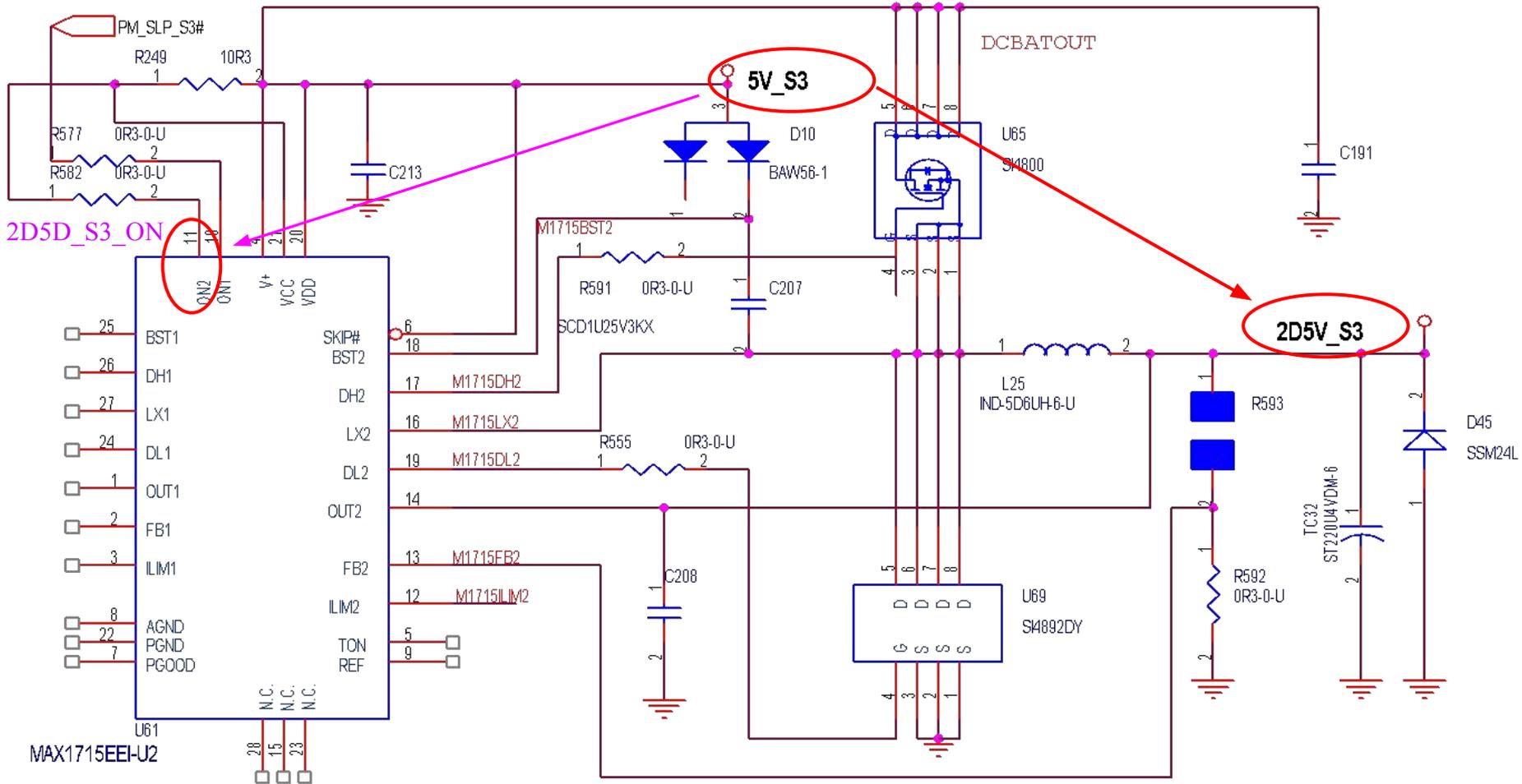
c. Circuit operation – 2D5V_S3 :

When 5V_S3 power was building, MAX1715 pin – 11 is pulled hi, and 2D5V_S3 will be turned on .



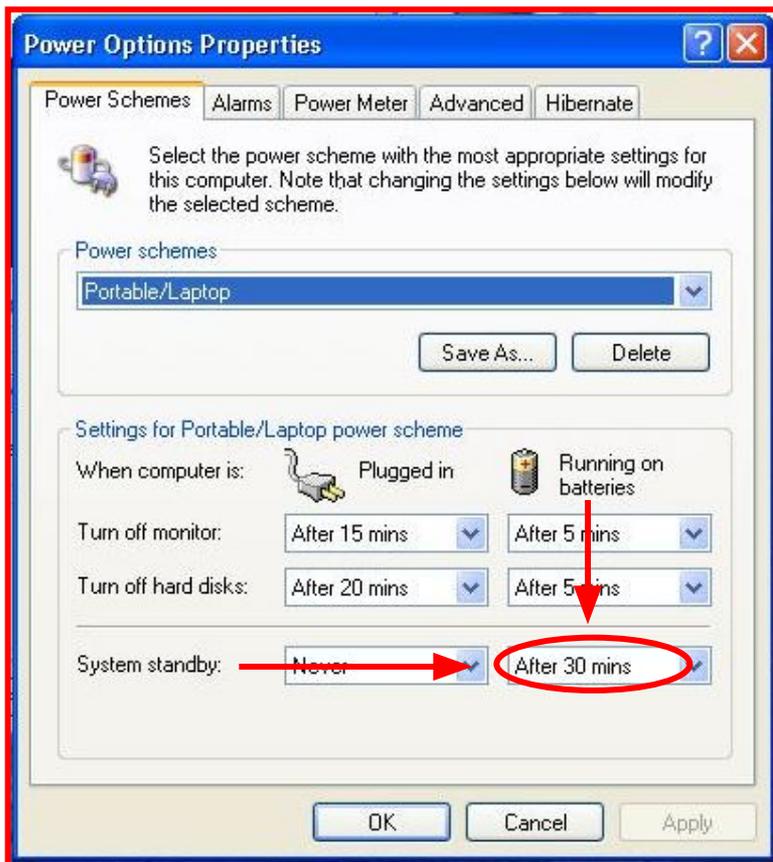d. S3 power Purpose : Why Notebook needs S3 power – Stand-by mode function

Функция режима ожидания для экономии энергии, когда система не работает так же, как ниже настройки. Так, мощность S3 для такого использования.




- Система войдет в режим ожидания, если NB остается в бездействии в течение 30 минут.
- В режиме ожидания, если кнопка питания нажата, система вернется в предыдущее состояние в 5 сек.
- Из-за состояния возобновляется из памяти, мы должны S3 власть, чтобы North Bridge & DDR работает стоя на. В этом состоянии, ток утечки батареи при 30 мА.

1.2.3 S0_Power:

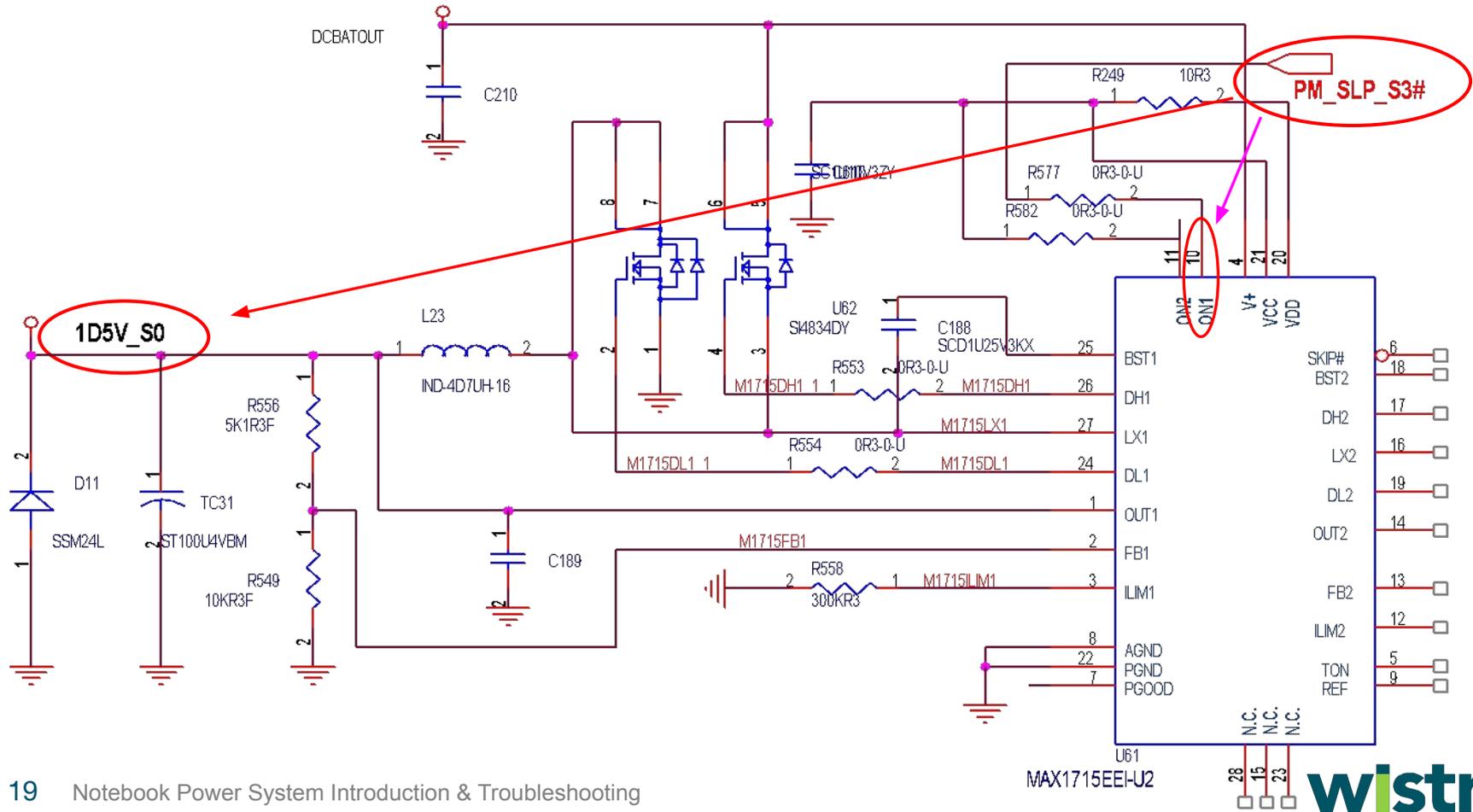
a. Circuit operation – 1D5V_S0 :

After PM_SLP_S4# signal was generated for a few μ sec , the South Bridge will output PM_SLP_S3# on hi level, and 1D5V_S0 will be turned on .



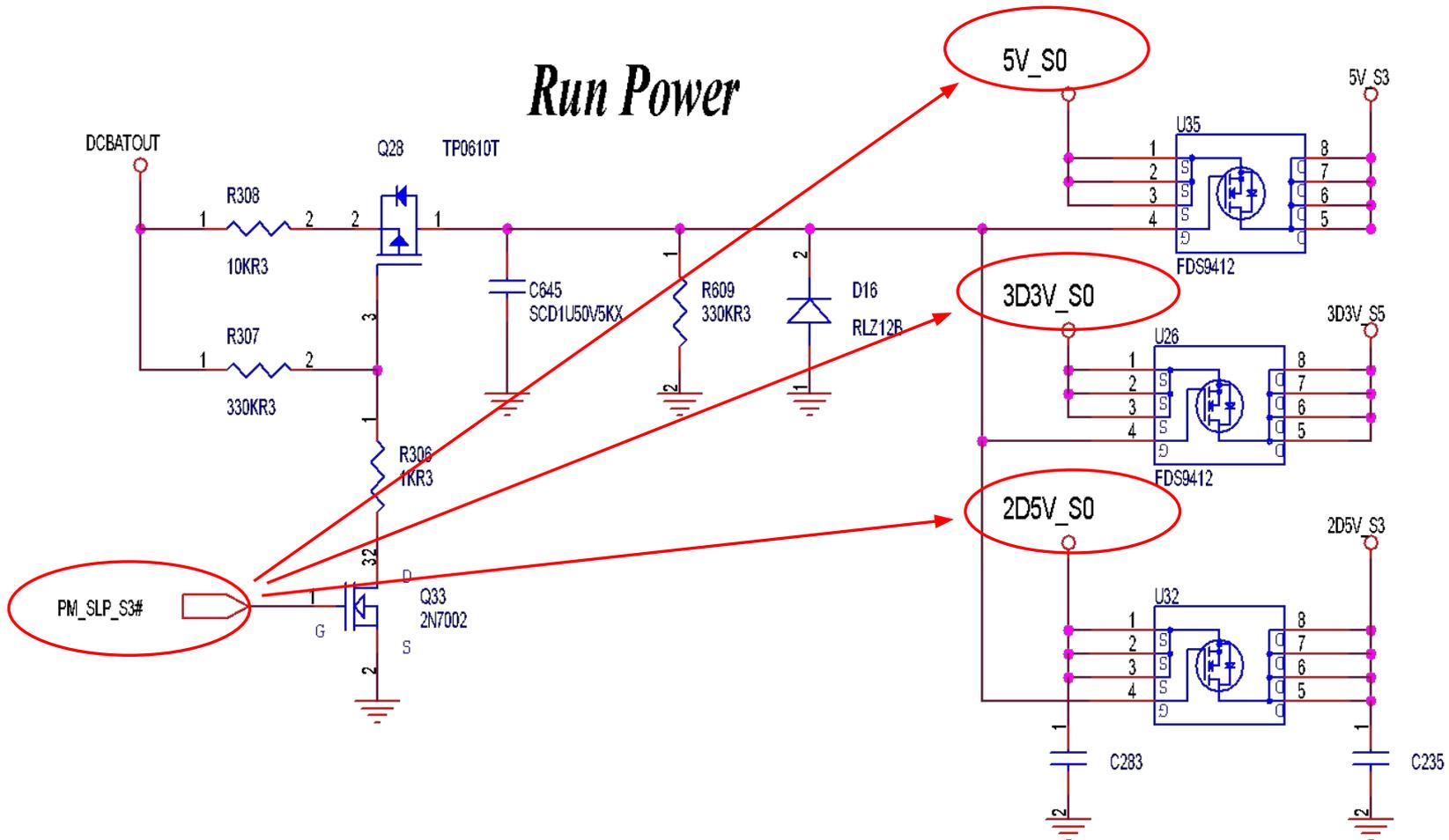
b. Circuit operation – 5V,3D3V,&2D5V_S0 :

PM_SLP_S3# signal is also used to turn on 5V、3D3V、2D5V_S0.




c. Circuit operation – P4 CPU VCC_CORE_S0 :

-- P4 CPU_VCO power – architecture :

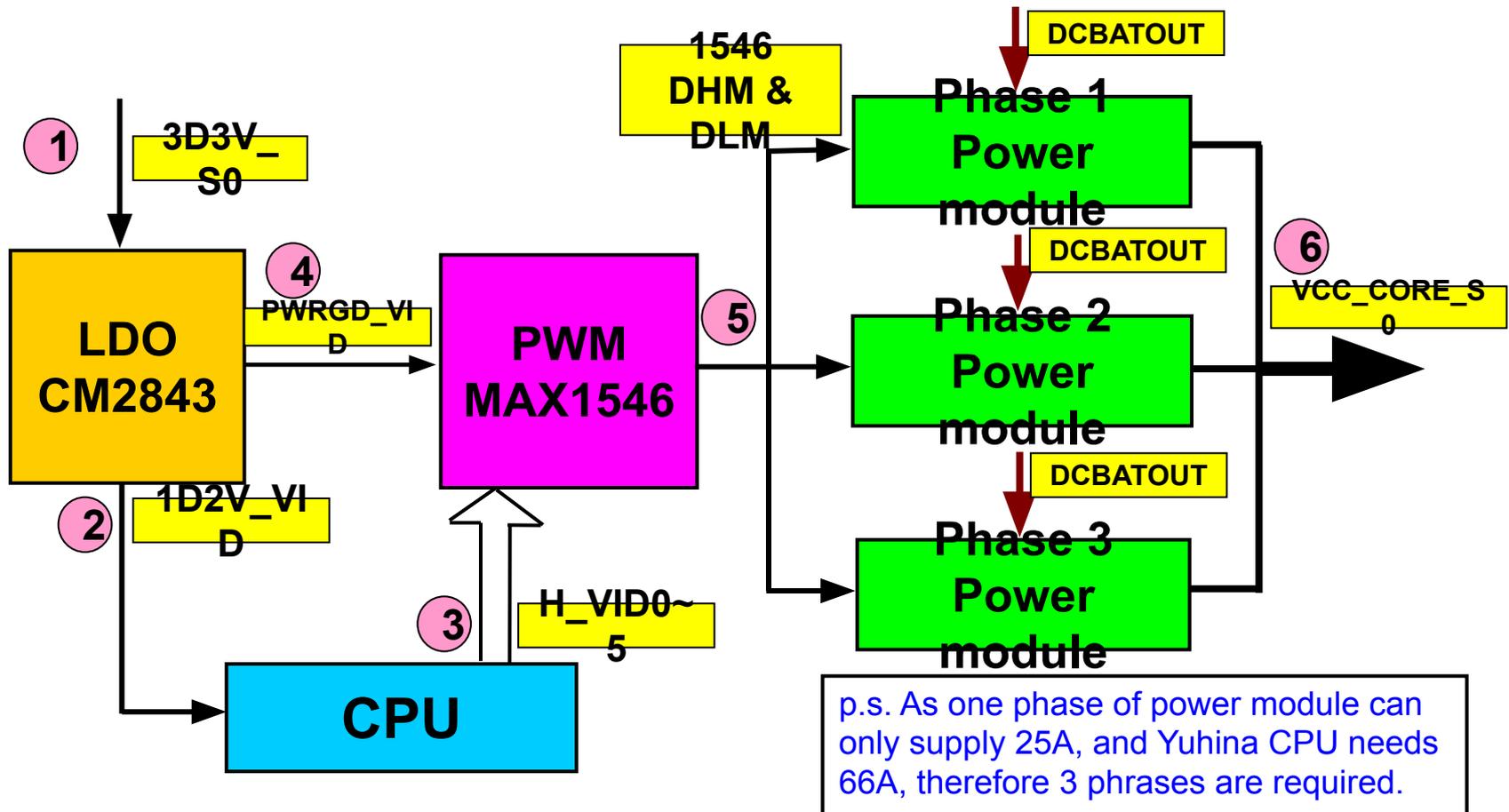

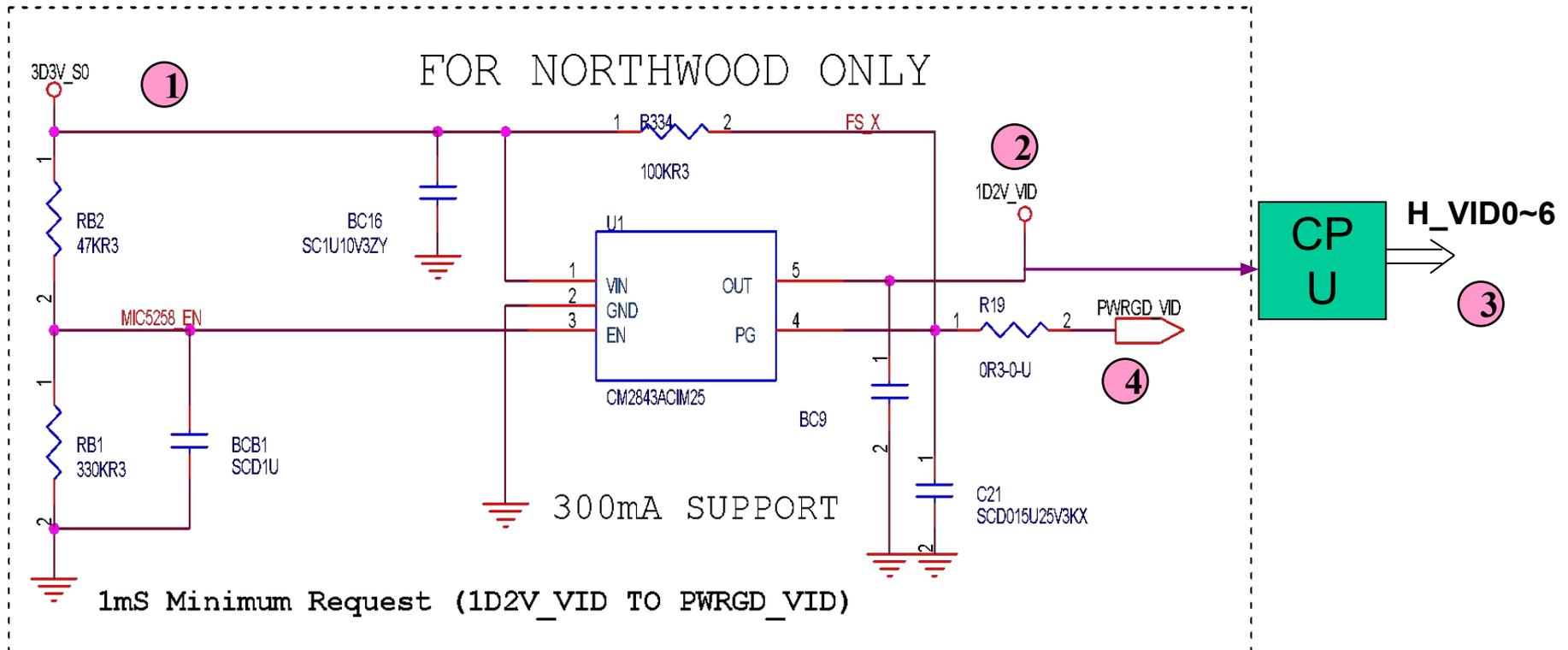c. Circuit operation – P4 CPU VCC_CORE_S0 :


- ① 3D3V_S0 power on .
- ② CM2843 provides 1D2V_VID to CPU.
- ③ CPU provides VID code
- ④ PWRGD_VID, which is provided by CM2843, will delay 1ms while 1D2V_VID is on. So it will be turned on after the CPU VID code.



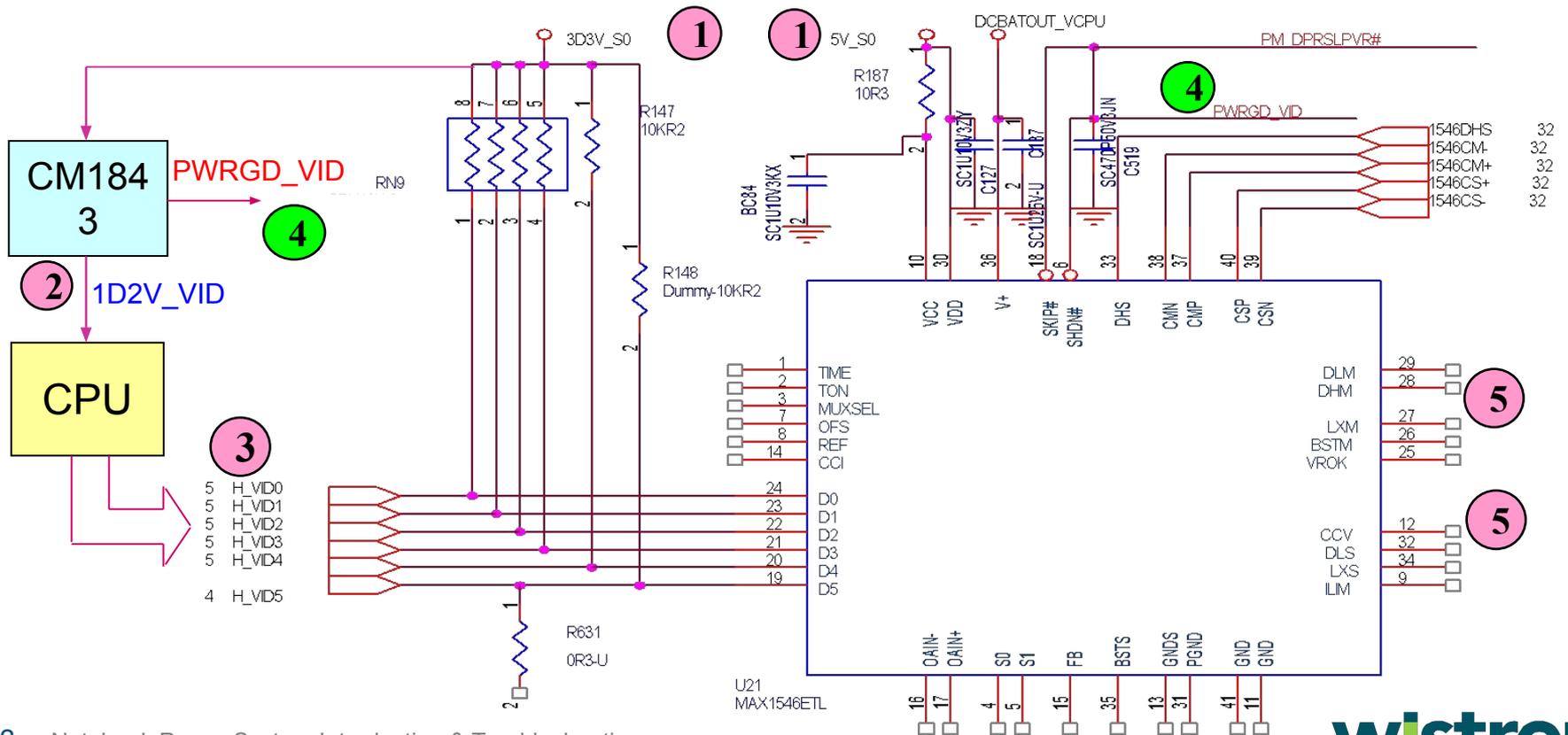c. Circuit operation – P4 CPU VCC_CORE_S0 :


3 of 4

- ① MAX1546 Power is ready .
- ② CM1843 generates 1D2V_VID to CPU.
- ③ CPU provides the VID0~5 to the MAX1546 ..
- ④ CM1843 will send PWRGD_VID as Hi after 1ms that 1D2V_VID was generated.
- ⑤ MAX1546 will output the switching signal .



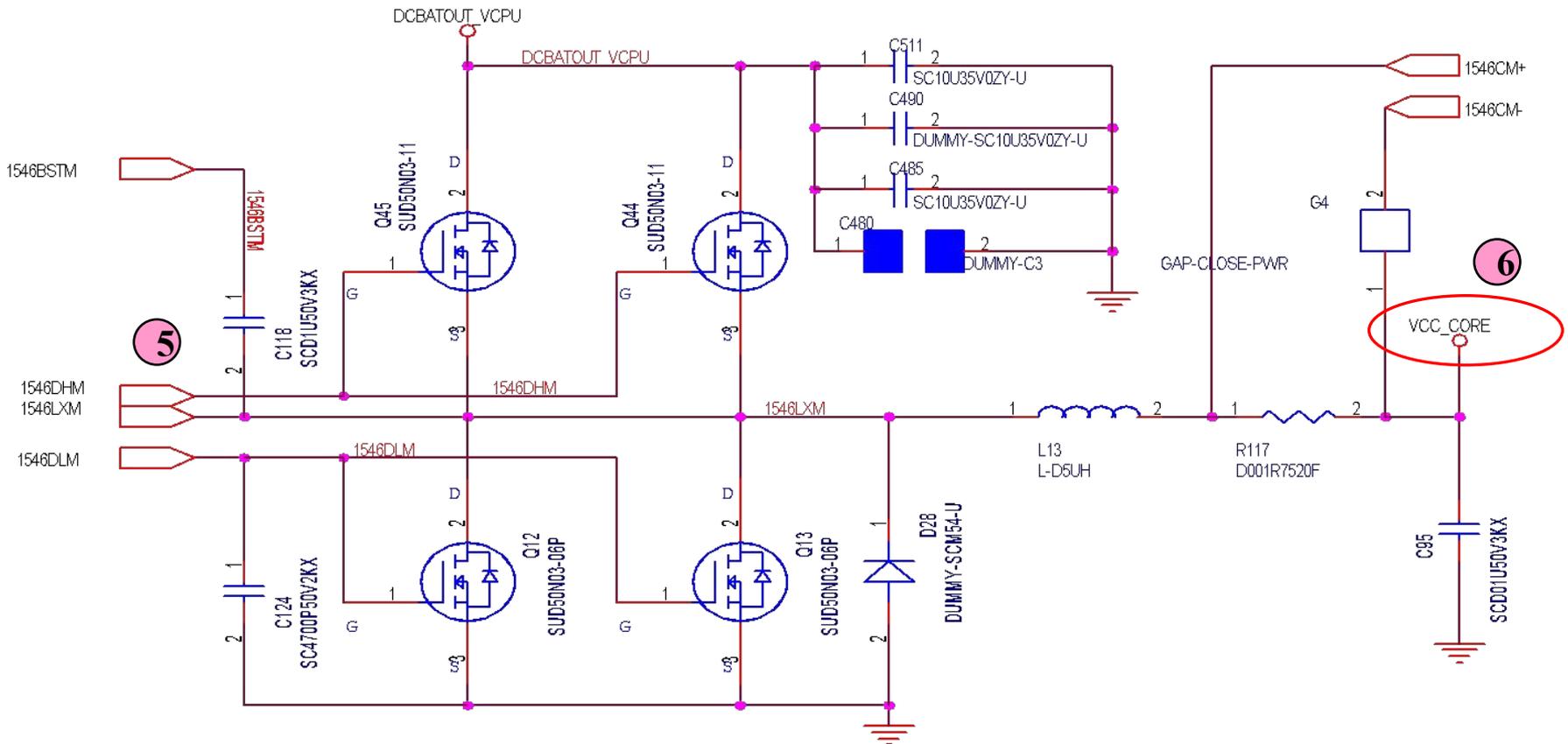
c. Circuit operation – P4 CPU VCC_CORE_S0 :

- 5 The step-down circuit starts working as soon as the switch signal begins.
- 6 The VCC_CORE is produced and will provide the CPU's working power . PS. This is one of the three phases in VCC_CORE.



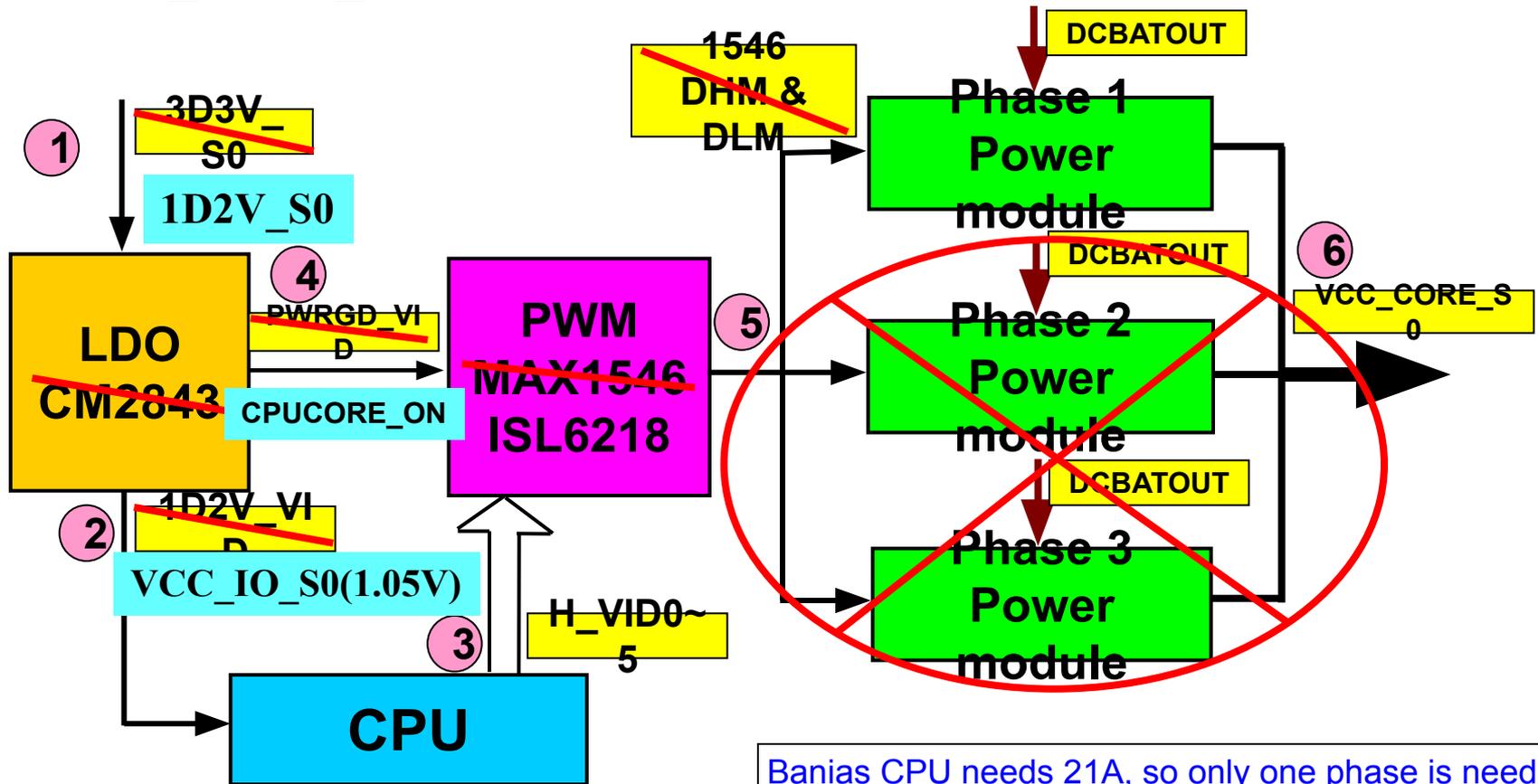d. P4 & Banias CPU VCC_CORE_S0 difference :

The power system can separate two kinds of architecture for CPU. But the only difference between **P4** and **Banias** CPU power architecture is VCC_COER_S0. Such as below :





2. Power plan introduction :

By now we have learned how NB power is generated and why it must be done in a specific sequence. You might start to wonder, “What is other Power application?” In the following section, I will show you the power consumption of all devices in a NB. You will learn:

- 2.1 Power budget block diagram
- 2.2 NB power application
- 2.3 Multi–power device



2. Power plan introduction :(cont'd)

Create a NB power system with fixed procedure, so we can know the power budget of all devices from the power plan procedure .

Design procedure


a. Power budget :

We must first know the power category and consumption of all devices, and then we can start to define the SPEC of power.

b. Power application :

After power SPEC was defined, we need to confirm the timing & sequence when power is turned on. And separate them with S5,S3,S0, etc. for the purpose of power saving.

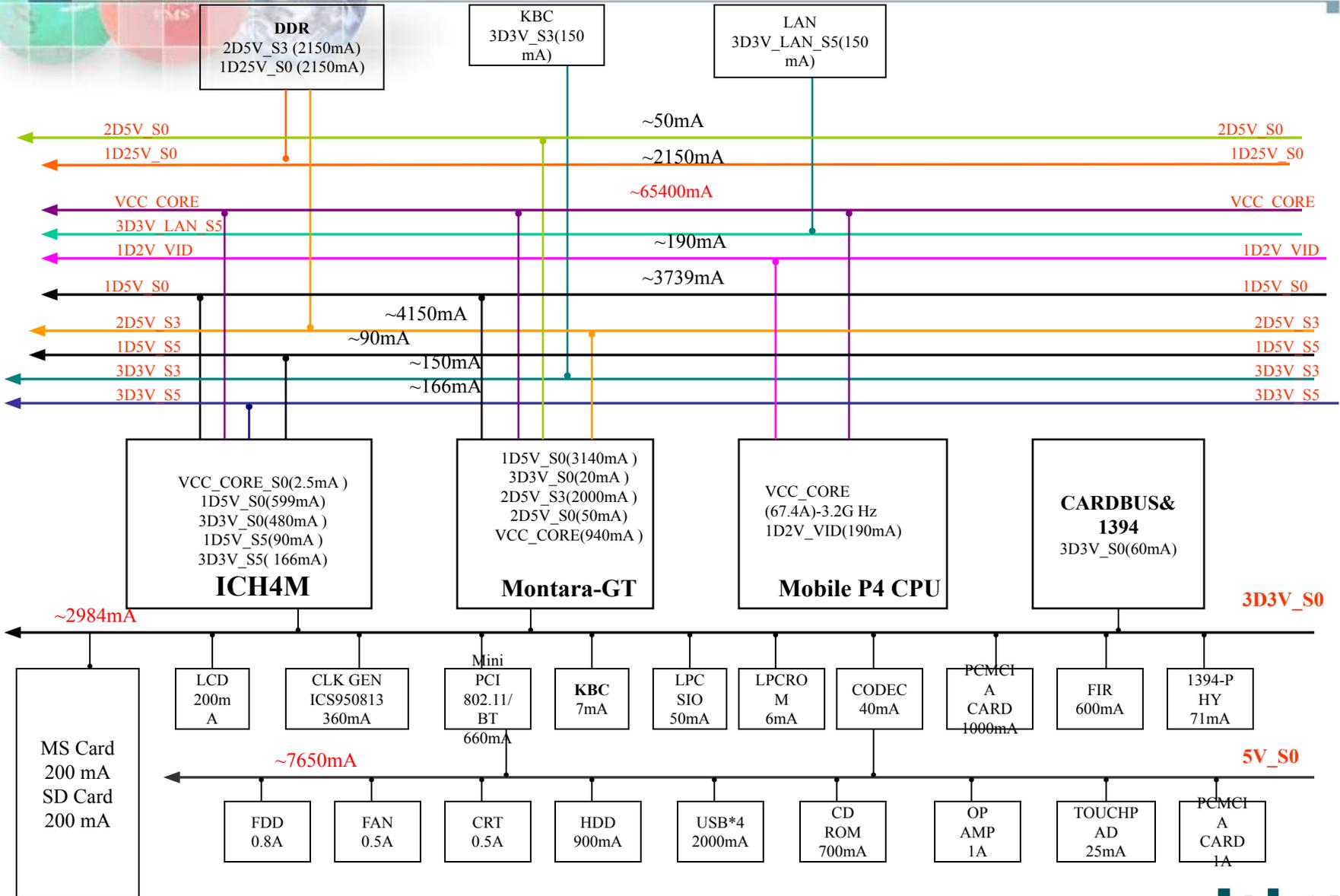2.1 NB (Yuhina) Power Budget Block Diagram



2.2 NB power application :

2.2.1 3D3V Device

S5	ICH4M	LAN	
S3	KBC		
S0	Montara-GT	ICH4M	LPC SIO
	Mini PCI	CODEC	LPC ROM
	1394-PHY	KBC	CLK GEN
	PCMCIA card	LCD	CARBUS
	MS/SD card	FIR	



2.2.2 5V Device :

S5			
S3			
S0	Mini PCI	FDD	CD ROM
	CODEC	HDD	USB*4
	Touch PAD	CRT	OP AMP
	PCMCIA card	FAN	

2.2.3 2D5V Device

:

S5		
S3	DDR	Montara - GT
S0	Montara - GT	



2.2.4 1D5V Device :

S5	ICH4M	
S3		
S0	ICH4M	Montara_GT

2.2.5 1D25V Device :

S0	DDR
----	-----

2.2.6 1D2V_VID Device :

S0	CPU
----	-----

2.2.7 VCC_CORE Device :

S0	CPU	ICH4M	Montara-GT
----	-----	-------	------------

2.3 Multi-power device :

Device	Power source				
ICH4M (South Bridge)	3D3V_S5	3D3V_S0	1D5V_S5	1D5V_S0	VCC_CORE
Montara _ GT (North Bridge)	3D3V_S0	2D5V_S3	2D5V_S0	1D5V_S0	VCC_CORE
Mobile P4 CPU	1D2V_VID	VCC_CORE			
DDR	2D5V_S3	1D25V_S0			



3. No power troubleshooting

No power define :

No power means when the power button is pressed, the power LED is not turned on, and the system is not booted. We can separate no power in four kinds of states :

3.1 No power debug notice & sequence

3.2 No DCBATOUT or short to GND

3.3 S5 Power No Good

3.4 Power on logic No Good


If power system is good & power LED turned on, but the system still N.G., it means the system is “No work”. You must follow the “No work debugging” process to troubleshoot the problems.

3.1 No power debug notice & sequence :

3.1.1 debug Notice :

- For safety's sake, please use adapter to supply the Notebook power when you execute the debug process .
- This debug procedure can only cover about 90% no power Problems.

3.1.2 debug Sequence :

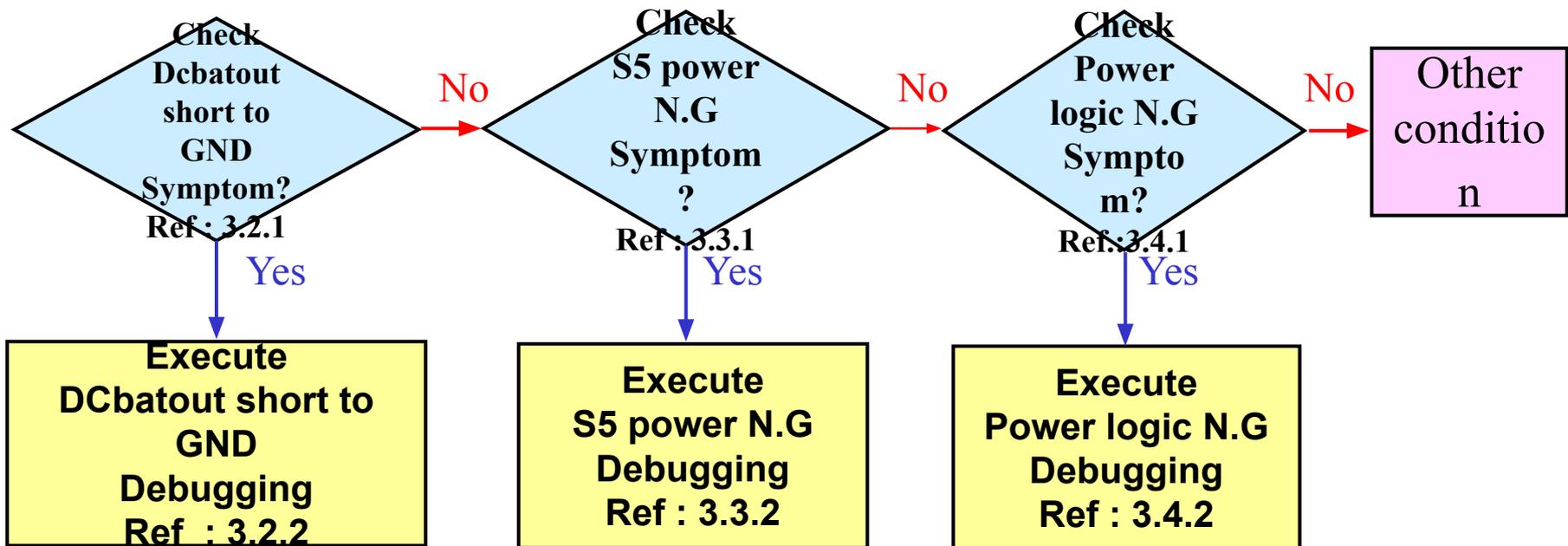


3.2 DCBATOUT short to GND :

3.2.1 Symptoms:

- There is no any response when the power button was pressed and adaptor was already inserted .
- Adaptor power LED flashes or shuts down .

Solution: Open the system case and use the multi-meter 200V scale to check AD+ or DCBATOUT between GND as below . If the voltage is less than 5V,we can make sure it is short to GND .

Adaptor in to generate DCBATOUT

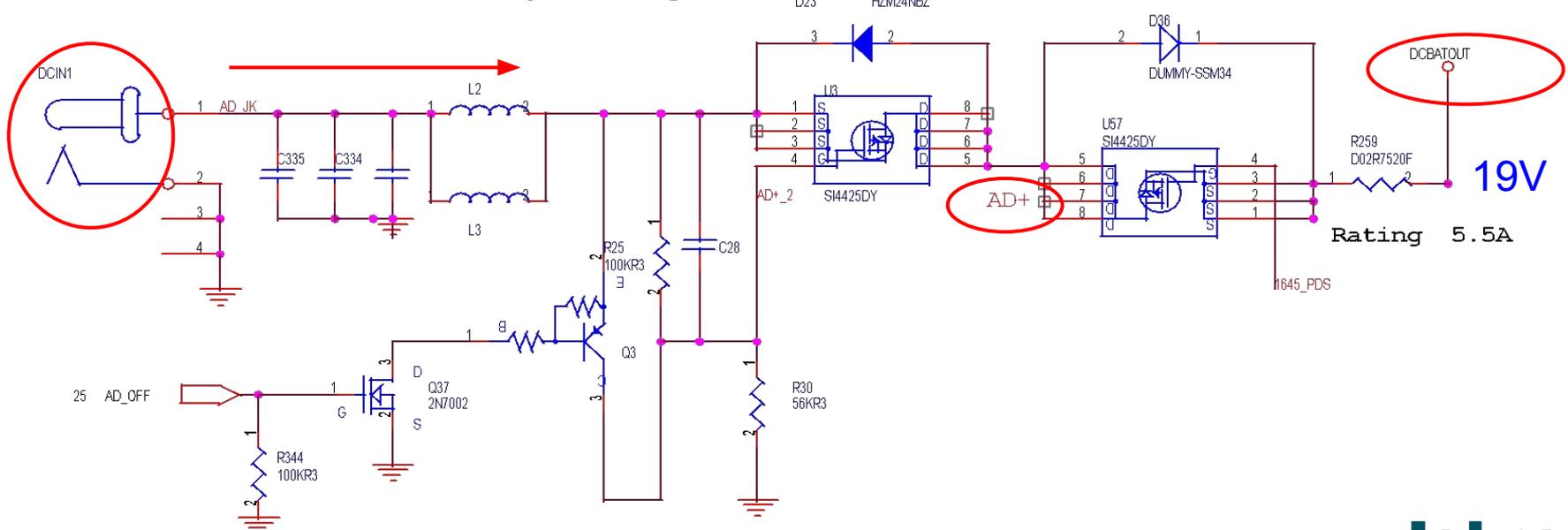


3.2.2 Debugging : (cont'd)

2 of 2

Following is an example of the 2D5V power source.

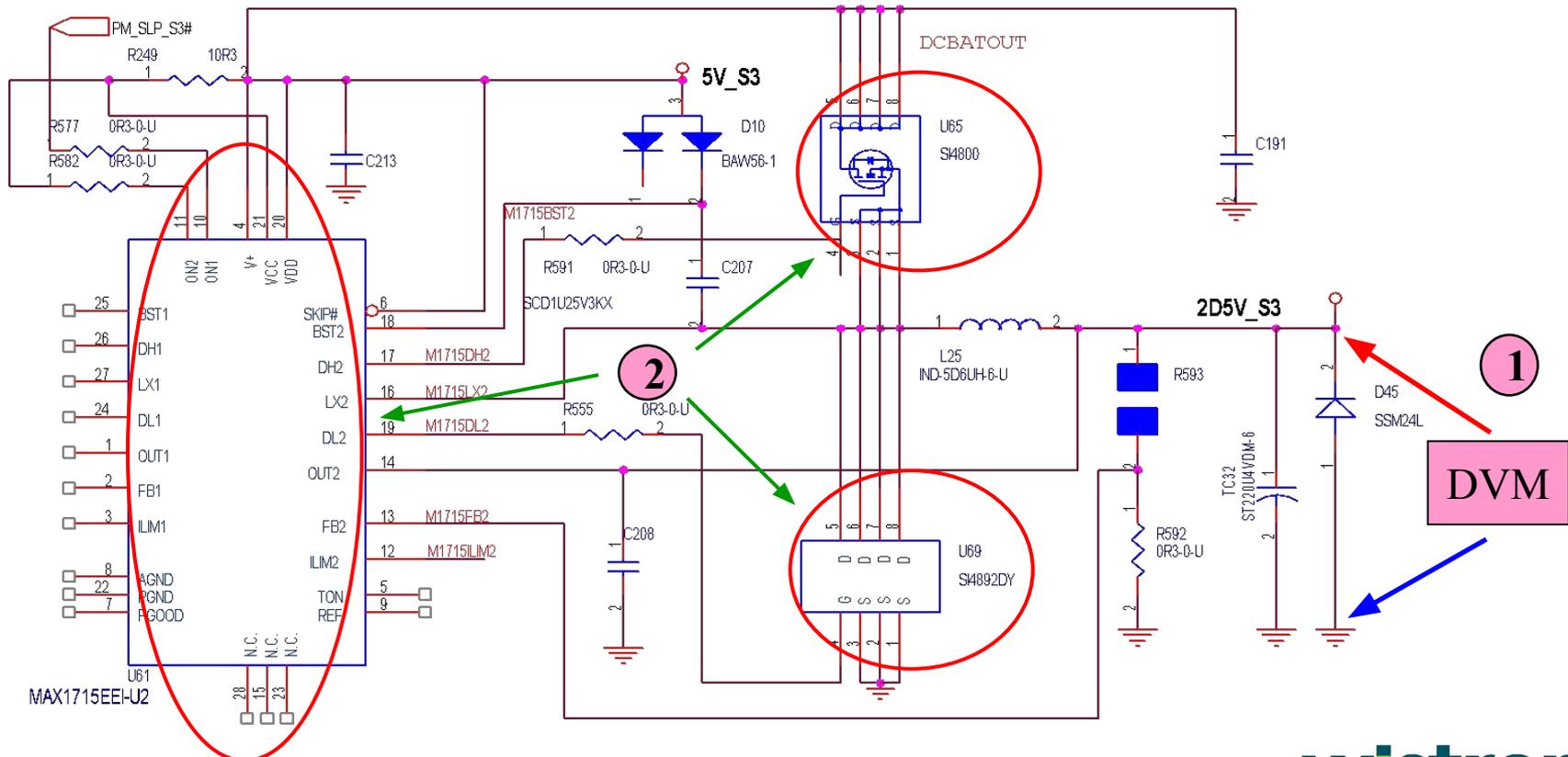- 1 Use multi-meter 200 Ω scale to check TC32. The impedance must be bigger than 200 Ω . If not, it means something short to GND, and we need to find out why.
- 2 Usually we would remove hi & low side MOS (U65 & U69) and MAX1715. If it's still short to GND, it means some output devices are damaged, and we must try to remove them one by one .




3.3 S5 Power No Good :

3.3.1 Symptoms:

- There is no any response when the power button was pressed and adaptor has already plugged-in.
- Adaptor power LED is normal .

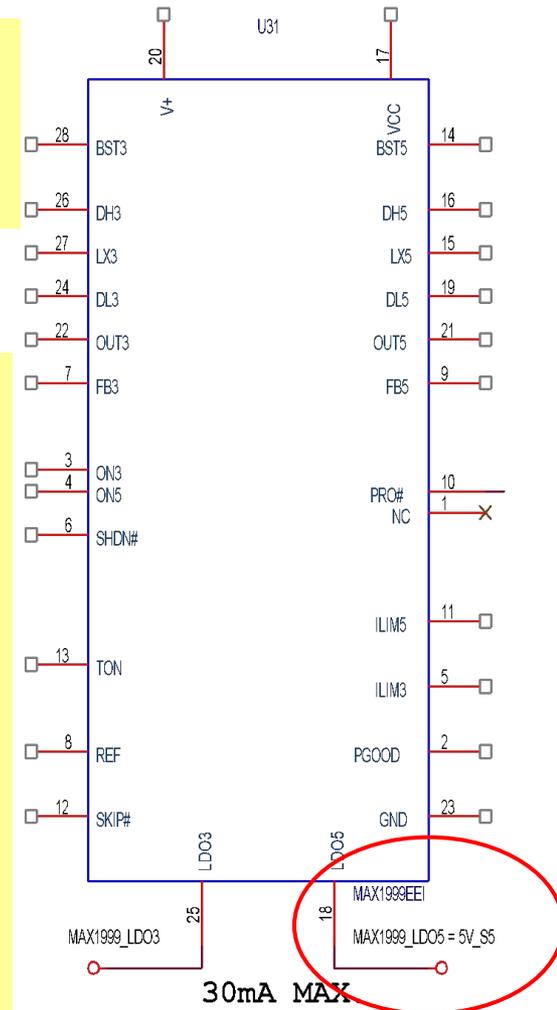
3.3.2 Debugging :

- Open the case, use multi-meter to check if MAX1999 pin18 5V_S5 power is good.
- If not, it means MAX1999 or some 5V_S5 devices are damaged. Remove all powers, use multi-meter to check MAX1999 pin18 Impedance .
- If the impedance is smaller than 200Ω , it means some 5V_S5 devices are damaged, and we must try to remove the component one by one.
- If the impedance is more than 200Ω , it means the MAX1999 have some problem, and it must be changed.



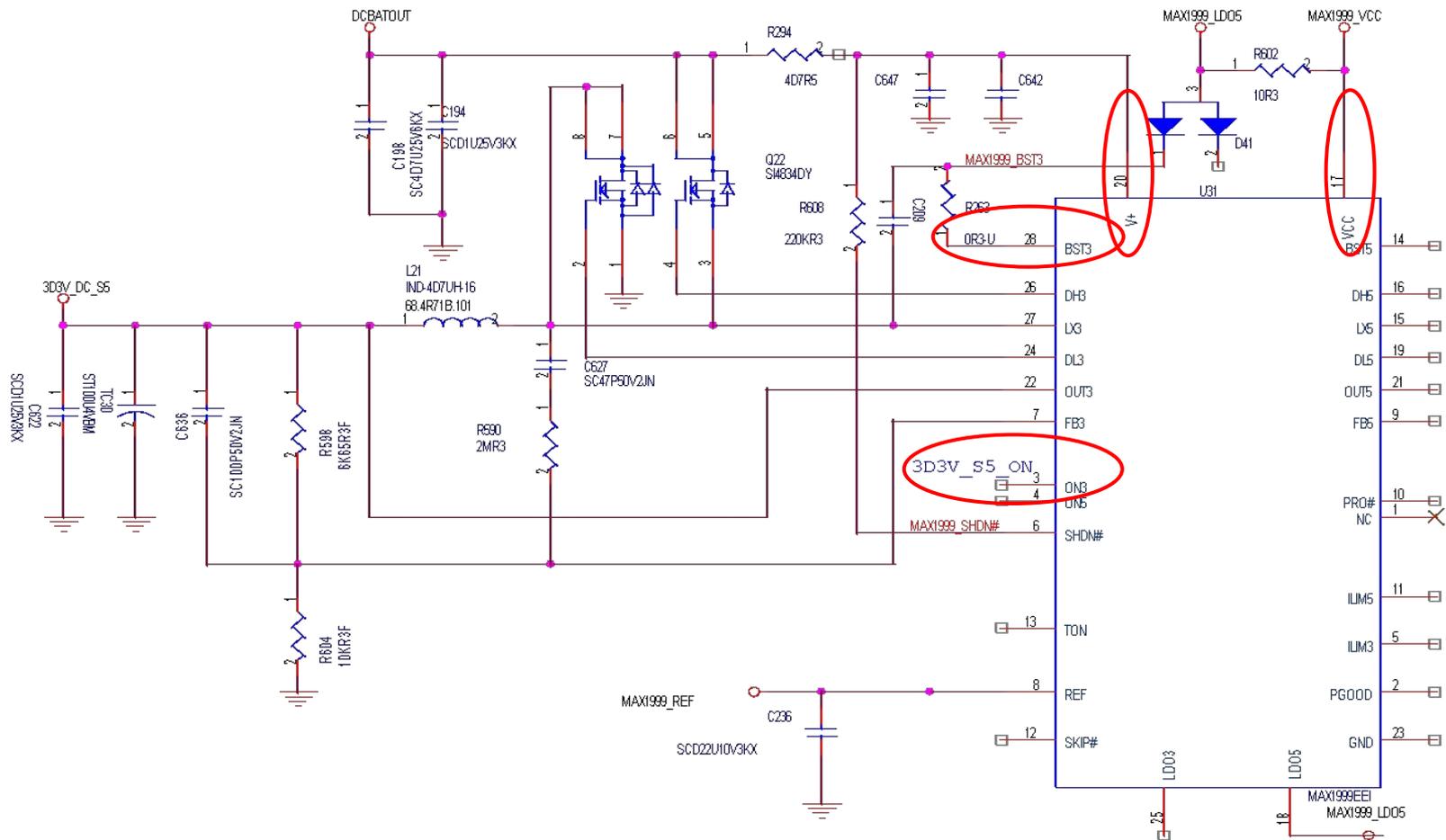
3.3.2 Debugging : (cont'd)

- Next we must check 3D3V_S5. If 3D3V_DC_S5 is N.G, we could use multi-meter to check MAX1999 pin20 (19V), pin17, 28, 3 (5V) if powers are all good. If N.G, please check the source component.



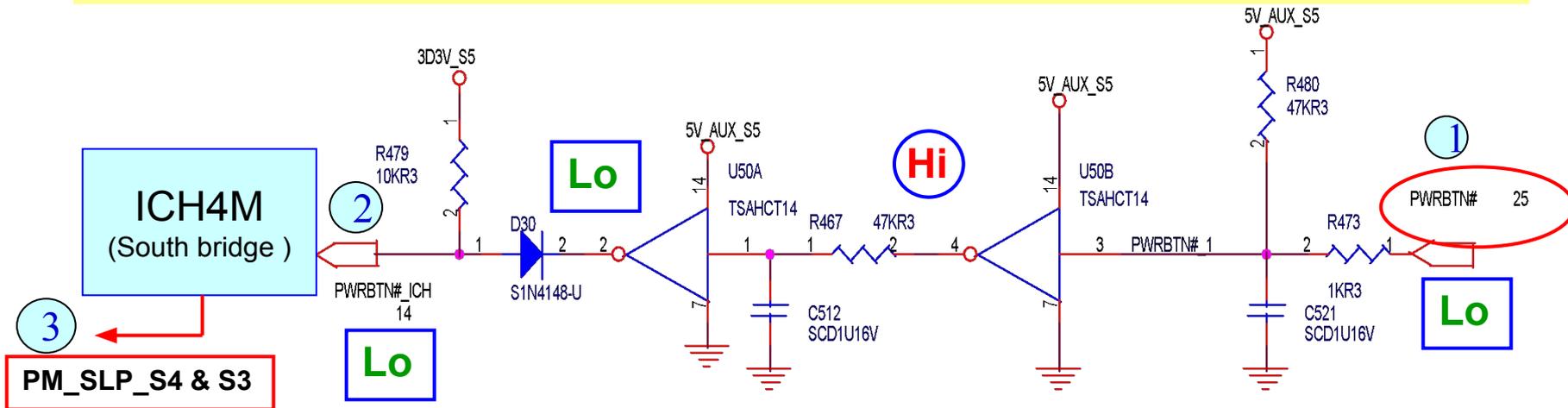3.4.1 Symptom :

- If the power on logic circuit is correct, we can track the south bridge trigger logic .
 - ① When the power button is pressed, PWRBTN# will be pulled low ,
 - ② After the logic action, the **PWRBTN#_ICH** will also be pulled low. It will trigger south bridge to send **PM_SLP_S4 & S3** signal to turn
 - ③ on S3 & S0 power .





3. No Power Debug

3.4.2 Debugging :

- If **SHUTDOWN_S5** is not pulled low, it means some logic ICs or components during this path are N.G.. If it is the case, then just follow the circuit to find out the problems, and replace them.
- If the **PWRBTN#_ICH** is not pulled low, it means some logic ICs or components during this path are N.G. If it is the case, then just follow the circuit to find out the problems, and replace them.
- If the **PM_SLP_S4 & S3** is not pulled hi, maybe the south bridge is damaged .