

# Power Converter Systems

---

## Graduate Course EE8407

**Bin Wu** PhD, PEng

**Professor**  
ELCE Department  
Ryerson University

### Contact Info

Office: ENG328  
Tel: (416) 979-5000 ext: 6484  
Email: [bwu@ee.ryerson.ca](mailto:bwu@ee.ryerson.ca)  
<http://www.ee.ryerson.ca/~bwu/>



**Ryerson Campus**

## Topic 5

---

# Two-Level Voltage Source Inverter (VSI)



Source:  
Alstom

**VDM5000 Two-level VSI**

# Two Level Voltage Source Inverter

---

## Lecture Topics


- Sinusoidal PWM
- Space vector modulation

## Why Use PWM Techniques?

- To control inverter output frequency (fundamental)
- To control inverter output voltage (fundamental)
- To minimize harmonic distortion

# Sinusoidal PWM

## • Inverter Configuration

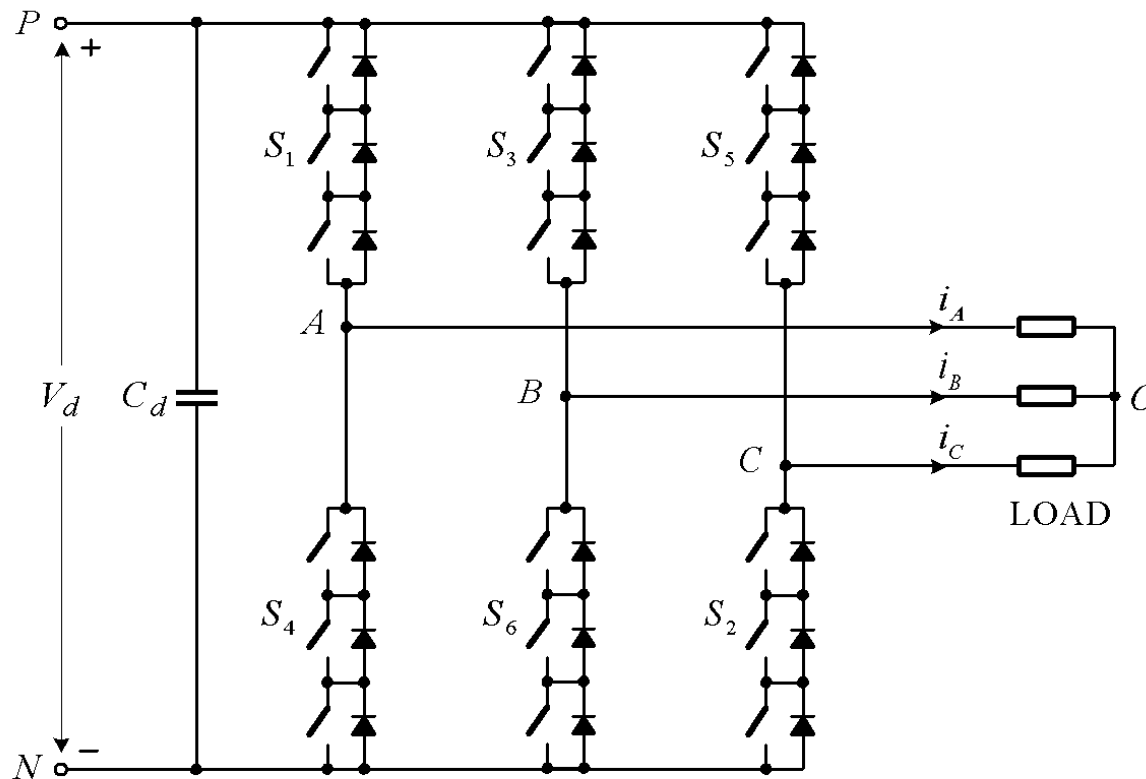


**Assumption:**

**dc capacitor very large  $\rightarrow$  dc voltage ripple free**

# Sinusoidal PWM

## • Modulating and Carrier Waves

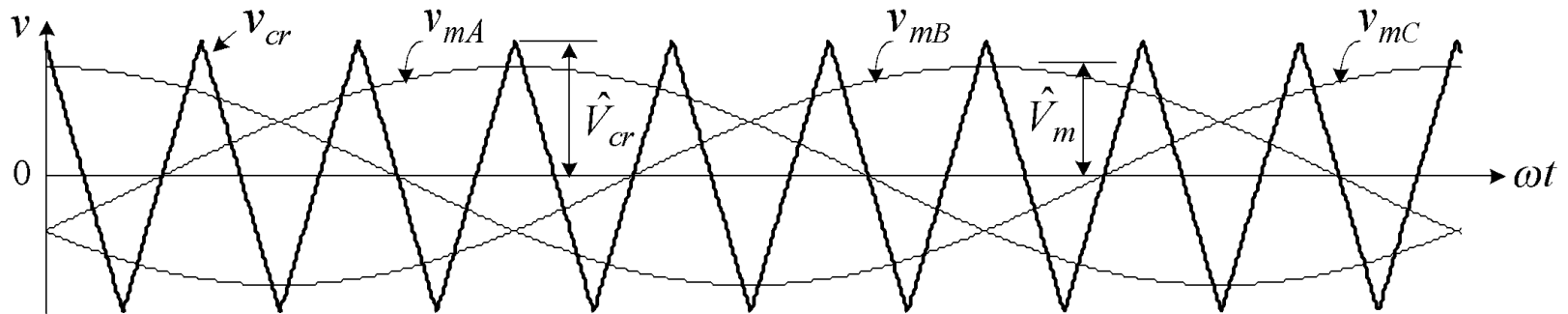

•  $V_{cr}$  – Carrier wave (triangle)

• Amplitude modulation index

$$m_a = \frac{\hat{V}_m}{\hat{V}_{cr}}$$


•  $V_m$  – Modulating wave (sine)

• Frequency modulation index

$$m_f = \frac{f_{cr}}{f_m}$$

# Sinusoidal PWM

- Gate Signal Generation

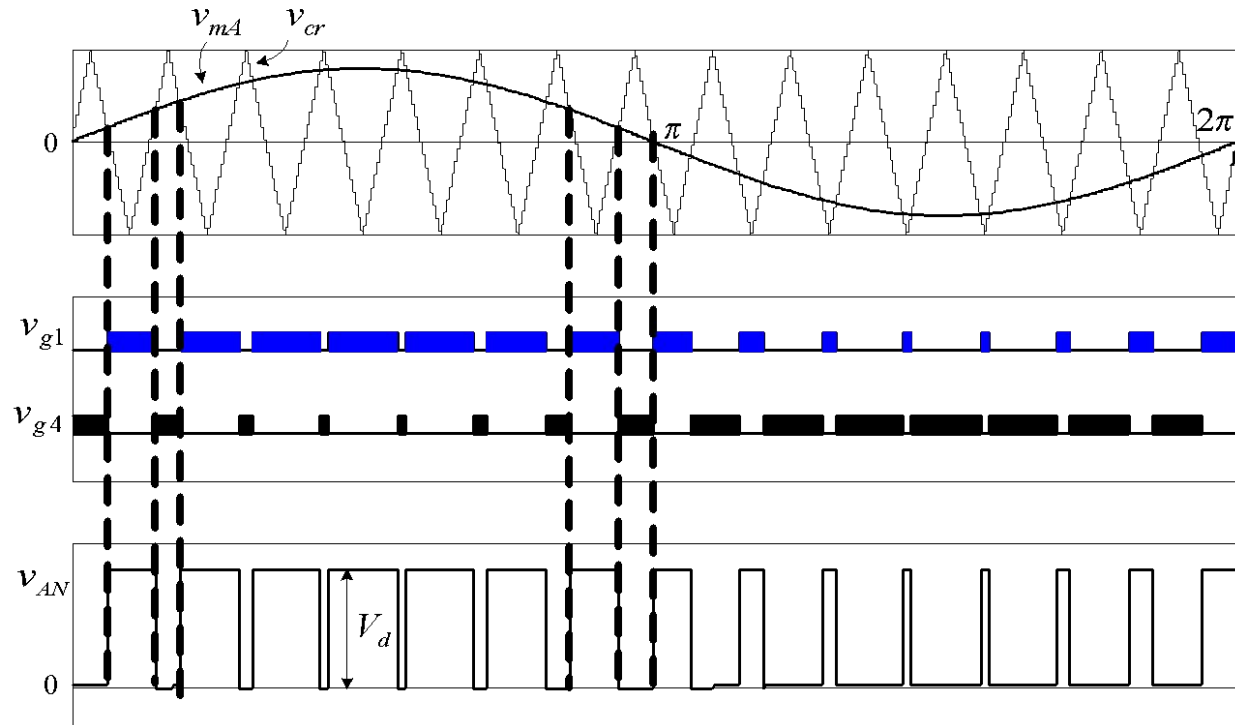


Phase $A$	$v_{mA} > v_{cr}$	$v_{g1} > 0$ ( $v_{g4} < 0$ )	$S_1$ on ( $S_4$ off)	$v_{AN} = V_d$
	$v_{mA} < v_{cr}$	$v_{g4} > 0$ ( $v_{g1} < 0$ )	$S_4$ on ( $S_1$ off)	$v_{AN} = 0$

$V_{g1}$  and  $V_{g4}$  are complementary




# Sinusoidal PWM

## • Line-to-Line Voltage $V_{AB}$

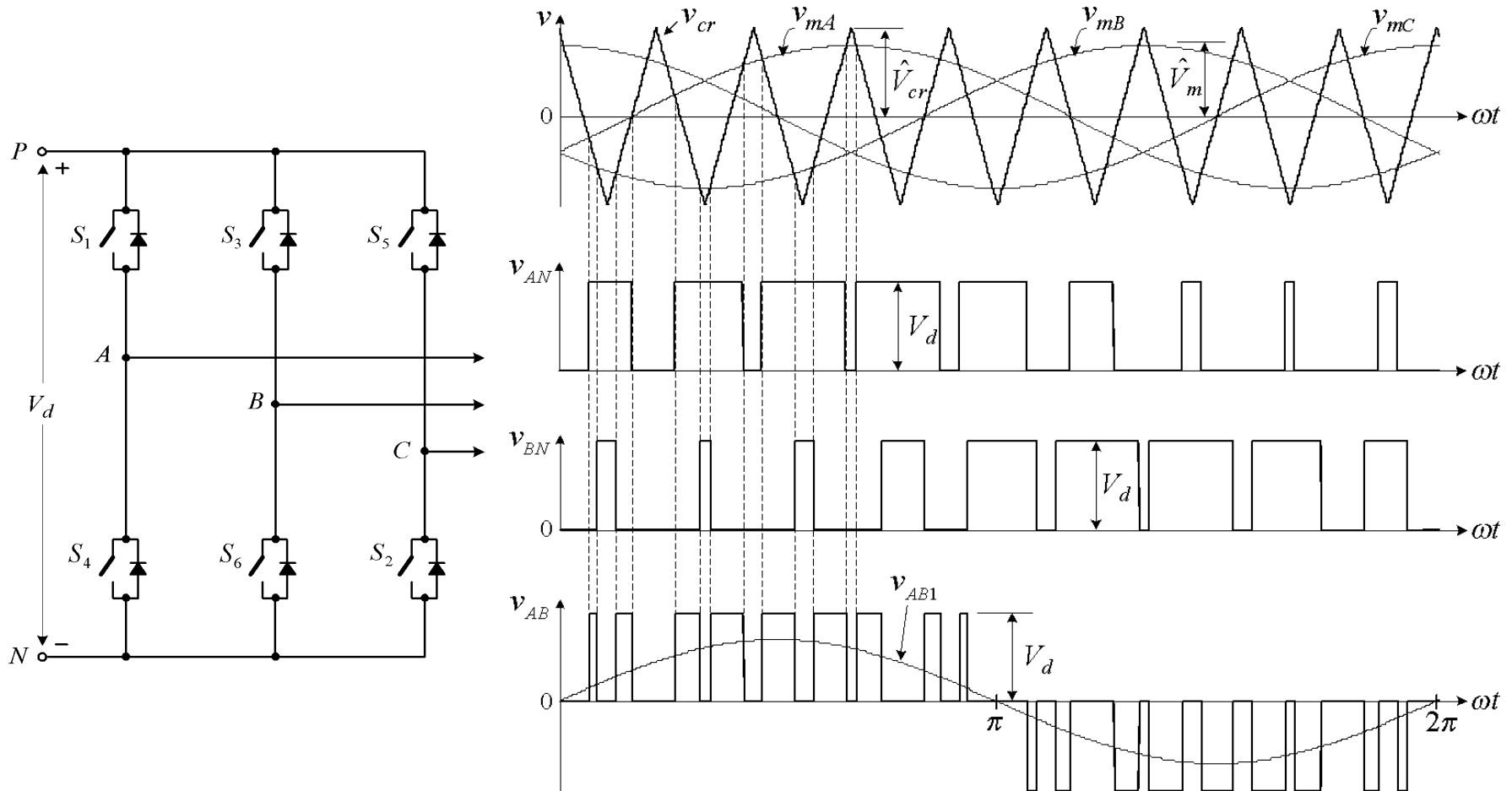

# Sinusoidal PWM


## • Waveforms and FFT

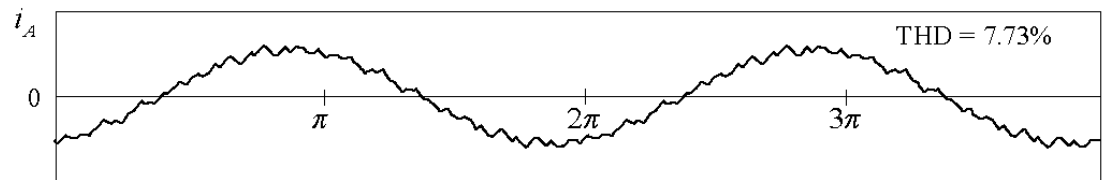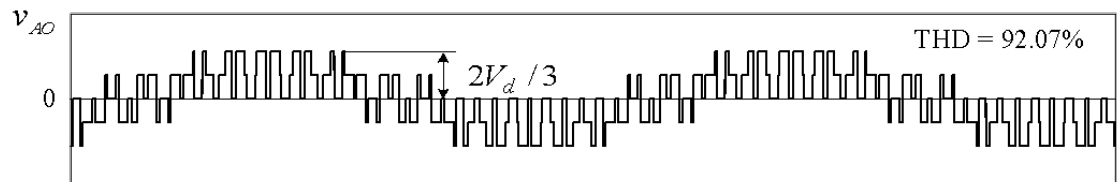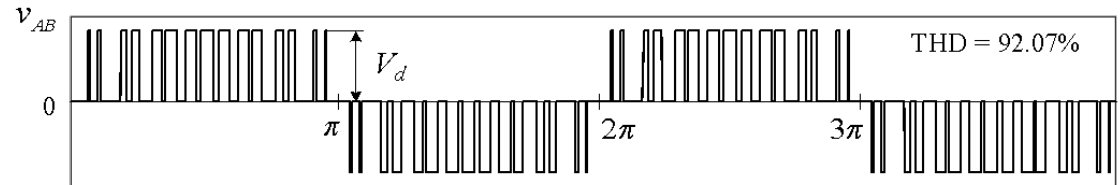

- $m_a = 0.8$ ,  $m_f = 15$ ,  
 $f_m = 60\text{Hz}$ ,  $f_{cr} = 900\text{Hz}$

## • Switching frequency

- $f_{sw} = f_{cr} = 900\text{Hz}$

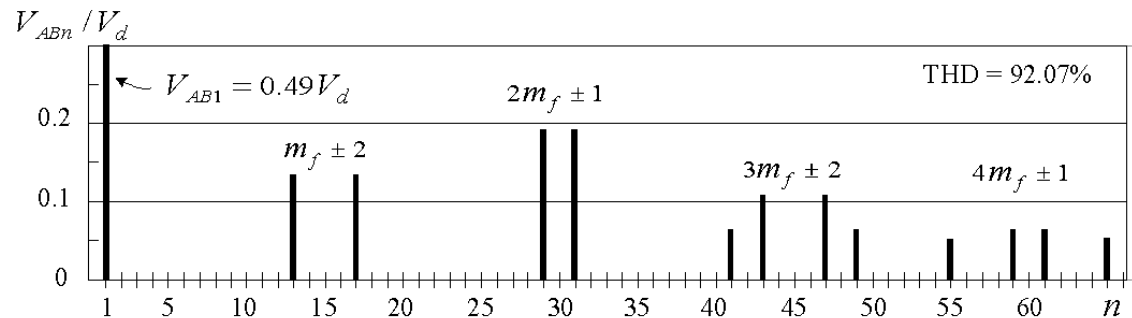




# Sinusoidal PWM




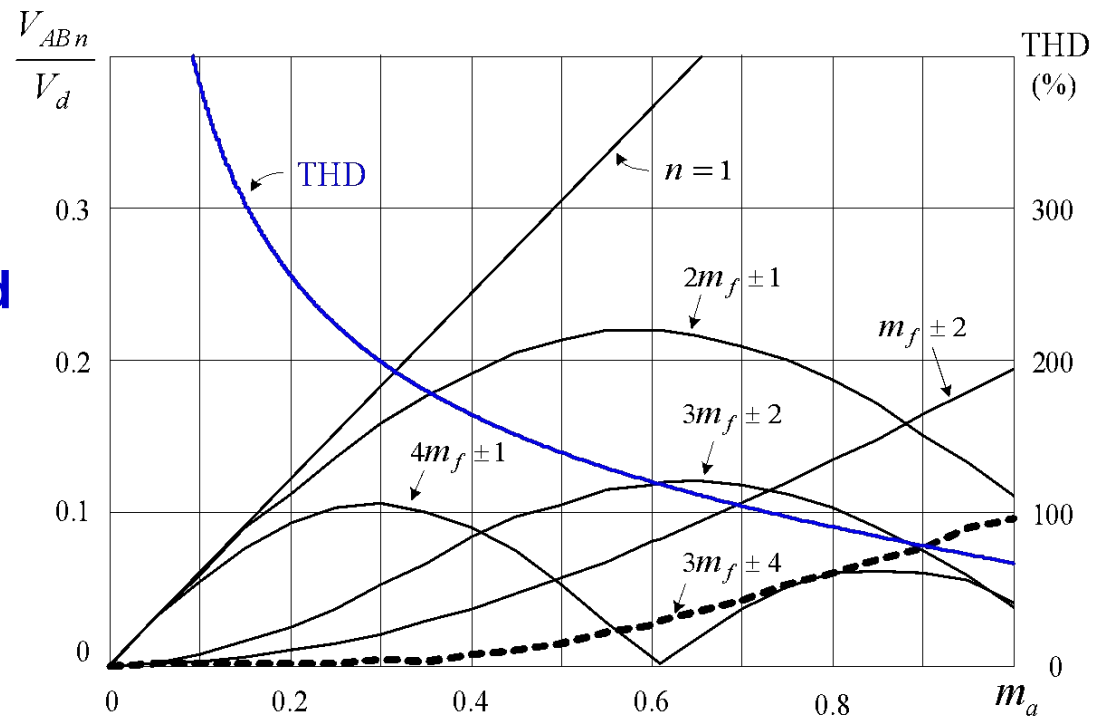
## • Harmonic Content

- Low order harmonics  $n < (m_f - 2)$  are eliminated
- $V_{AB1}$  versus  $m_a$  is linear
- $V_{AB1,max} = 0.612V_d$



# Sinusoidal PWM

- Over-Modulation

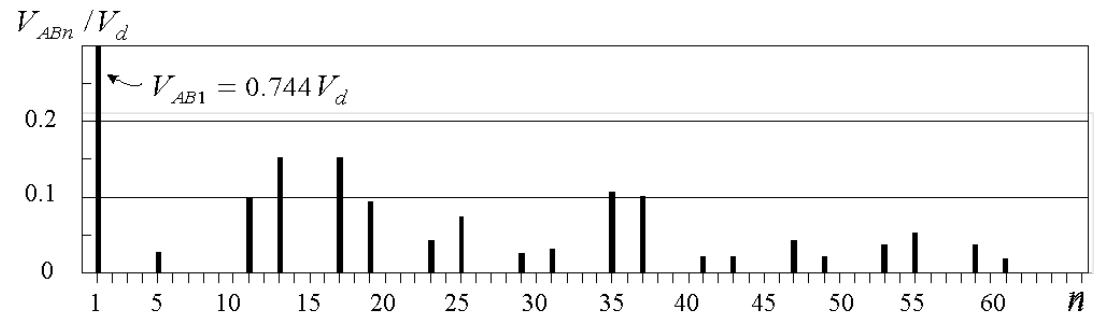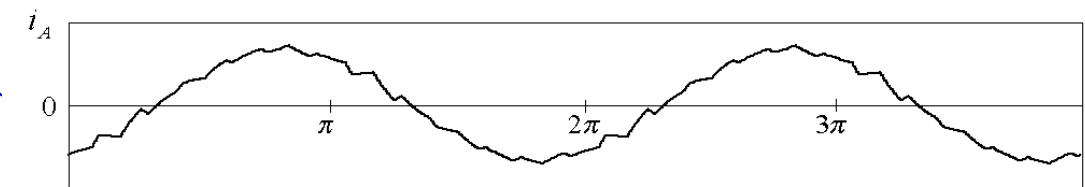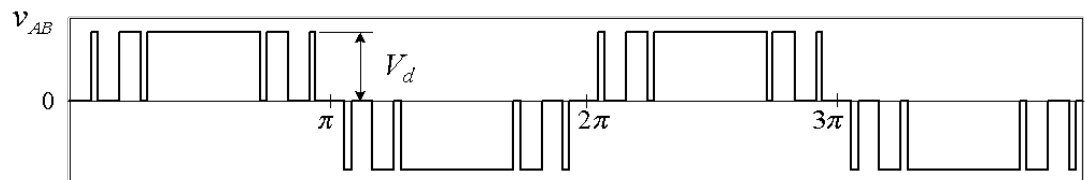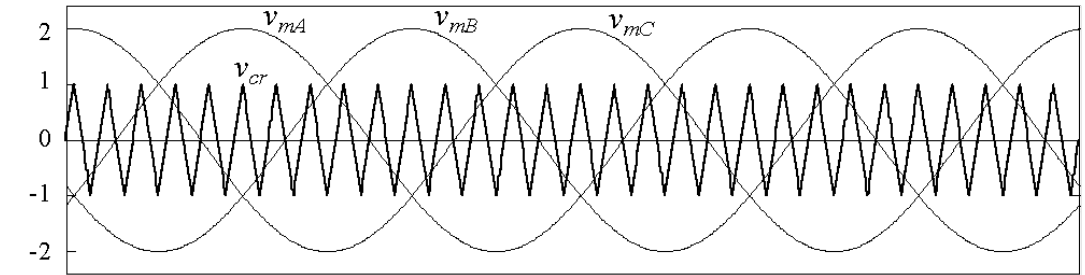


- Fundamental voltage  $\uparrow$

- Low-order harmonics  $\uparrow$

# Sinusoidal PWM


## • Third Harmonic Injection PWM

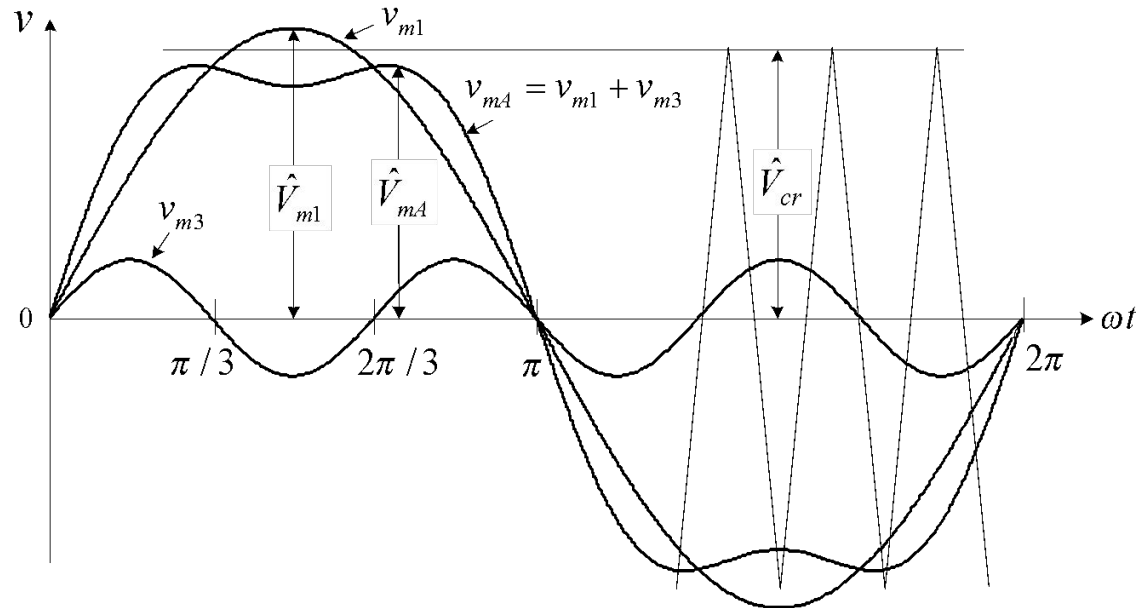

- $\hat{V}_{m1} > \hat{V}_{cr}$  **Fundamental voltage increased**
- $\hat{V}_{mA} \leq \hat{V}_{cr}$  **No low order harmonics produced**
- **3<sup>rd</sup> harmonic – zero sequence** (to appear in  $v_{AN}$  and  $v_{BN}$ )
- **No triplen harmonics in  $v_{AB}$**  ( $v_{AB} = v_{AN} - v_{BN}$ )

# Space Vector Modulation


## • Switching States

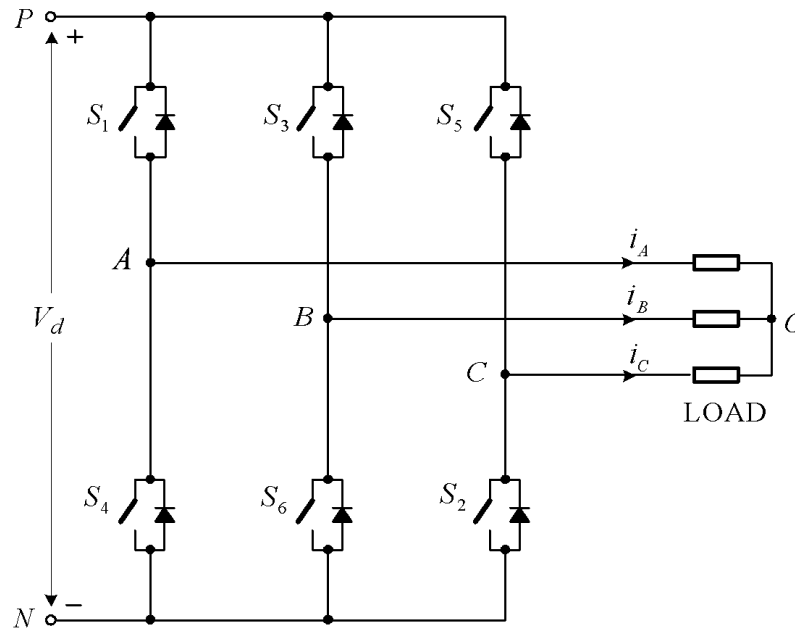

Switching State	Leg A			Leg B			Leg C		
	$S_1$	$S_4$	$V_{AN}$	$S_3$	$S_6$	$V_{BN}$	$S_5$	$S_2$	$V_{CN}$
P	On	Off	$V_d$	On	Off	$V_d$	On	Off	$V_d$
O	Off	On	0	Off	On	0	Off	On	0

# Space Vector Modulation

- Switching States (Three-Phase)

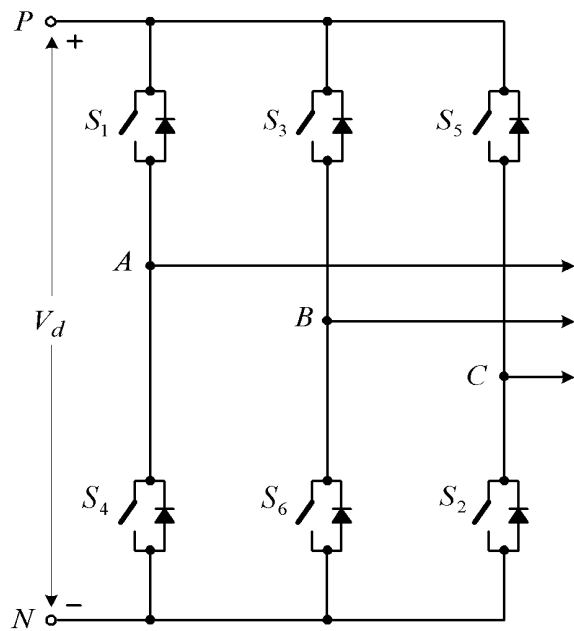

Switching State (Three Phases)	On-state Switch
[PPP]	$S_1, S_3, S_5$
[OOO]	$S_4, S_6, S_2$
[POO]	$S_1, S_6, S_2$
[PPO]	$S_1, S_3, S_2$
[OPO]	$S_4, S_3, S_2$
[OPP]	$S_4, S_3, S_5$
[OOP]	$S_4, S_6, S_5$
[POP]	$S_1, S_6, S_5$

- Eight switching states


# Space Vector Modulation

## • Space Vector Diagram

• **Active vectors:**  $\vec{V}_1$  to  $\vec{V}_6$   
(stationary, not rotating)

• **Zero vector:**  $\vec{V}_0$

• **Six sectors:** I to VI

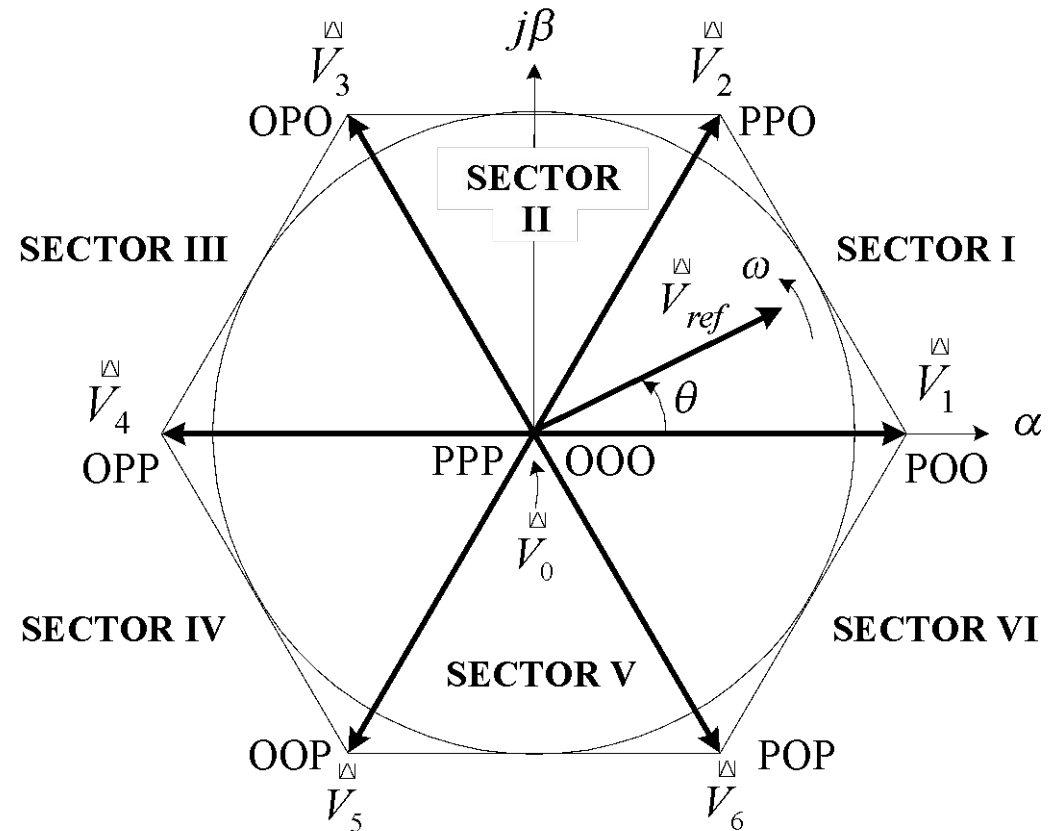

# Space Vector Modulation

---

## • Space Vectors

### • Three-phase voltages

$$v_{AO}(t) + v_{BO}(t) + v_{CO}(t) = 0 \quad (1)$$

### • Two-phase voltages

$$\begin{bmatrix} v_{\alpha}(t) \\ v_{\beta}(t) \end{bmatrix} = \frac{2}{3} \begin{bmatrix} \cos 0 & \cos \frac{2\pi}{3} & \cos \frac{4\pi}{3} \\ \sin 0 & \sin \frac{2\pi}{3} & \sin \frac{4\pi}{3} \end{bmatrix} \begin{bmatrix} v_{AO}(t) \\ v_{BO}(t) \\ v_{CO}(t) \end{bmatrix} \quad (2)$$

### • Space vector representation

$$\vec{V}(t) = v_{\alpha}(t) + j v_{\beta}(t) \quad (3)$$

(2)  $\rightarrow$  (3)

$$\vec{V}(t) = \frac{2}{3} \left[ v_{AO}(t) e^{j0} + v_{BO}(t) e^{j2\pi/3} + v_{CO}(t) e^{j4\pi/3} \right] \quad (4)$$

where  $e^{jx} = \cos x + j \sin x$

# Space Vector Modulation

## • Space Vectors (Example)

Switching state [POO]  $\rightarrow$   $S_1$ ,  $S_6$  and  $S_2$

ON

$$v_{AO}(t) = \frac{2}{3}V_d, \quad v_{BO}(t) = -\frac{1}{3}V_d \quad \text{and} \quad v_{CO}(t) = -\frac{1}{3}V_d \quad (5)$$


(5)  $\rightarrow$  (4)

$$\vec{V}_1 = \frac{2}{3}V_d e^{j0} \quad (6)$$

Similarly,

$$\vec{V}_k = \frac{2}{3}V_d e^{j(k-1)\frac{\pi}{3}} \quad (7)$$


$$k = 1, 2, \dots, 6.$$

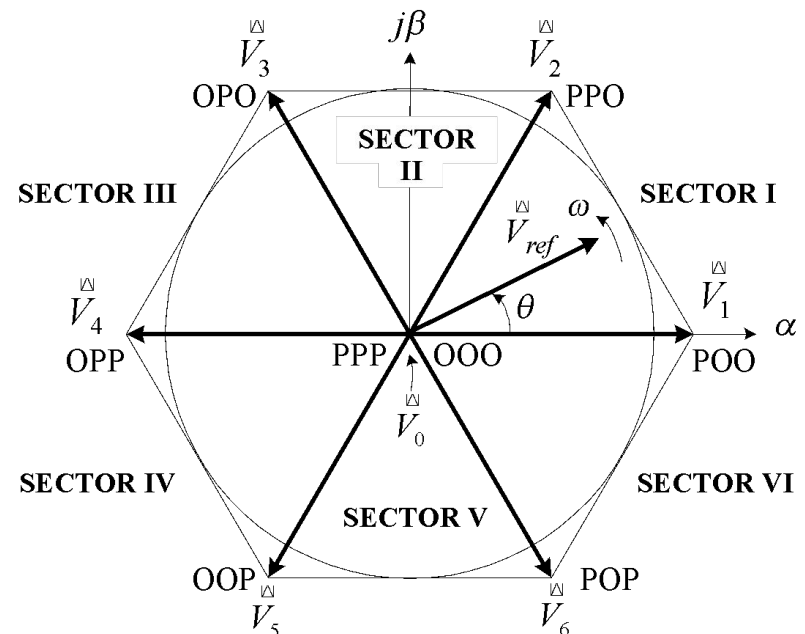



# Space Vector Modulation

## • Active and Zero Vectors

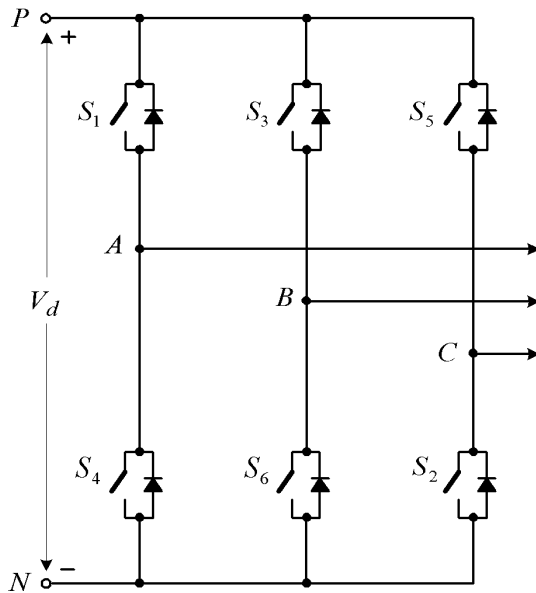

Space Vector		Switching State (Three Phases)	On-state Switch	Vector Definition
Zero Vector	$\vec{V}_0$	[PPP]	$S_1, S_3, S_5$	$\vec{V}_0 = 0$
		[OOO]	$S_4, S_6, S_2$	
Active Vector	$\vec{V}_1$	[POO]	$S_1, S_6, S_2$	$\vec{V}_1 = \frac{2}{3}V_d e^{j0}$
	$\vec{V}_2$	[PPO]	$S_1, S_3, S_2$	$\vec{V}_2 = \frac{2}{3}V_d e^{j\frac{\pi}{3}}$
	$\vec{V}_3$	[OPO]	$S_4, S_3, S_2$	$\vec{V}_3 = \frac{2}{3}V_d e^{j\frac{2\pi}{3}}$
	$\vec{V}_4$	[OPP]	$S_4, S_3, S_5$	$\vec{V}_4 = \frac{2}{3}V_d e^{j\frac{3\pi}{3}}$
	$\vec{V}_5$	[OOP]	$S_4, S_6, S_5$	$\vec{V}_5 = \frac{2}{3}V_d e^{j\frac{4\pi}{3}}$
	$\vec{V}_6$	[POP]	$S_1, S_6, S_5$	$\vec{V}_6 = \frac{2}{3}V_d e^{j\frac{5\pi}{3}}$

- **Active Vector: 6**
- **Zero Vector: 1**
- **Redundant switching states: [PPP] and [OOO]**

# Space Vector Modulation

- Reference Vector  $\underline{V}_{ref}$

- Definition


$$\underline{V}_{ref} = V_{ref} e^{j\theta}$$

- Rotating in space at  $\omega$

$$\omega = 2\pi f \quad (8)$$


- Angular displacement
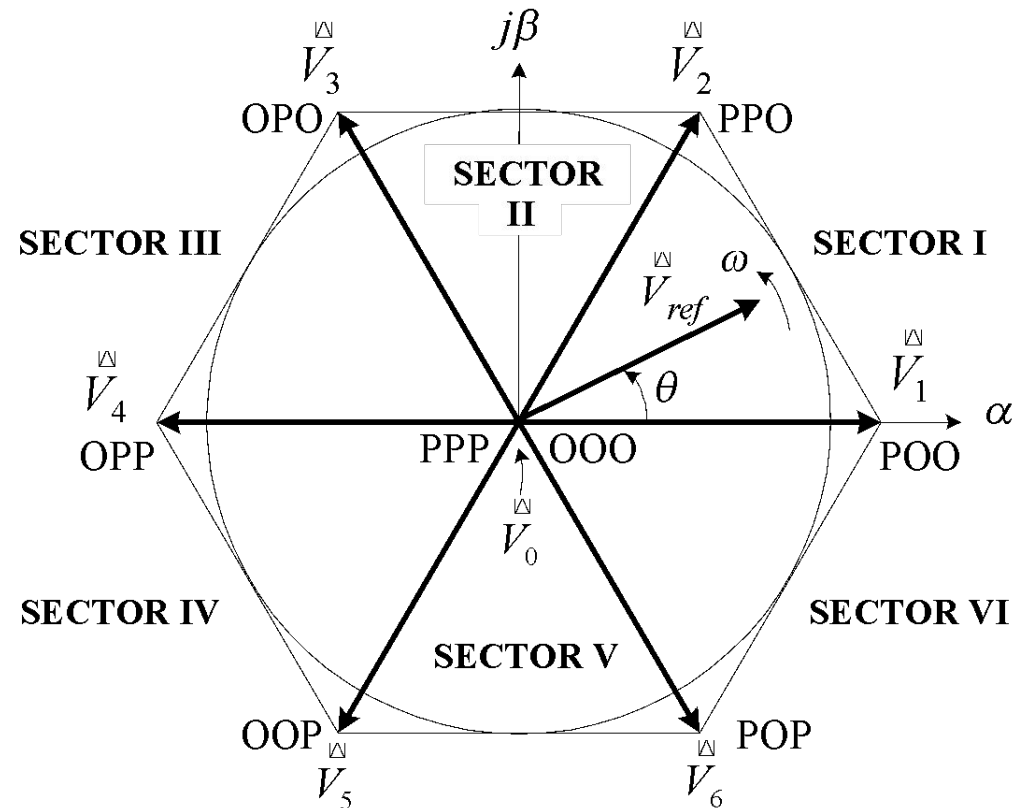
$$\theta(t) = \int_0^t \omega dt \quad (9)$$


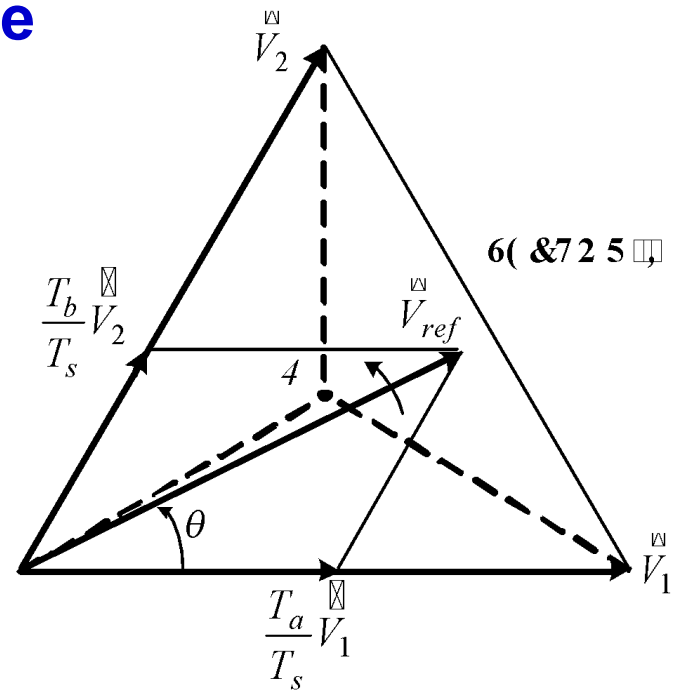
# Space Vector Modulation

- Relationship Between  $V_{ref}$  and  $V_{AB}$
- $V_{ref}$  is approximated by two active and a zero vectors
- $V_{ref}$  rotates one revolution,  $V_{AB}$  completes one cycle
- Length of  $V_{ref}$  corresponds to magnitude of  $V_{AB}$



# Space Vector Modulation

## • Dwell Time Calculation

### • Volt-Second Balancing

$$\begin{cases} \vec{V}_{ref} T_s = \vec{V}_1 T_a + \vec{V}_2 T_b + \vec{V}_0 T_0 \\ T_s = T_a + T_b + T_0 \end{cases} \quad (10)$$

•  $T_a$ ,  $T_b$  and  $T_0$  – dwell times for  $\vec{V}_1$ ,  $\vec{V}_2$  and  $\vec{V}_0$


•  $T_s$  – sampling period

### • Space vectors

$$\vec{V}_{ref} = V_{ref} e^{j\theta}, \quad \vec{V}_1 = \frac{2}{3} V_d, \quad \vec{V}_2 = \frac{2}{3} V_d e^{j\frac{\pi}{3}} \quad \text{and} \quad \vec{V}_0 = 0 \quad (11)$$

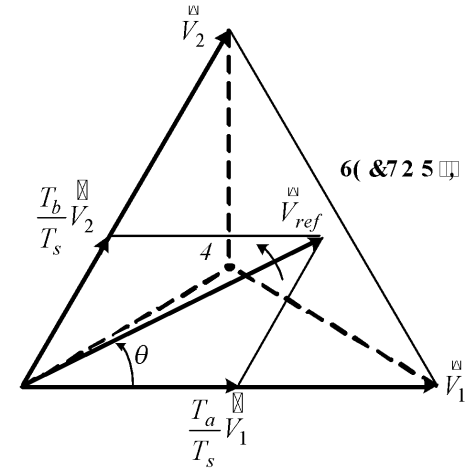(11)  $\rightarrow$  (10)

$$\begin{cases} \text{Re: } V_{ref} (\cos \theta) T_s = \frac{2}{3} V_d T_a + \frac{1}{3} V_d T_b \\ \text{Im: } V_{ref} (\sin \theta) T_s = \frac{1}{\sqrt{3}} V_d T_b \end{cases} \quad (12)$$



# Space Vector Modulation

---


- Dwell Times

Solve (12)

$$\left\{ \begin{array}{l} T_a = \frac{\sqrt{3} T_s V_{ref}}{V_d} \sin\left(\frac{\pi}{3} - \theta\right) \\ T_b = \frac{\sqrt{3} T_s V_{ref}}{V_d} \sin\theta \\ T_0 = T_s - T_a - T_b \end{array} \right. \quad 0 \leq \theta < \pi/3 \quad (13)$$

# Space Vector Modulation

- $V_{ref}$  Location versus Dwell Times

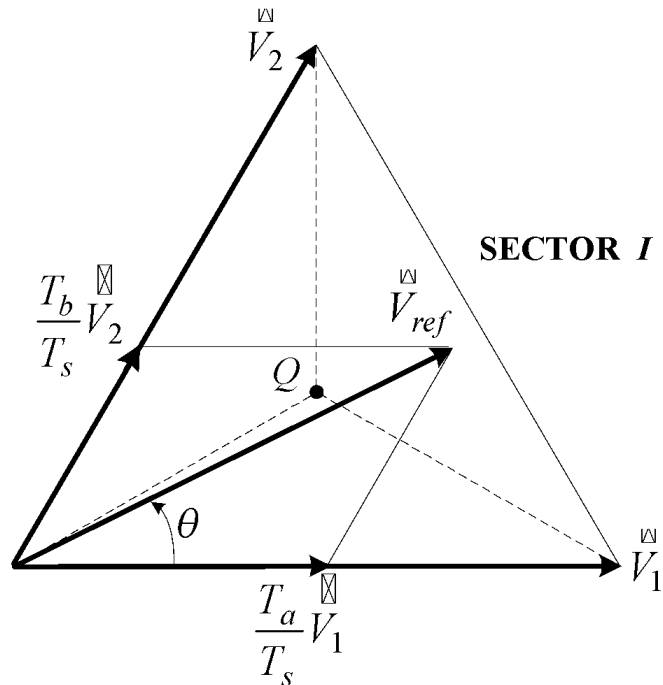

$V_{ref}$ Location	$\theta = 0$	$0 < \theta < \frac{\pi}{6}$	$\theta = \frac{\pi}{6}$	$\frac{\pi}{6} < \theta < \frac{\pi}{3}$	$\theta = \frac{\pi}{3}$
Dwell Times	$T_a > 0$ $T_b = 0$	$T_a > T_b$	$T_a = T_b$	$T_a < T_b$	$T_a = 0$ $T_b > 0$

# Space Vector Modulation

---

- Modulation Index

$$\begin{cases} T_a = T_s m_a \sin\left(\frac{\pi}{3} - \theta\right) \\ T_b = T_s m_a \sin\theta \\ T_c = T_s - T_b - T_a \end{cases} \quad (15)$$

$$m_a = \frac{\sqrt{3} V_{ref}}{V_d} \quad (16)$$

# Space Vector Modulation

## • Modulation Range


### • $V_{ref,max}$

$$V_{ref,max} = \frac{2}{3} V_d \times \frac{\sqrt{3}}{2} = \frac{V_d}{\sqrt{3}} \quad (17)$$

(17)  $\rightarrow$  (16)

### • $m_{a,max} = 1 \rightarrow$
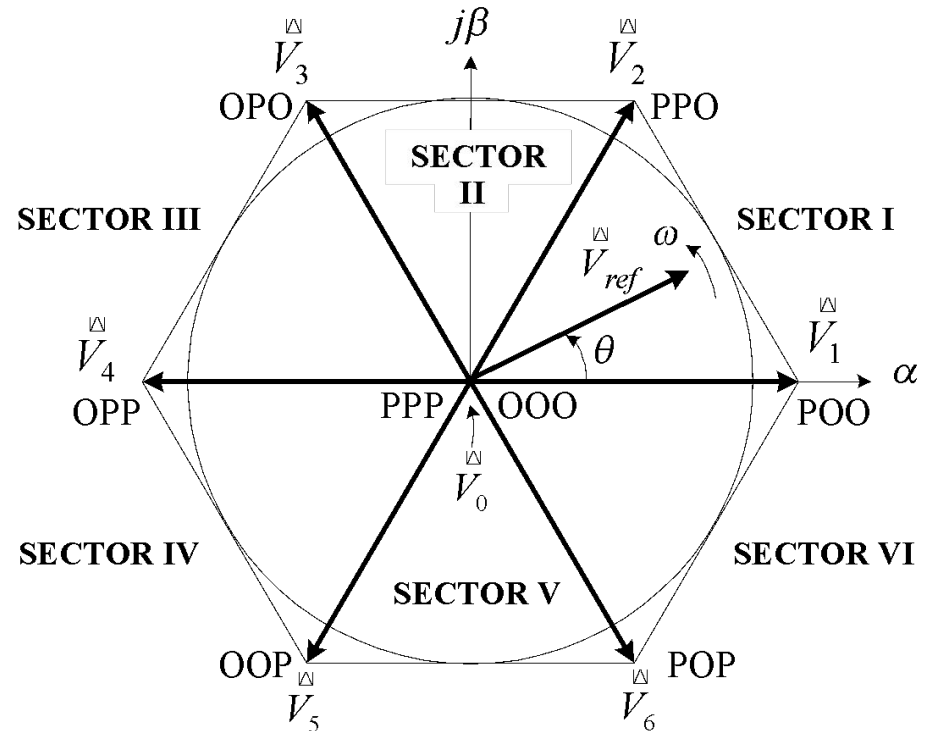
### • Modulation range: $0 \leq m_a \leq 1$ (18)





# Space Vector Modulation

---

- **Switching Sequence Design**
  - **Basic Requirement:**

Minimize the number of switchings per sampling period  $T_s$
  - **Implementation:**


Transition from one switching state to the next involves only two switches in the same inverter leg.

# Space Vector Modulation

## • Seven-segment Switching Sequence

- Selected vectors:  $V_0$ ,  $V_1$  and  $V_2$


- Dwell times:  $T_s = T_0 + T_a + T_b$

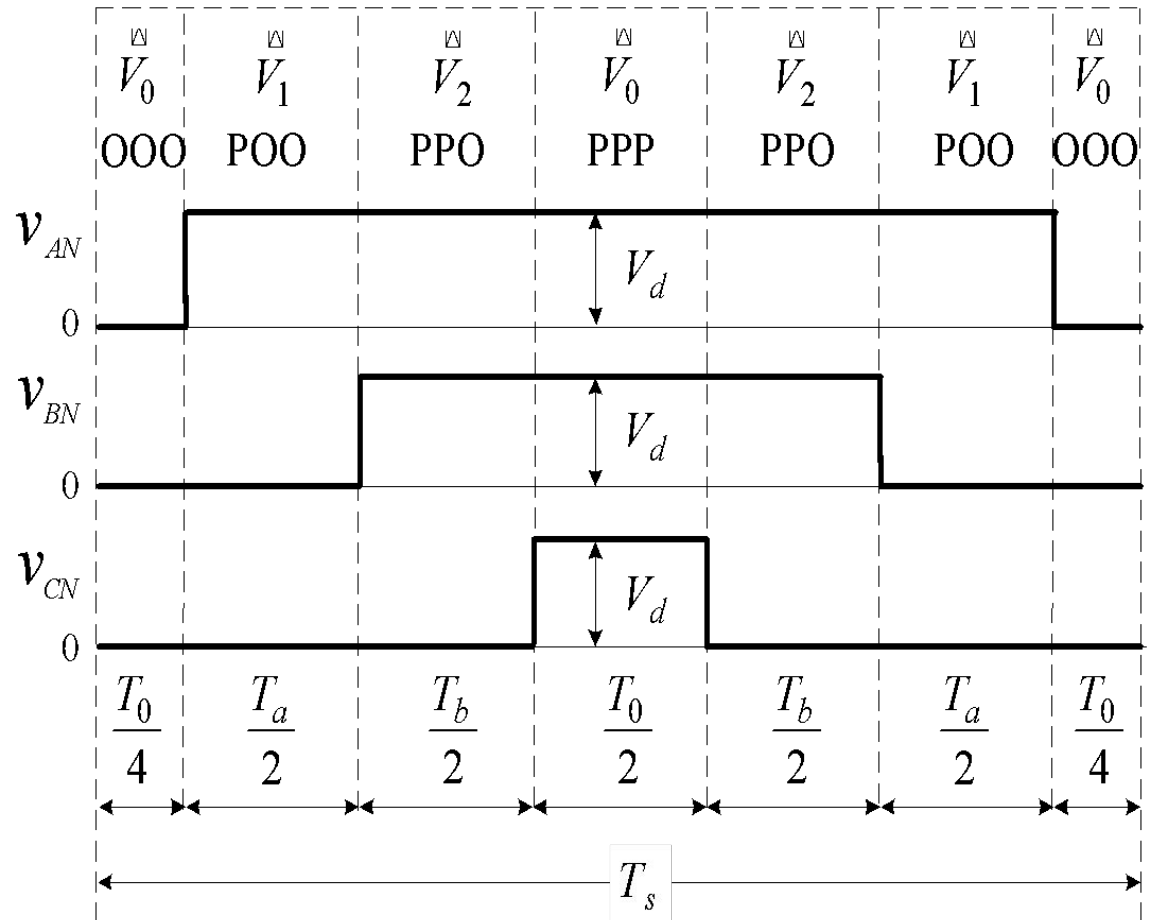

- Total number of switchings: 6
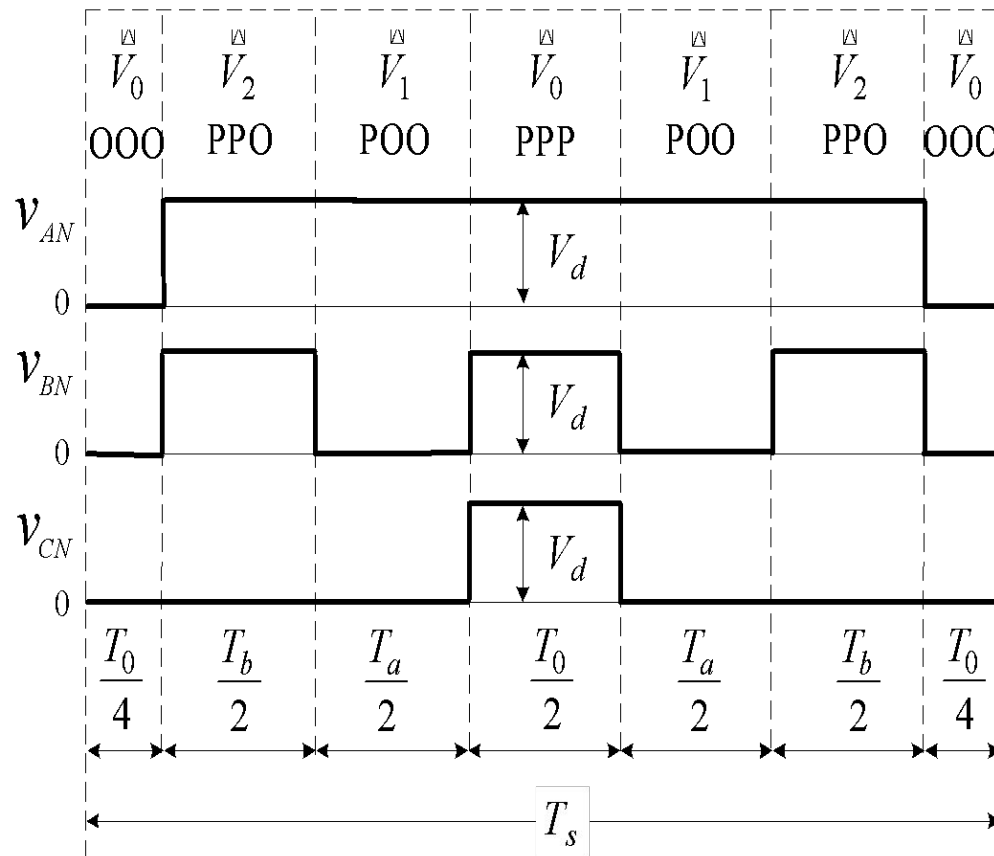
# Space Vector Modulation

- Undesirable Switching Sequence
  - Vectors  $V_1$  and  $V_2$  swapped



- Total number of switchings: 10

# Space Vector Modulation


## • Switching Sequence Summary (7-segments)

Sector	Switching Sequence						
I	$V_0$	$V_1$	$V_2$	$V_0$	$V_2$	$V_1$	$V_0$
	OOO	POO	PPO	PPP	PPO	POO	OOO
II	$V_0$	$V_3$	$V_2$	$V_0$	$V_2$	$V_3$	$V_0$
	OOO	OPO	PPO	PPP	PPO	OPO	OOO
III	$V_0$	$V_3$	$V_4$	$V_0$	$V_4$	$V_3$	$V_0$
	OOO	OPO	OPP	PPP	OPP	OPO	OOO
IV	$V_0$	$V_5$	$V_4$	$V_0$	$V_4$	$V_5$	$V_0$
	OOO	OOP	OPP	PPP	OPP	OOP	OOO
V	$V_0$	$V_5$	$V_6$	$V_0$	$V_6$	$V_5$	$V_0$
	OOO	OOP	POP	PPP	POP	OOP	OOO
VI	$V_0$	$V_1$	$V_6$	$V_0$	$V_6$	$V_1$	$V_0$
	OOO	POO	POP	PPP	POP	POO	OOO

**Note: The switching sequences for the odd and even sectors are different.**

# Space Vector Modulation





## • Simulated Waveforms

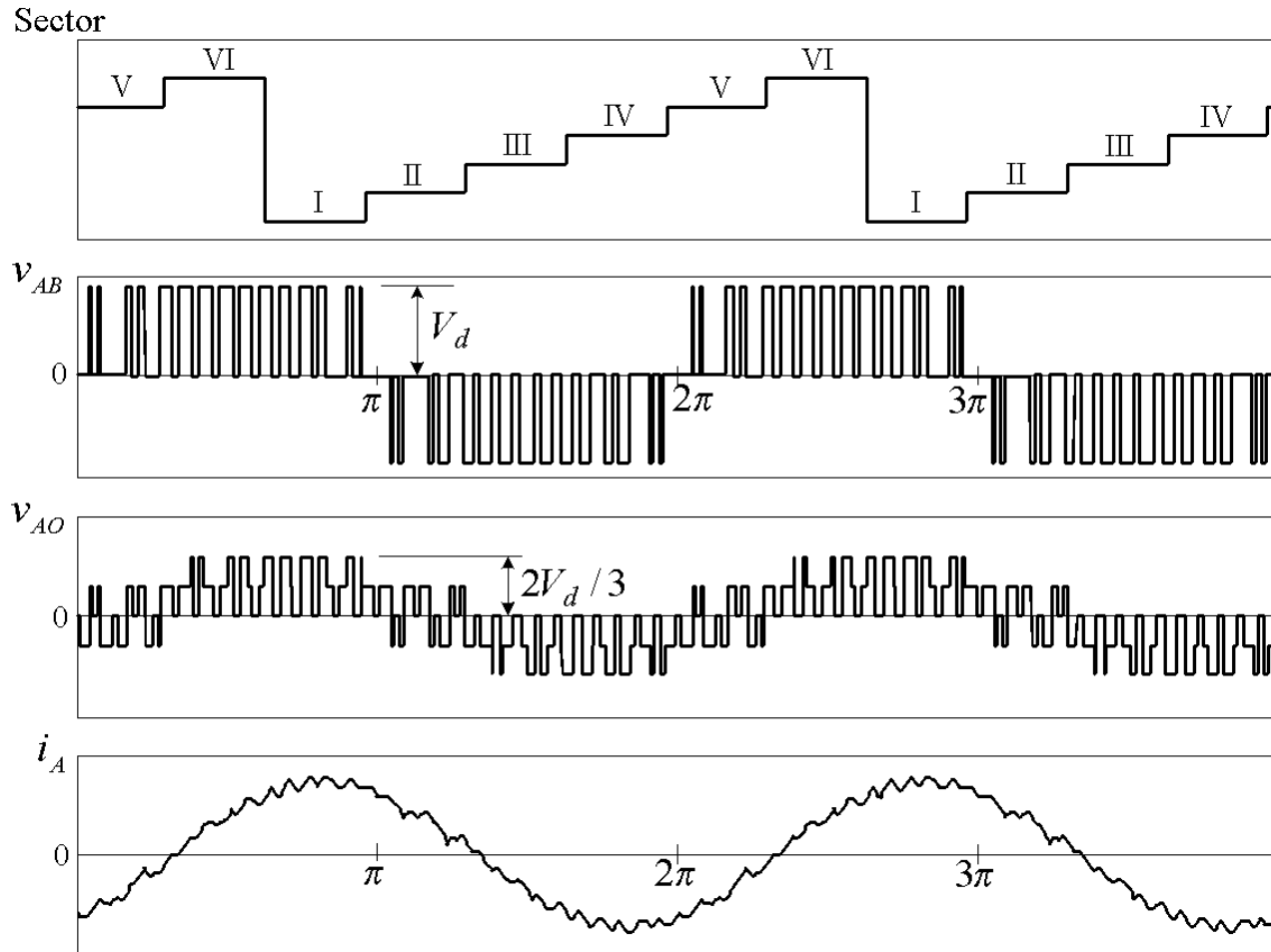

$$f_1 = 60\text{Hz}, f_{sw} = 900\text{Hz}, m_a = 0.696, T_s = 1.1\text{ms}$$


# Space Vector Modulation

## • Waveforms and FFT

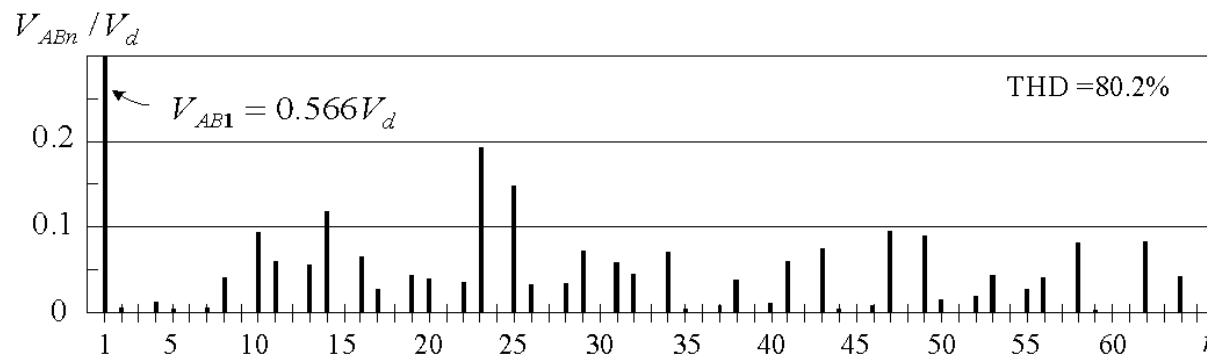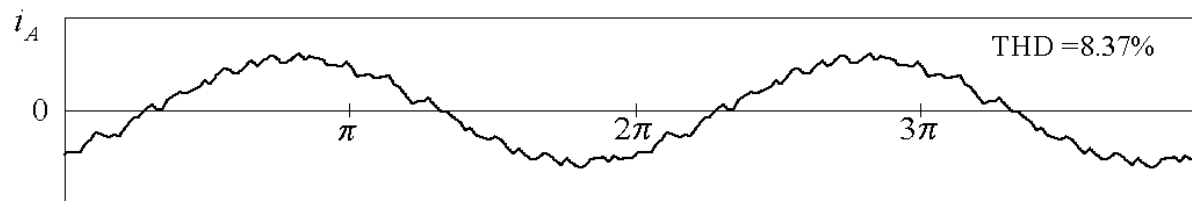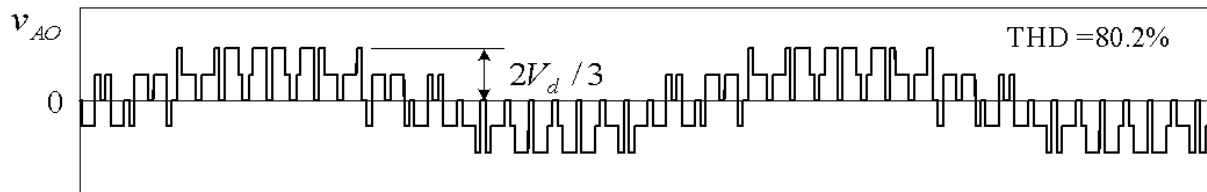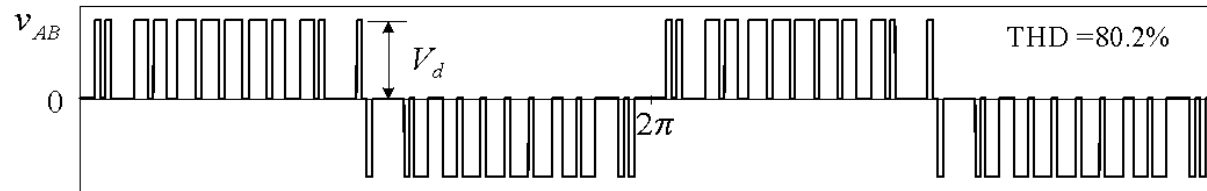


# Space Vector Modulation

- Waveforms and FFT (Measured)

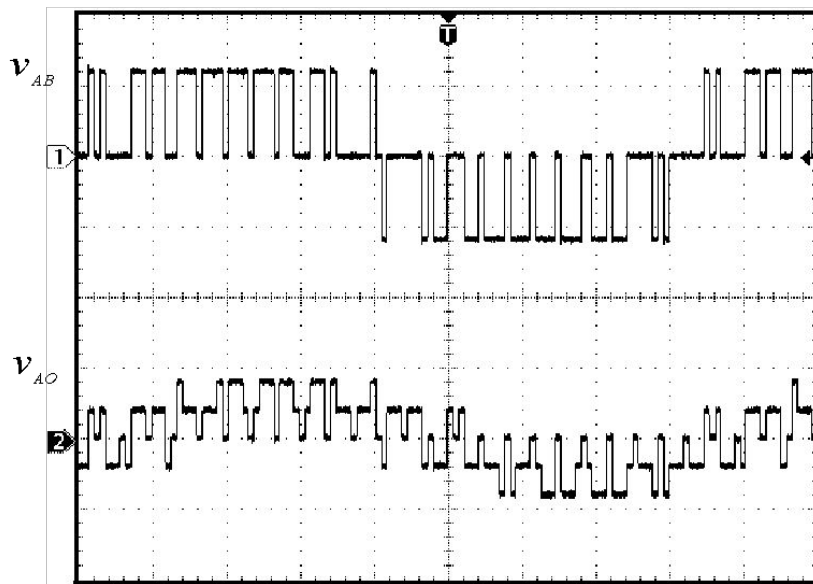


(a) Waveforms 2ms/div

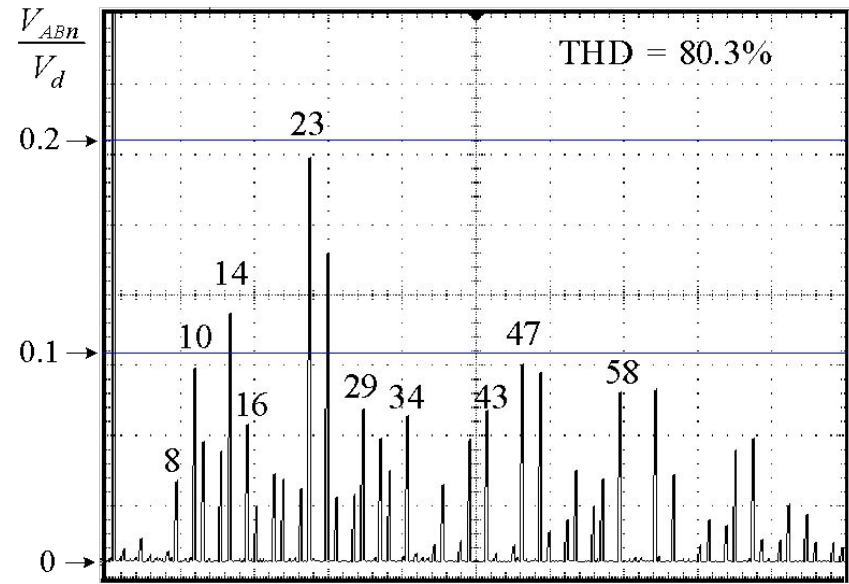


(b) Spectrum (500Hz/div)

# Space Vector Modulation

## • Waveforms and FFT (Measured)

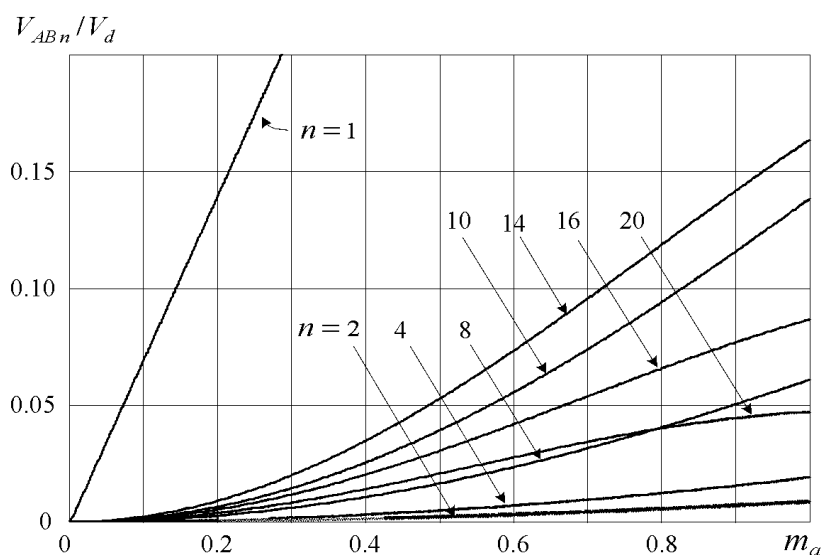

(a) Even order harmonics

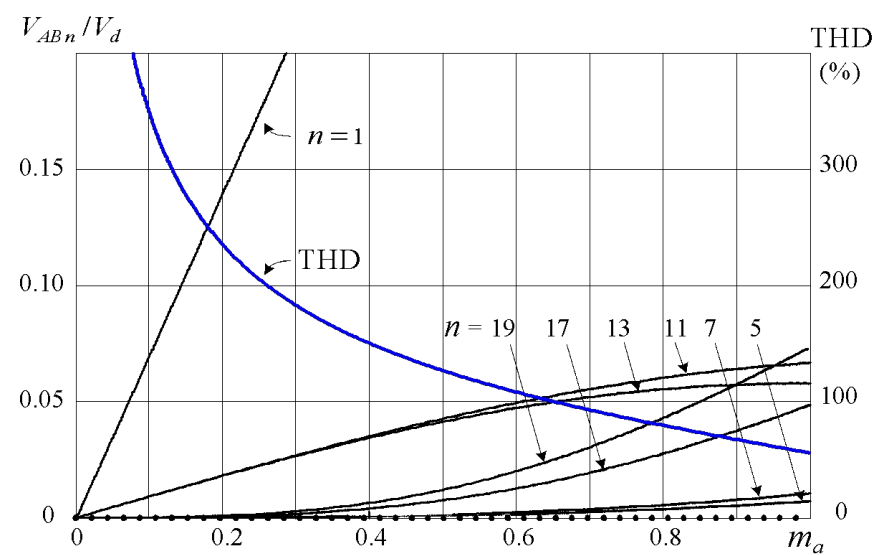


(b) Odd order harmonics

$$( f_1 = 60\text{Hz} \quad \text{and} \quad T_s = 1/720 \text{ sec} )$$




# Space Vector Modulation

## • Even-Order Harmonic Elimination

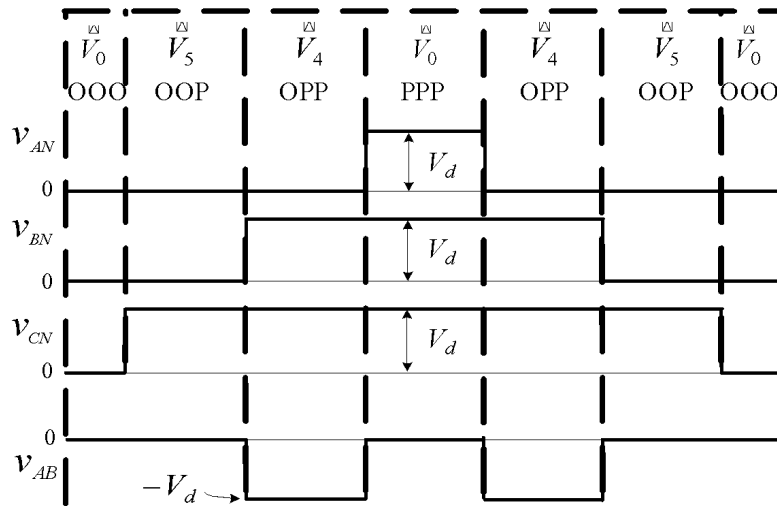

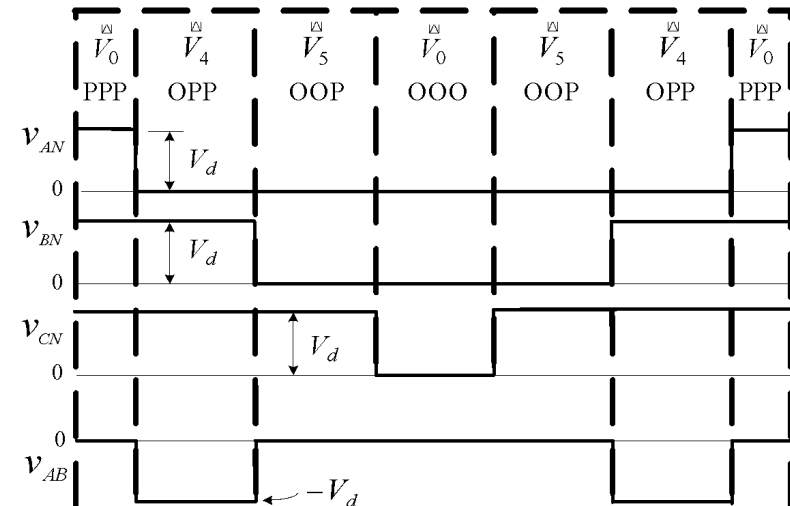
**Type-A sequence**  
(starts and ends with [000])



**Type-B sequence**  
(starts and ends with [PPP])

# Space Vector Modulation


## • Even-Order Harmonic Elimination

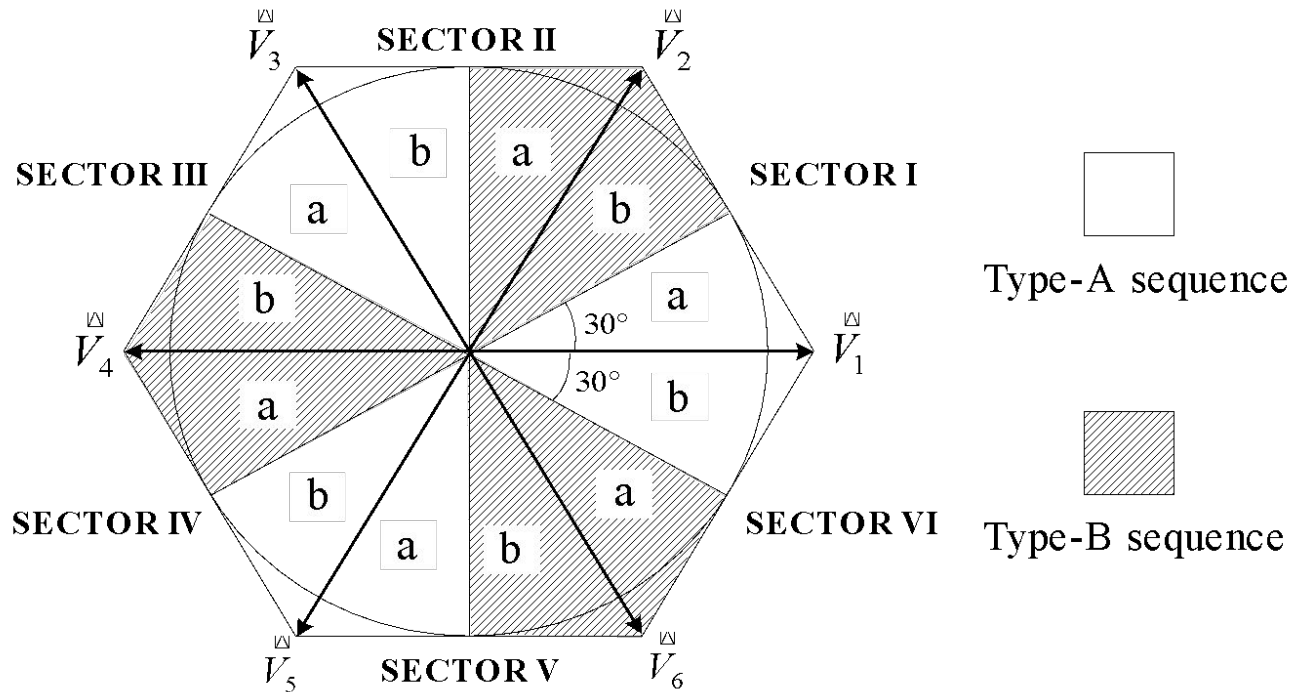


Space vector Diagram

# Space Vector Modulation

- Even-Order Harmonic Elimination

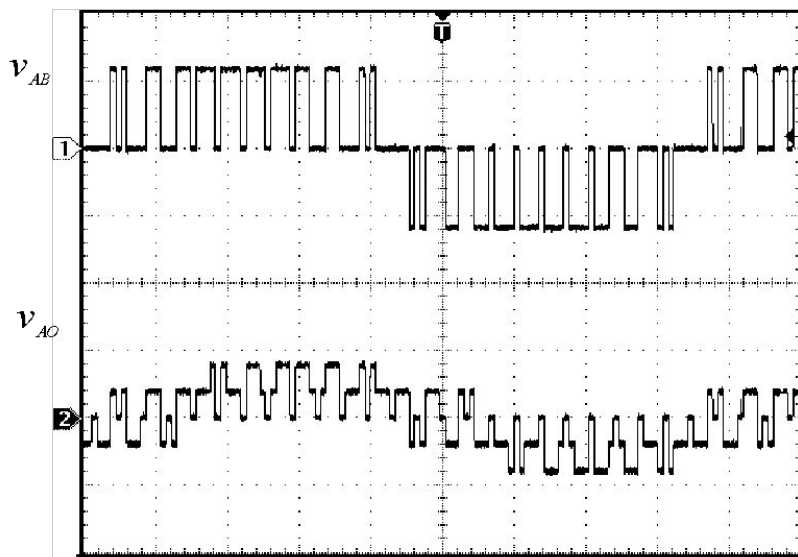

(a) Waveforms 2ms/div

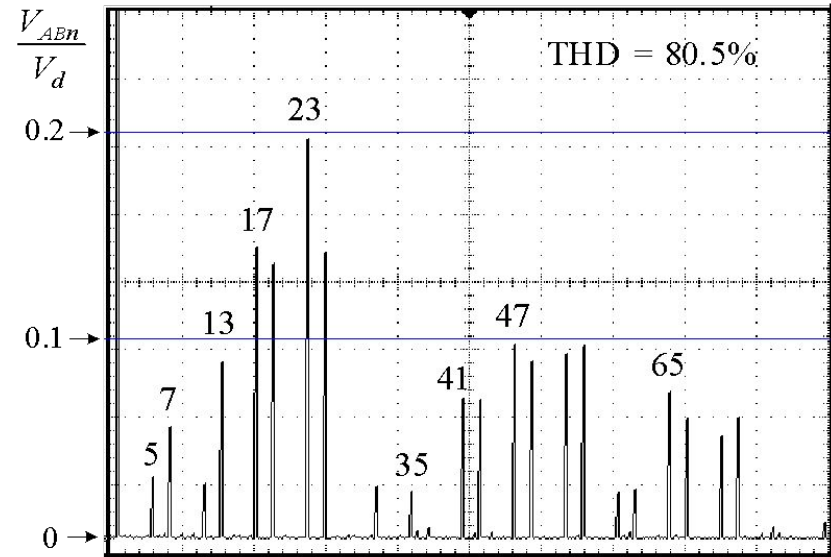


(b) Spectrum (500Hz/div)

- Measured waveforms and FFT

# Space Vector Modulation


## • Even-Order Harmonic Elimination

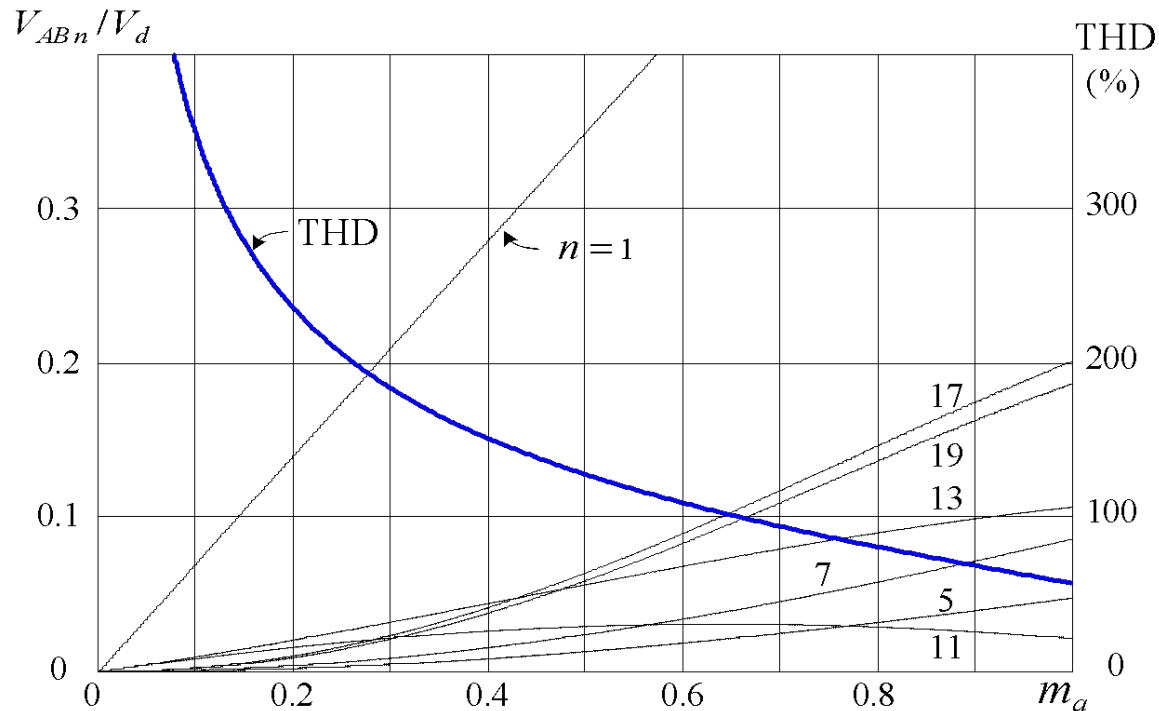

(  $f_1 = 60\text{Hz}$  and  $T_s = 1/720 \text{ sec}$  )

# Space Vector Modulation

## • Five-segment SVM

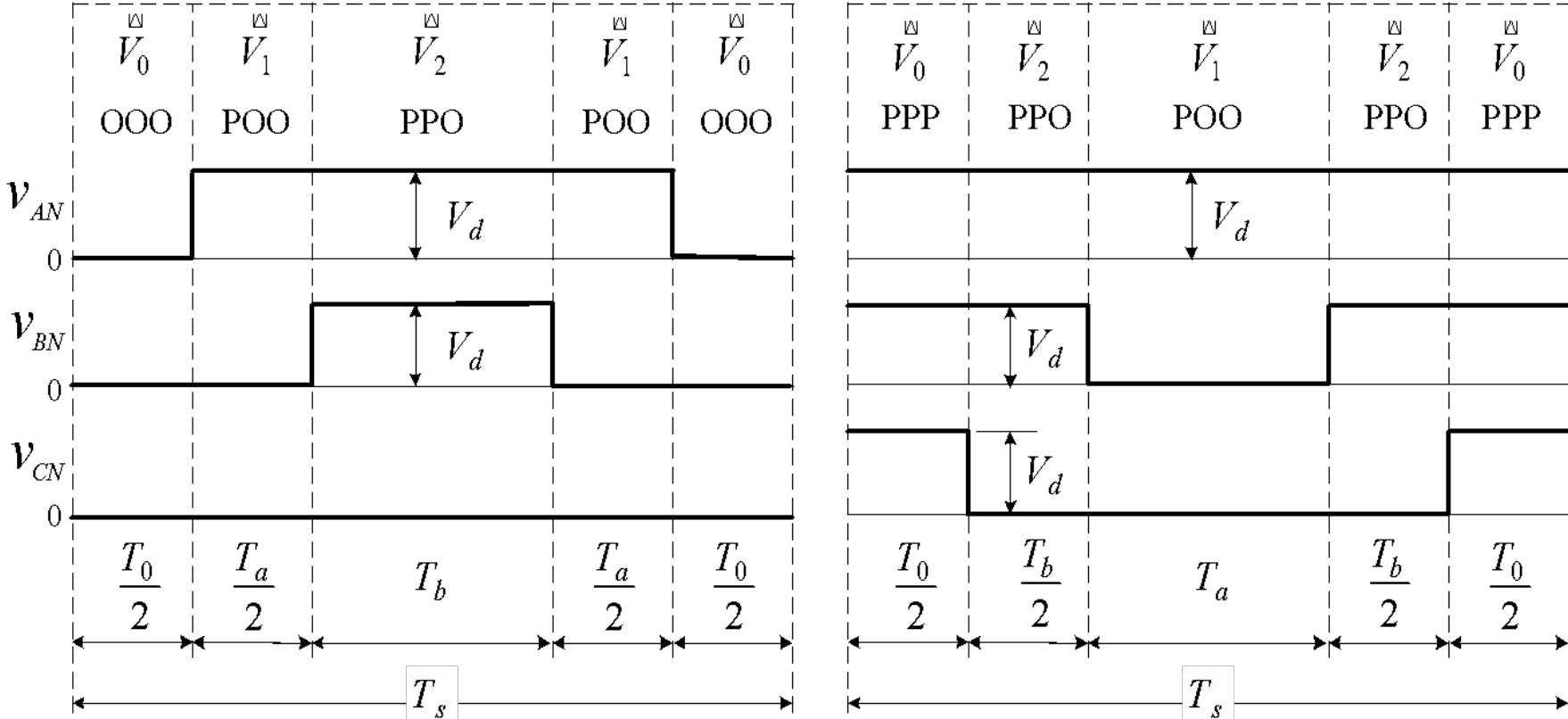

(a) Sequence A

(b) Sequence B


# Space Vector Modulation

## • Switching Sequence ( 5-segment)

Sector	Switching Sequence (A)					
<i>I</i>	$V_0$	$V_1$	$V_2$	$V_1$	$V_0$	$v_{CN} = 0$
	OOO	POO	PPO	POO	OOO	
<i>II</i>	$V_0$	$V_3$	$V_2$	$V_3$	$V_0$	$v_{CN} = 0$
	OOO	OPO	PPO	OPO	OOO	
<i>III</i>	$V_0$	$V_3$	$V_4$	$V_3$	$V_0$	$v_{AN} = 0$
	OOO	OPO	OPP	OPO	OOO	
<i>IV</i>	$V_0$	$V_5$	$V_4$	$V_5$	$V_0$	$v_{AN} = 0$
	OOO	OOP	OPP	OOP	OOO	
<i>V</i>	$V_0$	$V_5$	$V_6$	$V_5$	$V_0$	$v_{BN} = 0$
	OOO	OOP	POP	OOP	OOO	
<i>VI</i>	$V_0$	$V_1$	$V_6$	$V_1$	$V_0$	$v_{BN} = 0$
	OOO	POO	POP	POO	OOO	

# Space Vector Modulation

## • Simulated Waveforms ( 5-segment)

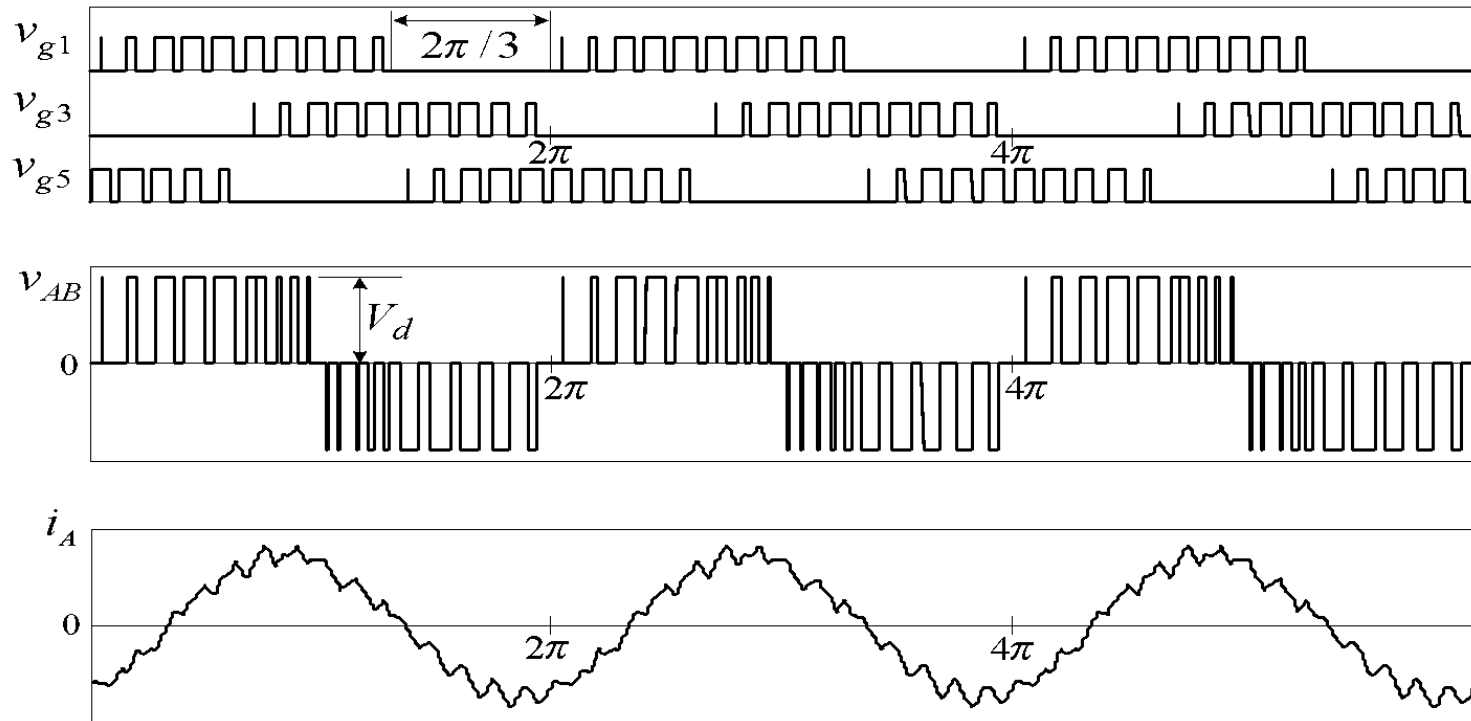

- $f_1 = 60\text{Hz}$ ,  $f_{sw} = 600\text{Hz}$ ,  $m_a = 0.696$ ,  $T_s = 1.1\text{ms}$

- No switching for a  $120^\circ$  period per cycle.
- Low switching frequency but high harmonic distortion



Thanks