

Power Converter Systems

Graduate Course EE8407

Bin Wu PhD, PEng

Professor
ELCE Department
Ryerson University

Contact Info

Office: ENG328
Tel: (416) 979-5000 ext: 6484
Email: bwu@ee.ryerson.ca
<http://www.ee.ryerson.ca/~bwu/>



Ryerson Campus

Topic 5

Two-Level Voltage Source Inverter (VSI)



Source:
Alstom

VDM5000 Two-level VSI

Two Level Voltage Source Inverter

Lecture Topics


- Sinusoidal PWM
- Space vector modulation

Why Use PWM Techniques?

- To control inverter output frequency (fundamental)
- To control inverter output voltage (fundamental)
- To minimize harmonic distortion

Sinusoidal PWM

• Inverter Configuration

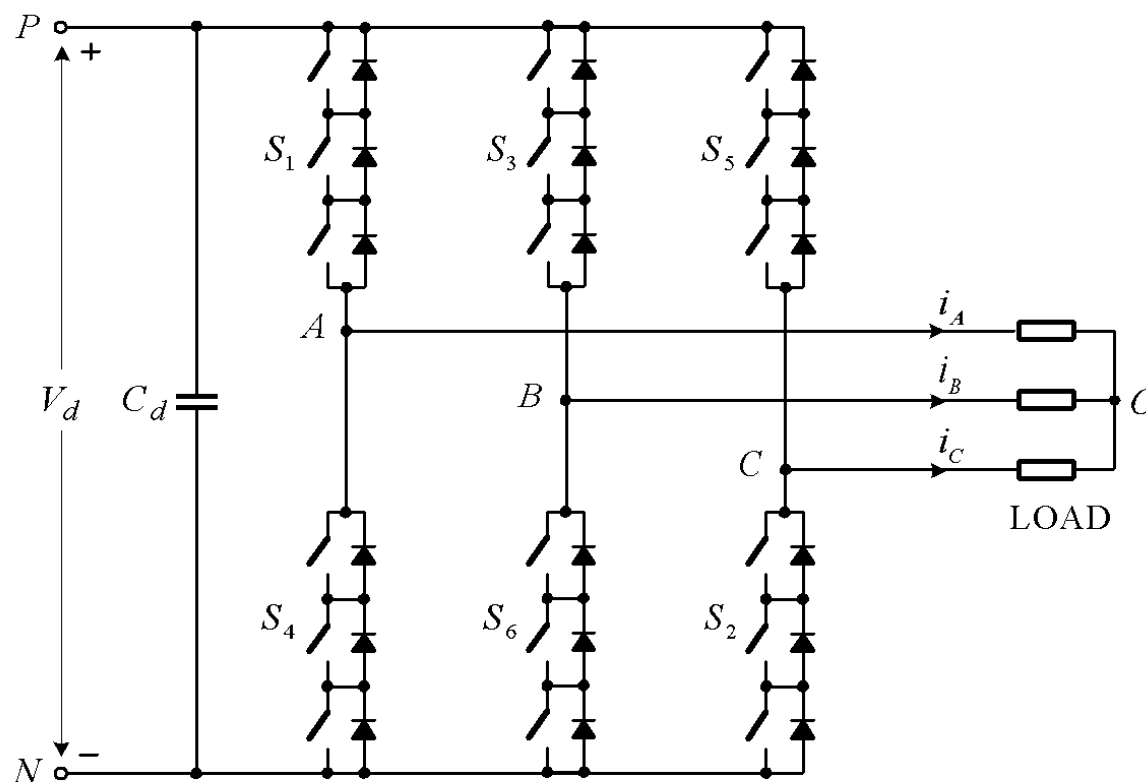


Assumption:

dc capacitor very large \rightarrow dc voltage ripple free

Sinusoidal PWM

• Modulating and Carrier Waves

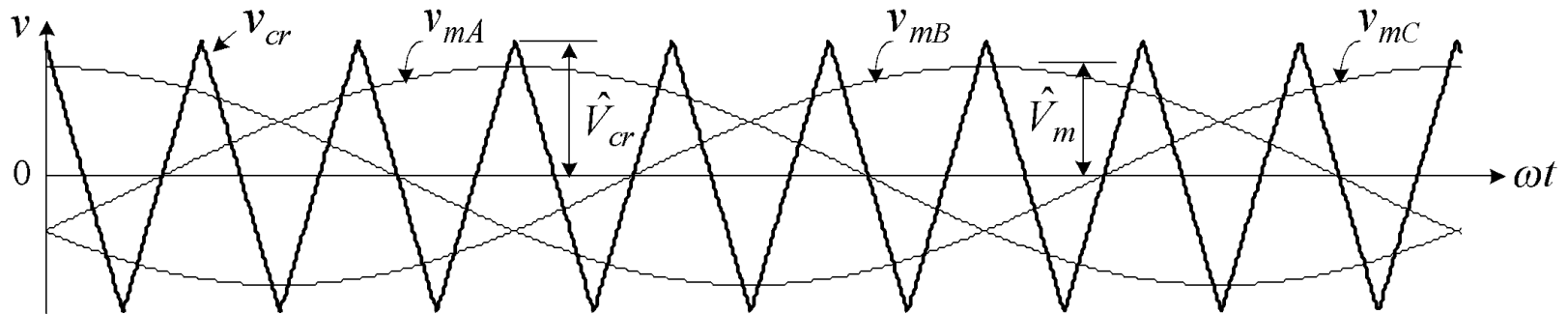

• V_{cr} – Carrier wave (triangle)

• Amplitude modulation index

$$m_a = \frac{\hat{V}_m}{\hat{V}_{cr}}$$


• V_m – Modulating wave (sine)

• Frequency modulation index

$$m_f = \frac{f_{cr}}{f_m}$$

Sinusoidal PWM

- Gate Signal Generation

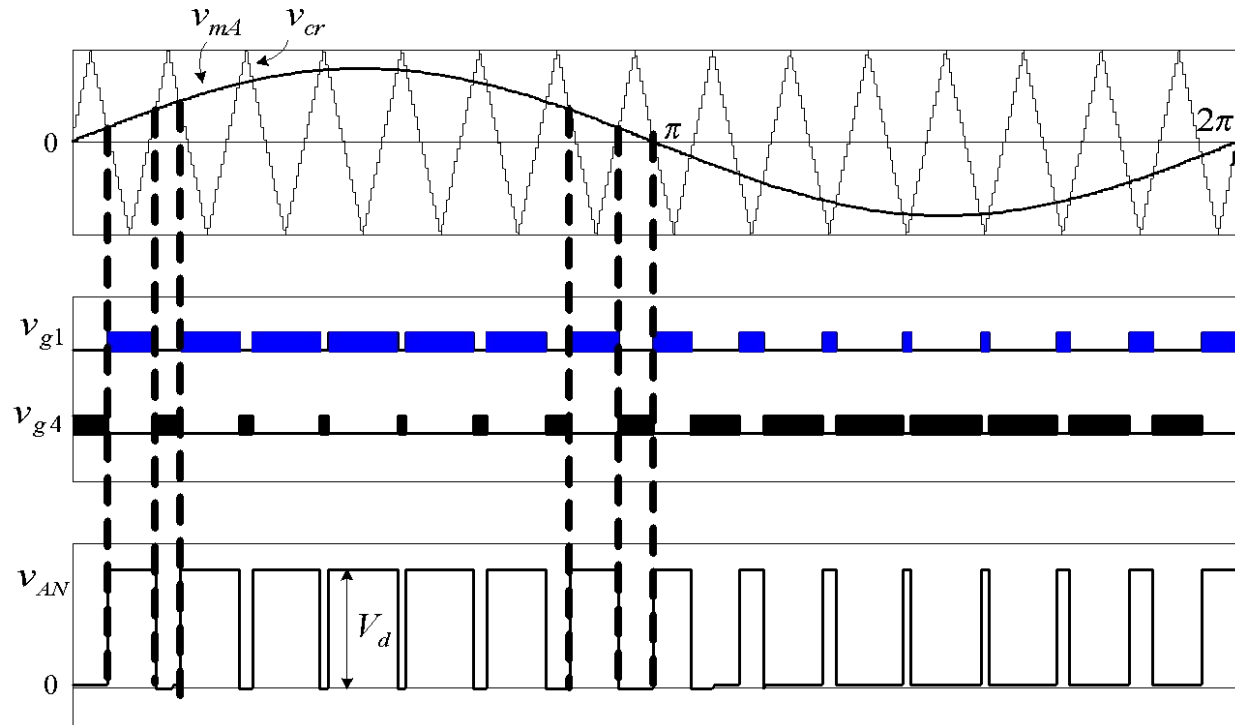


Phase A	$v_{mA} > v_{cr}$	$v_{g1} > 0$ ($v_{g4} < 0$)	S_1 on (S_4 off)	$v_{AN} = V_d$
	$v_{mA} < v_{cr}$	$v_{g4} > 0$ ($v_{g1} < 0$)	S_4 on (S_1 off)	$v_{AN} = 0$

V_{g1} and V_{g4} are complementary




Sinusoidal PWM

• Line-to-Line Voltage V_{AB}

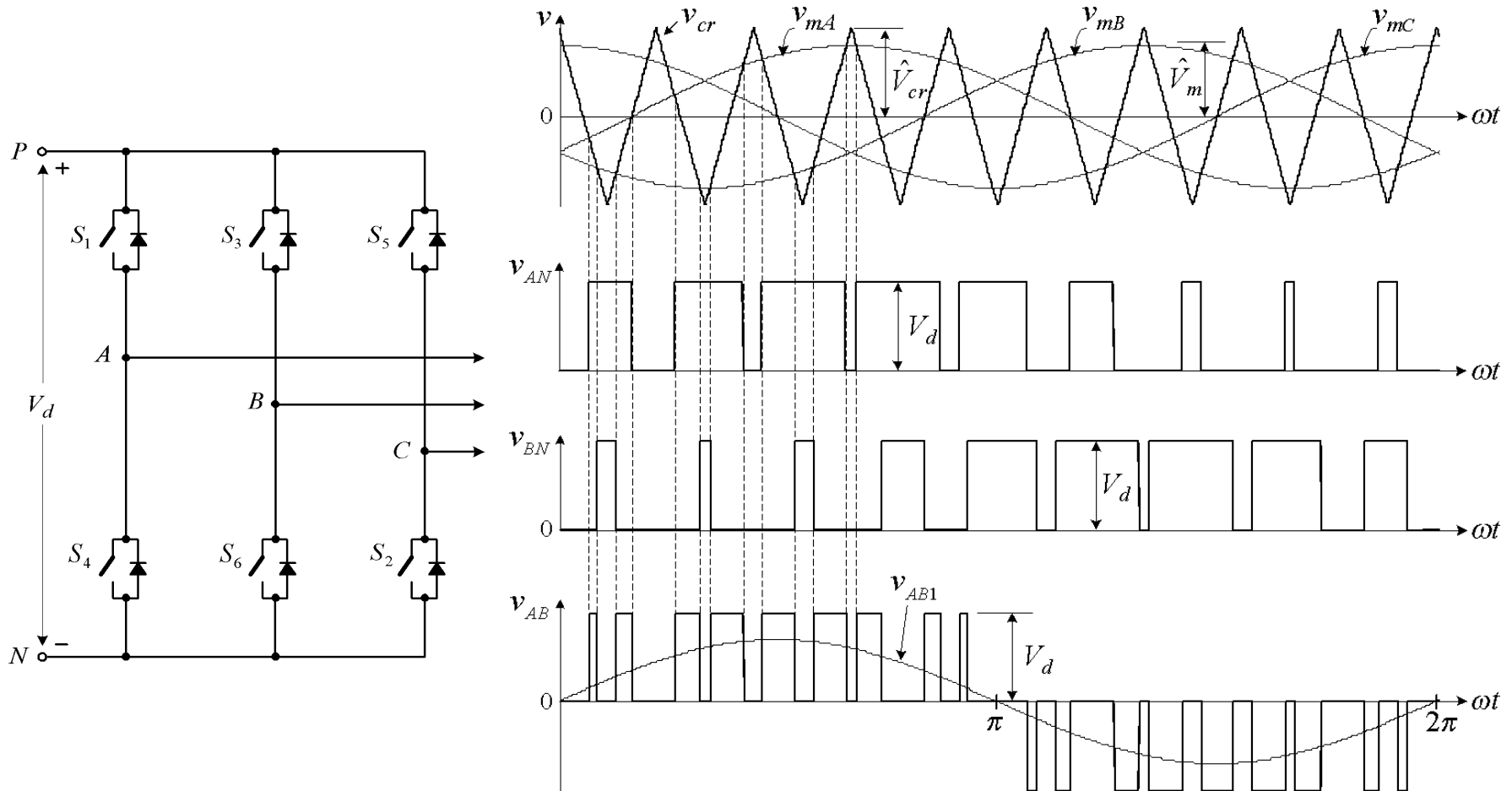

Sinusoidal PWM


• Waveforms and FFT

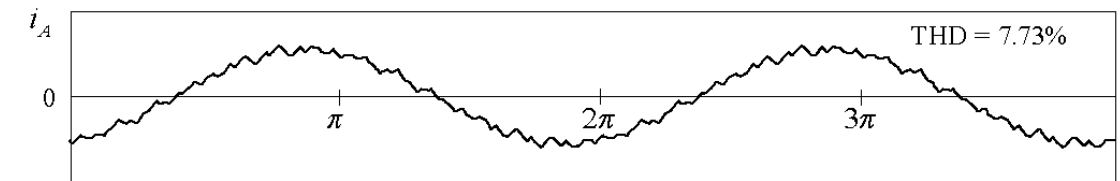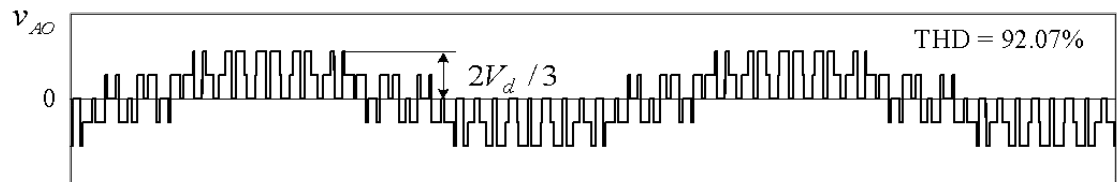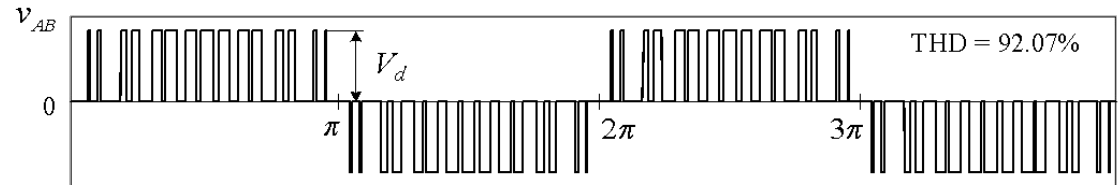

- $m_a = 0.8$, $m_f = 15$,
 $f_m = 60\text{Hz}$, $f_{cr} = 900\text{Hz}$

• Switching frequency


- $f_{sw} = f_{cr} = 900\text{Hz}$

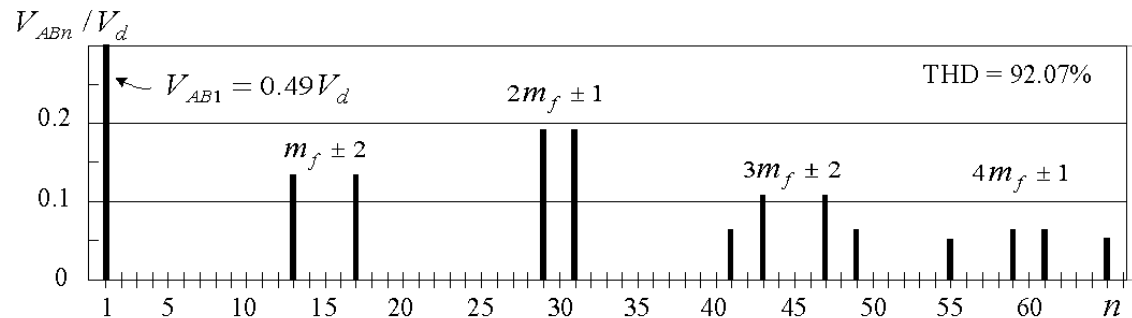

Sinusoidal PWM





• Harmonic Content

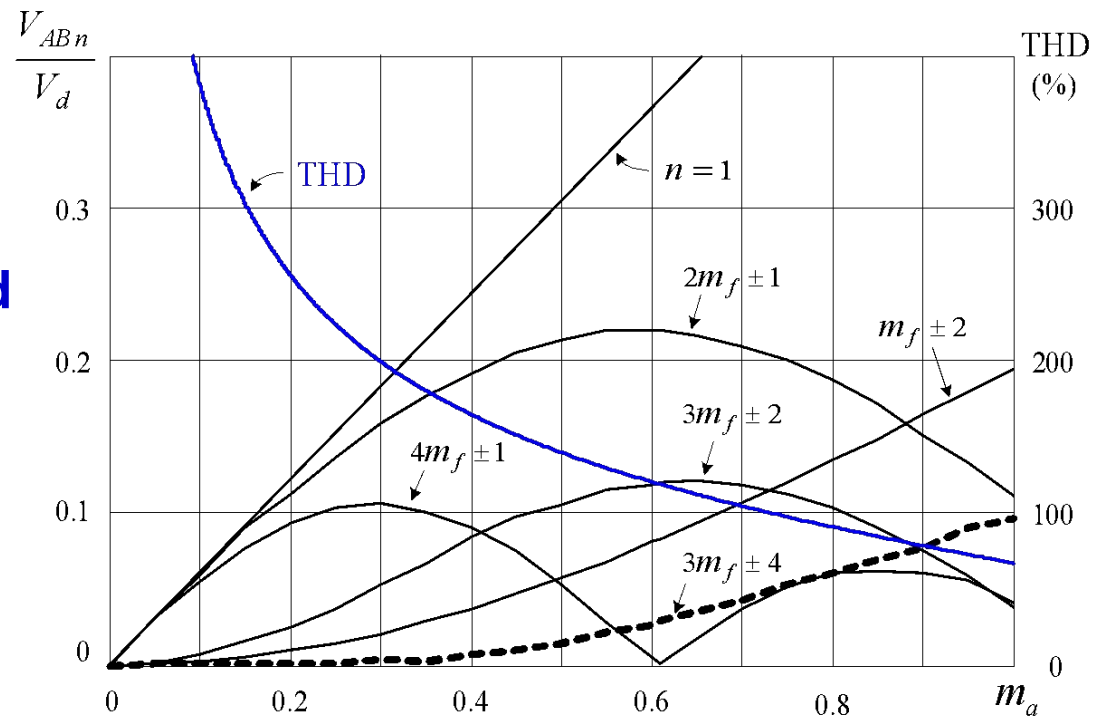- Low order harmonics $n < (m_f - 2)$ are eliminated
- V_{AB1} versus m_a is linear
- $V_{AB1,max} = 0.612V_d$



Sinusoidal PWM

- Over-Modulation

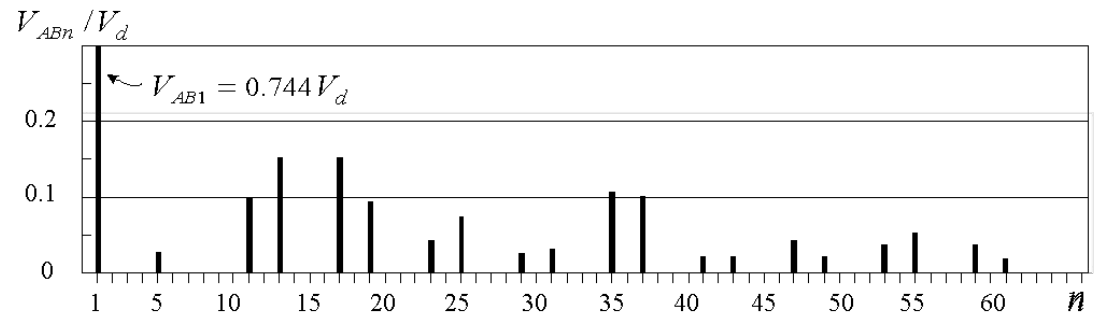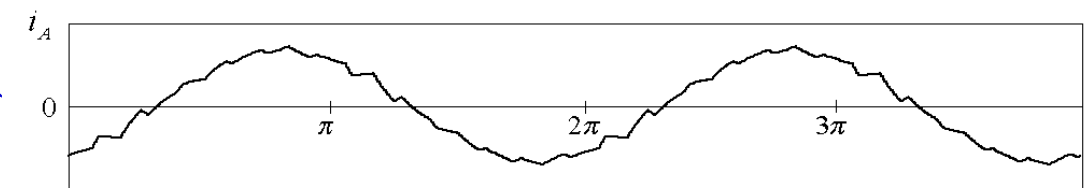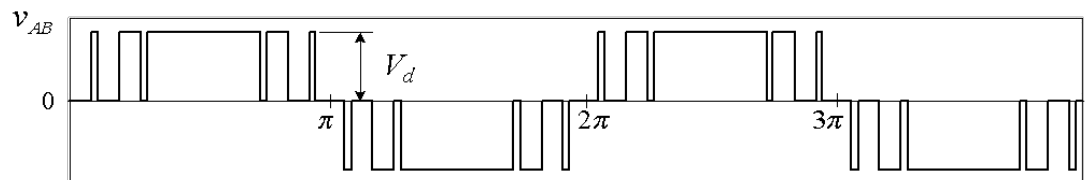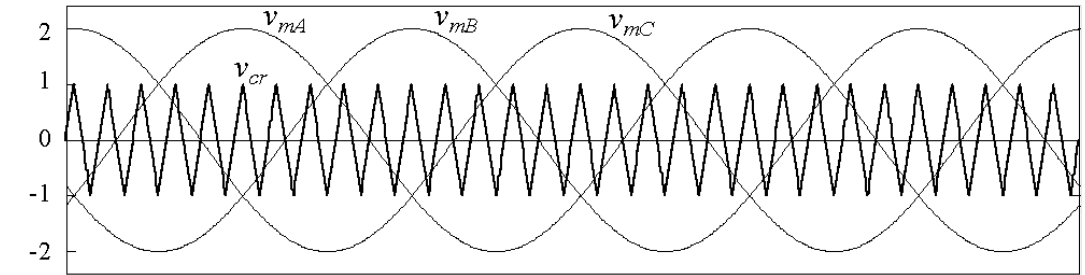


- Fundamental voltage \uparrow

- Low-order harmonics \uparrow

Sinusoidal PWM


• Third Harmonic Injection PWM

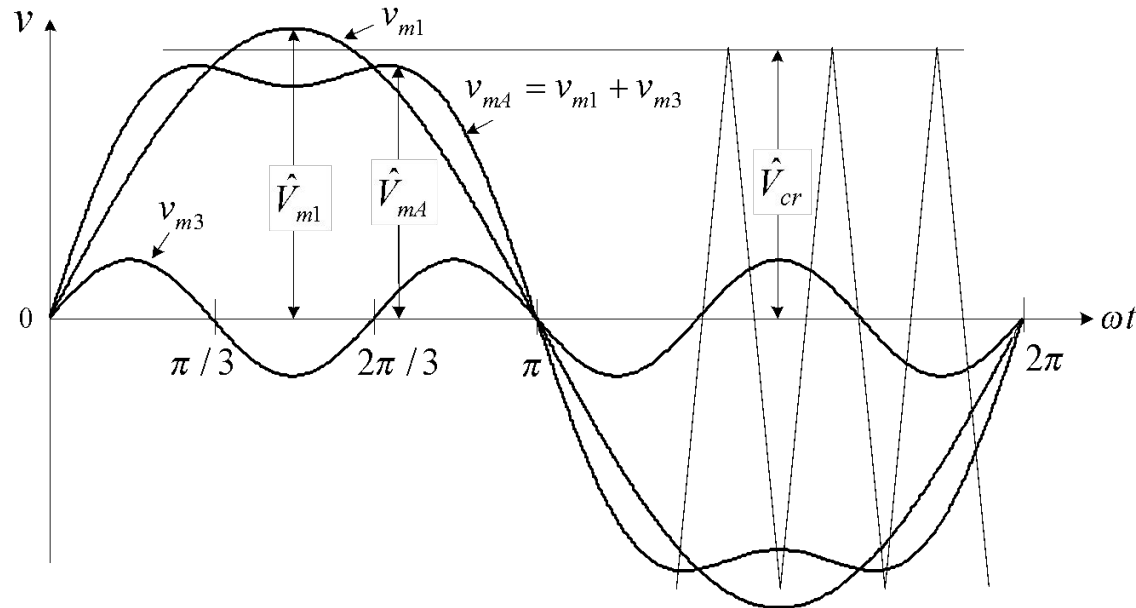

- $\hat{V}_{m1} > \hat{V}_{cr}$ **Fundamental voltage increased**
- $\hat{V}_{mA} \leq \hat{V}_{cr}$ **No low order harmonics produced**
- **3rd harmonic – zero sequence** (to appear in \mathbf{v}_{AN} and \mathbf{v}_{BN})
- **No triplen harmonics in \mathbf{v}_{AB}** ($\mathbf{v}_{AB} = \mathbf{v}_{AN} - \mathbf{v}_{BN}$)

Space Vector Modulation


• Switching States

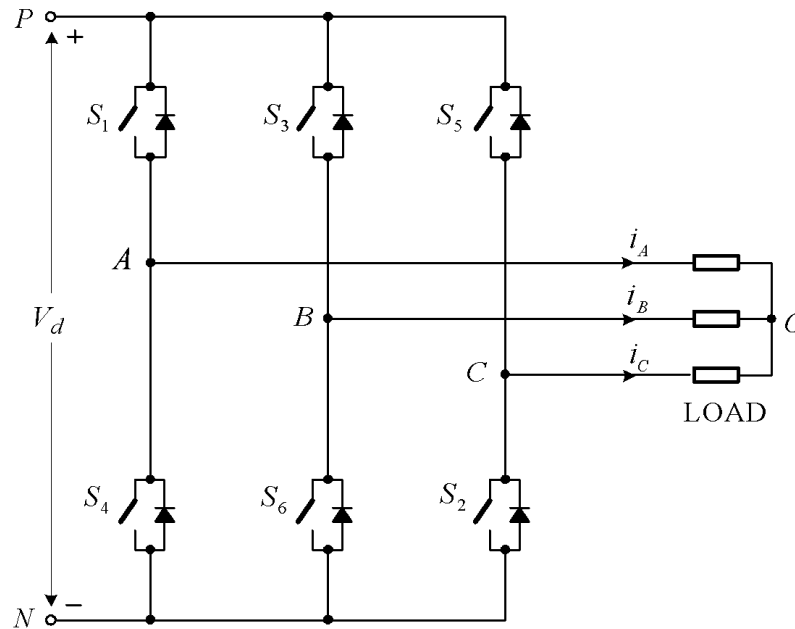

Switching State	Leg A			Leg B			Leg C		
	S_1	S_4	V_{AN}	S_3	S_6	V_{BN}	S_5	S_2	V_{CN}
P	On	Off	V_d	On	Off	V_d	On	Off	V_d
O	Off	On	0	Off	On	0	Off	On	0

Space Vector Modulation

- Switching States (Three-Phase)

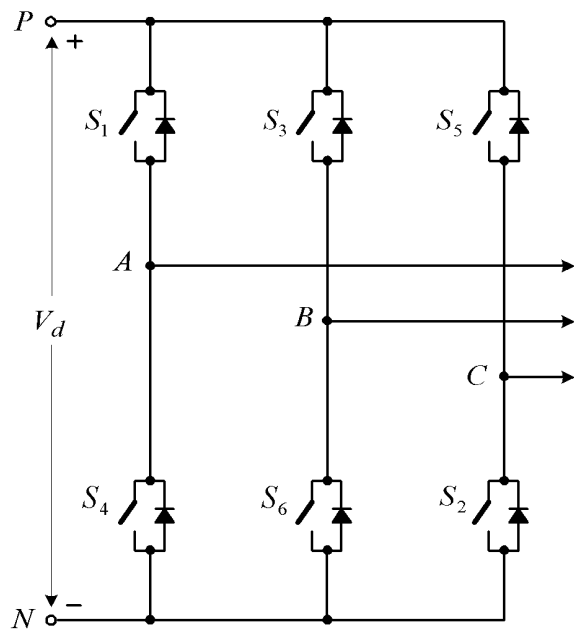

Switching State (Three Phases)	On-state Switch
[PPP]	S_1, S_3, S_5
[OOO]	S_4, S_6, S_2
[POO]	S_1, S_6, S_2
[PPO]	S_1, S_3, S_2
[OPO]	S_4, S_3, S_2
[OPP]	S_4, S_3, S_5
[OOP]	S_4, S_6, S_5
[POP]	S_1, S_6, S_5

- Eight switching states


Space Vector Modulation

• Space Vector Diagram

• **Active vectors:** \vec{V}_1 to \vec{V}_6
(stationary, not rotating)

• **Zero vector:** \vec{V}_0

• **Six sectors:** I to VI

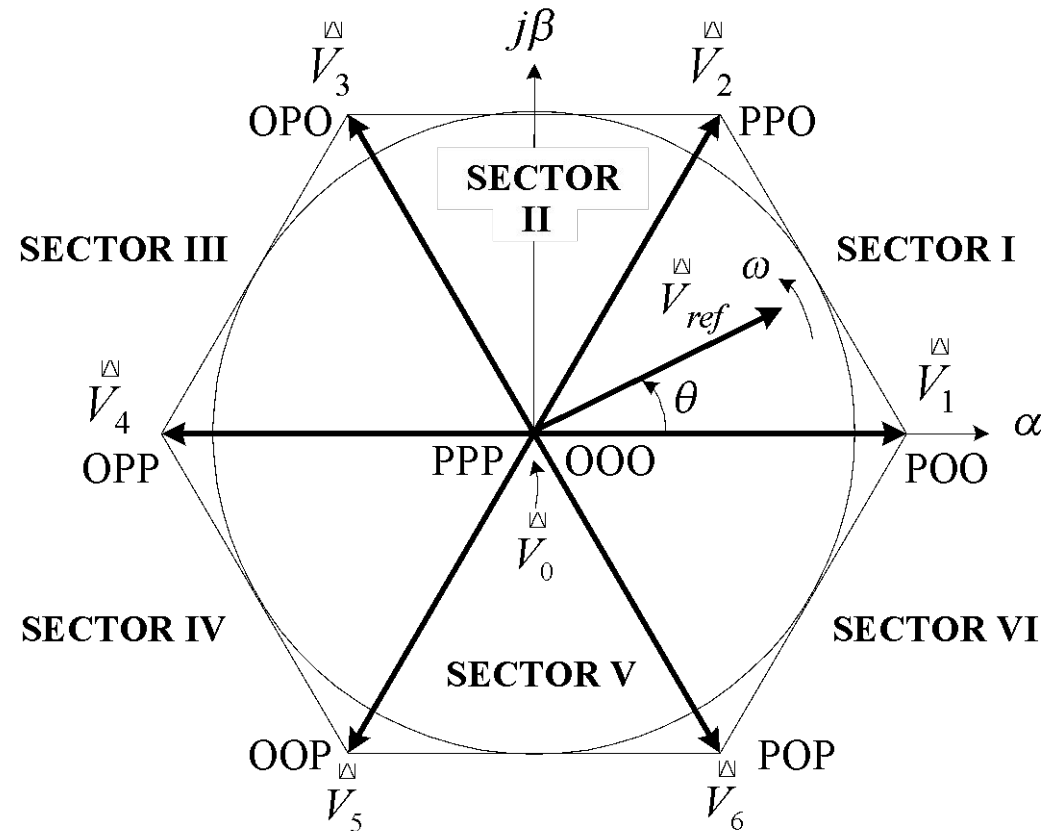

Space Vector Modulation

• Space Vectors

• Three-phase voltages

$$v_{AO}(t) + v_{BO}(t) + v_{CO}(t) = 0 \quad (1)$$

• Two-phase voltages

$$\begin{bmatrix} v_{\alpha}(t) \\ v_{\beta}(t) \end{bmatrix} = \frac{2}{3} \begin{bmatrix} \cos 0 & \cos \frac{2\pi}{3} & \cos \frac{4\pi}{3} \\ \sin 0 & \sin \frac{2\pi}{3} & \sin \frac{4\pi}{3} \end{bmatrix} \begin{bmatrix} v_{AO}(t) \\ v_{BO}(t) \\ v_{CO}(t) \end{bmatrix} \quad (2)$$

• Space vector representation

$$\vec{V}(t) = v_{\alpha}(t) + j v_{\beta}(t) \quad (3)$$

(2) \rightarrow (3)

$$\vec{V}(t) = \frac{2}{3} \left[v_{AO}(t) e^{j0} + v_{BO}(t) e^{j2\pi/3} + v_{CO}(t) e^{j4\pi/3} \right] \quad (4)$$

where $e^{jx} = \cos x + j \sin x$

Space Vector Modulation

• Space Vectors (Example)

Switching state [POO] \rightarrow S_1 , S_6 and S_2

ON

$$v_{AO}(t) = \frac{2}{3}V_d, \quad v_{BO}(t) = -\frac{1}{3}V_d \quad \text{and} \quad v_{CO}(t) = -\frac{1}{3}V_d \quad (5)$$


(5) \rightarrow (4)

$$\vec{V}_1 = \frac{2}{3}V_d e^{j0} \quad (6)$$

Similarly,


$$\vec{V}_k = \frac{2}{3}V_d e^{j(k-1)\frac{\pi}{3}} \quad (7)$$

$$k = 1, 2, \dots, 6.$$

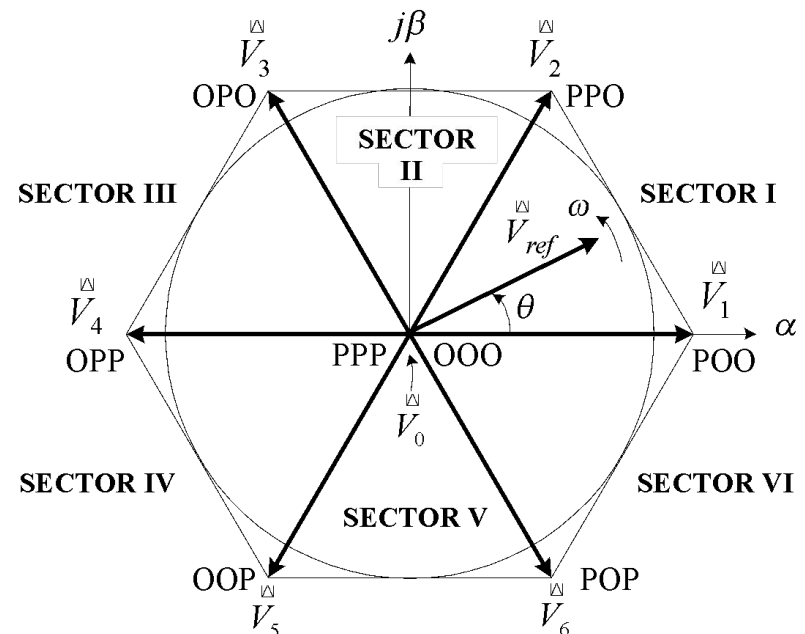

Space Vector Modulation

Active and Zero Vectors

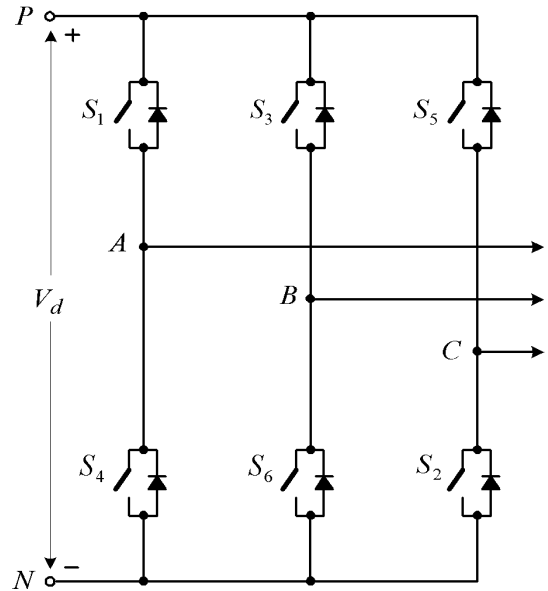

Space Vector		Switching State (Three Phases)	On-state Switch	Vector Definition
Zero Vector	\vec{V}_0	[PPP]	S_1, S_3, S_5	$\vec{V}_0 = 0$
		[OOO]	S_4, S_6, S_2	
Active Vector	\vec{V}_1	[POO]	S_1, S_6, S_2	$\vec{V}_1 = \frac{2}{3}V_d e^{j0}$
	\vec{V}_2	[PPO]	S_1, S_3, S_2	$\vec{V}_2 = \frac{2}{3}V_d e^{j\frac{\pi}{3}}$
	\vec{V}_3	[OPO]	S_4, S_3, S_2	$\vec{V}_3 = \frac{2}{3}V_d e^{j\frac{2\pi}{3}}$
	\vec{V}_4	[OPP]	S_4, S_3, S_5	$\vec{V}_4 = \frac{2}{3}V_d e^{j\frac{3\pi}{3}}$
	\vec{V}_5	[OOP]	S_4, S_6, S_5	$\vec{V}_5 = \frac{2}{3}V_d e^{j\frac{4\pi}{3}}$
	\vec{V}_6	[POP]	S_1, S_6, S_5	$\vec{V}_6 = \frac{2}{3}V_d e^{j\frac{5\pi}{3}}$

- Active Vector: 6
- Zero Vector: 1
- Redundant switching states: [PPP] and [OOO]

Space Vector Modulation

- Reference Vector \underline{V}_{ref}

- Definition


$$\underline{V}_{ref} = V_{ref} e^{j\theta}$$

- Rotating in space at ω

$$\omega = 2\pi f \quad (8)$$


- Angular displacement
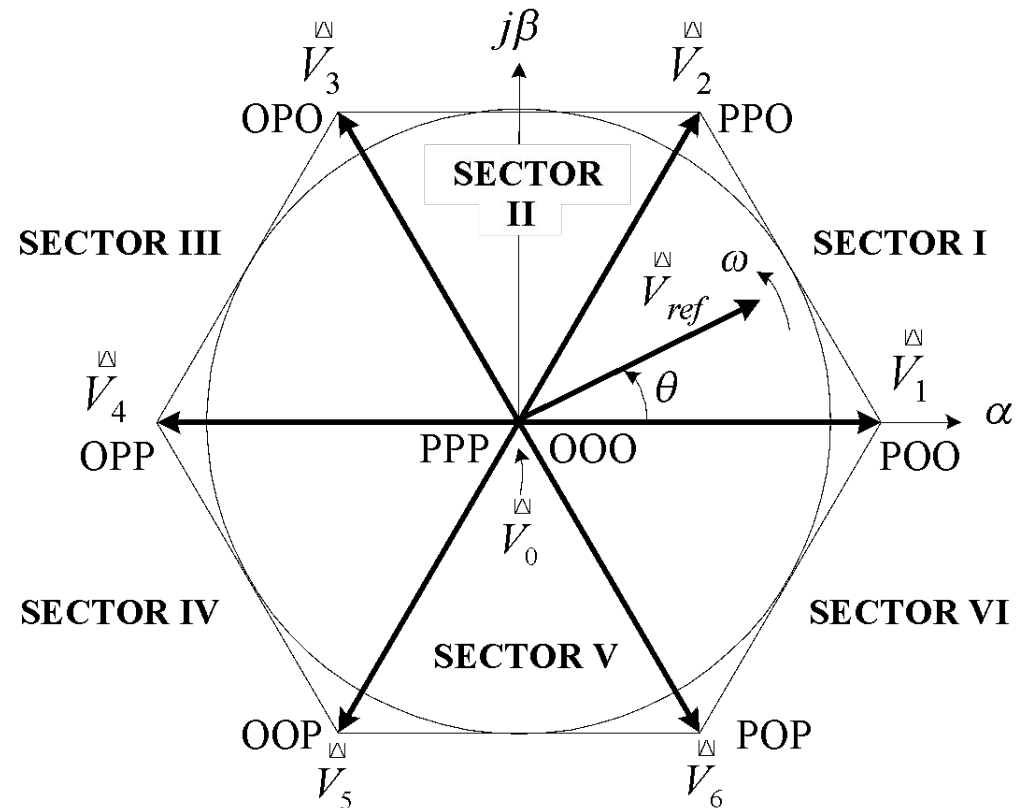
$$\theta(t) = \int_0^t \omega dt \quad (9)$$



Space Vector Modulation

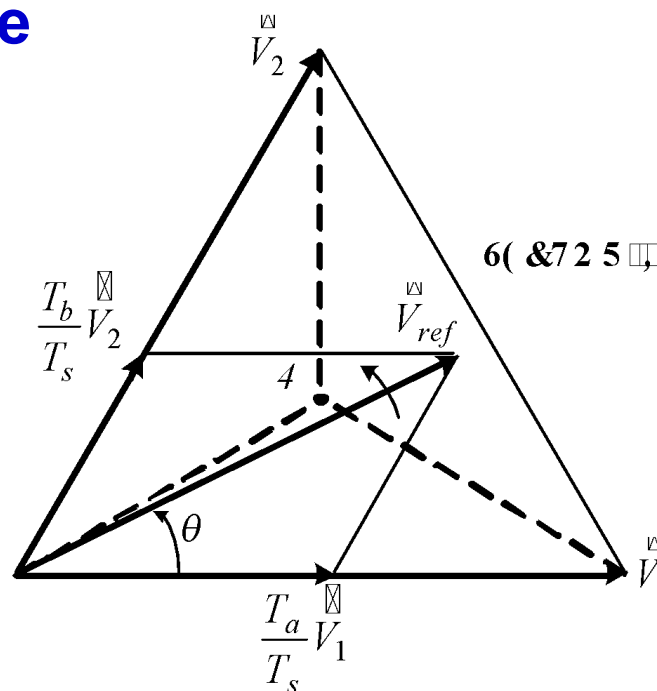- Relationship Between V_{ref} and V_{AB}
- V_{ref} is approximated by two active and a zero vectors
- V_{ref} rotates one revolution, V_{AB} completes one cycle
- Length of V_{ref} corresponds to magnitude of V_{AB}



Space Vector Modulation

• Dwell Time Calculation

• Volt-Second Balancing

$$\begin{cases} \vec{V}_{ref} T_s = \vec{V}_1 T_a + \vec{V}_2 T_b + \vec{V}_0 T_0 \\ T_s = T_a + T_b + T_0 \end{cases} \quad (10)$$

• T_a , T_b and T_0 – dwell times for \vec{V}_1 , \vec{V}_2 and \vec{V}_0


• T_s – sampling period

• Space vectors

$$\vec{V}_{ref} = V_{ref} e^{j\theta}, \quad \vec{V}_1 = \frac{2}{3} V_d, \quad \vec{V}_2 = \frac{2}{3} V_d e^{j\frac{\pi}{3}} \quad \text{and} \quad \vec{V}_0 = 0 \quad (11)$$

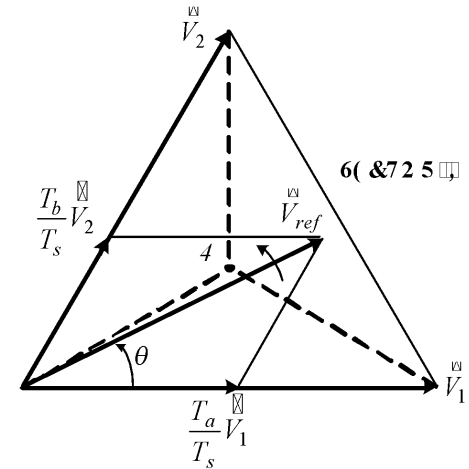(11) \rightarrow (10)

$$\begin{cases} \text{Re: } V_{ref} (\cos \theta) T_s = \frac{2}{3} V_d T_a + \frac{1}{3} V_d T_b \\ \text{Im: } V_{ref} (\sin \theta) T_s = \frac{1}{\sqrt{3}} V_d T_b \end{cases} \quad (12)$$



Space Vector Modulation


- Dwell Times

Solve (12)

$$\left\{ \begin{array}{l} T_a = \frac{\sqrt{3} T_s V_{ref}}{V_d} \sin\left(\frac{\pi}{3} - \theta\right) \\ T_b = \frac{\sqrt{3} T_s V_{ref}}{V_d} \sin\theta \\ T_0 = T_s - T_a - T_b \end{array} \right. \quad 0 \leq \theta < \pi/3 \quad (13)$$

Space Vector Modulation

• V_{ref} Location versus Dwell Times

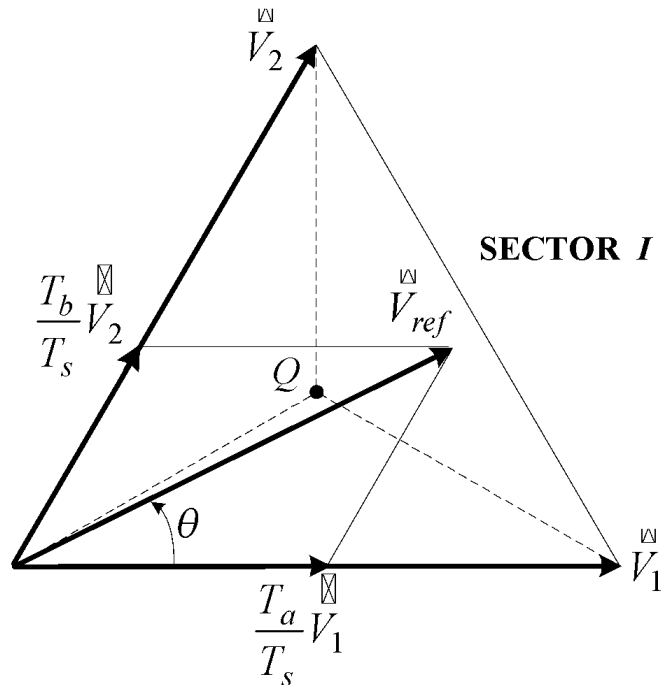

V_{ref} Location	$\theta = 0$	$0 < \theta < \frac{\pi}{6}$	$\theta = \frac{\pi}{6}$	$\frac{\pi}{6} < \theta < \frac{\pi}{3}$	$\theta = \frac{\pi}{3}$
Dwell Times	$T_a > 0$ $T_b = 0$	$T_a > T_b$	$T_a = T_b$	$T_a < T_b$	$T_a = 0$ $T_b > 0$

Space Vector Modulation

- Modulation Index

$$\begin{cases} T_a = T_s m_a \sin\left(\frac{\pi}{3} - \theta\right) \\ T_b = T_s m_a \sin\theta \\ T_c = T_s - T_b - T_a \end{cases} \quad (15)$$

$$m_a = \frac{\sqrt{3} V_{ref}}{V_d} \quad (16)$$

Space Vector Modulation

• Modulation Range


• $V_{ref,max}$

$$V_{ref,max} = \frac{2}{3} V_d \times \frac{\sqrt{3}}{2} = \frac{V_d}{\sqrt{3}} \quad (17)$$

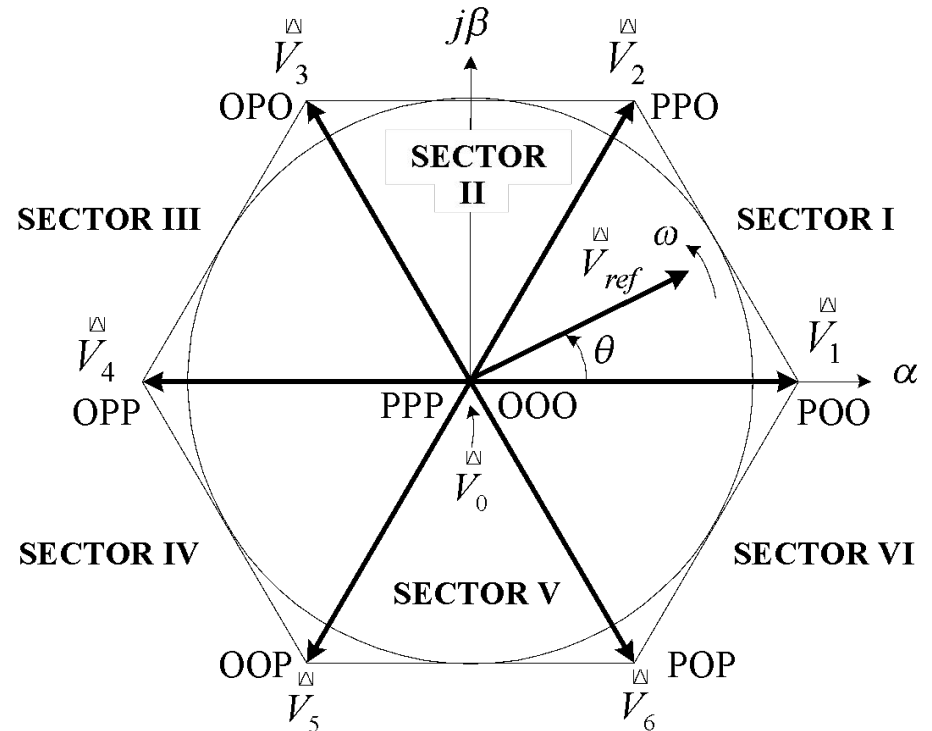(17) \rightarrow (16)

• $m_{a,max} = 1 \rightarrow$

• Modulation range: $0 \leq m_a \leq 1$ (18)



Space Vector Modulation

- **Switching Sequence Design**
 - **Basic Requirement:**

Minimize the number of switchings per sampling period T_s
 - **Implementation:**


Transition from one switching state to the next involves only two switches in the same inverter leg.

Space Vector Modulation

• Seven-segment Switching Sequence

- Selected vectors:
 V_0 , V_1 and V_2


- Dwell times:
 $T_s = T_0 + T_a + T_b$

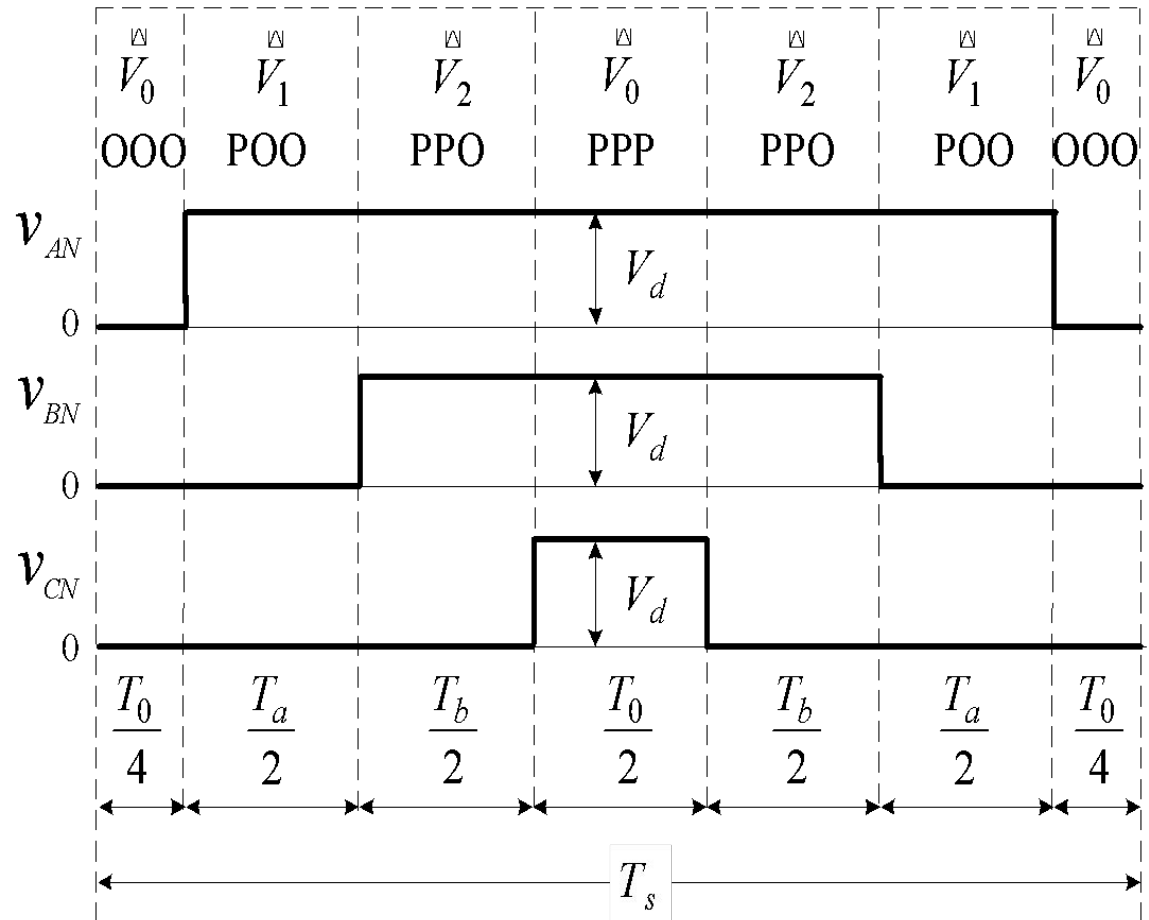

- Total number of switchings: 6

Space Vector Modulation

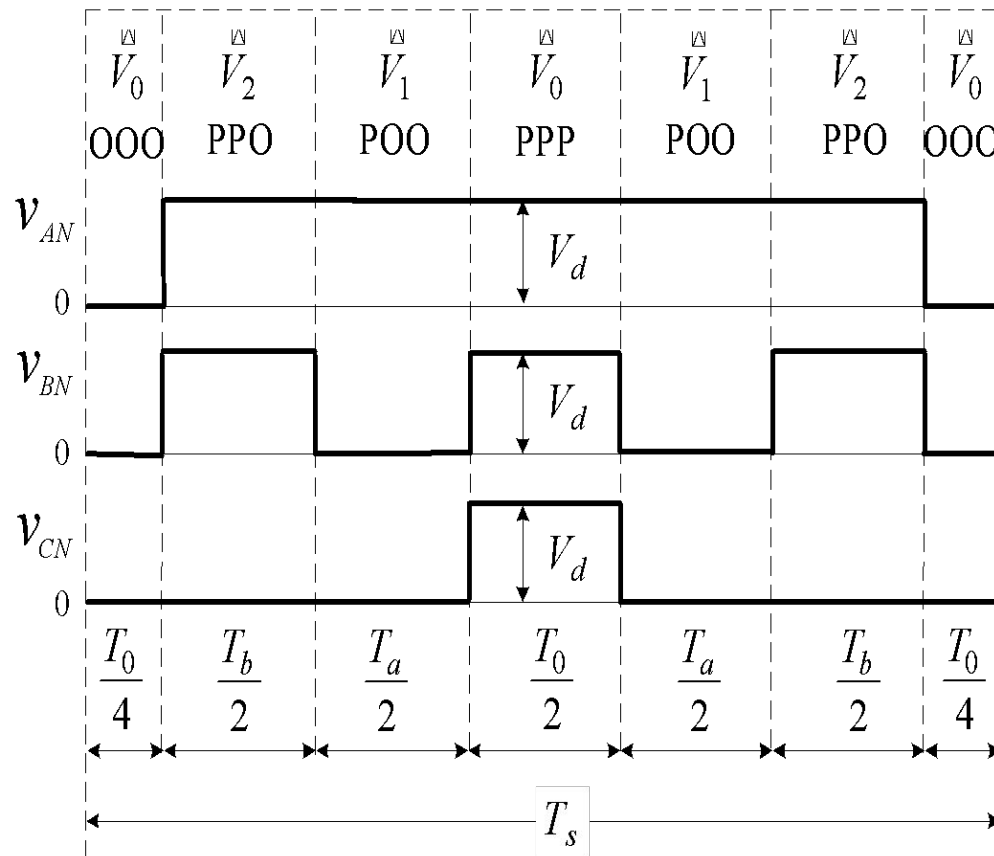- Undesirable Switching Sequence
 - Vectors V_1 and V_2 swapped



- Total number of switchings: 10

Space Vector Modulation


• Switching Sequence Summary (7-segments)

Sector	Switching Sequence						
I	V_0	V_1	V_2	V_0	V_2	V_1	V_0
	OOO	POO	PPO	PPP	PPO	POO	OOO
II	V_0	V_3	V_2	V_0	V_2	V_3	V_0
	OOO	OPO	PPO	PPP	PPO	OPO	OOO
III	V_0	V_3	V_4	V_0	V_4	V_3	V_0
	OOO	OPO	OPP	PPP	OPP	OPO	OOO
IV	V_0	V_5	V_4	V_0	V_4	V_5	V_0
	OOO	OOP	OPP	PPP	OPP	OOP	OOO
V	V_0	V_5	V_6	V_0	V_6	V_5	V_0
	OOO	OOP	POP	PPP	POP	OOP	OOO
VI	V_0	V_1	V_6	V_0	V_6	V_1	V_0
	OOO	POO	POP	PPP	POP	POO	OOO

Note: The switching sequences for the odd and even sectors are different.

Space Vector Modulation





• Simulated Waveforms

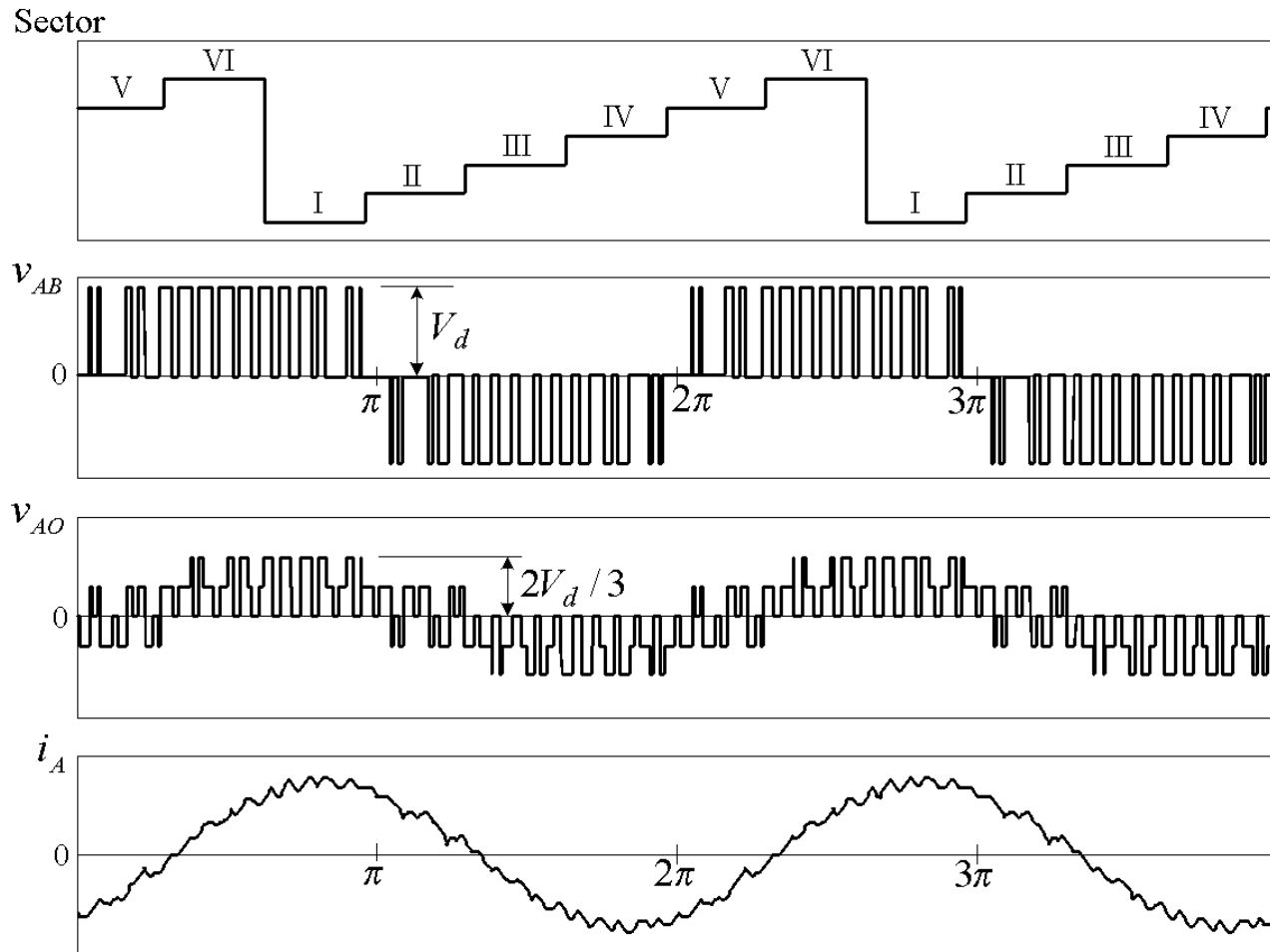

$$f_1 = 60\text{Hz}, f_{sw} = 900\text{Hz}, m_a = 0.696, T_s = 1.1\text{ms}$$


Space Vector Modulation

• Waveforms and FFT

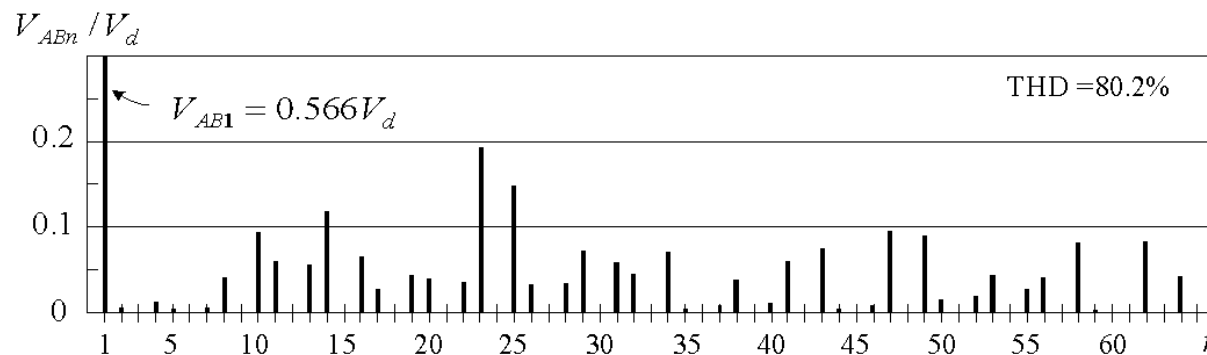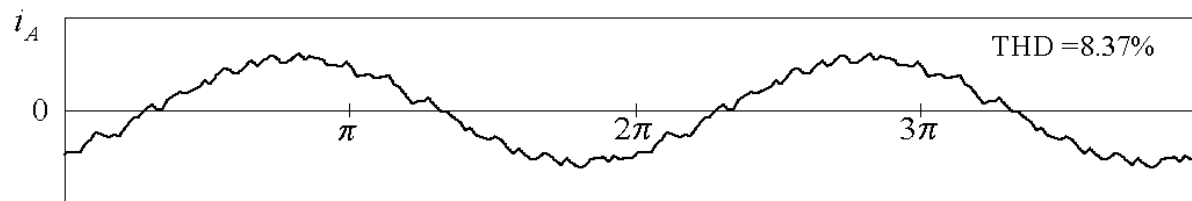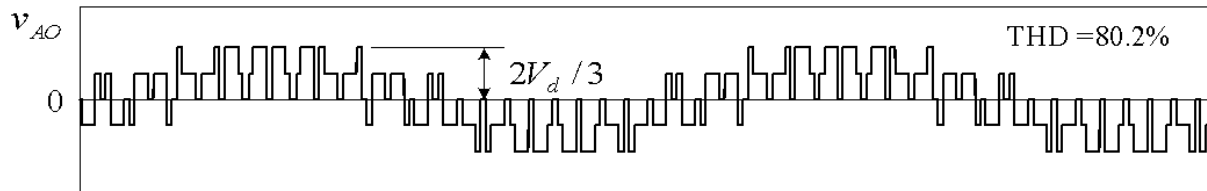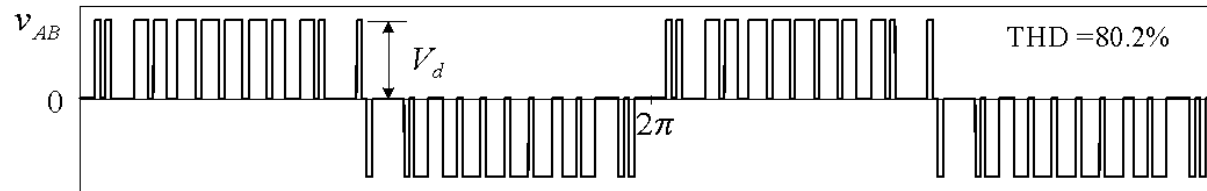


Space Vector Modulation

- Waveforms and FFT (Measured)

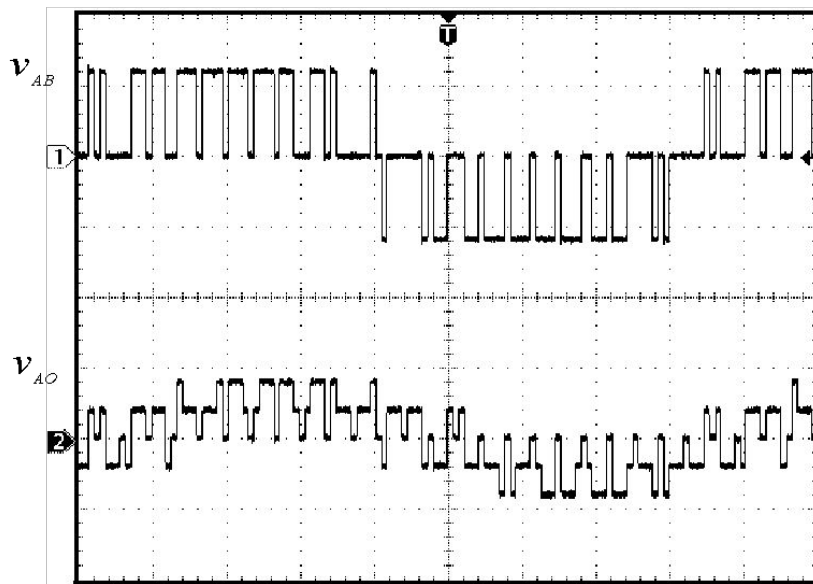


(a) Waveforms 2ms/div

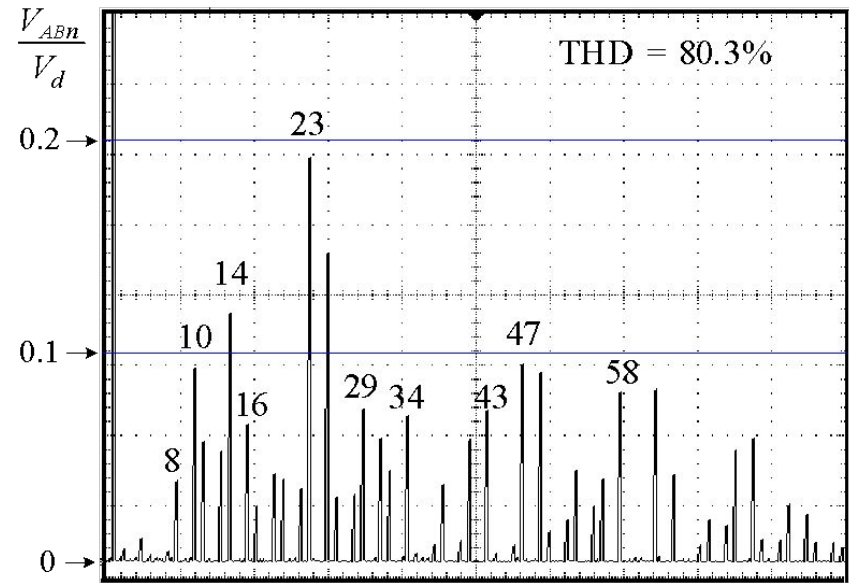


(b) Spectrum (500Hz/div)

Space Vector Modulation

• Waveforms and FFT (Measured)

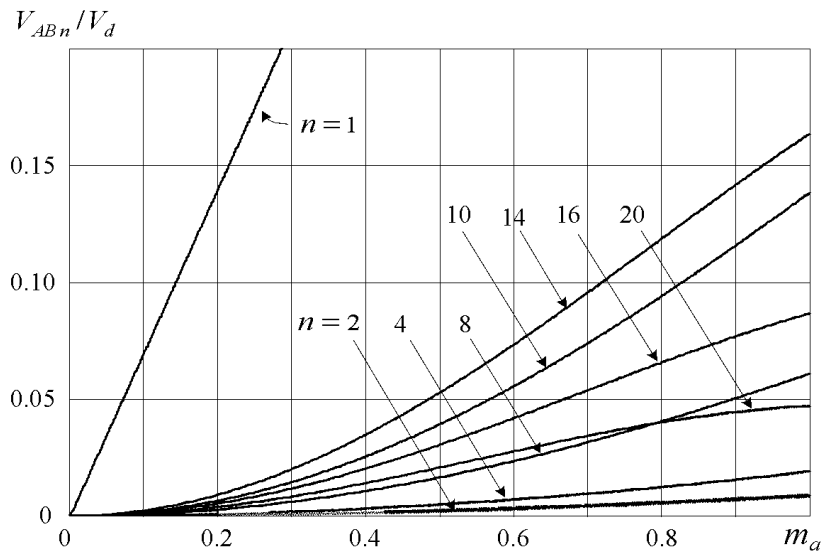

(a) Even order harmonics

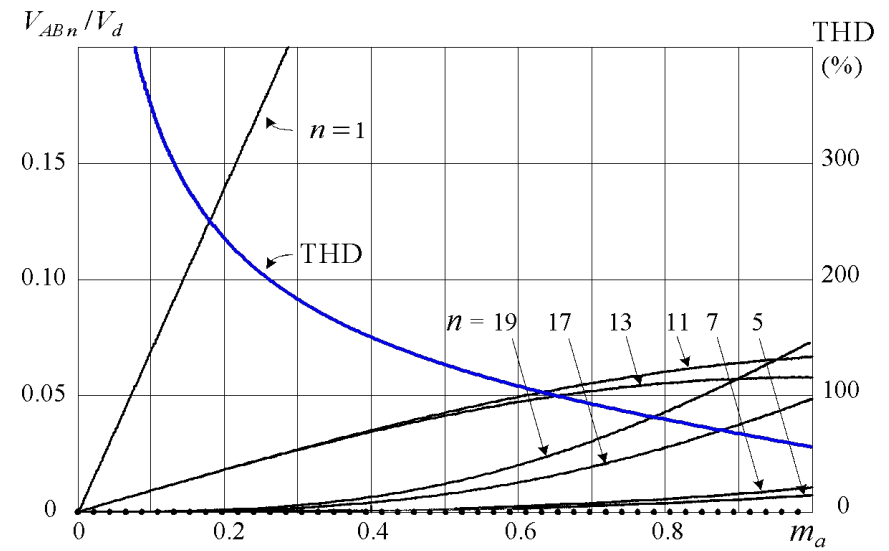


(b) Odd order harmonics


$$(f_1 = 60\text{Hz} \quad \text{and} \quad T_s = 1/720 \text{ sec})$$

Space Vector Modulation

• Even-Order Harmonic Elimination

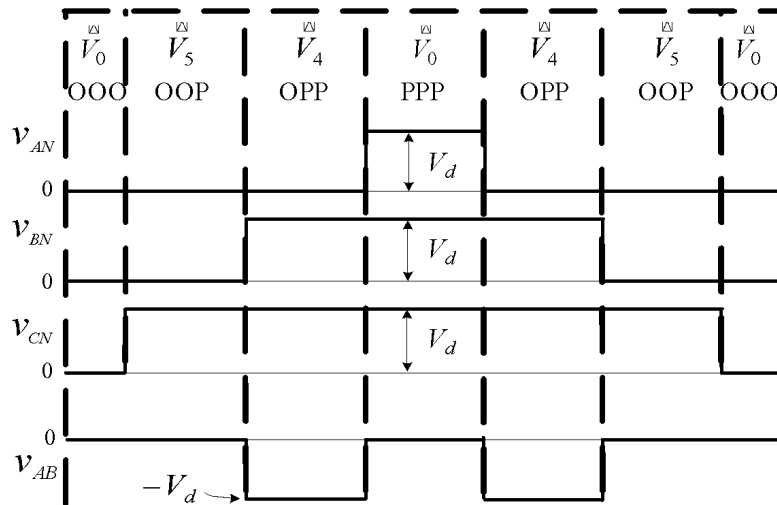

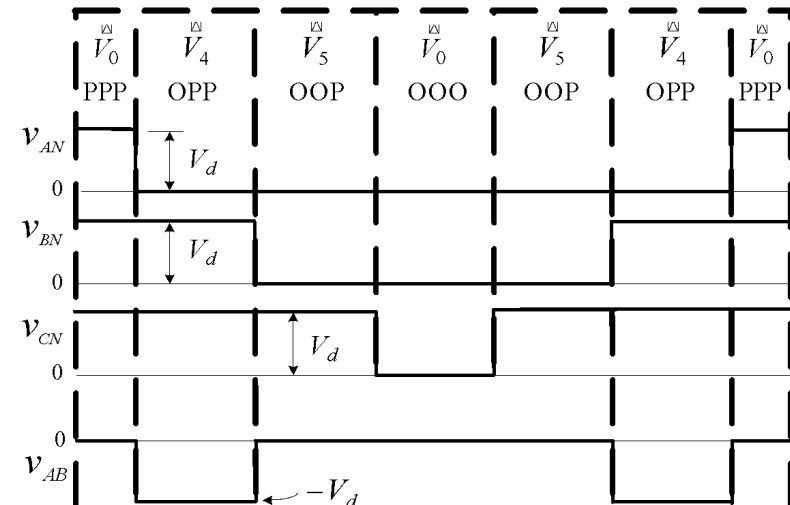
Type-A sequence
(starts and ends with [OOO])



Type-B sequence
(starts and ends with [PPP])

Space Vector Modulation


• Even-Order Harmonic Elimination

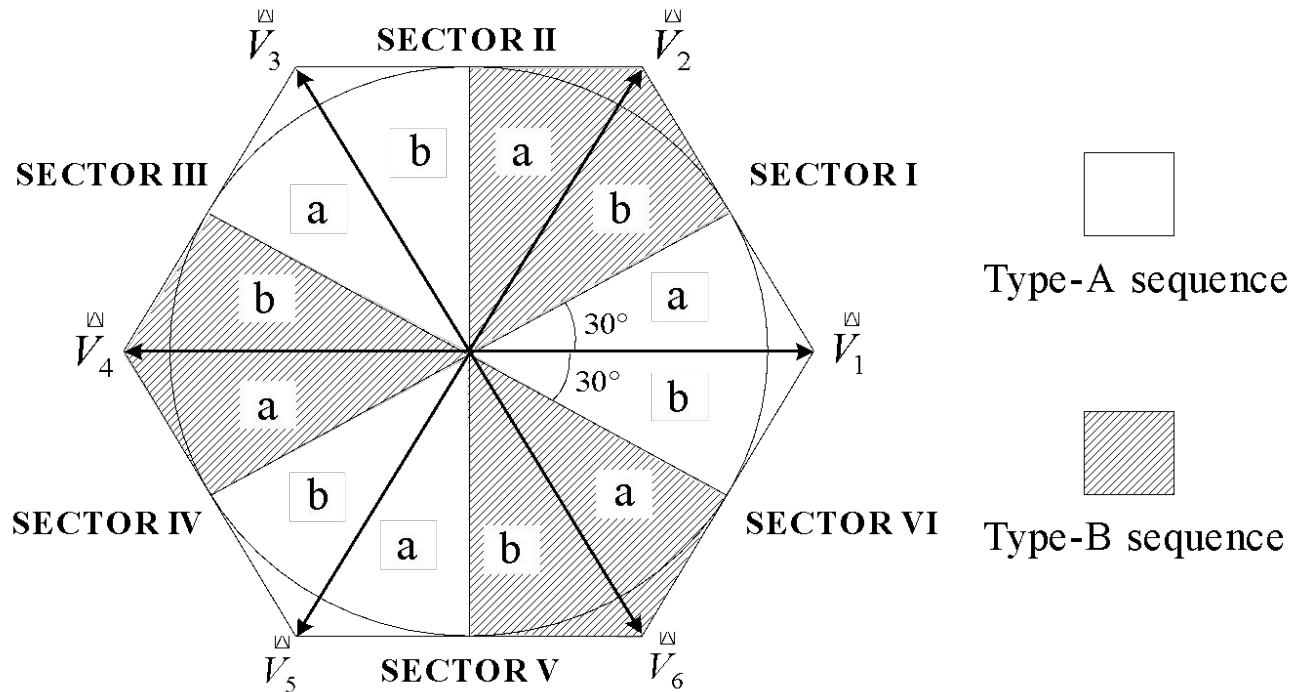


Space vector Diagram

Space Vector Modulation

- Even-Order Harmonic Elimination

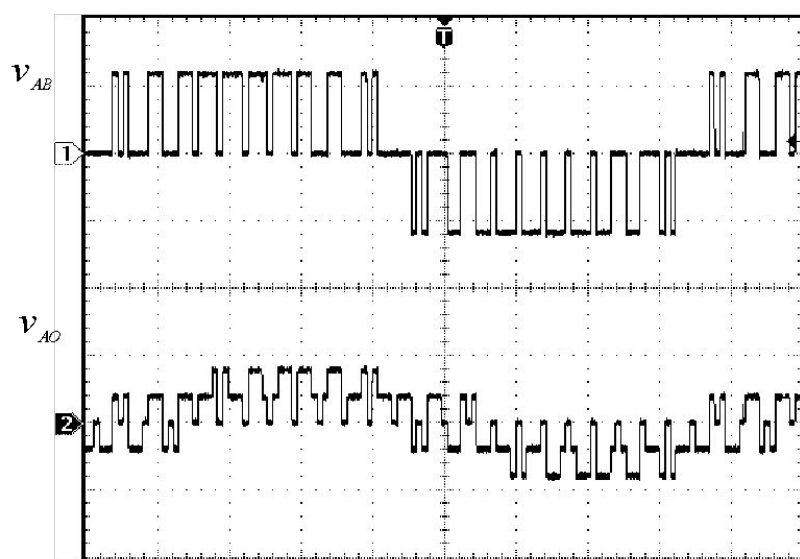

(a) Waveforms 2ms/div

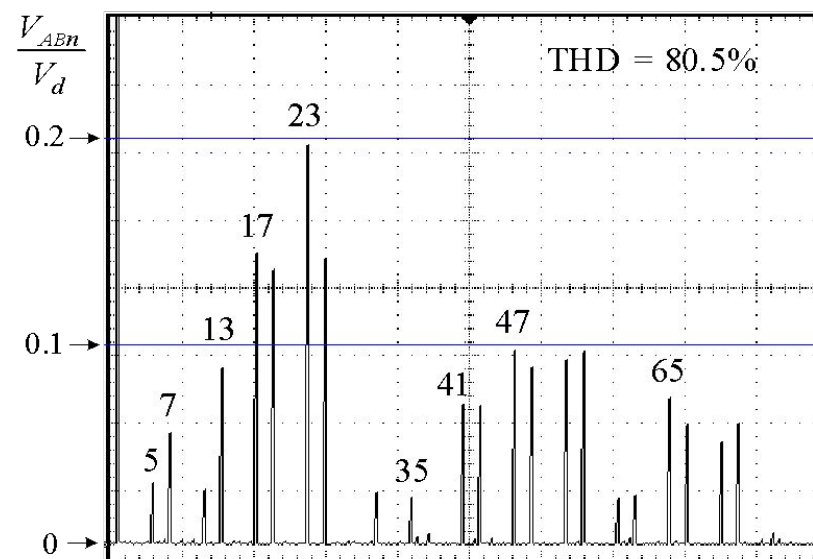


(b) Spectrum (500Hz/div)

- Measured waveforms and FFT

Space Vector Modulation


• Even-Order Harmonic Elimination

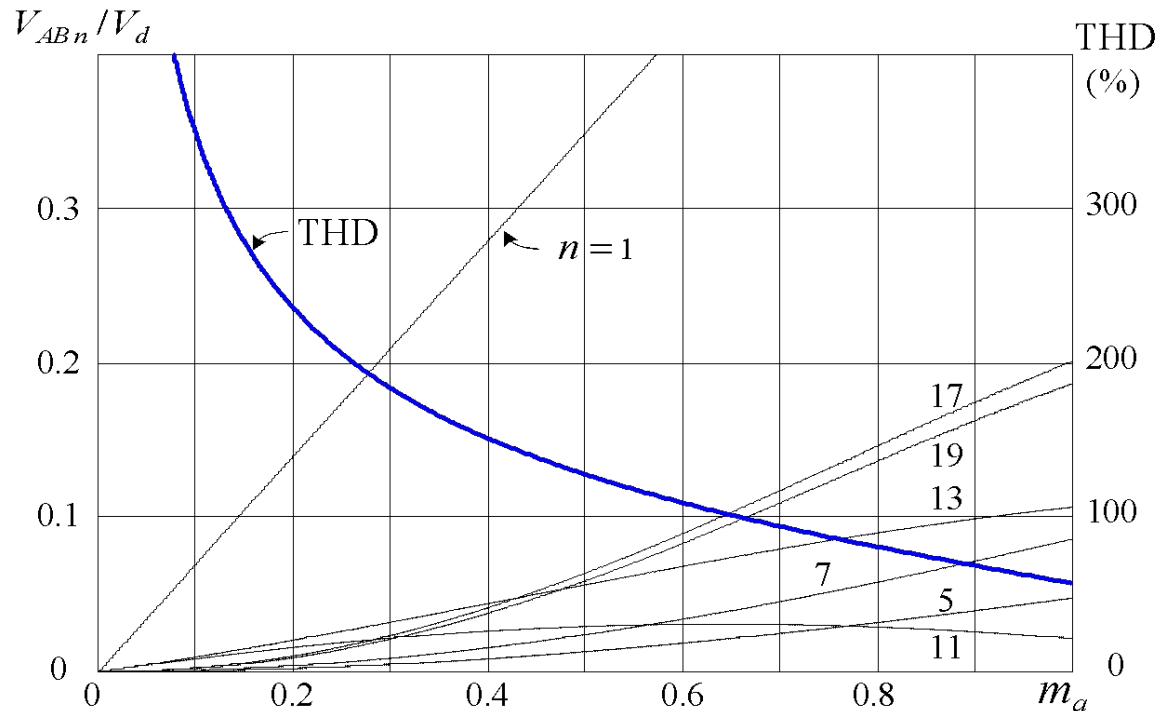

($f_1 = 60\text{Hz}$ and $T_s = 1/720 \text{ sec}$)

Space Vector Modulation

• Five-segment SVM

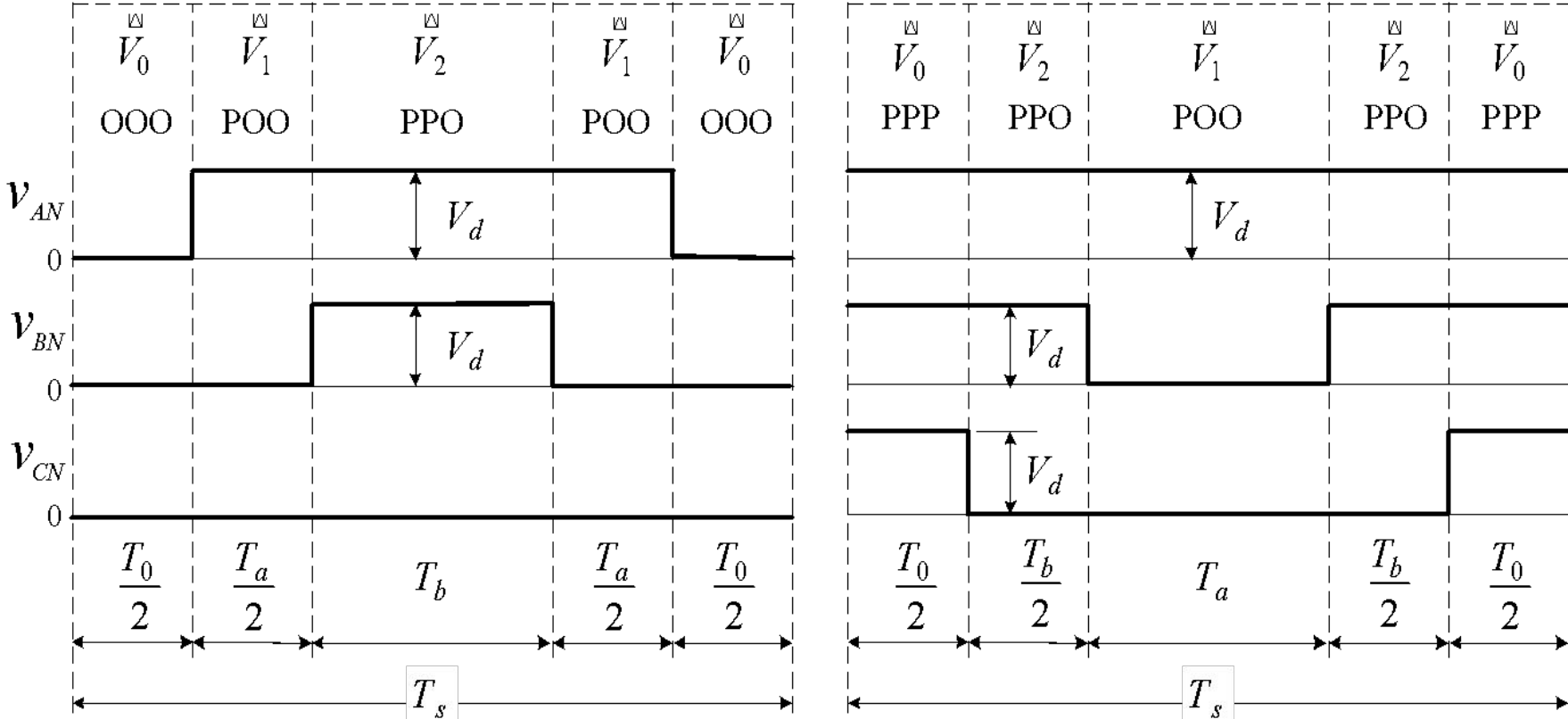

(a) Sequence A

(b) Sequence B


Space Vector Modulation

• Switching Sequence (5-segment)

Sector	Switching Sequence (A)					
<i>I</i>	V_0	V_1	V_2	V_1	V_0	$v_{CN} = 0$
	OOO	POO	PPO	POO	OOO	
<i>II</i>	V_0	V_3	V_2	V_3	V_0	$v_{CN} = 0$
	OOO	OPO	PPO	OPO	OOO	
<i>III</i>	V_0	V_3	V_4	V_3	V_0	$v_{AN} = 0$
	OOO	OPO	OPP	OPO	OOO	
<i>IV</i>	V_0	V_5	V_4	V_5	V_0	$v_{AN} = 0$
	OOO	OOP	OPP	OOP	OOO	
<i>V</i>	V_0	V_5	V_6	V_5	V_0	$v_{BN} = 0$
	OOO	OOP	POP	OOP	OOO	
<i>VI</i>	V_0	V_1	V_6	V_1	V_0	$v_{BN} = 0$
	OOO	POO	POP	POO	OOO	

Space Vector Modulation

• Simulated Waveforms (5-segment)

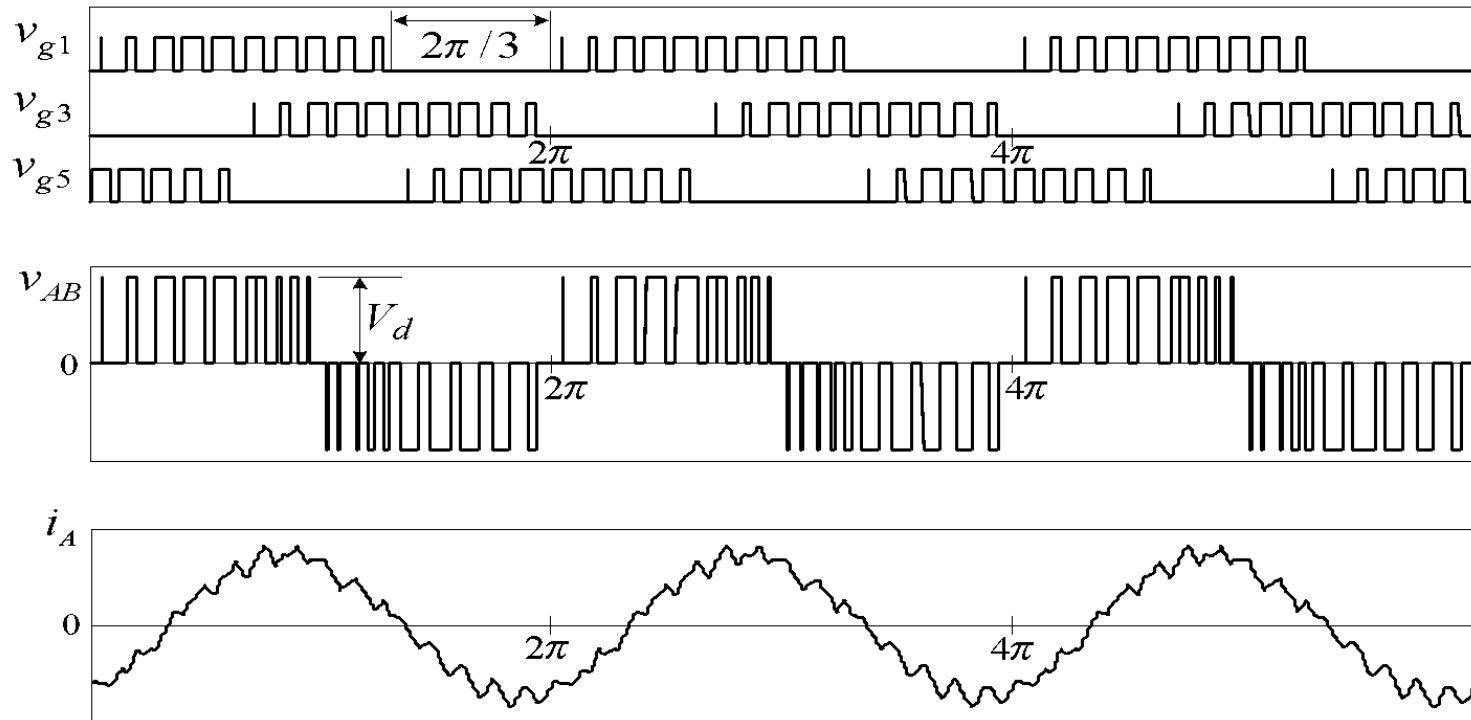

- $f_1 = 60\text{Hz}$, $f_{sw} = 600\text{Hz}$, $m_a = 0.696$, $T_s = 1.1\text{ms}$

- No switching for a 120° period per cycle.
- Low switching frequency but high harmonic distortion



Thanks