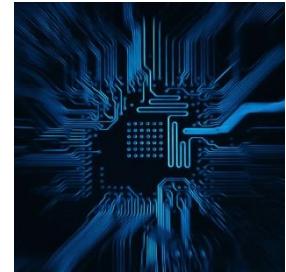


Практика

Описание комбинационных устройств на VHDL

Пример 1. Проверка на четность




```
library ieee;
use ieee.std_logic_1164.all;

entity parity_check is
    port(
        a: in std_logic_vector(7 downto 0);
        x: out std_logic
    );
end parity_check;

architecture cond_arch of parity_check is
begin
    x <=      '1' when (a(0) = '0') else
        '0';
end cond_arch;
```

input s	output x
00	a
01	b
10	c
11	d


Пример 2. Проверка на четность (if)

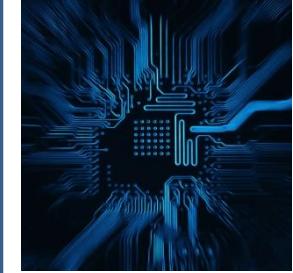

```
architecture cond_arch of parity_check is
begin
process(a)
begin
If (a(0) = '0') then
x <= '1';
else
x <= '0';
end if;
end process;
end cond_arch;
```

input	output
s	x
00	a
01	b
10	c
11	d


Пример 3. Делимость на 4

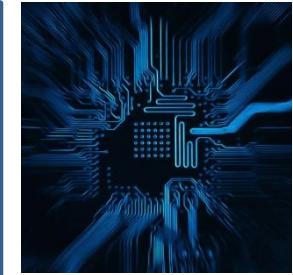

```
architecture cond_arch of check_4 is
begin
process(a)
begin
If ((a(0) = '0') and (a(1) = '0')) then
x <= '1';
else
x <= '0';
end if;
end process;
end cond_arch;
```


input s	output x
00	a
01	b
10	c
11	d

Пример 4. Делимость на 4 без and

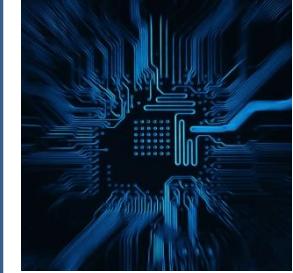

```
architecture cond_arch of check_4 is
begin
process(a)
begin
If (a(1 downto 0) = "00") then
x <= '1';
else
x <= '0';
end if;
end process;
end cond_arch;
```

input s	output x
00	a
01	b
10	c
11	d

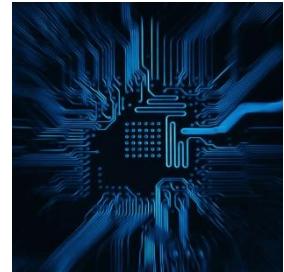

Пример 5. Дектор кодов

0101 – 11; 1010 – 10; 11111 – 01; x - 00

```
architecture cond_arch of parity_check is
begin
process(a)
begin
If (a(3 downto 0) = "0101" then
x <= "11";
elsif (a(3 downto 0) = "1010" then
x <= "10";
elsif (a(4 downto 0) = "11111" then
x <= "01";
else
x <= "00";
end if;
end process;
end cond_arch;
```

Пример 6. Сумма двух двоичных четырехразрядных чисел

```
library ieee;
use ieee.std_logic_1164.all;
entity adder_4_2 is
  port(
    a,b: in std_logic_vector(3 downto 0);
    x: out std_logic_vector(4 downto 0)
  );
end adder_4_2;
```

```
architecture test1 of adder_4_2 is
signal s: std_logic_vector (3 downto 0);
begin
  x(0) <= a(0) xor b(0);
  s(0) <= a(0) and b(0);
  x(1) <= (a(1) xor b(1)) xor s(0);
  s(1) <= ((a(1) xor b(1)) and s(0)) or (a(1) and b(1));
  x(2) <=
  s(2) <=
  x(3) <=
  x(4) <=
end test1;
```

